

# Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

## COVER STORY

### DIGITAL THERMOMETER

Add it to your DMM. It reads out in °C or °F at the flip of a switch and it's a cinch to build. Turn to page 29

### DARKROOM TIMER

Digital countdown in seconds or minutes and seconds controls your enlarger. Puts your darkroom into the year 2001. Turn to page 33

### VIDEO MODULATORS


Roundup of all that we could locate. Use them to turn any TV into a video monitor. Story starts on page 38

### INVESTMENT

A computer program that lets you compare dollars in the bank with your pet investment. Story is on page 32.
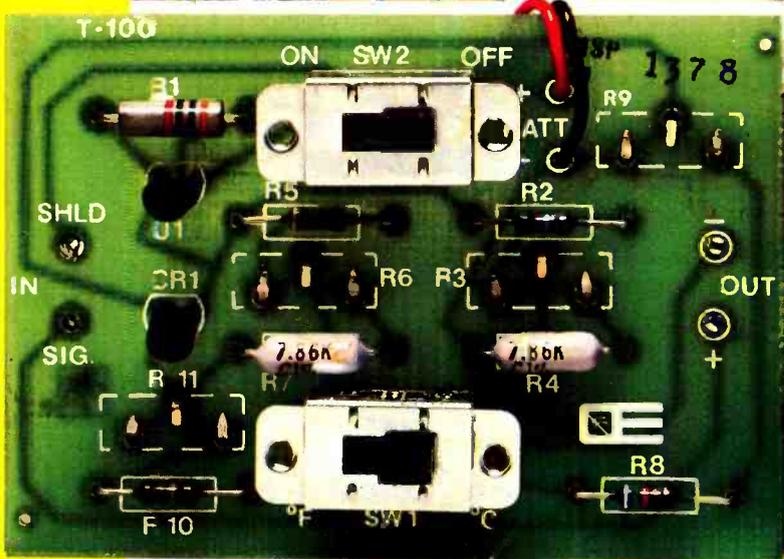
### PLUS

- ★ Computer Corner  
Programmable timer
- ★ Hobby Corner  
Build expanded-scale voltmeter
- ★ Service Clinic  
Pulse-width modulated DC powersupplies
- ★ R-E Tests Revox B-760 Tuner
- ★ R-E Tests Shure V15 — Type IV Cartridge
- ★ State Of Solid State




# NEW ASTRO-FANTOM™


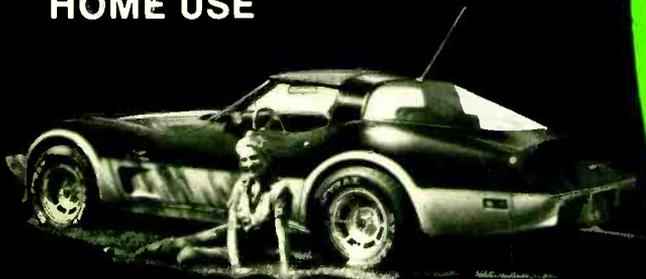
## CB ANTENNA

**GOES WHERE  
NO CB  
ANTENNA  
HAS GONE  
BEFORE!**

**SUPERIOR  
PERFORMANCE FOR  
AUTO, TRUCK, MARINE,  
RV, MOTORCYCLES AND  
HOME USE**



**avanti® antennas**

AVANTI RESEARCH AND DEVELOPMENT, INC.  
340 Stewart Avenue, Addison, IL 60101  
IN CANADA: Lenbrook Industries,  
1145 Bellamy, Scarborough, Ontario M1H 1H5

## It Mounts On Glass Transmits and Receives THRU Glass

Now from the AVANTI Research Laboratories comes a sleek, 22" full 1/2 wave antenna, so unique that it mounts on glass, transmits through glass and receives through glass...yet requires no grounding to metal as do conventional 1/4 wave antennas. No holes to drill...no clamps, clips or magnets to ever mar or scratch your car's finish! No pinched cables to run in through doors, windows or trunk. The Astro-Fantom is a handsome, low profile antenna that provides the ultimate in convenience!

**EASY INSTALLATION.** The Astro-Fantom is so uncomplicated that installation takes only five minutes and requires no tools. It bonds securely to the glass with an all weather tested 3M press-on adhesive, yet can be quickly transferred when desired. The fiberglass whip removes instantly for storage, car wash or theft protection.

**ONE MOUNT SATISFIES EVERY NEED.** Astro-Fantom's unique mount attaches anywhere there's a metal framed window. Front, side, or rear of vehicle, boat and motorcycle windshields, even home installation.

**CLEAREST COMMUNICATIONS.** Avanti's exclusive space age co-inductive™ coupling box actually rejects static and interference as it establishes a highly tuned circuit to transmit and receive radio signals through the glass.

**FULL 360° SIGNAL.** Astro-Fantom's full 1/2 wave design eliminates dead spots and directional problems found in conventional CB antennas.



PATENT PENDING **Model AV-200**  
Length 22"

CIRCLE 33 ON FREE INFORMATION CARD



© 1978, all rights reserved



# Pocket Yellow Pages

*Let your fingers do the data entry with America's first computerized pocket telephone directory.*

You're stuck. You're at a phone booth trying to find a phone number, and people are waiting. You feel the pressure.

To the startled eyes of those around you, you pull out your calculator, press a few buttons, and presto—the phone number appears on the display of your calculator. A dream? Absolutely not.

Space-age technology has produced the Canon Directory—a calculator that stores 20 of your most frequently called numbers in its memory and let's you recall them simply by entering the person's name or initials.

The keyboard has letters as well as numbers (like the touch-tone pad on a telephone), so it's easy to enter data and use. Want to call Jim? You enter J I M, and your display shows Jim's phone number. Even when you shut your unit off, it retains your complete directory in its large memory.

Ever forget to shut your calculator off when you slipped it in your pocket? No problem with the Canon Directory. The system was built like a liquid crystal digital watch. Its display can remain on constantly without draining the two long-lasting hearing aid batteries which you get with your unit. A low battery indicator also warns you well enough in advance when it's time to change batteries.

#### STORE IN CONFIDENCE

If you lost your little black book with all those confidential numbers, you might get in trouble. Not so with the Directory. Without knowing the specific initials or name, you can't access the numbers.

And then there's convenience. You carry your calculator with you anyway. Why not add the convenience of a telephone directory to a full-function calculator? When it comes to calculating, the Canon is no slouch either.

There's a fully-addressable memory, square root, and an add-on discount percentage system.

#### EASY TO OPERATE

Just enter the name and number you want stored and press a few buttons. That's all there is to it. Changing an entry is just as easy. You can also store credit card numbers, important serial numbers, birthdays, and anniversaries. For example, enter the next birthday or important date you should remember under "DATE." This date will appear each time you enter the word "DATE." By getting in the habit of doing that each week, the Canon won't let you forget. Or have you ever been stuck at a phone booth with no pen to write your messages? With the Canon, you can enter them directly into your unit—name and number.

The Canon Directory is a new breakthrough in recent calculator technology. The large-scale integrated circuit is programmable by the user—something nearly impossible just a few short months ago.

#### TEST IT FOR A MONTH

Order the Directory. Quickly program it with your most frequently called numbers. (You'll be amazed at how many 20 numbers seem when you sort out your personal directory.) Then use it every day. Program those important dates, your social security number, the phone numbers of your favorite restaurants, airlines, or movie theaters. Test the batteries by leaving your unit on for a week.

See how easy it makes life. Then within 30 days, decide if you want to keep it. If not, no problem. Just slip it in its handy mailer and send it back. We won't be upset, and in fact, we'll thank you for at least giving our unique product a test.

JS&A is America's largest single source of space-age products—a substantial company which has been in business for over a decade. Canon is the famous company that manufactures quality cameras, calculators, and other precision quality instruments.

If service is ever required, just slip your three-ounce unit in an envelope and mail it to Canon's national service-by-mail center. It's just that easy. Service should never be required since practically all components are on a single integrated circuit, but we wanted to assure you that a service program is an established part of Canon's program. The unit is 2 3/4" x 5 1/2" and only one centimeter thick.

To order your own Canon Directory, send \$79.95 plus \$2.50 for postage and handling to the address below (Illinois residents, please add 5% sales tax), or call our toll-free number below. By return mail you will receive your unit, a handy wallet-style carrying case, and a one-year limited warranty.

This year, let the sophistication of space-age technology and your fingers do all the walking. Order your Pocket Yellow Pages at no obligation, today.

**JS&A** NATIONAL SALES GROUP

Dept. RA One JS&A Plaza  
Northbrook, Ill. 60062 (312) 564-7000  
Call TOLL-FREE ..... 800 323-6400  
In Illinois Call ..... (312) 498-6900

©JS&A Group, Inc., 1978

NOW PRODUCED IN NEW, LARGE **Xcelite** FACILITY

# every electronic hand tool you'll ever need



The new, ultra-modern Xcelite manufacturing plant . . . the most advanced in the world for producing top quality forged tools . . . is now turning them out in record numbers to meet the ever-growing demand for the world's finest family of electronic hand tools. And at no-nonsense, competitive prices.

Employing the latest in manufacturing technology and quality controls, with every step in the production process under one roof, this new, large facility is continuing evidence that Xcelite . . . the

pioneer that brought you so many innovations in electronic hand tool design . . . is also the front-runner in production innovations.

Whatever your needs for electronic product assembly, service, or maintenance, the Xcelite line, finest and most diverse available anywhere, offers your best answers . . . perfectly aligned, hand-honed pliers and cutters, precision-machined screwdrivers and nutdrivers, exclusive thin-pattern adjustable wrenches, plus dozens of related tools and kits you might require.

It was no accident that Xcelite long ago earned . . . and still holds . . . "Preferred Status" among electronics professionals. So keep expecting leadership from Xcelite . . . and see your distributor for today's most wanted hand tools made by tomorrow's production methods.



**The Cooper Group**  
**Electronics Division**

WELLER® • WISS® • XCELITE®

CIRCLE 4 ON FREE INFORMATION CARD

P.O. BOX 728, APEX, NORTH CAROLINA 27502, 919/362-7511

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

AUGUST 1978 Vol. 49 No. 8

## SPECIAL FEATURES

- 38 **Video Modulator Roundup**  
A look at the many different units currently available, their circuitry, their specs, and what we think of them.
- 47 **Using RF Generators**  
The easy way to troubleshoot stereo systems.

## BUILD ONE OF THESE

- 29 **Digital Thermometer Add-On For Your DMM**  
Connect it to your digital multimeter and read temperature in °C or °F. An extremely accurate yet easy-to build unit.
- 33 **Digital Darkroom Timer**  
*Part II:* Final construction and adjustment procedures get this unit ready for your darkroom.

## GENERAL ELECTRONICS

- 3 **Looking Ahead**  
Tomorrow's news today.
- 56 **Reducing TV Interference**  
Use the right test equipment and it's easy to prevent unwanted interference from CB transceivers.
- 66 **Hobby Corner**  
Build an inexpensive expanded-scale voltmeter to monitor AC line voltage.
- 72 **State-Of-Solid-State**  
Temperature transducer and precision voltage reference all in one IC.

## STEREO HI-FI

- 42 **R-E Lab Tests Revox FM Tuner**  
B-760 Stereo tuner earns a "Very Good" for overall FM performance.
- 44 **R-E Lab Tests Shure V15 Type IV**  
New stereo cartridge rates a "Superb."

## COMPUTERS

- 32 **Investment Evaluation Program**  
Lets you determine if your investment earned more for you than a savings account.
- 64 **Computer Corner**  
Intel 8253—a programmable interval timer.

## TELEVISION


- 24 **Equipment Report**  
American Technology GTS-10 General Television Servicer
- 74 **Jack Darr's Service Clinic**  
Pulse-width modulated DC power supplies and how to troubleshoot them.

## DEPARTMENTS


- |     |                           |    |               |
|-----|---------------------------|----|---------------|
| 110 | Advertising Index         | 16 | Letters       |
| 14  | Advertising Sales Offices | 82 | Market Center |
| 14  | Editorial                 | 6  | New & Timely  |
| 111 | Free Information Card     | 79 | New Products  |
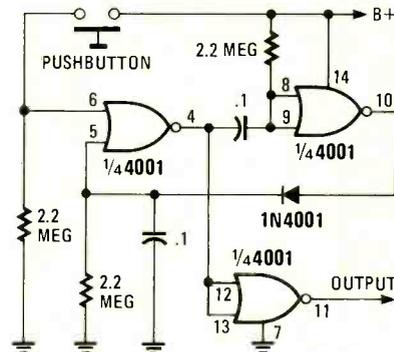
## ON THE COVER

Sitting on a background of video modulators is a digital thermometer add-on for a digital multimeter. It's a highly accurate instrument that reads out in both °C and °F at the flip of a switch. Story starts on page 29.



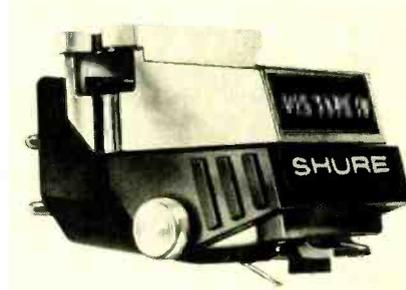**SIMPLE TEST CIRCUIT** is used to set up your new digital darkroom timer. For details on how to build the timer turn to page 33.



**NEW PHONO CARTRIDGE** plays stereo discs so well that it earns a "Superb" from our test lab. For all the details turn to page 44.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98. Other countries, \$14.98. Single copies \$1.00. © 1978 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**Subscription Service:** Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

# looking ahead

**Calculator evolution:** Just a short time ago, it seemed that the pocket calculator market was about to dry up. Prices were tumbling well below \$10, and it was evident that sooner or later everybody would have one, and that would be it. Well, calculators are doing nicely, thank you. World production this year will be about 70 million units, and the little calculators are being introduced in forms which were unheard-of just a couple of years ago.

It's no longer price, but sophistication, which sells calculators. Of course, not everyone needs a complex scientific calculator, but we are now seeing a marked trend to ultrasophisticated calculators just about anyone can use—even people who have never heard of a logarithm or a cosine. One manifestation of the trend is the slim calculator, about the size of a credit card, with liquid crystal readout—some with a battery life so long that replacement probably won't be needed for the life of the instrument. Another is the calculator combination—such as the combination calculator, pocket watch, stopwatch, perpetual calendar and alarm clock.

The next generation pocket calculator almost certainly will be microprocessor-equipped, with alphanumeric keyboard and display. One of the forerunners of this trend is the Toshiba Electronic Notebook, which contains a CPU and a RAM chip. In addition to traditional calculator functions it has a secret memory—or rather 30 memories that can store information for recall at will. By punching in letters or numbers, or combinations of both, the user can use it to store telephone numbers, addresses, remind him of appointments, and so forth. For example, you might punch in the name of your wife and the readout will display her birthday. Of course, you can do the same thing with a memo pad, but this is electronic, and it's only \$80.

Obviously, the line between calculators and mini- or microcomputers is blurring rapidly. A far more deluxe gadget than the Electronic Notebook, but performing some of the same functions, is the Mind Reader, developed by a California company called CTI. This \$495 desktop accessory has an alphanumeric keyboard, electronic alarm and a 12-digit fluorescent display, and can be programmed as a complete office reminder—alerting its owner to the time of a meeting, the subject and so forth.

And while we're on bigger-than-pocket gadgets, the latest in computer chess games is a compact unit named Boris, which can play at all skill levels—and also kibitzes. The digital readout talks back to the player with such words and phrases as "Stalemate," "Is this a trap?" and "Congratulations." It's \$300.

Back to the pocket. Calculators are changing so fast that John McDonald, president of Casio U.S.A., says the life of a calculator model is now only one year before it's replaced by an updated unit. As to the average life of a calculator itself, he estimates it's about four years before it's replaced—not because it wears out but because the user finds something better or more titillating. This suggests that we're becoming a nation of calcoholics.

**CATV vs. VCR:** "Record one TV program while you watch another." So proclaim the ads for home videocassette recorders, or VCR's. But some VCR buyers are finding out

this isn't always completely true. The fact is that under certain conditions, cable TV subscribers who own VCR's must choose between the ability to record all available channels or to watch one channel while taping another.

This is true when the home cable terminal has a converter box to provide extra channels above and beyond the 12 conventional VHF ones. These channels are the so-called mid-band and super-band channels, usually identified by letters instead of numbers and they often include any pay-cable channels such as Home Box Office, which present top commercial-free entertainment, including recent movies—obviously prime home taping material.

The problem is that cable TV channels in these cases are selected through a converter box, normally connected between the cable and the TV set. The VCR has its own tuner, of course, which can select only the standard VHF and UHF channels, but not the special lettered channels. If the converter is connected directly to the home cable input and its output to the VCR, the tuner in the converter governs the signal fed to both the VCR and the TV. All the channels may be tuned, but the VCR can record only the same signal which is being fed to the TV. If the setup is changed and the cable fed directly into the VCR, with the converter installed between the VCR and the TV, the VCR can tune only to the numbered channels, while the TV can receive any of the cable channels since it (but not the VCR) is governed by the converter. Thus, if a viewer should wish to record Home Box Office he must use the first setup and can't view another program at the same time. If he wants to watch one show and tape another, he can't tape Home Box Office.

Most VCR suppliers who are aware of the problem, as well as most cable companies, suggest the addition of a second converter, available from the cable company at an additional monthly charge. In many such cases the cable companies insist on doing the installation themselves (at a fee) to assure that their equipment is operating properly. [Perhaps some **R-E** readers can offer a better—or cheaper—solution; we'd like to hear from you.]

**VCR's to come:** It's new-model time, and this applies to VCR's as well as TV sets. In addition to updating its basic Betamax unit with built-in electronic clock-timer and remote pause control (**Radio-Electronics**, June, 1978), Sony also unveiled the first home portable VCR, which weighs about 17 pounds, can be operated from battery or AC and can be carried by a shoulder strap. As a companion, Sony will have a color camera weighing less than five pounds. They're both due later this year.

Among other coming VCR attractions will be a portable recorder and camera from Panasonic, and a home VCR from JVC which permits still-frame and slow motion as well as letting the user scan the picture during the fast-forward process for accurate location of any scene. And RCA is expected to introduce a VCR with built-in one-week programmer to permit automatic channel-switching and off-on cycling during unattended recording.

**DAVID LACHENBRUCH**  
CONTRIBUTING EDITOR

**Here's a new tool  
repair shops can really use.**

**5yr.  
warranty**

**ON REPLACEMENT TV PICTURE TUBES.**

Aside from your fine work, what are you doing to make your customers return to you with more repairs? A nice smile and "thank you, please call again" may not be enough.

Well, Sylvania has come up with a new tool that's sure to help you turn every customer into a steady customer. It's a 5-year warranty\* that you can now offer on replacement picture tubes.

So now not only can you offer the best in replacement tubes, but also have a 5-year backing from GTE Sylvania—one of the largest electronics corporations in the world.

For more information on how we can help your repair shop business just contact your nearest Sylvania distributor or GTE Sylvania, Distributor and Special Markets Division, Seneca Falls, N.Y. 13148

**SYLVANIA**

**GTE**

\*LIMITED WARRANTY. LABOR NOT INCLUDED.

CIRCLE 27 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

## 1977—a banner year for CB applications and sales

The Federal Communications Commission reports receiving almost five million CB radio applications in 1977 (1976 saw more than five million such applications).

John Sodolski, vice president of the Electronics Industries Association and head of EIA's Communications Division, adds that more CB transceivers were sold at retail in 1977 than since 1958. With such a good sales record, Sodolski feels confident that "consumer interest in CB radio is still running high." The use of CB radios in such crises as the blizzards and floods of recent months, he notes, are a clear indication that people are buying CB's for emergency use and for the peace of mind that results from knowing that these devices can be used in emergency situations. It is estimated that at present there are about 30 million CB's in use.

## Computer-controlled optical scanning machine can read to blind

The New York Public Library has recently installed what has been described as one of the "most valuable rehabilitation aids (for the blind) since the invention of Braille." This device is a machine containing an optical scanner that actually "reads" material via a computer-generated voice.

The scanner began life as a computer science project developed by an M.I.T. student who, later realized its potential as an aid to the blind. What it does is beam a ray of white light across a printed page, and then convert the material into digital data that the computer analyzes and converts into an actual voice reading. The machine reads a selection by consulting 1000 pre-programmed pronunciation rules and exceptions; it recognizes each letter by its shape. There are controls for adjusting voice speed, repeating sentences or phrases, or spelling out words. So far, the only complaint seems to be that the New York Library machine speaks in a foreign accent!

James Gashel of the National Federation of the Blind asserts that "the device would make pleasure reading possible for those whose literary diets had been limited to Braille textbooks" and some recorded material. A blind reader can learn to operate the machine in 20 hours, as opposed to the many months (and even years) involved in learning Braille. The New York Library's machine is one of 15 in existence and the only one installed in a public library.

## Electronic bank machines prey to fraud and embezzlement

Along with the convenience and speed of electronic bank transactions (i.e., cash machines) has come a perhaps not-unexpected side effect—criminals and con men

## ULTRA-THIN BATTERY FOR WATCHES



AN ULTRA-THIN SILVER-OXIDE BATTERY, developed by Panasonic, is suitable for electronic watches using LCD displays as well as for any other application requiring a low-profile cell. Called the *model WL-5*, the battery has a diameter of 0.4555 inch and measures only 0.085-inch thick. The battery has a nominal output voltage of 1.5 VDC 40 mA over a temperature range of  $-10^{\circ}\text{C}$  to  $60^{\circ}\text{C}$ ; a long storage capacity; and, because the silver oxide allows for a minimum variation in the internal resistance, the voltage is stable.

(and women) have learned how to manipulate the machine and the system to defraud both the public and the banks. Although some of the reported cases involve mail fraud, the main weakness lies in the machines themselves, which require you to dip a card and use a special code to withdraw, deposit, transfer funds and pay bills.

While most of these transactions are undertaken without incident, almost all the cases of theft involve the misuse of the cash dispenser cards. Bank officials, wary of the adverse publicity and unwilling to advertise the vulnerability of the machines, have tended to soft-pedal the incidents. However, it was estimated that in 1977 the total nationwide loss of both consumer funds and bank assets ran into \$2.5 million.

Some of the ways criminals have taken advantage of the card system:

- Preventing a customer from completing a transaction by posing as an official, then completing the transaction themselves.
- Intercepting bank cash cards and code numbers sent via the mail.
- In one bizarre case, a customer was mugged outside a cash machine and forced to hand over both card and code. The thieves made off with about \$400, although the victim's bank balance only contained \$130!

Banks by and large have tried to make up the losses privately on a case-by-case basis. Many have strengthened their security systems and attempted to close system loopholes. The U.S. Congress is presently reviewing legislation that would limit customer liability, require bank receipts from automatic tellers, and make some transactions reversible. And in N.Y. State the Attorney General is trying to stop the unsolicited mailing of cash credit cards.

## Top-name computer equipment sold at auction

Some famous names in computer equipment will fall under the auctioneer's gavel this summer. The auction is run by Newman

Computer Exchange, which buys up quantity lots of new and reconditioned equipment from leading manufacturers and sells them via mail-order catalogs. The auctioned items are selected from overstocked merchandise or slow movers.

Minimum bids are established on the equipment (which this year includes some top-rated items such as Commodore's PET). The equipment is sold at the highest bid above the minimum price set, regardless of the loss to the company.

Chuck Newman, vice president of the firm, stressed that only mail bids would be accepted, and individuals appearing in person at the auction cannot outbid the highest mailed-in bid received.

The estimated value of the merchandise to be auctioned this year will exceed \$1,000,000. Opening date for the bids has been set for July 31. For further information, write Newman Computer Exchange, Dept. R58, Box 8610, Ann Arbor, MI 48107, or call Chuck Newman (313) 994-3200.

## Hickok/Forest Belt Workshops drawing nets Grand Prize winner

Hickok Electrical Instrument Company and the Forest Belt Training Workshops



GRAND PRIZE WINNER at opening ceremony for Forest Belt's 1978 Training Workshops is William T. Ricks (left). He is shown being presented with a Hickok instrument by Forest Belt (right). Karen Ruff (center) drew Ricks' name from a list of six finalists.

*continued on page 12*

# We've done the impossible again!

## A versatile and superior frequency counter kit for only \$89.95



### Brief Specifications

- Frequency Range: 20 Hz to 100 MHz guaranteed (10 Hz to 120 MHz typical)
- Sensitivity: 25 mV RMS, 20 Hz to 70 MHz (20 mV typical); 45 mV RMS, 70 MHz to 120 MHz (30 mV typical)
- Selectable Impedance: 1 MΩ at 25 pF, or 50 Ω
- Selectable Attenuation: X1, X10, or X100
- Accuracy: ± 1 Hz plus time-base accuracy
- Ageing rate: ± 5 ppm/yr
- Temperature stability: ± 10 ppm, 0° to 50°C
- Selectable Gate-time: 0.1 sec, 1 sec., or 10 sec.
- 8-digit LED display with floating D.P., overflow indication
- Input: 9-15 VDC, 350 mA (550 mA with optional prescaler)
- Input protection: 150 V RMS, 20 Hz to 10 kHz; 30 V RMS to 2 MHz; and 3 V RMS to 100 MHz
- Optional prescaler extends frequency range to 650 MHz. (Available soon)

Get about price/performance trade-offs in a frequency counter. In Sabtronics' features you once expected to pay dollars for. But you pay only our low,

performance and input characteristics. You will see guaranteed all the way to input impedance allows you operation. And you'll see a the frequency range; con- or best resolution; and an optional pre-scaler. ease, and its excellent tics. And a full 8-digit point, leading zero

comes together only Sabtronics' ad- your own skill follow instruc- ve this fine ould other-

### New School offers audio electronics workshop for beginners

The New School for Social Research in New York City this past summer provided a workshop for beginning electronics students. The three-hour-per-week, six-session course emphasized basic skills and information needed to assemble kits, purchase components and design and construct audio-digital equipment. Students learned how to solder, prepare PC boards and point-to-point wiring techniques. The course fee was \$75, and students were asked to bring their own tools.

Steve Ohr, the New School's audio-visual director and course instructor, believes that "providing individuals with a working knowledge of electronics will serve them in many ways long after the course has been completed."

days. If or full

To: Sabtronics International, Inc.  
13426 Floyd Circle, Dallas, TX 75243

Please send me \_\_\_\_\_ Sabtronics Model 8100 Frequency Counter Kit(s) at \$89.95 each \$ \_\_\_\_\_  
Texas Residents add Sales Tax \$ \_\_\_\_\_  
Shipping and handling, \$5.00 per unit \$ \_\_\_\_\_  
(USA only) \$ \_\_\_\_\_

Payment enclosed   
Charge my Master Charge   
Visa

Account No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

\*Canada \$6.50. All other countries \$19.00 Airmail.

RE 6



Information center with 24 hours service and fuel economy \$400.

# Learn digital computer

**NRI trains you on a real digital computer you actually assemble as you learn.**

Learn computer design, construction, maintenance and programming techniques on your own programmable digital computer.

Qualified technicians are urgently needed for careers in the exciting new field of digital and computer electronics . . . and the best way to learn digital logic and operations is now available to you in NRI's Complete Computer Electronics Course.

This exclusive course . . . at home or . . . computer . . . ner's . . . complete . . . computer . . . m

displays

The NRI . . . of 10 kit . . . NRI C . . . tron . . . ur

Continued from page 6

## new & timely

recently conducted a final drawing for the Grand Prize offered to six finalists from earlier contests sponsored by the 1977 Workshops. Last year, each Workshop culminated in an Awards Banquet, at which the first drawing was held. The first name drawn had the option of selecting either a Grand Prize, or electing to go for the would "get what was left."

393  
Washi

At the San Antonio Awards Banquet, the second name was that of William T. Ricks, who automatically became a finalist in the Grand Prize contest. This year, at an opening ceremony for the 1978 Forest Belt Workshops, his name was drawn from among the six finalists. The Grand Prize was the Comm-Line CB Service Rack, consisting of seven test instruments and accessories, which Ricks will find most useful for his modest repair business near Dallas. Both Hickok and Forest Belt have announced that Hickok test instruments will be awarded during the five Forest Belt Workshops planned for 1978. For details, write: Forest Belt's Training Workshops, Box 68-120, Indianapolis, IN 46268.

### Automotive computer handles 24 different functions

A self-contained 24-function automotive computer called the Prince On-Board Computer has been developed by the OBC Products Division of Prince Corporation, Holland, MI. The computer is compact, weighs less than 1 pound, is easy to operate and presents no installation problems. It can be connected via a speed transducer and a fuel flow transducer, both supplied with the unit; and it can be mounted on or under the dash or overhead. Now as to what it can do: An LED display provides information on such vital statistics as miles to destination, vehicle location (by time), ETA, miles per gallon, cost per time of arrival, fuel need, time of day, and, in addition, the unit contains an alarm, five memories with

individual entry and recall and automatic memory scan. All the controls are easy to get at and color-coded. In sum, the On-Board Computer provides significantly more information to the driver than has been available up until now and, it is hoped, will provide a safer and more hassle-free drive. The company estimates the cost of the On-Board Computer will be about \$400 and that it will appear on the market by early 1979.

### Inadequate field service can jeopardize future of computer companies

Speaking before the Association of Field Service Managers (AFSM), George Harmon warned that lack of adequate field servicing could cause many new computer companies to go out of business. Harmon, president of AFSM and vice president of the Service Division of Pertec Computer Corporation, emphasized that servicing a data-processing system requires the same dedication as that given other office machinery, "but it is almost impossible for a small computer company to position a repairman 20 minutes from each customer—and not go broke."

on, would be to offer sales to regions that can be serviced within a one-hour travel-time limit. Whatever solution is tried, it is important to keep in mind that with computer service proliferating almost everywhere . . . if a company doesn't have service operations under control, the distinct possibility of going

### Two new Forest Belt scheduled for late 1978

Two new Training Workshops added to the Forest Belt series. The first, Video Servicing, is scheduled for late October 1978. The second, FL (at T), is scheduled for late November 1978. Both are being held at either

AUGUST 1978

# We've done the impossible again!

## A versatile and superior frequency counter kit for only \$89.95



Now you can forget about price/performance trade-offs when you select a frequency counter. In Sabtronics' Model 8100 you get features you once expected to pay several hundreds of dollars for. But you pay only our low, low price of \$89.95!

**Dare to Compare.** This frequency counter, using LSI technology, has the performance and input characteristics you demand. Note the specifications: You will see that the frequency range is guaranteed all the way to 100 MHz; and a high or low input impedance allows you to select for high-frequency operation. And you'll see a sensitivity that holds well over the frequency range; convenient selectable gate-time for best resolution; and selectable attenuation; and even an optional pre-scaler. Note the highly accurate time base, and its excellent ageing and temperature characteristics. And a full 8-digit LED display with floating decimal point, leading zero suppression, and overflow indicator.

You would expect to find all these features together only on a much higher-priced instrument. But Sabtronics' advanced digital technology combines with your own skill — you assemble this kit from our easy-to-follow instructions — to make it possible for you to have this fine frequency counter at a fraction of what you would otherwise expect to pay.

### Free 10-day trial

Examine the 8100 Frequency Counter Kit for 10 days. If not completely satisfied, return unassembled for full refund of \$89.95 purchase price.

**sabtronics**   
INTERNATIONAL INC.

13426 Floyd Circle • Dallas, Texas 75243  
Telephone 214/783-0994

### Brief Specifications

- Frequency Range: 20 Hz to 100 MHz guaranteed (10 Hz to 120 MHz typical)
- Sensitivity: 25 mV RMS, 20 Hz to 70 MHz (20 mV typical); 45 mV RMS, 70 MHz to 120 MHz (30 mV typical)
- Selectable Impedance: 1 M $\Omega$  at 25 pF, or 50  $\Omega$
- Selectable Attenuation: X1, X10, or X100
- Accuracy:  $\pm 1$  Hz plus time-base accuracy
- Ageing rate:  $\pm 5$  ppm/yr
- Temperature stability:  $\pm 10$  ppm, 0 $^{\circ}$  to 50 $^{\circ}$ C
- Selectable Gate-time: 0.1 sec, 1 sec., or 10 sec.
- 8-digit LED display with floating D.P., overflow indication
- Input: 9-15 VDC, 350 mA (550 mA with optional prescaler)
- Input protection: 150 V RMS, 20 Hz to 10 kHz; 30 V RMS to 2 MHz; and 3 V RMS to 100 MHz
- Optional prescaler extends frequency range to 650 MHz. (Available soon)

To: Sabtronics International, Inc.  
13426 Floyd Circle, Dallas, TX 75243

RE 8

Please send me \_\_\_\_\_ Sabtronics Model 8100

Frequency Counter Kit(s) at \$89.95 each \$ \_\_\_\_\_

Texas Residents add Sales Tax \$ \_\_\_\_\_

Shipping and handling, \$5.00 per unit (USA only)\* \$ \_\_\_\_\_

Payment enclosed  \$ \_\_\_\_\_

Charge my Master Charge

Visa

Account No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

\*Canada \$6.50. All other countries \$19.00 Airmail.

# Learn digital computer

**NRI trains you on a real digital computer you actually assemble as you learn.**

Learn computer design, construction, maintenance and programming techniques on your own programmable digital computer.

Qualified technicians are urgently needed for careers in the exciting new field of digital and computer electronics . . . and the best way to learn digital logic and operations is now available to you in NRI's Complete Computer Electronics Course.

This exclusive course trains you at home on your own digital computer! This is no beginner's "logic trainer", but a complete programmable digital computer that contains a memory and is fully automatic. You build it yourself and use it to define and flow-chart a program, code your program, store your program and data in the memory bank. Press the start button and the computer solves your problem and

displays the result instantly.

The NRI digital computer is one of 10 kits you receive in the NRI Complete Computer Electronics Course. You build and use your own TVOM, and experiment with NRI's exclusive Electronics Lab. You perform hundreds of experiments, building hundreds of circuits, learning organization, operation, trouble-shooting and programming.

## **New NRI Memory Expansion Kit**

The Model 832 NRI Digital Computer now comes with a new Memory Expansion Kit. Installed and checked out in 45 minutes, it doubles the size of the computer's memory, significantly increasing the scope and depth of your knowledge of digital computers and programming. With the large-scale IC's you get the only home training in machine language programming . . . experience essential to trouble-shooting digital computers.



# electronics at home.

## NRI offers you five TV/Audio Servicing Courses

NRI can train you at home to service Color TV equipment and audio systems. You can choose from 5 courses, starting with a 48-lesson basic course, up to a Master Color TV/Audio Course, complete with designed-for-learning 25" diagonal solid state color TV and a 4-speaker SQ™ Quadraphonic Audio System. NRI gives you both TV and Audio servicing for hundreds of dollars less than the two courses as offered by another home study school.

All courses are available with low down payment and convenient monthly payments. All courses



provide professional tools and "Power-On" equipment along with NRI kits engineered for

training. With the Master Course, for instance, you build

your own 5" wide-band triggered sweep solid state oscilloscope, digital color TV pattern generator, CMOS digital frequency counter, and NRI electronics Discovery Lab.



\*Trademark of CBS Inc.

## NRI's Complete Communications Course includes your own 400-channel VHF transceiver

NRI's Complete Communications Course will train you at home for one of the thousands of service and maintenance jobs opening in CB; AM and FM transmission and reception; TV broadcasting; microwave, teletype, radar, mobile, aircraft, and marine electronics. The complete program includes 48 lessons, 9 special reference texts, and 10 training kits. Included are: your own "designed-for-learning" 400-channel VHF transceiver; electronics Discovery Lab™; CMOS digital frequency counter; and more. You also get your all



important FCC Radio-telephone License, or you get your money back.



## CB Specialist Course also available



NRI also offers a 37-lesson course in CB Servicing with your own CB Transceiver, AC power supply, and multimeter. Also included are 8 reference texts and 14 coaching units to make it easy to get your Commercial Radiotelephone FCC License.

## You pay less for NRI training and you get more for your money.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

## More than one million students have enrolled with NRI in 62 years.

Mail the insert card and discover for yourself why NRI is the recognized leader in home training. Do it today and get started on that new career. No salesman will call.

If card is missing write:

**NRI** NRI SCHOOLS  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Avenue  
Washington, D.C. 20016

recently conducted a final drawing for the Grand Prize offered to six finalists from earlier contests sponsored by the 1977 Workshops. Last year, each Workshop culminated in an Awards Banquet, at which the first drawing was held. The first name drawn had the option of selecting either a prize on the spot, or electing to go for the Grand Prize; the second name drawn would "get what was left."

At the San Antonio Awards Banquet, the second name was that of William T. Ricks, who automatically became a finalist in the Grand Prize contest. This year, at an opening ceremony for the 1978 Forest Belt Workshops, his name was drawn from among the six finalists. The Grand Prize was the *Comm-Line* CB Service Rack, containing seven test instruments and accessories, which Ricks will find most useful for his modest repair business near Dallas.

Both Hickok and Forest Belt have announced that Hickok test instruments will be awarded during the five Forest Belt Workshops planned for 1978. For details, write: Forest Belt's Training Workshops, Box 68120, Indianapolis, IN 46268.

### Automotive computer handles 24 different functions

A self-contained 24-function automotive computer called the *Prince On-Board Computer* has been developed by the OBC Products Division of Prince Corporation, Holland, MI. The computer is compact, weighs less than 1 pound, is easy to operate and presents no installation problems. It can be connected via a speed transducer and a fuel flow transducer, both supplied with the unit; and it can be mounted on or under the dash or overhead.

Now as to what it can do: An LED display provides information on such vital statistics as miles to destination, vehicle location (at any time), ETA, miles per gallon, cost per mile, time of arrival, fuel need, time of day, etc. In addition, the unit contains an alarm set/audio pulse alarm, five memories with

individual entry and recall and automatic memory scan. All the controls are easy to get at and color-coded.

In sum, the *On-Board Computer* provides significantly more information to the driver than has been available up until now . . . and, it is hoped, will provide a safer and more hassle-free drive. The company estimates the cost of the *On-Board Computer* will be about \$400 and that it will appear on the market by early 1979.

### Inadequate field service can jeopardize future of computer companies

Speaking before the Association of Field Service Managers (AFSM), George Harmon warned that lack of adequate field servicing could cause many new computer companies to go out of business. Harmon, president of AFSM and vice president of the Service Division of Pertec Computer Corporation, emphasized that servicing a data-processing system requires the same dedication as that given other office machinery, "but it is almost impossible for a small computer company to position a repairman 20 minutes from each customer—and not go broke."

The problem lies in not being able to control where sales originate. For instance, a first customer can be based in one city (with a service technician placed close by), but then subsequent sales could come from areas far removed from that of the original sale. The manufacturer is then faced with either extensive travel costs and/or the necessity of placing service reps to take care of each new customer. Such costs can result in staggering losses to many young, small companies in the mini and microcomputer field.

One answer to the problem is "third party maintenance" such as that offered by Pertec, in which the computer manufacturer can assign service responsibility to a company having offices in many diverse areas. Another alternative, Harmon went

on, would be to offer sales to regions that can be serviced within a one-hour travel-time limit. Whatever solution is tried, it is important to keep in mind that with computer companies proliferating almost daily, field service is a "major factor in product costing . . . if a company doesn't have its service operations under control, it faces the distinct possibility of going out of business."

### Two new Forest Belt Workshops scheduled for late 1978

Two new Training Workshops have been added to the Forest Belt 1978 CB Service series. The first is a three-day Advanced Video Servicing Workshop, to be conducted twice—one in Indianapolis, September 18-20, and again in Captiva Island FL (at The South Seas Plantation) on November 13-17. The latter workshop session offers two extra days that can be used either for personal consultation or relaxation. The other workshop offered will be in Advanced Communications Servicing, also to be held twice—Indianapolis, September 11-13, and Florida, November 6-10.

The Advanced Video Servicing Workshop will deal with video cassette recorders, digital TV tuning, VIR color control, plus new alignment and troubleshooting procedures. The Advanced Communications Servicing Workshop will feature FM two-way radio systems, advanced PLL, SSB, marine radio and more.

Fees for the Indianapolis Workshops, \$495; for Florida, \$595. Included in the fees are lodging; breakfast, lunch and coffee breaks; and an Awards Banquet. Spouses are invited to attend on a no-workshop fee basis. Enrollments close August 4 for Indianapolis; September 15 for Florida. Send check or money order to: Forest Belt's Training Workshops, Box 68120, Indianapolis, IN 46268.

### New School offers audio electronics workshop for beginners

The New School for Social Research in New York City this past summer provided a workshop for beginning electronics students. The three-hour-per-week, six-session course emphasized basic skills and information needed to assemble kits, purchase components and design and construct audio-digital equipment. Students learned how to solder, prepare PC boards and point-to-point wiring techniques. The course fee was \$75, and students were asked to bring their own tools.


Steve Ohr, the New School's audio-visual director and course instructor, believes that "providing individuals with a working knowledge of electronics will serve them in many ways long after the course has been completed." **R-E**



**AUTOMOTIVE COMPUTER** provides motorists with a driver controlled information center with 24 functions. At a touch of the button, vehicle location, trip information, time of day and fuel economy data can be displayed on the LED digital display. The unit is expected to retail for \$400.
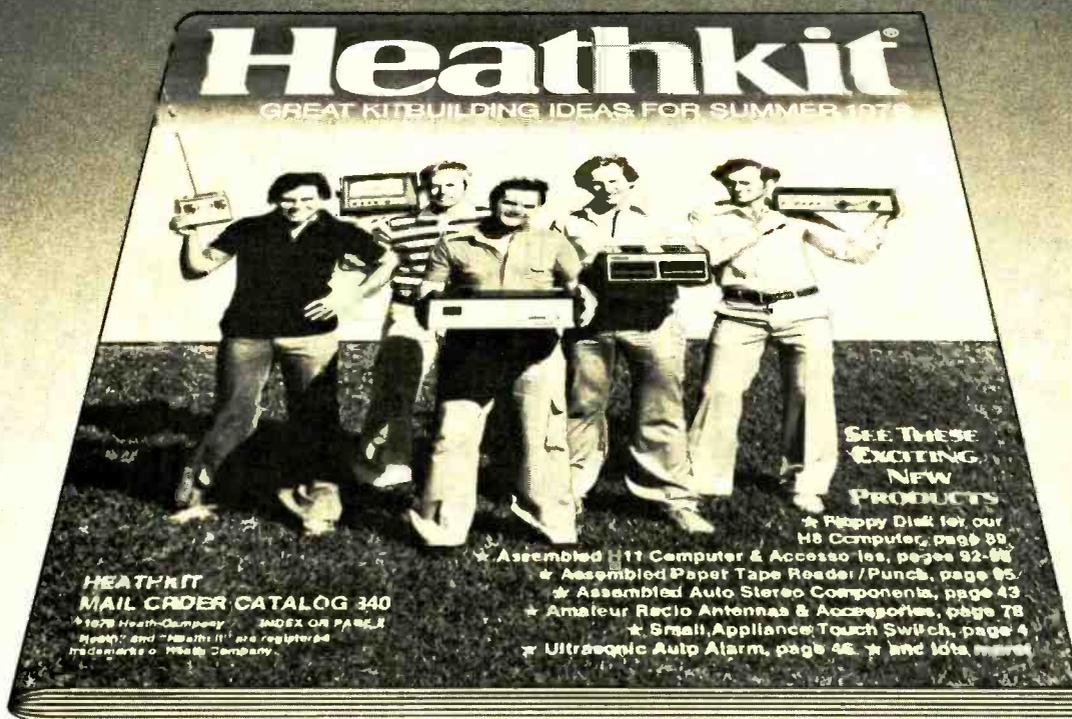
# FREE

The world's largest catalog  
of easy-to-build, money-saving  
electronic kits



- Personal Computer Systems now including Floppy Disk Storage
- Power Supplies ● Oscilloscopes ● Frequency Counters ● VTVM's and VOM's
- Ham Radio Gear ● Digital Programmable Color TV ● Hi-Fi Components
- Electronic Clocks and Weather Instruments ● Self-instruction Electronics Programs
- Auto, Fishing, Marine and Aircraft Accessories — nearly 400 kits in all!

Every Heathkit product comes with a fully-illustrated, step-by-step assembly manual that tells you everything you need to know to make kitbuilding fun and easy. Thousands of people have discovered the satisfaction — and value — of handcrafting electronic equipment. You can build it better... let us show you how.

**Send for your FREE Catalog today! ▶**

OR pick it up at the Heathkit Electronic Center (Units of Schlumberger Products Corporation) nearest you, where Heathkit products are sold, displayed and serviced. Retail prices on some products may be slightly higher. See the white pages of your phone book.

Heath Company, Dept. 020-440, Benton Harbor, Michigan 49022

HEATH Schlumberger	Heath Company, Dept. 020-440 Benton Harbor, Michigan 49022	<b>FREE</b>
Please rush me my FREE Heathkit Catalog. I am not on your mailing list.		
NAME _____		
ADDRESS _____		
CITY _____		STATE _____
CL-659		ZIP _____

CIRCLE 100 ON FREE INFORMATION CARD

## A Computer In Every Home— Fact Or Fantasy

NOT SO LONG AGO, INDUSTRY EXPERTS WERE PREDICTING THAT CALCULATORS AND DIGITAL watches were going to be the next major revolution in consumer electronics. Soon afterwards, when the markets for these items became saturated and sales leveled off, the consumer electronics industry turned its attention to CB radio. With a little bit of help from the Federal Government (40 channels or bust), sales of CB radios nose-dived and a new, more lucrative, product was needed. Out of this search came projection TV, video games, VTR's and home computers.

Although sales predictions for these products vary widely, my concern is with one product that is doomed to failure—the *home* computer. Keep in mind that there is a definite and distinct line drawn between the hobby and home computer markets. **Hobby computers** are those systems designed for electronics enthusiasts, those that will take the system home, experiment with it, learn about it and then modify it. Whether the hobbyist intends to use his computer for stock market analysis, personal finances, income tax preparation or just plain game-playing, matters little. The point is that he will be learning about computers, how they work, how to program them and, more important, how the microprocessor works. After gaining the necessary knowledge, he will look towards applying the computer and the microprocessor to solve real everyday problems.

The **home computer**, however, is directed toward the masses. Here the industry is looking for mass volume sales and is touting the home computer as a home appliance able to solve a host of problems for the homeowner. Who is the industry trying to fool? Does the industry really expect John Q. Public to take the computer home, learn to program it, interface it and use it to solve problems? The same John Q. Public that calls a service technician only to discover that the line cord isn't plugged into the wall outlet? And what sort of problems does the industry expect the home computer to solve? Can anyone name a single application that is more meaningful to the home-owner than a \$1000 solar energy converter? The silence is deafening. To put the home computer in perspective, it's a solution looking for a problem.

There are those that tout the computer as a central control unit for the home. It could handle such tasks as controlling lights, appliances, lawn sprinkler systems and the like. Total nonsense! Do we need a \$1000 system for these tasks? We certainly don't need a CRT, a floppy disc and 32K of RAM. Microprocessor IC's are inexpensive. The control tasks can be handled easily with an 8008; an 8080 or Z-80 simply isn't required. Why not put a microprocessor IC in each appliance we wish to control rather than building a single central control unit. This would certainly be more economically desirable.

As far as hobby computers are concerned, the knowledge gained from these systems is worth every penny spent. It is the users of these systems that will find meaningful applications for the microprocessor. **Radio-Electronics** will, therefore, continue to provide tutorial, applications and construction-oriented hobby computer articles.

How about sending us your opinion on the future of the home computer? What problems around the home do you foresee the microprocessor solving? Get busy designing circuits to solve those problems. For it is you that comprise that segment of the population that comprehends, understands and has the know-how to accomplish these feats. And it is you, therefore, that is a most vital force within the consumer electronics industry.



**ART KLEIMAN**  
Managing Editor

# Radio-Electronics®

**Hugo Gernsback** (1884-1967) founder  
**M. Harvey Gernsback**, editor-in-chief and publisher  
**Larry Steckler**, KTX-3644, CET, editor  
**Arthur Kleiman**, KTZ-3288, managing editor  
**Robert F. Scott**, CET, W2PWG, KXK-8533, technical editor  
**Sonia Greenbaum**, copy editor  
**Jack Darr**, CET service editor  
**Leonard Feldman** contributing high-fidelity editor  
**Karl Savon**, semiconductor editor  
**David Lachenbruch**, contributing editor  
**Earl "Doc" Savage**, K4SDS, hobby editor  
**Vincent P. Cicenja**, production manager  
**Harriet I. Matysko**, circulation director  
**Sheila Wertling**, circulation assistant  
**Arline R. Bailey**, advertising coordinator

Cover design by Louis G. Rubsamen  
Cover photo by Mike Wilson

**Radio Electronics** is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.  
200 Park Ave. S., New York, NY 10003  
(212) 777-6400  
President: M. Harvey Gernsback  
Vice President: Larry Steckler  
Treasurer: Carol A. Gernsback  
Secretary: Bertina Baer

### ADVERTISING SALES

Paul McGinnis  
Director of Marketing

### EAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
(212) 777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
The Ralph Bergen Co.  
540 Frontage Road—Suite 361-A  
Northfield, Illinois 60093  
(312) 446-1444

### PACIFIC COAST

**Mountain States**  
Jay Eisenberg  
J.E. Publishers Representative Co.,  
8732 Sunset Blvd.,  
4th Floor,  
Los Angeles, CA 90069  
(213) 659-3810  
Sales Mart Building  
1485 Bayshore Blvd., Box 140  
San Francisco, CA 94124  
(415) 467-0125

### SOUTHEAST

J.E. Publishers Representative Co.,  
214-387-2424



# NTS trains you on tomorrow's equipment. Today.

Microcomputers, digital systems and more...  
from the first name in home study.



Now NTS training programs include an even wider choice of solid-state digital equipment than ever before offered in any electronic home study course. Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath digital computer, digital test equipment, digital stereo receiver (70 watts per channel) plus much more state-of-the-art equipment to make your training exciting and relevant. Learn servicing and maintenance easily with step-by-step Project Method lessons and kits.

An all-new full color catalog shows you exactly what each of the fourteen courses cover, and every piece of equipment you receive.

Send for it today and see for yourself what's really happening in electronics training technology at NTS. It's free. Just send the coupon.

**NO OBLIGATION. NO SALESMAN WILL CALL.  
APPROVED FOR VETERAN TRAINING.**

## NATIONAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 South Figueroa St., Los Angeles, Calif. 90037

**NATIONAL TECHNICAL SCHOOLS** Dept. 206-088  
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- |   |   |
|---|---|
| <input type="checkbox"/> Color TV Servicing           | <input type="checkbox"/> Electronics Technology         |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Audio Electronics Servicing    |
| <input type="checkbox"/> FCC License Course           | <input type="checkbox"/> Digital Electronics            |
| <input type="checkbox"/> Electronic Communications    | <input type="checkbox"/> MicroComputers/MicroProcessors |

Name \_\_\_\_\_

Address \_\_\_\_\_

Apartment Number \_\_\_\_\_ Age \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

- Check if interested in G.I. Bill information.  
 Check if interested ONLY in classroom training in Los Angeles.

# letters

## TV AUDIO-TO-STEREO ADAPTER

With reference to Robert E. Thomas II's letter in the January 1978 issue regarding his attempts to feed TV audio into his hi-fi system, I have been conducting numerous experiments of this type for many years, and have made several observations:

1. If you wish to feed the audio from your TV into the input of your mono or stereo amplifier or receiver, be *sure* both sets have power supplies that are fully transformer-isolated. Many portable and low-priced sets do not, and have their chassis connected directly to one side of the AC line and are dangerous to connect into. To find out, check your set's schematic.


2. If your TV set is a tube type, it probably has a high-output, high-impedance quadrature detector. If so, a cathode follower must be installed in the set, close to the sound detector tube or the volume control. A suitable circuit is shown in the diagram. This cathode follower can be built in a mini-box, and takes its heater and B+ voltage from the TV set.

3. If the set is solid-state, its detector is of a lower impedance and can be tapped

directly. However, use low-capacitance shielded cable and keep it as short as possible. Include a 1.0  $\mu$ F, 100-volt capacitor in the hot side of this lead (at the TV end) to prevent unwanted DC voltages from

control and must be traced with a scope. Again, check the set schematic.

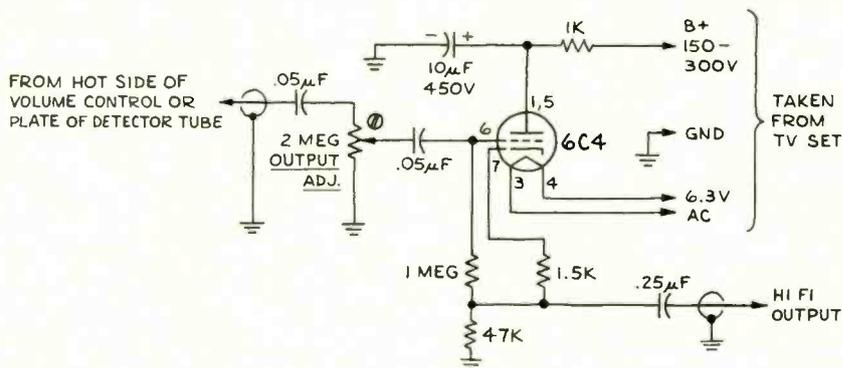4. Even if the set has no power transformer, you can still disconnect the small speaker in the set and bring leads out to a



being coupled. As with tube sets, the volume control immediately follows the sound detector in most cases. This, in turn, varies the gain of an amplifier stage. If so, audio does not appear on the volume

better speaker. Be sure that the impedance of the new speaker matches the original and insulate all connections, since they may be hot. Select an efficient speaker

*continued on page 22*

## Everything you've dreamed of in a scope...including a sensible price.



See them at your VIZ distributor.

Whether it be for servicing or scientific research, the new WO-527A 15MHz 5" triggered-sweep oscilloscope is designed for a wide range of applications. With its host of useful functions and its advanced solid-state integrated circuits, it's hard to believe it's so reasonably priced.

- Easy-to-use pushbutton controls
- Triggered or automatic sweep; ac or dc triggered
- Unique trigger level control with LED polarity indicators
- 10mV to 20V/cm in 11 ranges
- 19 calibrated sweep ranges
- Preset, automatic TV sync separation circuits
- Built-in calibrated time-base
- Special line selector for TV line-by-line display
- 10 times sweep magnifier

**VIZ Test Instruments Group**  
of VIZ Mfg. Co.

335 E. Price St., Philadelphia, PA 19144

Formerly


**RCA**  
Instruments
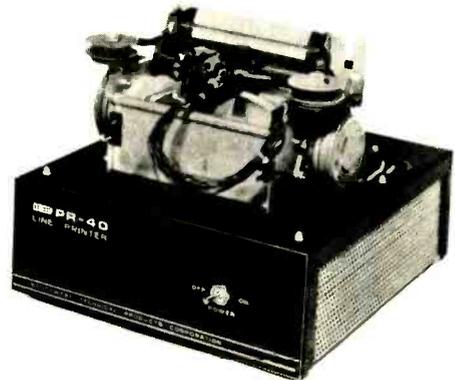
# A \$\$ COMPETITIVE SYSTEM



**YOU CAN OWN A VERSATILE  
6800 COMPUTER SYSTEM  
FOR AS LITTLE AS \$799.50!**

MP-68/1 Computer Kit ..... \$395.00  
 CT-64 Terminal Kit (less monitor) ..... \$325.00  
 AC-30 Cassette Interface Kit. .... \$ 79.50



You can add a 40-column printer and a professional quality data terminal monitor for only **\$460.00**

PR-40 Printer Kit ..... \$250.00  
 MP-L Interface Kit ..... \$ 35.00  
 CT-VM Data Terminal Monitor ..... \$175.00



You can expand to a full-scale personal computer system with dual disk drives for only **\$1,445.00**

MF-68 Dual Disk System Kit. .... \$995.00  
 MP-16 16K Memory (assembled). .... \$450.00

...OR buy the complete system at our special low price of **\$2,595.00**

- YOU GET:**
- ▶ A 20K byte computer
  - ▶ A true "stand alone" data terminal and monitor
  - ▶ A 40-column dot matrix printer
  - ▶ A dual drive 200K byte disk system
  - ▶ Disk BASIC with file handling

These are the same proven, reliable components used in our industrial and business systems. Why settle for the limitations of a so-called "personal computer" or hobby system?




**SOUTHWEST TECHNICAL PRODUCTS CORPORATION**  
 219 W. RHAPSODY  
 SAN ANTONIO, TEXAS 78216

CIRCLE 21 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# You gotta shop around.

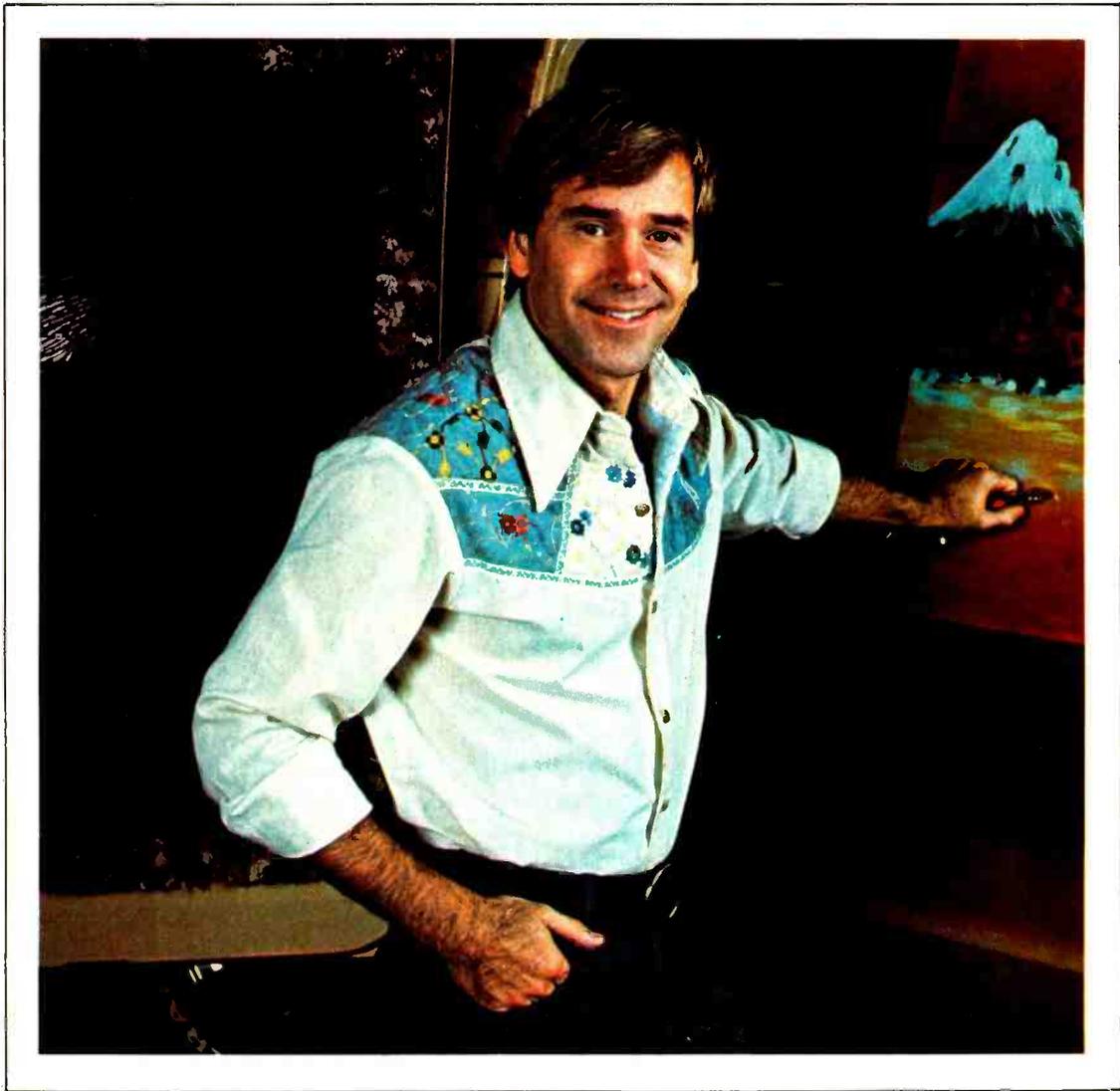

**When you do, you'll probably pick CIE.  
You can't afford to settle for  
less when it comes to something like  
electronics training that could  
affect your whole life.**

**W**hen you shop around for tires, you look for a bargain. After all, if it's the same brand, better price — why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

\* \* \*

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

### Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type — with serious career goals in electronics — take a close look at what we've planned for you at CIE.

### What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries — on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them — before you start using them!

### How practical is the training?

This is the next big important question. After all, your career will be built on what you can do — and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

**With CIE's Experimental Electronics Laboratory...**



you learn and review the basics — perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



**When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope** you take your first real professional step. You use it as a doctor uses an X-ray machine — to "read" waveform patterns... lock them in... study, understand and interpret them!

**When you get your Zenith 19-inch Diagonal Solid-State Color TV** you



Pattern simulated.

apply your new skills to some real on-the-job-type troubleshooting! You learn to trace signal flow... locate malfunctions... restore perfect operating standards — just as with any sophisticated electronics equipment!



**When you work with a completely Solid-State Color Bar Generator** — actually a TV signal transmitter — you study up to ten different patterns on your TV screen... explore digital logic circuits... observe the action of a crystal-controlled oscillator!

Of course, CIE offers a more advanced training program, too. But the main point is

simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

### Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

For some troubleshooting jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of specific knowledge and skills!

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

### Shop around... but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon — or write: CIE, 1776 East 17th St., Cleveland, OH 44114.

## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member: National Home Study Council

**YES...** I'm shopping around for the **right** kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information! RE-42

Print Name \_\_\_\_\_  
Address \_\_\_\_\_ Apt. \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_  
Age \_\_\_\_\_ Phone \_\_\_\_\_ (area code)

Check box for G.I. Bill information:  
 Veteran  Active Duty

**Mail today!**

# Learn Electronics along with MATHEMATICS

The Grantham Electronics -With-Mathematics SERIES — in five volumes, written in *home-study-course* style — now available by mail order...

- Introductory Electricity With Mathematics. Size, 7 x 10½. 288 p... \$12.75
- Fundamental Properties of AC Circuits. Size, 7 x 10½. 267 pages . . . . . \$12.75
- Mathematics for Basic Circuit Analysis. Size, 7 x 10½. 352 pages . . . \$12.75
- Basic Electronic Devices and Circuits. Size, 7 x 10½. 431 pages . . . . . \$14.75
- Antennas, Transmission Lines, & Microwaves. Size, 7 x 10½. 315 pages . . . . . \$12.75

The books listed above were written by Donald J. Grantham, whose 25 years of teaching—in print and in the classroom—enable him to anticipate questions in these subjects and thus answer them in these books: 16 lessons and 16 multiple-choice tests in each book (except for the last one, which has ten lessons and ten tests); many circuit diagrams with detailed explanations; many sample problems with step-by-step solutions; many practice problems with answers given; easy-to-understand language; *in-depth* explanations. Order from *GSE Book Company*—at address below.

## Prepare for Your F.C.C. LICENSE

- Grantham's FCC License Study Guide. Size, 7 x 10½. 377 pages . . . . . \$12.75

This not a Q & A book, not a correspondence course, but simply an authoritative down-to-earth presentation of what you should know to pass FCC license exams for 3rd, 2nd, and 1st class radiotelephone licenses. Four information sections. 1465 FCC-type multiple-choice questions, with more than 65,000 words "explaining" the correct answers. Self-study presentation. Order from GSE —address at bottom of page.

## OTHER GSE BOOKS

- Improve Your Technical Communication (How to write technical reports, manuals, proposals, articles, etc.). Size, 7 x 10½. 216 pages . . . . . \$4.95
- Geometry for Science and Technology. Size, 7 x 10½. 141 pages . . . . . \$5.95
- Modern Electronic Calculations. Size, 7 x 10½. 207 pages . . . . . \$6.95
- Answers in the Mail (The author, a correspondence instructor in electronics, physics, and math, gives examples of questions written in by students, along with his detailed replies.) Size, 6 x 9. 217 pages . . . . . \$4.95

**TO ORDER** any of the books listed above, check off the ones you want, compute the total price, *add only 75c* (regardless of the number of books you are ordering) for postage and handling, and mail this ad with your name and address and payment (no C.O.D.s) to:

**GSE Book Company**  
(2000 Stoner Avenue)  
P.O. Box 25992, Los Angeles, CA 90025

## LETTERS

*continued from page 16*

since you will have only one or two watts to work with.

5. Don't expect concert-hall sound from TV programs. Most TV stations compress the audio rather tightly, and the frequency response is about 100 Hz to 5 kHz, mainly due to the narrowband telephone lines used by the networks in their audio links. You will, nonetheless, overcome the worst villain in TV sound reception—the obnoxious resonances and distortion characteristics of the small speakers used in most sets.

MICHAEL KILEY  
Palos Heights, IL

## DIGITAL CLOCKS

I enjoyed the article "Unusual Electronic Clocks" (April, 1978, page 40) since I have constructed many digital clock kits from past articles.

The electronic designs are unique, but the designers do not seem to understand the geometry of a mechanical clock's pendulum. The centers of the pendulum radii are too low to make it a realistic "swing." Mechanical pendulum centers are around the "12 o'clock" position. The Bullet clock is the worst offender.

There is also a serious problem in the mechanism of the face of the Amelect Grandfather Clock. The hours *only* advance when the minutes reach 60, so that when the minutes are at say 55, you do not know what hour it is five minutes before.

The hours should progress 1/60th for every 12 minutes, just as a mechanical clock does.

HAROLD CORNELL  
Big Flats, NY

*Regarding your comments about the physical appearance of the electronic pendulums of the Amelect, Bullet and Solid State Time clocks, I can only assume that, similar to myself and others, the designers of these electronic simulations were not aware of the normal mechanical parameters associated with pendulum geometry.*

*As for the Amelect clock not having more hourly positions, this was certainly a reasonable design compromise to reduce the components count (your suggestion would require 48 more LED's) and design complexity (extra counting circuitry would be needed). If you simply read hours, minutes and seconds in that sequence, there's no ambiguity.*

FRED BLECHMAN

## COMPUTER CORNER ERROR

The Computer Corner column in the February 1978 issue uses an erroneous example for the relative addressing mode. The machine instruction given (30EE<sub>16</sub>) will jump to address 9F0<sub>16</sub>, since EE<sub>16</sub> equates to a displacement of -18<sub>10</sub>. To jump from address 1002<sub>16</sub> to 10F0<sub>16</sub> would require a displacement of 238<sub>10</sub>, which is outside the range of this addressing mode.

ROGER J. HENN  
Offutt AFB, NE

*As the text preceding the example indicates, a displacement of 238<sub>10</sub> is outside the range of the relative jump. Mr. Henn is correct in stating that the example is wrong. The example should have read:*

```
JR NC, 1080H 00110000 01111110
                    byte 1  byte 2
JR instruction is at location 100016. A
jump is executed if carry flag = 0. The
jump address is 100216 (program counter
contents) + 7E16 or 108616.
```

*However, Mr. Henn's correction is in itself wrong. The machine instruction 30EE will jump to FF0<sub>16</sub> rather than 9F0<sub>16</sub>. Score two more victims (Mr. Henn and me) for the rigors of hand-assembling instructions. A microcomputer would never have made the error.*

WILLIAM BARDEN

## REAL ENERGY CRISIS

In the editorial in the April issue of *Radio-Electronics*, you say that you would like to have intensive work carried out to raise the efficiency of photovoltaic cells to 50%.

It may surprise you, as indeed it surprised me, to learn that it is physically impossible even to reach 30%.

You will agree that the theoretical maximum efficiency of an internal combustion engine is a figure quite a bit lower than 100% and that there is just no way to exceed this.

I would suggest that while work on alternative forms of energy proceeds, the waste of petroleum should be slowed down.

G. W. SMILES  
Ontario, Canada

R-E

**FREE**  
- SHOP SUPPLIES

**NATCAM**  
**catalog**  
Shopping center for small and precision tools

A fine selection of small tools, measuring instruments, hard-to-find items for shop, home and lab. Convenient one-stop shopping for technicians, engineers, craftsmen, hobbyists. Major credit cards accepted, satisfaction assured. Get your NATCAM catalog today.

**National Camera, Inc.**  
2000 West Union Ave., Dept. GBF  
Englewood CO 80110 USA

CIRCLE 14 ON FREE INFORMATION CARD

# Radio Shack: No. 1 Parts Place

## Low Prices and New Items Everyday!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Always count on Radio Shack for the finest quality electronic parts!

### Linear ICs

By National Semiconductor and Motorola — first quality

Type	Cat. No.	ONLY
301CN	276-017	49¢
324N	276-1711	1.49
339N	276-1712	1.49
386CN	276-1731	99¢
555CN	276-1723	79¢
566CN	276-1728	1.39
566CN	276-1724	1.89
567CN	276-1721	1.99
723CN	276-1740	69¢
741CN	276-007	49¢
741H	276-010	49¢
3900N	276-1713	99¢
3909N	276-1705	99¢
3911N	276-1706	1.99
4558CN	276-038	79¢
75491	276-1701	99¢
75492	276-1702	99¢
7805	276-1770	1.29
7812	276-1771	1.29
7815	276-1772	1.29

### Computer Chip



**8-Bit Data Bus, 16-Bit Address Bus**  
**8080A Microprocessor.** 100% prime CPU handles up to 65K bytes memory. 276-2510. Reg. 17.95 ..... **Sale 12.95**

### RAM Memory IC



**Under 450 nS Access Time**

**2102 1K Static RAM.** Low power version. 16-pin DIP. Buy 8 and save! 276-2501 ..... **2.49 Ea. or 8/14.95**

### TTL and CMOS Logic ICs

Full-Spec Devices Direct from Motorola and National Semiconductor



Type	Cat. No.	ONLY
7400	276-1801	35¢
7402	276-1811	35¢
7404	276-1802	35¢
7406	276-1821	49¢
7410	276-1807	39¢
7413	276-1815	79¢
7420	276-1809	39¢
7427	276-1823	49¢
7432	276-1824	49¢
7441	276-1804	99¢
7447	276-1805	99¢
7448	276-1816	99¢
7451	276-1825	39¢
7473	276-1803	49¢
7474	276-1818	49¢
7475	276-1806	79¢
7476	276-1813	59¢
7485	276-1826	1.19
7486	276-1827	49¢
7490	276-1808	79¢
7492	276-1819	69¢
74123	276-1817	99¢
74145	276-1828	1.19
74150	276-1829	1.39
74154	276-1834	1.29
74192	276-1831	1.19
74193	276-1820	1.19
74194	276-1832	1.19
74196	276-1833	1.29
4001	276-2401	49¢
4011	276-2411	49¢
4013	276-2413	89¢
4017	276-2417	1.49
4020	276-2420	1.49
4027	276-2427	89¢
4049	276-2449	89¢
4050	276-2450	89¢
4511	276-2447	1.69
4518	276-2490	1.49

## NEW EDITION!

Update Your Semiconductor Library Now!




**BONUS OFFER**  
**Only 99¢**  
 With Any \$5 Parts Purchase

**REGULARLY \$1.95.** Archer® Semiconductor Reference and Application Handbook. Complete specs and application data on every Archer semiconductor — display devices, too! 46,000 cross-reference/substitution listings plus glossary of words, symbols, abbreviations. 276-4002 ... **With Any \$5 Parts Purchase, Only 99¢**

Offer good at participating Radio Shack stores and dealers

### Wire Wrapping Accessories

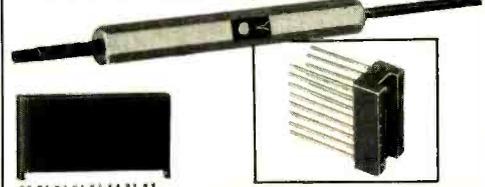

IC Socket Wrapping Tool. Strips and wraps 30-gauge wire. 276-1570 ..... **6.95**  
 14-Pin Wire Wrapping Sockets. 276-1993 ..... **2/1 29**  
 16-Pin Wire Wrapping Sockets. 276-1994 ..... **2/1 39**  
 DIP Header. 16 pins. 276-1980 ..... **1.29**  
 50' Red 30-ga. Kynar® Wire. 278-501 ..... **1.99**  
 50' White 30-ga. Kynar Wire. 278-502 ..... **1.99**  
 50' Blue 30-ga. Kynar Wire. 278-503 ..... **1.99**

### Metal Project Cabinets



**Slope Front.** Sloping top panel — ideal for lab projects. 1 3/8" to 2 3/4" x 7 7/8" x 5 7/8". 270-265 ..... **6.99**  
**Project Cabinet.** 20 ga. steel cover with 16 ga. aluminum chassis. 2 7/16" x 4 1/2" x 6 1/4". 270-268 ..... **5.99**  
 3 1/2" x 7 7/8" x 5 1/4". 270-269 ..... **7.99**

### Low-Cost Power Transformers

• Primaries Designed to Operate from 120VAC, 60 Hz  
 • Solder Lugs for Easy Wiring or PC Board Mounting

Volts	Current	Cat. No.	Each	Volts	Current	Cat. No.	Each
6.3	1.2A	273-050	2.49	6.3 CT	3A	273-1510	3.99
6.3	300 mA	273-1384	1.99	12.6 CT	3A	273-1511	4.69
12	300 mA	273-1385	1.99	25.2 CT	2A	273-1512	4.99
24	300 mA	273-1386	2.49	12	5A	273-1513	8.95
24	1.2A	273-1480	2.99	18 CT*	4A	273-1514	8.95
12.6 CT	1.2A	273-1505	2.89				

\*Ideal for 5V (using CT) or 12V solid-state regulators

### Solar Cell

**NEW**




**2 1/4" Round Silicon Device**

High efficiency — provides approximately 0.5 volt at 400 mA. For higher voltage or current outputs use several in series or parallel. 276-121 ..... **5.99**
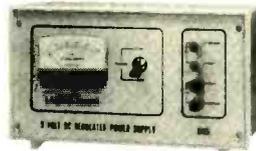
### Archer® Project-Boards — Ready to Build

All Include Finished Circuit Board, Front Panel Trim and Manual



**5V, 3-Amp Power Supply.** Metered output current, foldback limiting. Remote sensing. For all 5V TTL projects. 277-119 (PCB less parts, case) ..... **7.95**



**Time Base Generator.** Built-in 10 MHz xtal or ext. input. Decade selector, switch. TTL output. Requires 5VDC. Reg. \$5.99. 277-115. (PCB less parts, case) ..... **Sale 3.99**



**2-Watt IC Stereo Amp.** Uses LM377 IC for 2 watts RMS/channel into 8 ohms. Dual volume controls, headphone jack, phono/tape inputs. Output current limiting, thermal protection. Reg. \$5.99. 277-118. (PCB less parts, case) ..... **Sale 3.99**

Shown Built with Recommended Parts and Cases

### Electret Mike Element



Condenser mike element for new or replacement use. Built-in FET preamp. 30-15,000 Hz audio response. Requires 2 to 10VDC. 270-092 ..... **2.49**

### Epoxy-Glass Plug-In PC Boards




For 22-pin connectors. 4 1/2" x 4 1/2". 1/16" grid. 3 styles available. Standard. 276-155 ..... **4.99**  
 Digital. 276-156 ..... **4.99**  
 Op-Amp. 276-157 ..... **4.99**  
**22-Pin Connector.** 276-1551 ..... **2.99**

### High-Brightness Neon Panel Lamp



High-intensity rectangular lamp assembly can be seen across the room. Mounts in 3/16" dia. hole. For 120VAC. 272-706 ..... **1.89**

### Extra Length Test Clips

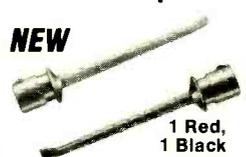

Ideal clips for precision testing of components on PC boards or chassis. 3" each. 270-352 ..... **Pkg. of 2, 1.59**

**WHY WAIT FOR MAIL ORDER DELIVERY? IN STOCK NOW AT OUR STORE NEAR YOU!**

# Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102  
 OVER 7000 LOCATIONS IN NINE COUNTRIES

Prices may vary at individual stores and dealers

# equipment report

## American Technology Corp. Model GTS-10 General Television Servicer



CIRCLE 101 ON FREE INFORMATION CARD

ABOUT TWO YEARS AGO, THE AMERICAN TECHNOLOGY Corporation (225 Main Street, Canon City, CO 81212) developed a color-bar generator, the *model ATC-10*, that they called a TV Servicing System. Now, we have the second generation, *model GTS-10*. It looks similar to

the earlier model at first glance, but there are significant differences. ATC has used the feedback received from TV technicians all over the country to make some changes. All the most useful functions of the earlier *model ATC-10* have been retained, some of the less-useful ones have been deleted and others have been added.

The *model GTS-10* still provides three color-bar patterns: The standard; the Vector (a color-bar pattern without the brightness component to create sharper "petals"; and the invaluable 3.58 Monitor. The latter pattern creates color bars with the burst gated-out so that the color oscillator can be checked without your having to add any jumpers, etc., to the set. The pure red raster is still there (for fast purity checks), and blue and green rasters have been added.

Another new feature is the Color Trio: The top half of the screen shows a saturated red, the lower left blue and the right green. All colors are fully saturated for checking the TV set's automatic color control, etc. This feature can also display a handy three-leaf vector pattern. For quick gray-scale adjustment, the Gray Quad pattern is divided into four seg-

ments—white, light gray, dark gray and black. This can be used to instantly check the video response, especially for low frequencies.

For convergence, the *model GTS-10* provides a special pattern called Hatchdots. This is a standard crosshatch, with dots in the squares around the outside of the pattern, and one center dot. If you prefer using dots only, they can be produced by using the next switch position. The center dot is marked by omission of the dots above and below it. And I almost forgot to mention that the sixth bar of all color-bar patterns is also marked by gating out a portion in the center. This gives positive identification of the blue bar for tint-control tests, etc.

All three input signals needed for TV servicing are present: RF, IF and video. The RF/IF control is the attenuator for both of these. To obtain an RF signal, push the gain-control knob in; for an IF signal, pull the knob out. Both RF and IF signals come out at the BNC jack just below and through the same output cable. Baluns are provided for the RF output so that any TV input can be matched. A pair of clips on the IF adapter lets you connect to the


*continued on page 27*


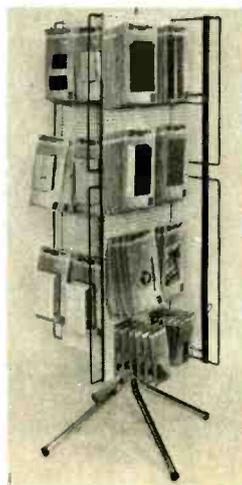
# It's All On The Cards

... and the deck is stacked in your favor. VERO, known throughout the industry for quality, is now offering a wide selection of electronic components for the serious hobbyist or home builder. These fine products have all passed the demanding requirements of one of the most demanding industries in the country — the electronics industry.

From basic breadboards to exciting enclosures, VERO products offer you proven capability and reliability *and* an affordable price. So, next time you are in the mood to build something



great, insist on the finest component parts — insist on VERO.

If your dealer does not stock VERO, drop us a line and we will send him all the necessary information required to get him started. You'll be doing him a favor if you do!



171 Bridge Road, Hauppauge, N.Y. 11787  
(516) 234-0400 TWX: 510-227-8890

# Fed up trying to find the right semiconductors? Look to the Mallory PTC line to help you out.

Your Mallory distributor has a complete up-to-date line of quality PTC semiconductors keyed to your needs.

He also has the Mallory complete semiconductor guide and cross reference to take the guesswork out of buying.

Components for the latest TV, stereo Hi-Fi, CB radio and many MRD applications are available now in convenient poly-bag pack-

ages. Contents are clearly marked, so you can't go wrong.

See your Mallory distributor for the convenience and economy of simplified one-source buying or contact us for more information. Mallory Capacitor/Distributor Products Company, a division of P. R. Mallory & Co. Inc., Box 1284, Indianapolis, Indiana 46206. (317) 856-3731.



# MALLORY

CIRCLE 29 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)



## For a limited time only WESTON offers this handsome carrying case...FREE...with any Model 6000 DMM you buy.

That's right! With any Weston Model 6000 DMM you buy between May 1 and August 31, you will get . . . absolutely FREE . . . this handsome, sturdy carrying case. Leather grained for a look of elegance, the expanded vinyl is rugged and easy to keep clean. The pouch style makes it simple to remove or replace the meter. The case, worth more than \$15, comes with a handle for easy carrying, and a snap-loop for hanging from a belt.

The Model 6000 is the renowned "Drop-Proofed" digital multimeter with standard built-in autoranging for its five measurement functions over 26 broad ranges. All ranges, including resistance, are provided with complete overload protection and automatic zero calibration.

The Model 6000 comes with a "Hold" feature to retain the LCD reading after the probe is removed. This allows measurements to be made in crowded circuitry or high voltage areas with greater safety. The meter is housed in a high impact molded plastic case to isolate inputs and to provide greater ruggedness and durability. The inside of the 6000 is coated with a conductive paint to shield the circuits

from industrial radio frequency interference noise and insure more accurate readings. A sturdy, patented plastic handle makes the meter easy to carry, acts as a tilt stand during bench operation, and folds down to protect the display face during storage.

The Model 6000 also has two new optional features . . . a manual range hold button to override autoranging, and a display backlight button for reading the meter in very low illumination areas.

You get all of these features in the Weston Model 6000 DMM . . . and you also get, absolutely FREE, a handsome, sturdy carrying case for extra protection. Be sure to get in on this FREE, limited-time offer. Call your nearest Weston sales office now!

SANGAMO WESTON

Schlumberger

WESTON INSTRUMENTS

a DIVISION of SANGAMO WESTON, INC.

614 Frelinghuysen Avenue, Newark, New Jersey 07114 Tel. (201) 242-2600

Canada: 1480 Dundas Highway, Mississauga, Ontario (416) 277-3191

Europe: Ingolstadter Str. 67a 8München 46, W. Germany (49-89) 31-70-31

CIRCLE 26 ON FREE INFORMATION CARD

www.americanradiohistory.com

**EQUIPMENT REPORTS**  
continued from page 24

TV set's IF input for tuner-substitution tests. The video output has its own output jack and control on the left of the front panel. The video signal level ranges from 0 volt to 1.6 volts P-P. Either positive-going or negative-going sync may be used. Again, just push or pull the control knob. This output is ideal for tests on either VTR's or video tape players. The Chroma control adjusts the saturation of the color bars. Pulling this control knob out turns on a 4.5-MHz signal for fine-tuning the TV set. The RF output is crystal-controlled on Channel 2 or Channel 3, this is optional. Signal levels can be varied from about 5  $\mu$ V to 100,000  $\mu$ V for an excellent check of tuner sensitivity, automatic-gain control, etc. Horizontal or vertical trigger signals are available at three front-panel jacks. This helps lock the scope patterns very solidly for easier evaluation. Both video and RF/IF outputs can be used simultaneously.

This instrument lets you make some fast signal-tracing tests through the color, video stages, etc. With a dual-trace scope, feed the video signal into the upper trace, then check the output of the stage on the lower trace. Any loss of gain, distortion, ringing, or other problems will show up instantly. Sync problems can be adjusted by injecting the RF/IF signal into the front end. This feature is handy for those sets that have a sync takeoff ahead of the video detector.

The 4.5-MHz and the 3.58-MHz outputs (actually, the latter is 3.579545 on the nose!) can be used to set the 4.5-MHz trap to eliminate beats (worms) in the color, as well as for correct fine-tuning of the TV receiver. Any of the video patterns can be used as a video signal from this output.

The problem of whether to "interlace or not interlace" signals in color-bar generators has been neatly solved—in the *model GTS-10* you can do either. In most older TV sets and many new ones, a noninterlaced signal yields more stable convergence patterns without a 30-Hz beat. In normal operation, the *model GTS-10*'s signals are not interlaced. However, some late-model sets using countdown circuitry do not operate well with a noninterlaced signal. So, for interlaced signals, just turn the function selector knob all the way to the last clockwise position marked # START I'LACE. This is a spring-return control, so after setting you can just release it. From then on, all the signals will be interlaced. For noninterlaced signals, turn the knob back counterclockwise to OFF and then back to ON, and there you are.

All video patterns, sweep signals, burst, etc.,

are developed by crystal oscillators and IC countdown circuitry. There are two master clock oscillators (used for different purposes)—one at 14.318182 MHz, the other at 14.255245 MHz (they are separated by four times the line-scanning frequency). The first is counted down to give a precise frequency of 3.579545 MHz, the standard color-oscillator reference frequency used in broadcasting. A total of five crystal oscillators are used.

The instruction manuals are worthy of special mention—they are a two-volume set! The first manual, entitled *In The Home Servicing*, is small and discusses in great detail the many previously rough tests that can be made with the *model GTS-10*: video frequency response, tuner sensitivity, automatic-gain control action, color-oscillator check or setup, and many others. Volume 2, entitled *In-Shop Servicing*, shows bench-type tests using a scope. With a dual-trace scope, you can make instant in-out signal-tracing tests of any TV stage—video, color, etc. For instance, as mentioned before, you can feed the video signal into the top trace and the stage output to the lower trace. Stage gain, frequency response, distortion and even that most difficult test, phase-shift—all can be read off the screen. Any of the video or color patterns can be used for these tests. Vector-scope analysis is equally simple, especially with a dual-trace scope.

Full calibration data is also given, if it is ever needed, plus simple accuracy tests for clock oscillators, etc. The schematic diagram is included, as well as 8 pages of logic diagrams for all circuits. The *model GTS-10* uses standard transistors and IC's, and is covered by a two-year warranty.

All test leads and cables stow in a compartment in the back of the handy, all-metal case, which also has aluminum side bars to protect the front panel plus a carrying strap.

By the way, the first instruction manual shows how you can instantly identify those pesky hum-bars and crawling lines in the TV picture. (These could be caused by the TV set itself or by the input signal from CATV/MATV systems.) Just place one of the convergence patterns of the *model GTS-10* on the TV set. If the bars are still there, with the control knob set to interlace, and the signals originate in the TV set, the bars will crawl slowly up the screen. Switch to the noninterlace position on the switch, the bars move down. This gives positive proof that the bars are caused by a fault in the TV set itself and not by the cable system. To see shading bars at their worst, select the Vector and noninterlace positions. This instrument is handy for bench troubleshooting.

The price tag on the *model GTS-10* is \$349. **R-E**

# WESTON® FREE Case Offer

Contact Your Nearest Distributor

- ALABAMA**  
Brownell Electro  
Mobile (205) 765-2222  
Cramer/Alabama  
Huntsville (205) 539-5722  
Forbes  
Decatur (205) 353-4762
- ARIZONA**  
Cramer/Arizona  
Phoenix (602) 263-1112
- CALIFORNIA**  
Acro  
San Diego (714) 282-8115  
Cramer/Los Angeles  
Irvine (714) 979-3000  
Cramer/San Diego  
San Diego (714) 565-1881  
Cramer/San Francisco  
Sunnyvale (408) 739-3011  
Dunlap Electronics  
Sacramento (916) 444-8070  
Metermaster, Inc.  
Palo Alto (415) 968-0313  
Metermaster, Inc.  
Los Angeles (213) 685-4340  
Wemco  
Oakland (415) 452-1936  
Western Electronics Supply  
Glendale (213) 849-3451
- COLORADO**  
Cramer/Denver  
Denver (303) 758-2100
- CONNECTICUT**  
Cramer/Connecticut  
North Haven (203) 239-5641  
The Mancini Company  
Middletown (203) 346-6646
- FLORIDA**  
Brownell Electro, Inc.  
Orlando (305) 843-6775  
Cramer/E. W. Hollywood  
Hollywood (305) 923-8181  
Cramer/E. W. Orlando  
Orlando (305) 894-1511
- GEORGIA**  
Brownell Electro, Inc.  
Atlanta (Hapeville) (404) 762-6181  
Cramer/Atlanta  
Norcross (404) 448-9050
- ILLINOIS**  
Cramer/Chicago  
Mt. Prospect (312) 593-8230  
Newark Electronics Corp.  
Chicago (312) 638-4411  
McNamara Supply  
Chicago (312) 922-5032  
Pacific Indicator  
Oak Park (312) 261-1330  
W. H. Leary Co.  
Chicago (312) 721-3832
- LOUISIANA**  
Butler & Land, Inc.  
Kenner (504) 722-6363  
Industrial Electronic Supply  
Shreveport (318) 222-9459  
Industrial Instruments Works  
Harahan (504) 733-8355  
Ralph Electronics  
Lafayette (318) 234-4507
- MARYLAND**  
Cramer/E. W. Washington  
Gaithersburg (301) 948-0110  
Cramer/E. W. Baltimore  
Hanover (301) 796-5790  
Pioneer Instrumentation  
Gaithersburg (301) 948-1012
- MASSACHUSETTS**  
Brownell Electro, Inc.  
Cambridge (617) 864-7500  
Cramer Electronics, Inc.  
Newton (617) 969-7700  
Metermaster  
Billerica (617) 667-8346
- MICHIGAN**  
Ram Meter, Inc.  
Ferndale (313) 547-1000
- MINNESOTA**  
Cramer/Bonn  
Edina (612) 835-7811  
Instrumentation Services, Inc.  
Minneapolis (612) 544-8916
- MISSOURI**  
Industrial Service Labs  
St. Louis (314) 533-5760  
Olive Electronics  
St. Louis
- MONTANA**  
Flamand Electronics Supply  
Belgrade (406) 388-6606
- NEW JERSEY**  
Brownell Electro, Inc.  
South Plainfield (201) 753-4600  
Cramer/Pennsylvania  
Cherry Hill (609) 424-5993  
Cramer/New Jersey  
Moonachie (201) 935-5600
- NEW MEXICO**  
Cramer/New Mexico  
Albuquerque (505) 265-5767
- NEW YORK**  
Baldwin Hall Co., Inc.  
Syracuse (315) 463-9251  
Cramer/Long Island  
Hauppauge (516) 231-5600  
Cramer/Rochester, Inc.  
Rochester (716) 275-0300  
Cramer/Syracuse  
Syracuse (315) 437-6671  
Electronic Devices Co.  
Albuquerque (505) 293-1935  
E. E. Taylor Company, Inc.  
Albany (518) 489-5600  
Summit Distributors  
Buffalo (716) 884-3450  
Trott Electronics  
Ciarence (716) 634-8500
- NORTH CAROLINA**  
Cramer/Winston-Salem  
Winston-Salem (919) 725-8711
- OHIO**  
Cramer/Cleveland  
Cleveland (216) 248-8400  
Hughes-Peters, Inc.  
Columbus (614) 294-5351  
Pioneer  
Cleveland (216) 587-3600  
Pioneer/Dayton  
Dayton (513) 236-9900
- OKLAHOMA**  
Electronics Supply  
Oklahoma City (405) 232-5215  
Hunzicker Bros., Inc.  
Oklahoma City (405) 239-7771  
Tri-State Instrument Lab, Inc.  
Tulsa (918) 838-8883
- PENNSYLVANIA**  
Pioneer/Pittsburgh  
Pittsburgh (412) 782-2300  
Process Engineering  
Pittsburgh (412) 516-5050
- TEXAS**  
Butler & Land  
Houston (713) 464-4662  
Meters & Instruments  
Houston (713) 644-1631  
Straughn Electronics, Inc.  
Beaumont (713) 838-4563
- UTAH**  
Cramer/Utah  
Salt Lake City (801) 487-4131
- WASHINGTON**  
Almac/Stroum Electronics  
Seattle (206) 763-2300  
Branom Instrument Corp.  
Seattle (206) 762-6050  
Cramer/Seattle  
Seattle (206) 762-5755  
Elcher/Richards Co.  
Seattle (206) 523-7888
- WISCONSIN**  
Electro-Mechano Co.  
Milwaukee (414) 272-4050
- VIRGINIA**  
Instrument Technical Reps  
Richmond (804) 285-3931



I did not know they had Hi-Fi-stereo-Police here . . .

# Jim-pak<sup>®</sup>

electronic components

# One-Stop Component Center

## AUTHORIZED DEALERS

**ALABAMA**  
Mobile Lafayette Radio Electronics

**ALASKA**  
Anchorage Electronics Corp. of Alaska

**ARIZONA**  
Flagstaff Jim's Audio & Stereo Repair  
Fountain Hills P & C Communications  
Tempe Computerworld Inc.  
Sierra Vista B & S Electronics  
Yuma Yuma Electronics

**CALIFORNIA**  
Bellflower Earl's Hobby Shop  
Berkeley Al Lasher Electronics  
Brea Century Electronics  
Cypress SCR Electronics  
El Monte Kimball & Stark  
Fontana Fontana Electronics  
Fullerton Orvac Electronics Inc.  
Glendale Eagle Electronics  
Lake Tahoe, South CalPine Electronics  
Lancaster Consumer Electronics  
Long Beach Scott Radio Supply Inc.  
Mission Viejo Tower Electronics Corp.  
Modesto Computer Magic  
Monterey Zackit  
Oceanside Electronic Center  
Palmdale Radio Shack A.S.C. Palmdale  
Palo Alto Zack Electronics  
Pasadena Dow Radio Inc.  
Riverside Computer Center  
Sacramento Heathkit Electronic Center  
Sacramento The Radio Place  
Sacramento Zackit  
San Bernardino Inland Computer & Electronics

San Carlos J & H Outlet Store  
San Diego Radio Shack A.S.C. Mira Mesa  
San Diego Radio-Tronics Inc.  
San Fernando San Fernando Electronics  
San Francisco Zack Electronics  
San Francisco Zenith Distributing Corp.  
San Jose Quement Electronics  
San Luis Obispo Mid-State Electronic Supply  
San Rafael Electronics Plus  
Santa Barbara Lombard Electronics  
Santa Cruz Santa Cruz Electronics  
Santa Maria Caps Electronics  
Santa Monica Mission Control  
Sunnyvale Sunnyvale Electronics  
Torrance SE Electronics  
Vallejo Zackit  
Van Nuys Thrifty Electronics Supply  
Ventura Lombard's Electronics Inc.  
Walnut Creek Byte Shop of Walnut Creek  
Westminster JK Electronics  
Whittier D & S Electronics

**COLORADO**  
Aurora Com Co Electronics  
Steamboat Springs Norm's TV & Electronics

**CONNECTICUT**  
Bridgeport Bridgeport Computer

**FLORIDA**  
Ft. Lauderdale Computers For You  
Gainesville Lafayette Radio  
Lakeland Lakeland Specialty Electronics  
Orlando Altair Computer Center  
Tampa AMF Electronics  
Tampa Microcomputer Systems

**GEORGIA**  
Atlanta Atlanta Computer Mart

**HAWAII**  
Aiea Delcoms Hawaii  
Honolulu Integrated Circuit Supply

**IDAHO**  
Idaho Falls Audiotronics

**ILLINOIS**  
Carbondale Lafayette Radio  
Evanston Itty Bitty Machine Co.  
Evanston Tri-State Electronic Corp.  
Granite City Computer Systems Center  
Groveland Moyer Electronics  
Mount Prospect Tri-State Electronic Corp.  
Niles Computer Land  
Oak Park Spectronics Inc.  
Rockford Imperial Computer Systems  
Schaumburg Data Domain

**INDIANA**  
East Chicago Acro Electronics Corp.  
Hammond Quantum Computer Works

**IOWA**  
Clinton Bridge Elec. Computer Center  
Davenport Computer Store of Davenport  
Indianola Electronix Limited  
Kansas City Electronic Surplus Sales

**KANSAS (Continued)**  
Manhattan Communications Specialties Ltd.  
Wichita Amateur Radio Equipment Company

**KENTUCKY**  
Lexington Radio-Electronic Equipment Co.

**LOUISIANA**  
Baton Rouge Davis Electronics Supply Co.

**MARYLAND**  
Baltimore Computer Workshop of Baltimore  
Baltimore Everything Electronic  
La Vale J & M Electronics  
Rockville Computer Workshop  
Silver Spring Computers Etc.  
Towson Baynesville Electronic Inc.  
Towson Computers Etc.

**MASSACHUSETTS**  
Medford Tufts Electronics  
North Adams Electronics Supply Center  
Waltham Computer Mart Inc.  
Worcester RM Electronics Inc.

**MICHIGAN**  
Ann Arbor Airway Electronic Communications  
Flint Hobby Electronic Center  
Grand Rapids Micro Computer World  
Lansing Fulton Radio Supply Co.  
Mt. Clemens The Computer Store

**NEW YORK (Continued)**  
Rensselaer Com-Tech Electronics  
Rochester 2001 Microsystems  
Troy Trojan Electronics  
White Plains The Computer Corner  
Williamsville Hirsch Sales Co.

**NORTH CAROLINA**  
Durham Futureworld  
Greensboro Byte Shop  
Raleigh Byte Shop of Raleigh

**OHIO**  
Bucyrus Mead Electronics  
Cincinnati Digital Design  
Columbus Heathkit Electronic Center  
Dayton Altair Computer Center  
Reynoldsburg Universal Amateur Radio

**OKLAHOMA**  
Guymon Sound Service  
Oklahoma City Bits, Bytes & Micros  
Tulsa High Technology

**OREGON**  
Albany Oregon Ham Sales  
Beaverton Altair Computer Center  
Coos Bay Herrick Electronic  
Medford Portland Radio Supply  
Ontario Miller Electronics  
Portland Computer Pathways

**PENNSYLVANIA**  
Drexel Hill Kass Electronic Distributors  
Erie Warren Radio  
Hershey Microcomputer Systems Inc.  
Murrysville Computer Workshop of Pittsburgh

Phoenixville Stevens Electronics  
Pittsburgh Tydings Company  
Wilkesbore Hamline Electronics  
York G.Y.C. Company

**RHODE ISLAND**  
Cranston Jabbour Electronics City  
Pawtucket Jabbour Electronics City

**SOUTH CAROLINA**  
North Charleston Technical Services Inc.

**TENNESSEE**  
Chattanooga William's Data Comp Division  
Clarksville Masstronics  
Knoxville Byte Shop  
Memphis Bluff City Electronics  
Memphis Sere-Rose & Spencer Electronics  
Oak Ridge Computer Denn

**TEXAS**  
Amarillo Computer Encounters Inc.  
Dallas CompuShop  
Houston Altair Computer Center  
Houston Interactive Computers  
San Antonio Sherman Electronics Supply Inc.

**UTAH**  
Provo Alpine Electronic Supply Co.

**VIRGINIA**  
Alexandria Computer Hardware Store  
Alexandria Computers Plus Inc.  
Charlottesville Lafayette Electronics  
Hampton Lafayette Radio  
Richmond Computers-To-Go  
Roanoke The Computer Place  
Springfield Computer Workshop of North Virginia  
Virginia Beach Heathkit Electronic Center

**WASHINGTON**  
Bellevue Altair Computer Center  
Kennewick C & J Electronics  
Longview Progress Electronics  
Pasco Riverview Electronics  
Richland C & J Electronics  
Seattle C-Com  
Seattle Empire Electronics  
Spokane Personal Computers


**WEST VIRGINIA**  
Morgantown The Computer Corner  
Morgantown Electro Distributing Co.  
Ripley Thompson's Radio Shack

**CANADA**  
Alberta (Calgary) The Computer Shop  
Ontario (Willowdale) Home Computer Centre  
Quebec (Montreal) Wang's Microcenter

**PANAMA**  
Panama City Electrotecnia S.A.  
Panama City Sonitel, S.A.

**FRANCE**  
Paris Computer Boutique

**SINGAPORE**  
Inter-Trade (PTE) Ltd.

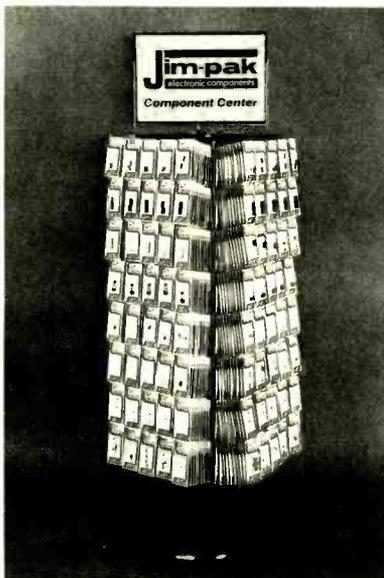

**MINNESOTA**  
Duluth Northwest Radio of Duluth  
Eagan Computer Room Inc.  
Hopkins Heathkit Electronic Center

**MISSOURI**  
El Dorado Springs Beckman Electronics  
Parkville Computer Workshop of Kansas City

**MONTANA**  
Billings Conley Radio Supply

**NEBRASKA**  
Lincoln Altair Computer Center  
North Platte Scott Radio Supply Corp.  
Omaha Omaha Computer Store

**NEVADA**  
Las Vegas Century 23

**NEW JERSEY**  
Bayville A.R.S. Communications Services  
Bricktown Radio Shack Associate Store  
Cherry Hill The Computer Emporium  
Hoboken Hoboken Computer Works  
Paterson All-tronics  
Pompton Lake Computer Corner of New Jersey  
Ramsey Typetronic Computer Store

**NEW YORK**  
Albany Fort Orange Electronics  
Kingston Greylock Electronics  
New York Computer Mart of New York

## SEE YOUR LOCAL Jim-pak<sup>®</sup> DEALER TODAY!

For Dealer Information, write or phone JIM-PAK<sup>®</sup>, 1021 Howard Ave., San Carlos, California 94070 (415) 592-8097

# BUILD

# Digital Thermometer

## Add-On for your DMM



*A simple, easy-to-build accessory converts your digital voltmeter into a handy thermometer for monitoring semiconductor case temperatures, photographic chemicals and numerous other uses around the lab, home and workbench.*

**BILL OWEN\***

HOW OFTEN HAVE YOU WORRIED ABOUT a component that was running hot to the touch? The part could be safely within specifications or in danger of burning out. If you include a digital thermometer as part of your test gear then you simply measure the component's temperature and check the data book for temperature limits. The capability to reliably and accurately measure temperature can also help to get a handle on more complex temperature problems such as specifying heat sinks, crystal oscillator drift and op-amp stability.

Several major manufacturers of digital multimeters now offer a thermometer option built in or as a separate accessory. Now you can build a simple thermometer conversion circuit for your digital voltmeter that is as good as any and better than most of the commercial units and at one-third the cost.

The temperature sensor is an integrated circuit developed by Analog Devices Inc. as a precision temperature-dependent current source. Of the many advantages this sensor enjoys over others, its accuracy of 0.5° and its range of from -55° to +150°C are most impressive. Because it is a current source with only two active leads, the sensor is virtually free from noise pickup even when remote over hundreds of feet of cable. Its tiny TO-52 metal-can transistor package allows for fast temperature response. Other features will be apparent as we use the temperature sensor to build the T-100

direct-reading thermometer.

The T-100 has a 10 mV-per-degree output that enables any digital or analog voltmeter to directly read Fahrenheit or Celsius by the flip of a switch. Resolution is to 0.1° with a 3½-digit voltmeter and to 0.01° with a 4¼-digit meter. Total current consumption is about 3 mA, giving the T-100 many hours of operation from an inexpensive 9-volt battery.

While we have mentioned only electronics, the T-100 is ideally suited for a wide variety of other applications. Simply dedicate a voltmeter to exclusive use and you have a thermometer to monitor inside, outside, aquarium, swimming pool, greenhouse, darkroom chemical, freezer, cooking, air conditioning and an almost infinite list of other temperatures.

### Circuit description

Figure 1 shows the AD590K temperature transducer's linear current output of 1 μA per degree Kelvin. The Kelvin degree is the same size as a Celsius degree; however, the Kelvin temperature scale is 273.16° higher than the Celsius scale. Zero degrees Kelvin is called absolute zero because it can be shown that colder temperatures cannot exist. There is also an absolute Fahrenheit temperature scale (Rankine) that is 459.69° higher than the regular Fahrenheit scale.

Figure 2 is the schematic of the thermometer accessory. The transducer's output current is scaled by the combination of resistors R10 and R11, or by R8 and R9 depending upon the position of the CELSIUS/FAHRENHEIT switch S1. The

voltage developed across scaling resistors R8 and R9 is equal to 10 mV per degree Kelvin or 10 mV per degree C + 2.73 volts. Similarly, the voltage across the R10, R11 combination is equal to 10 mV per degree F + 4.59 volts. These output voltages follow naturally from the Kelvin to Celsius and Kelvin to Fahrenheit conversion equations:

$$T \text{ Celsius} = T \text{ Kelvin} - 273.16^\circ$$

$$T \text{ Fahrenheit} = 9/5 T \text{ Kelvin} - 459.67^\circ$$

To read Celsius and Fahrenheit directly we must generate reference voltages of 2.73 and 4.59.

The LM334Z is a precision current source with a 2-mA output that is set by resistor R1. The current output is used to bias a LM329DZ precision 6.9-volt temperature compensated Zener reference.

This device is actually an integrated circuit with many advantages over the usual Zener diode. A big advantage is the low current level required (1 mA) for stable operation. The IC1/IC3 combination provides a very stable, low-power voltage reference for the voltage dividers. The voltage divider formed by R2, R3 and R4 generates the 2.73-volt reference and the divider formed by R5, R6 and R7 generates the 4.59-volt reference. The correct reference is selected by the switch S1 and connected to the "minus" output terminal. The thermometer's output then is the voltage difference between the + and - output terminals.

### Construction

Assembly of the thermometer circuit

\*Product Engineer, Optoelectronics, Inc., Ft. Lauderdale, FL

board is simple and straightforward. The foil pattern for the PC board is in Fig. 3 and the components placement is shown in Fig. 4. Trimmer resistors R3, R6, R9 and R11 are mounted on the foil side of the PC board. The thermometer shown here uses a custom aluminum enclosure for the circuit board and battery. The two slide switches were installed in the cabinet top and the PC board aligned for proper fit with the cabinet bottom before soldering. Grommets were fitted in each end of the cabinet top. Small diameter coax cable was inserted in the hole labeled PROBE and zip cord in the hole labeled VM in the cabinet top. The coax center conductor and shield are soldered to the PC connections labeled SIG and SHLD, respectively, in Fig. 4. The zip cord is soldered to the holes labeled OUT with the red banana plug soldered to the "+" wire and the black banana plug to the "-" wire. The 9-volt battery snap is connected to BATT holes with the red wire soldered to "+" and the black wire to "-"

The AD590K sensor was prepared by cutting off the case lead and staggering the + and - leads leaving the + lead longer. Figure 5 shows a cross section of the probe assembly. The sensor leads will not short together if the coax conductor and shield are staggered to match as shown. The shield lead is connected to the sensor's + lead. The sensor is soldered on the end of the coax and the connection potted in with epoxy glue to make it waterproof. A nylon shell was used to house the coax connection and provide a seal for the sensor. The shell was slid over the free end of the coax with the larger diameter end going on the cable first.

A 5-minute setting epoxy is used to pot the sensor. A very small amount was mixed and an even coat applied to the bottom of the sensor. The sensor was then held tightly against the end of the nylon shell and kept centered until the epoxy became set.

Next, an amount of epoxy to sufficiently fill the probe was thoroughly mixed. The probe tip was held down and epoxy was applied between the shell and coax using a toothpick. The epoxy flows down

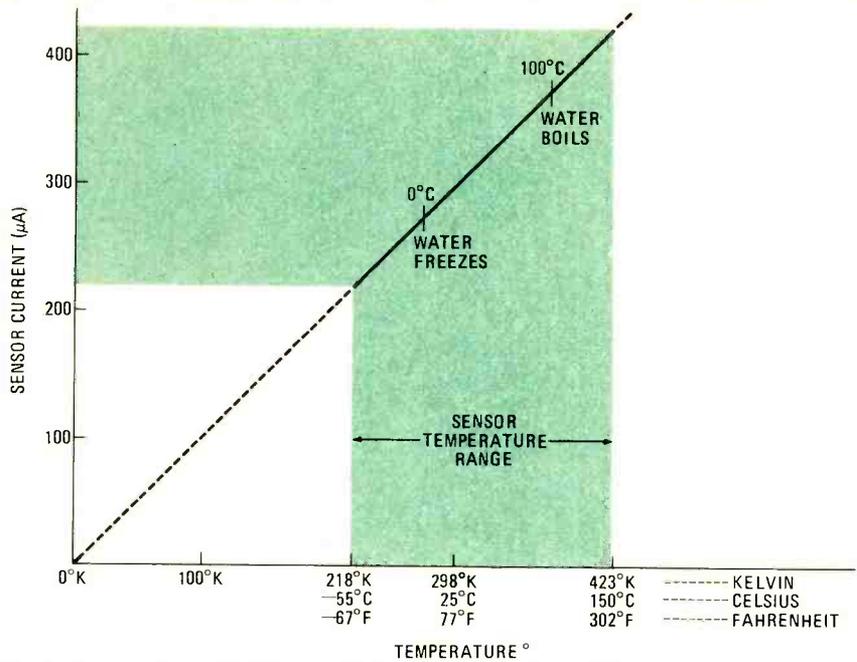


FIG. 1—CURRENT OUTPUT of the AD590 is linear at 1 µA per degree Kelvin.

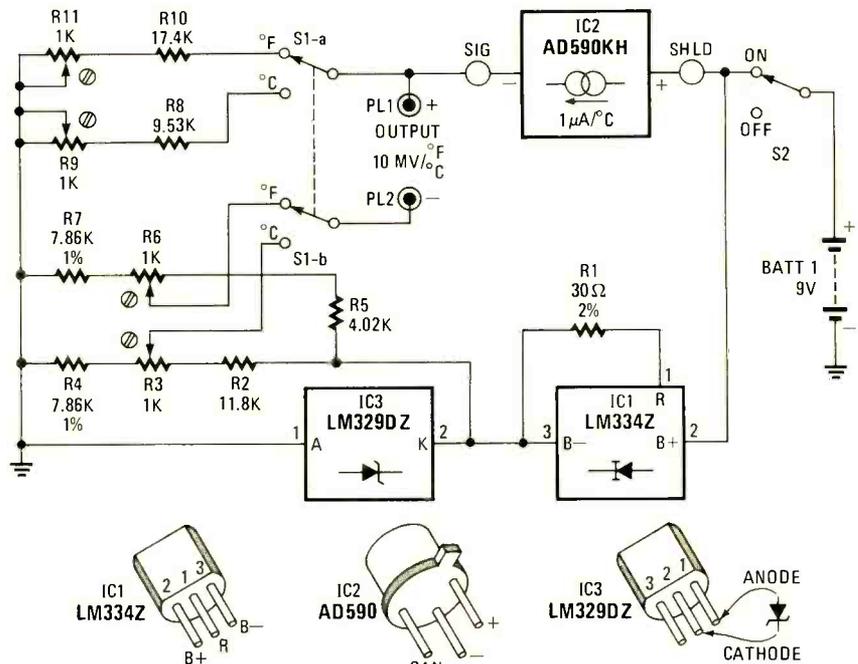


FIG. 2—SCHEMATIC OF THE T-100 thermometer accessory for a digital voltmeter. The circuit is essentially a resistive bridge with the temperature sensor as one of its legs.

### PARTS LIST

- R1—30 ohms, 2%
- R2—11,800 ohms, 1%
- R3, R6, R9, R11—1000 ohms PC mount trimmer potentiometer
- R4, R7—7860 ohms, 1%
- R5—4020 ohms, 1%
- R8—9530 ohms, 1%
- R10—17,400 ohms, 1%
- IC1—LM334Z constant-current source (National)
- IC2—AD590K linear temperature-dependent current source (Analog Devices)
- IC3—LM329DZ precision temperature-compensated voltage reference


- (National)
- S1, S2—miniature DPDT slide switch
- BATT1—9-volt battery, transistor radio type
- PL1, PL2—banana plugs, 1 red, 1 black
- Misc: RG-174/U coax, 4 feet or as needed; 2 feet of lightweight ZIP cord, nylon probe shell (see text), PC board, case screws and assorted hardware.

The following items are available from Optoelectronics, Inc., 5821 N.E. 14th Avenue, Ft. Lauderdale, FL 33334. Phones: (305) 771-2050 and 771-2051. Epoxy (used in probe assembly) and 9-volt battery must be purchased separately.

- Kit T-100RE—Complete parts kit less case and switches. \$30.00
- Kit CAB 10S—Deluxe prepunched gold anodized and screened aluminum cabinet with switches, screws, grommets and rubber feet. \$9.95.

- T-100WT—Factory-wired, tested and calibrated thermometer. \$59.95.
- TP-100K—Additional probe kit with 6 feet of coax. \$14.95.

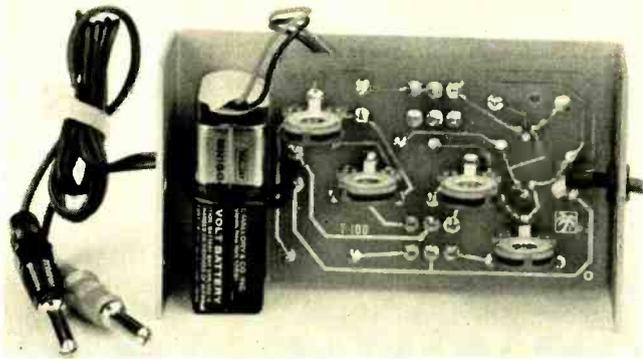Florida residents add state and local taxes as applicable.



**DIGITAL THERMOMETER** with rear cover removed shows internal layout. Note four trimmers are mounted on foil side of PC board.

the coax and into the space inside the shell. Tapping the probe tip on the table helps the epoxy flow. As the probe space fills, the epoxy seeps out of the vent holes in the sides of the shell. Any excess can be wiped away. Keep the coax centered in the end of the shell while the epoxy sets. Allow the epoxy to cure overnight before subjecting the probe to mechanical stress or excessive temperatures.

(The plastic probe shell is made from a 1-inch-long 1/4-inch O.D. plastic spacer with one end counterbored to accept the outside diameter of the RG-174/U coaxial cable. (See Fig. 5.) A reasonably good substitute can be made using 1/4-inch O.D. shrinkable tubing. Connect the cable to the sensor and fill the void in the tubing with the potting compound. When the compound has fully cured, apply just enough heat to shrink the tubing.—*Editor*)


### Calibration

The voltage reference in the thermometer can be more stable than the internal voltage references in some digital voltmeters. Calibration should be done with the voltmeter that will be used with the T-100.

Connect the negative voltmeter lead to thermometer ground. The center lugs (wipers) on trimmers R9 and R11 are grounded as is the black (negative) battery lead. Connect the voltmeter's positive lead to the center terminal on trimmer R3 and adjust R3 to read 2.73 volts. Move the voltmeter's positive lead over to the center terminal of trimmer R6 and adjust R6 to read 4.59 volts.


The thermometer's output is linear so calibration for the entire range can be performed at one known temperature. Although the AD590K had 0.5° linearity over its entire range, we have found that it is even more accurate between 0° and 100°C. This means that to realize the accuracy potential of the device, we should have a temperature standard accurate to 0.1°C or better. Certified thermometers accurate to 0.1° are expensive and not readily available. For calibration we must then rely on some less precise methods.

**Method 1.** A 50% mixture of water and

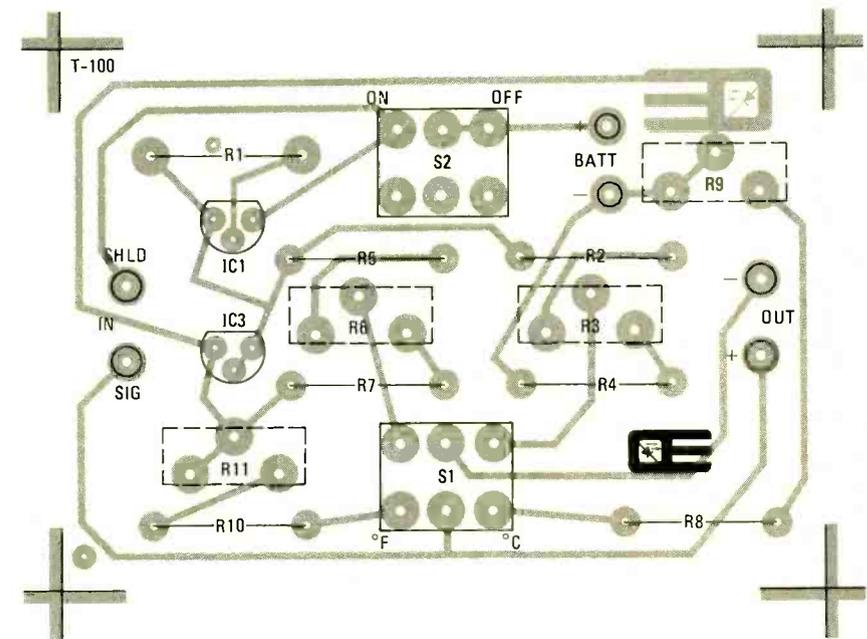

**FIG. 3—PRINTED CIRCUIT PATTERN** for the digital thermometer accessory.

**FIG. 4—THE PARTS LAYOUT** is an indication of the simplicity of the device.

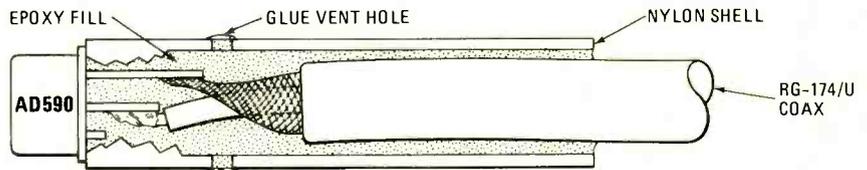

**FIG. 5—DETAILS OF THE PROBE ASSEMBLY.** The potting compound seals the probe against moisture and other contaminants.

crushed ice that is well stirred in a styrofoam container should come to equilibrium within 0.5°C of 0.0°C in 15 to 30 minutes.

**Method 2.** Boiling water, containing no chemical impurities at standard atmospheric pressure (29.92 inches of mercury) should come very close to 100.0°C. Altitude and pressure corrections must be made.

**Method 3.** A good-quality accurate clinical thermometer can be used to compare readings within its range. Errors arise in reading the thermometer as well as from trying to have two different sensors track a changing temperature

when they have differing time constants.

After calibration, the Celsius and Fahrenheit ranges on the thermometer should be reconciled using the conversion formulas:

$$T_F = 32^\circ F + 9/5 T_C$$

and

$$T_C = (T_F - 32) 5/9.$$

This completes the construction and calibration, and your thermometer accessory is ready to use. At first you'll probably have just one or two applications but as you become more familiar with it, the digital thermometer will become increasingly valuable.

R-E

# Investment Evaluation Program

FRED BLEECHMAN

HAVE YOU EVER MADE AN INVESTMENT IN stocks or metals and then wondered some time later if you would have been better off leaving the money in the bank? Or perhaps you'd like to know how much an investment must grow before it equals what you'd make leaving the money in the bank, at regular bank interest. The Investment Evaluation Program, written in TRS-80 Level I BASIC uses only 2464 bytes of RAM (Random Access Memory), so it can be run on the least expensive 4K RAM TRS-80.

The program is very straightforward, and has a handy subroutine for calculating the number of days between any two 20th century dates. The calculations are based on daily compounding of interest; if you want to change to monthly, quarterly or yearly compounding, you'll have to change lines 160, 170, 200, 250 and the subroutine starting at line 500.

Using the program is easy! After carefully entering and checking each line, type RUN and enter.

To illustrate, let's say that on July 20, 1974 you purchased 404 ounces of silver bullion for \$2098.38, including a service charge of 60¢ per ounce and 6% sales tax. You would like to know how the value of that bullion now compares with the same amount of money if it had been left in savings at, say, 5.25% annual interest, compounded daily. The day you want to calculate up to is July 1, 1978.

Set up the program on the computer and enter your name, social security number, 2098.38 invested at 5.25 as the questions are asked. Enter 0 for the days calculation, then enter 7,20,74 for the start date and 7,1,78 for the end date. The computer will tell you the number of investment days is 1442. Enter this number and the computer will print out, after about 40 seconds, the total interest (\$483.58) and the new principal of \$2581.80. (Don't mind the 16¢ error in addition of the interest and new principal. As a matter of fact, even the interest calculated is slightly off, due to rounding-off during the 1442 multiplications!).

Enter 404 for the number of ounces of silver bullion and the value of silver per ounce on the calculation end date—say, 5.28. The computer now displays that your investment is worth \$2133.12 and that you have now *lost* \$448.676 (there's that slight inaccuracy again!) compared to having left your money in your savings account. It also tells you that silver on that date would have to be worth \$6.39058 per ounce for you to just break even!

You can then press break to end the program, or perform another calculation. This same program can also be used to determine the future value of stock, bonds, gold, silver, etc., for break-even at some future date if you plan a particular investment. **R-E**

R-E will publish reader letters telling how to adopt this program to run on other hobby computers. Let us hear from you

```

100 CLS:P.
105 REM * COPYRIGHT 1978 FRED BLECHMAN * FOR TRS-80 I--4K *
110 P." INVESTMENT EVALUATION":P.:P.
112 P."THIS PROGRAM COMPARES AN INVESTMENT WITH PUTTING THE"
113 P."SAME AMOUNT OF MONEY IN A SAVINGS ACCOUNT WHERE IT EARNS"
114 P."DAILY INTEREST. IF YOU WISH TO CHANGE THE PERIOD TO"
115 P."MONTHLY OR YEARLY, CHANGE LINES 160,170,200 & 250. . . ."
116 P." . . . .AND THE SUBROUTINE STARTING AT LINE 500."
120 P.:P.
125 IN."WHAT IS YOUR FIRST NAME";A$
126 IN."WHAT IS YOUR SOCIAL SECURITY NUMBER";B$
130 A=0:B=0:C=0:D=0:E=0:F=0:G=0:H=0:I=0
131 J=0:K=0:L=0:M=0:N=0:O=0:P=0:Q=0:R=0
132 S=0:T=0:U=0:V=0:W=0:X=0:Y=0:Z=0
140 IN."WHAT IS THE DOLLAR AMOUNT INVESTED";P
150 IN."WHAT IS YOUR REGULAR SAVINGS INTEREST RATE(%);R
155 P.
160 P."HOW MANY DAYS ARE INVOLVED? IF YOU WANT THE NUMBER"
170 P."OF DAYS CALCULATED (20TH CENTURY ONLY) ENTER 0";D
180 IF D=0 GOSUB 500
185 IF D=0 GOTO 155
186 P.
190 P." . . . . .PATIENCE! . . . I'M CALCULATING THE ANSWER. . . ."
195 P." (TAKES ME ABOUT 10 SECONDS FOR 365 DAYS)"
200 S=R/36500:V=P
205 REM * CALCULATE INTEREST AND ADD TO PRINCIPAL *
210 FOR X=1 TO D
220 I=V*S:V=V+I:T=T+1
230 NEXT X
235 P.
240 P." THE TOTAL INTEREST IS";T
250 P."THE VALUE OF $";P;"AFTER";D;"DAYS AT";R;"% IS";V
255 P.
256 REM *COMPARE PRESENT VALUE OF INVESTMENT TO SAVINGS *
260 P."HOW MANY SHARES,BARS,OUNCES,ETC.,DO YOU OWN?"
265 IN." (TO RECALCULATE INVESTED AMOUNT,ENTER 0)";H
270 IF H=0 GOTO 130
275 P.
280 IN."WHAT IS THE PRESENT VALUE OF EACH SHARE,BAR,ETC.";M
290 Q=H*M
295 P.
300 P."YOUR INVESTMENT IS NOW WORTH $";Q;"";A$;" "
310 Z=V-Q
315 P.
320 IF Z>0 P.A$;"-";B$;" YOU HAVE LOST $";Z;"COMPARED TO SAVING!"
330 IF Z<0 P.A$;"-";B$;" YOU HAVE EARNED $";-Z;"MORE THAN SAVINGS!"
335 P.P."THE 'BREAK-EVEN' POINT IS $";V/H;"SHARES,BARS,ETC."
340 P.P."PRESS BREAK TO END PROGRAM. . . . ."
350 GOTO 130
360 END
500 REM * SUBROUTINE FOR CALCULATING DAYS *
510 DATA 0,31,28,31,30,31,30,31,31,30,31,30,31
520 REM * DETERMINE NUMBER OF DAYS FROM 0 TO START *
525 P.
530 IN."WHAT IS THE INVESTMENT START DATE(M,D,Y)";A,B,C
540 E=A
550 GOSUB 1000
560 F=F+B
570 G=F+C*365
580 REM * DETERMINE NUMBER OF DAYS FROM 0 TO END *
590 IN."WHAT IS THE INVESTMENT END DATE(M,D,Y)";J,K,L
600 E=J
610 GOSUB 1000
620 F=F+K
630 N=F+L*365
640 REM * CALCULATE AND ADD LEAP YEARS *
650 O=INT((L-1900)/4):U=INT((C-1900)/4):W=O-U
660 X=(N-G)+W
665 P.
670 P."THE NUMBER OF INVESTMENT DAYS IS";X
680 RETURN
1000 F=0
1010 FOR X=1 TO E
1020 READ Y
1030 IF Y=28 THEN IF (L/4)-INT(L/4)=0 THEN Y=29
1040 F=F+Y
1050 NEXT X
1060 RESTORE
1070 RETURN

```

# BUILD

## Digital Timer for your Darkroom

*The ideal timer for today's darkroom. This one counts down in your choice of minutes and seconds, or seconds only.*

RAYMOND G. KOSTANTY

LAST MONTH WE INTRODUCED THIS unique digital darkroom timer. In this issue we will complete the article, presenting the remaining construction details and final setup, test, and operating steps.

As stated, the timer's internal capacity is 8 digits. To alert you that more than 4 digits have been entered, the output of IC16-10, which is high if any digit is present, is combined with D5 in IC16 and used to unshort LED 3 (allowing it to light) if any digit is present in the D5 position.

In the minutes/seconds range, 41 must be subtracted each time a whole number of minutes (2:00, 5:00, etc.) is displayed. The zero-zero detector output, IC14-1, goes high if a zero is present in both D8 and D9 positions. Pin 11 of IC4 is low when a zero is detected. Recalling that D8 goes high before D9 does, IC15-4 will be high during D8 if a zero is present. Latch IC15-d remembers this high and enables IC14-6, the J input to a flip-flop. If the zero is also present during D9, IC15-3 will go high and clock IC14. This makes IC14-1 go high and enables IC8-13, which changes the normal —, delay, blank and 1 sequence to the required —, delay, 4 and 1 sequence. Latches IC14-a and IC15-b and d are reset each time IC6-3 is high.

Counter IC1 divides the 60-Hz square-wave generated on the power supply

board by 6 to produce 10 Hz. The PAUSE switch halts timer operation by grounding the base of Q1 and the clock pulses into IC1.

On the power supply board, Fig. 4, a 555 IC is connected as an astable oscillator to generate the audio tone when gated on by the signal at input K. The tone's frequency is inversely proportional to R6, R7 and C2.

The relay directly switches the line voltage to the low-power safelight outlet when de-energized, and indirectly switches line voltage via the triac to the high-power enlarger outlet when energized. The maximum load that can be connected to the enlarger outlet is determined solely by the triac rating. Heavier safelight loads can be driven by adding a second triac as shown in the Fig. 4 inset.

Transistor Q1 amplifies the half-wave rectified 60-Hz signal applied to its base and converts it to an approximate square-wave.

### Assembling the timer

Start assembly with the power supply. The board will accommodate speakers up to 2½ inches in diameter, but will be supplied with mounting holes for a 2-inch speaker. If using a larger speaker, drill one No. 28 hole (hole S in Fig. 9) such that the part of the hole closest to the speaker center is just tangent to the diameter of the speaker. Solder all small

components into their appropriate locations. If using a 309K as IC1, fasten it with two No. 6-32 × ⅜ screws with the head of one of them in firm contact with the foil which serves as the connection to the case of IC1, and install R1 and R2. Clip leads 1 and 2 to about ⅛ inch. Resistors R1 and R2 are not used when a 340-8 is used as IC1.

If the timer is to be used on 60-Hz power, do not use D2 or D3, but instead solder a jumper in the D2 position. (For 50-Hz operation, use a transformer with a 50-Hz or 50 to 60-Hz primary, and use D2 and D3, which will change the output of Q1 to 100 Hz. On the main board, cut the connection from IC1-1 to IC1-6, and jumper IC1-1 to IC1-13 to change IC1 to a decade divider to give the required 10-Hz output.) Mount the transformer with two No. 6-32 × ⅜ screws, again with the heads on the foil side. Solder the transformer, relay and IC2 in place. The IC may be soldered without a socket. The triac doesn't need a heat sink for loads up to 150 watts, and is supported by its leads. For loads between 150 and 600 watts, mount the triac on a heat sink whose thermal resistance doesn't exceed 3 °C-per-watt. In each of the three speaker holes, install a 6-32 × ⅜ screw, heads on the foil side, and fasten one nut firmly to each screw. If the holes were properly drilled, the speaker should be able to rest on the nuts just installed. Install one additional

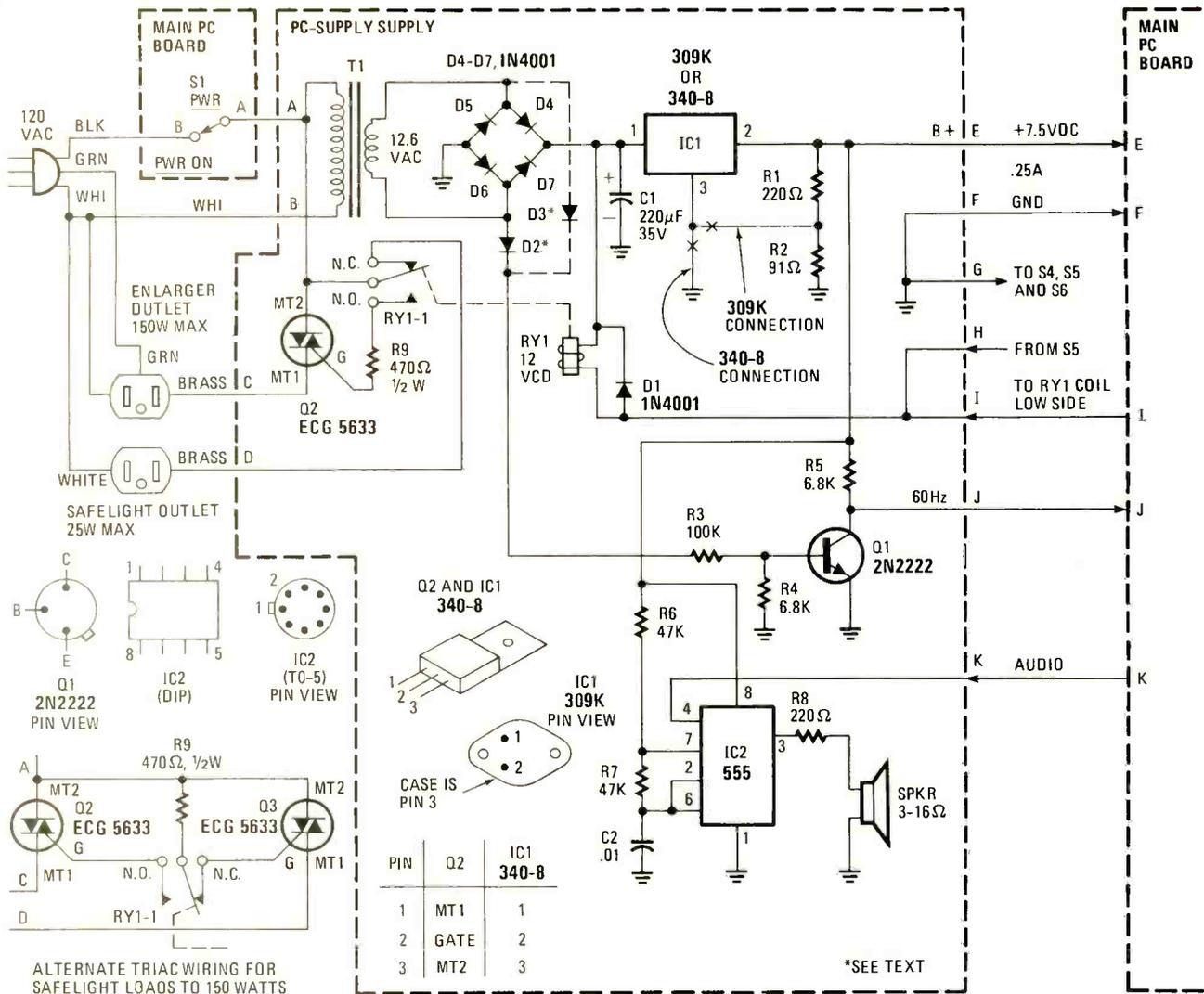


FIG. 4 (above)—POWER-SUPPLY CIRCUIT also contains the audio circuit that develops 1-second pulses.

FIG. 5 (left)—COMPONENTS SIDE of the main circuit board. Note the size marked.

FIG. 6 (bottom left)—FOIL PATTERN on the other side of the two-sided board.

nut on each screw to secure the speaker and solder the two speaker connections to their pads. Refer to Fig. 11 for details. Set the board aside.

Continue with the main board. Sockets are highly recommended for all IC's, and imperative for the calculator IC. The displays are installed in Molex *Soldercon* sockets. When using these sockets, do not press them directly against the board unless you are sure that they will not short to foil patterns running between them. All pushbuttons, rocker switches, LED's and displays go on one side, and the remaining parts and jumpers on the other. Mount components in this sequence: resistors, diodes, transistors, jumpers, capacitors and IC1-16's sockets. On the other side, mount the display's sockets and the three LED's. The LED's mentioned in the parts list were selected for their small diameter, .085 inch, and pleasing appearance. Their lead length, however, is only 0.25 inch. To raise the

## POWER SUPPLY PARTS LIST

All resistors 1/4 watt, 10%

- R1, R8—220 ohms
- R2—91 ohms
- R3—100,000 ohms
- R4, R5—6800 ohms
- R6, R7—47,000 ohms
- C1—220  $\mu$ F, 35 volts, electrolytic
- C2—.01  $\mu$ F
- Q1—2N222, RS-2031 (Radio Shack) or any NPN silicon transistor with a beta between 50 and 150
- Q2—200-volt, 10-amp triac. Sylvania ECG 5633 or equal
- Q3—Optional, same as Q2. See text.
- IC1—309K or 340-8 voltage regulator
- IC2—555 timer
- D1, D4—7—1N4001, Radio Shack 276-1101 or any 25-volt, 1-amp silicon diode
- D2, D3—Silicon diode, see text.
- RY1—Relay, SPDT contacts, 12-VDC coil. Guardian 1345-1C-12D, Essex 64-902 or Cornell-Dubilier 603-12V
- T1—Transformer, 120 volts to 12.6 volts, 300 mA. Radio Shack 273-1385 or equal
- Miscellaneous—Speaker, 3-16 ohms, 2-2 1/2 inches. Power cord, 8 feet, No. 18, 3 conductors. Strain relief.

tip of the LED's to the same height above the board as the 7-segment displays (0.6 inch), solder solid-wire extensions to the LED leads or use larger LED's. Finish by installing the switches. Do not install the IC's or displays at this time. Set the board aside.

The case can be easily made as shown in Figs. 10 and 11, or purchased ready-to-use. Strip about 18 inches of outer jacket from the line cord and install the cord through the side of the case with a strain


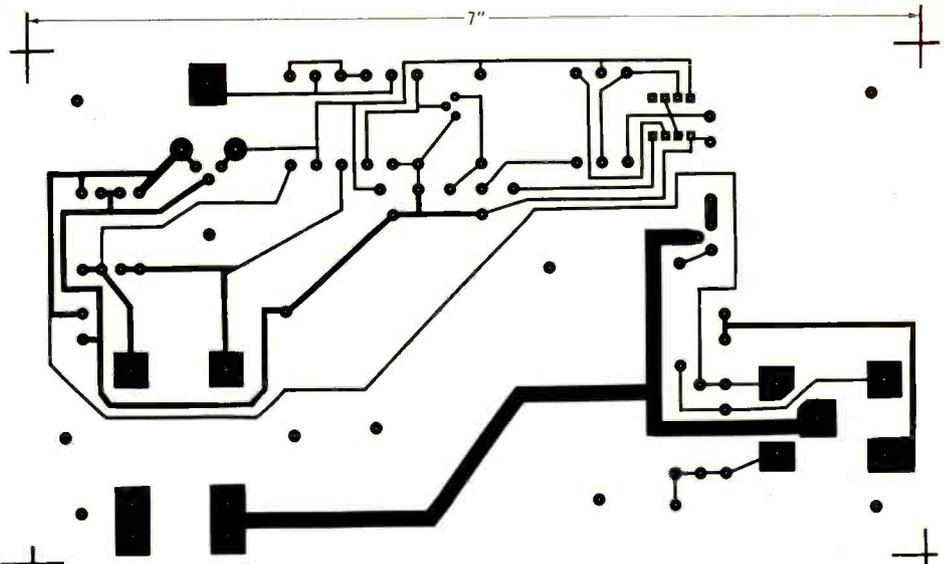


FIG. 7—THE POWER SUPPLY CIRCUIT BOARD is single-sided. Again, be sure to note the dimension across the top as this board is not drawn actual size.

relief. The duplex outlet will have 2 silvery screws in a silvery metal strip on its cold side, and a brass-colored metal strip with either 2 silver or 2 brass-colored screws on the hot side. Break the thin brass strip connecting the 2 screws on the hot side to isolate them from each other. Leave the 2 screws on the cold side in common with each other. Shorten the green and white leads on the line cord from 18 to 6 inches. Connect the green wire to the green screw on the outlet, and the white wire to one of the cold screws. Connect one end of the remaining 12 inches of white wire to the other cold screw, and the other end to one side of T1's primary (hole B in Fig. 9). Connect

one end of an 18-inch wire to each of the remaining holes on the power supply board. The wires to holes A and C should be No. 18 gauge. The remaining ones can be No. 24 or 26. Temporarily connect the wire from hole A to the black wire in the line cord. Interconnecting wires should be stranded.

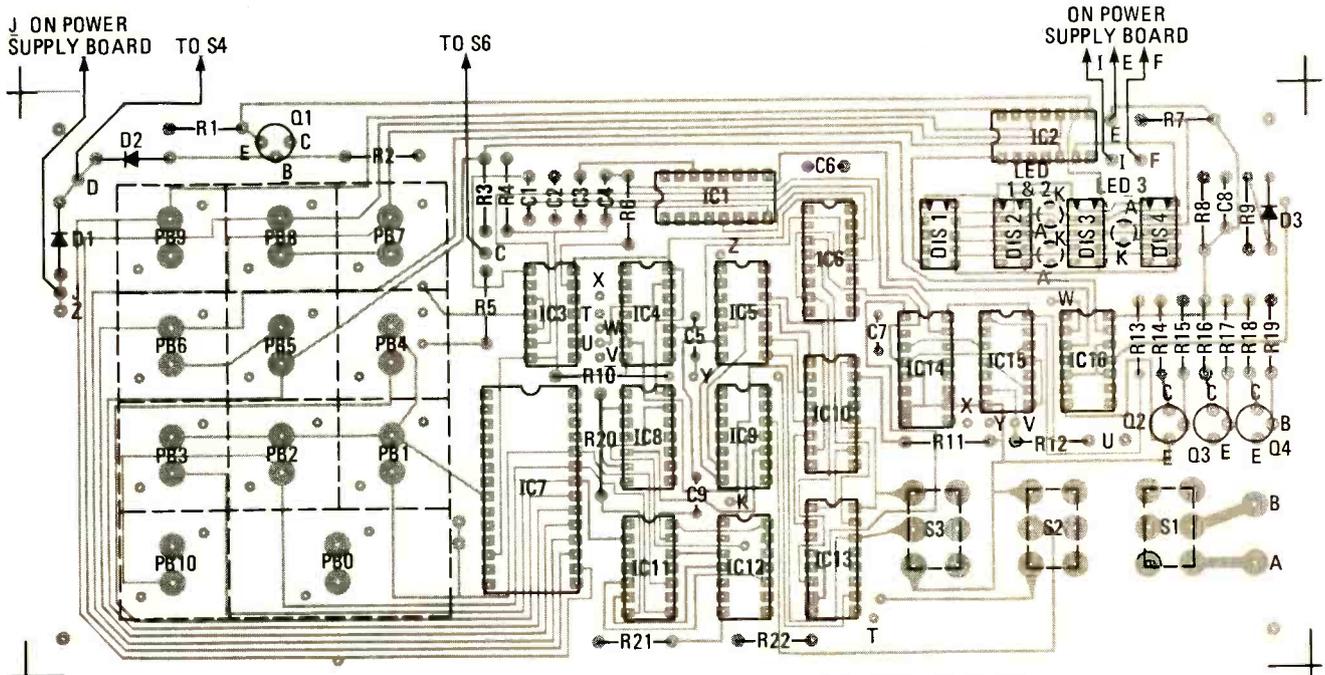Attach the board to the rear half of the case as shown in Fig. 11. Mount it so the transformer is toward the bottom of the case (when mounted on a wall). The outlets can be on either the right or left side to suit your darkroom's layout. Connect the No. 18 wire from the triac (hole C on the power supply board) to one of the unused hot screws on the outlet sock-



NOTE: HOLES A-A TO K-K ARE JUMPED EITHER TO POWER SUPPLY BOARD OR TO CABINET-MOUNTED COMPONENTS. HOLES T-T TO Z-Z ARE JUMPED TO EACH OTHER ON REAR SIDE OF BOARD.

FIG. 8—PARTS PLACEMENT ON THE MAIN CIRCUIT BOARD. Note that the keyboard mounts directly to this board too. As indicated, jumpers connect this board to the power supply board.

# VIDEO MODULATORS

*If you are into VTR's, TV games, home computers and TV modulator must be used to feed modulated RF to*


**FRED BLECHMAN K6UGT**



VD-1 by Ramsey




ATARI model CA-010410

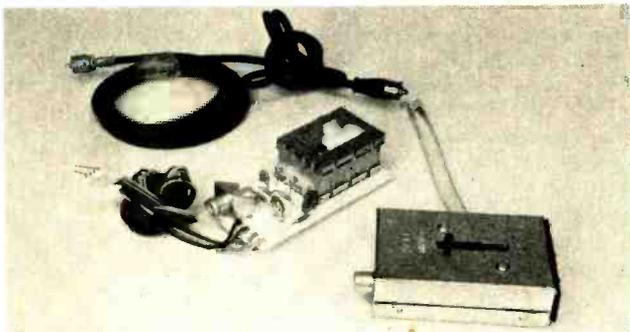


SUP "R" MOD II, cables and switch included



MODEL E & P

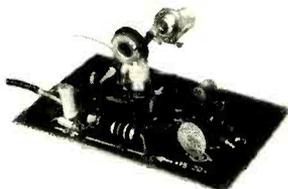

RF-1 RF modulator

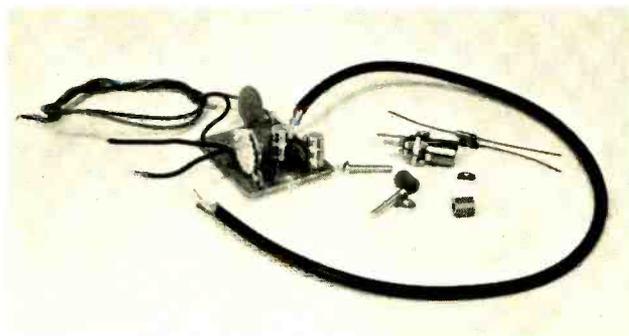

RFVM-1 sold by Vamp and Quest Electronics

IN THE LAST TWO YEARS FOUR "NEW" ELECTRONIC PRODUCTS have been introduced into the consumer marketplace—video games, video cassette recorders, video cameras and home computers. While these products have been available in some form for several years, their design finally became practical enough for consumer acceptance. Coincidentally, each product uses a video display for its output. A TV screen is essential for playing a video game or watching a video recorder, and most home computers use a video display for the readout, although printers can also be used. Video cameras, long used for closed-circuit security and surveillance systems, are growing in popularity now that video cassette recorders are available for making home movies, and, of course, cameras also use a video display.

Two basic methods make the video signal visible on a picture tube. The most efficient method is to feed the video output of a game, camera, video recorder or computer directly into the video amplifier of a video monitor or TV set. Since most TV sets require rewiring to provide direct access to the video amplifier (and those with a hot chassis can create a dangerous shock hazard), video monitors have generally been used. However, when home video games became popular, it was obvious that the public would not care to buy a special monitor to play the games. Therefore, an old video camera technique was revived—generating an RF signal on an unused TV channel and modulating it with the video signal! By connecting the modulated RF carrier to the antenna terminals of a standard TV set, you could watch the game by simply tuning to the unused channel.

In the beginning, video game manufacturers, to avoid interfering with VHF signals, created carriers in the high UHF band. Shielding problems, signal instability with temperature variation and other design considerations caused the shift to VHF carriers modulated by the video signal. Several million video games were sold (some for as little as \$25) complete with built-in video-modulated RF oscillators. The Federal Communications Commission (FCC) then cracked down on the manufacturers, requiring them to test units to rigorous specifications before type approval was issued, in order to try minimizing the spurious radiations being generated to neighboring TV sets—or even to other sets in the home!

With technological advances taking place in the game field, microprocessors and dedicated integrated circuits (IC's) became commonplace among experimenters. Home computers suddenly blossomed from garage and basement labs to full-blown manufacturing plants. Experimenters and hobbyists found an increasing need for some means to couple the video output of their devices to a display. Video monitors have remained a low-production item and are therefore high-priced. TV set manufacturers have not recognized the sales advantage of adding a switch and jack to existing designs to allow direct video input. Therefore, there has been a steadily increasing

# BUILD

## Digital Timer for your Darkroom

*The ideal timer for today's darkroom. This one counts down in your choice of minutes and seconds, or seconds only.*

RAYMOND G. KOSTANTY

LAST MONTH WE INTRODUCED THIS unique digital darkroom timer. In this issue we will complete the article, presenting the remaining construction details and final setup, test, and operating steps.

As stated, the timer's internal capacity is 8 digits. To alert you that more than 4 digits have been entered, the output of IC16-10, which is high if any digit is present, is combined with D5 in IC16 and used to unshort LED 3 (allowing it to light) if any digit is present in the D5 position.

In the minutes/seconds range, 41 must be subtracted each time a whole number of minutes (2:00, 5:00, etc.) is displayed. The zero-zero detector output, IC14-1, goes high if a zero is present in both D8 and D9 positions. Pin 11 of IC4 is low when a zero is detected. Recalling that D8 goes high before D9 does, IC15-4 will be high during D8 if a zero is present. Latch IC15-d remembers this high and enables IC14-6, the J input to a flip-flop. If the zero is also present during D9, IC15-3 will go high and clock IC14. This makes IC14-1 go high and enables IC8-13, which changes the normal —, delay, blank and 1 sequence to the required —, delay, 4 and 1 sequence. Latches IC14-a and IC15-b and d are reset each time IC6-3 is high.

Counter IC1 divides the 60-Hz square-wave generated on the power supply

board by 6 to produce 10 Hz. The PAUSE switch halts timer operation by grounding the base of Q1 and the clock pulses into IC1.

On the power supply board, Fig. 4, a 555 IC is connected as an astable oscillator to generate the audio tone when gated on by the signal at input K. The tone's frequency is inversely proportional to R6, R7 and C2.

The relay directly switches the line voltage to the low-power safelight outlet when de-energized, and indirectly switches line voltage via the triac to the high-power enlarger outlet when energized. The maximum load that can be connected to the enlarger outlet is determined solely by the triac rating. Heavier safelight loads can be driven by adding a second triac as shown in the Fig. 4 inset.

Transistor Q1 amplifies the half-wave rectified 60-Hz signal applied to its base and converts it to an approximate square-wave.

### Assembling the timer

Start assembly with the power supply. The board will accommodate speakers up to 2½ inches in diameter, but will be supplied with mounting holes for a 2-inch speaker. If using a larger speaker, drill one No. 28 hole (hole S in Fig. 9) such that the part of the hole closest to the speaker center is just tangent to the diameter of the speaker. Solder all small

components into their appropriate locations. If using a 309K as IC1, fasten it with two No. 6-32 × ⅜ screws with the head of one of them in firm contact with the foil which serves as the connection to the case of IC1, and install R1 and R2. Clip leads 1 and 2 to about ⅛ inch. Resistors R1 and R2 are not used when a 340-8 is used as IC1.

If the timer is to be used on 60-Hz power, do not use D2 or D3, but instead solder a jumper in the D2 position. (For 50-Hz operation, use a transformer with a 50-Hz or 50 to 60-Hz primary, and use D2 and D3, which will change the output of Q1 to 100 Hz. On the main board, cut the connection from IC1-1 to IC1-6, and jumper IC1-1 to IC1-13 to change IC1 to a decade divider to give the required 10-Hz output.) Mount the transformer with two No. 6-32 × ⅜ screws, again with the heads on the foil side. Solder the transformer, relay and IC2 in place. The IC may be soldered without a socket. The triac doesn't need a heat sink for loads up to 150 watts, and is supported by its leads. For loads between 150 and 600 watts, mount the triac on a heat sink whose thermal resistance doesn't exceed 3 °C-per-watt. In each of the three speaker holes, install a 6-32 × ⅜ screw, heads on the foil side, and fasten one nut firmly to each screw. If the holes were properly drilled, the speaker should be able to rest on the nuts just installed. Install one additional

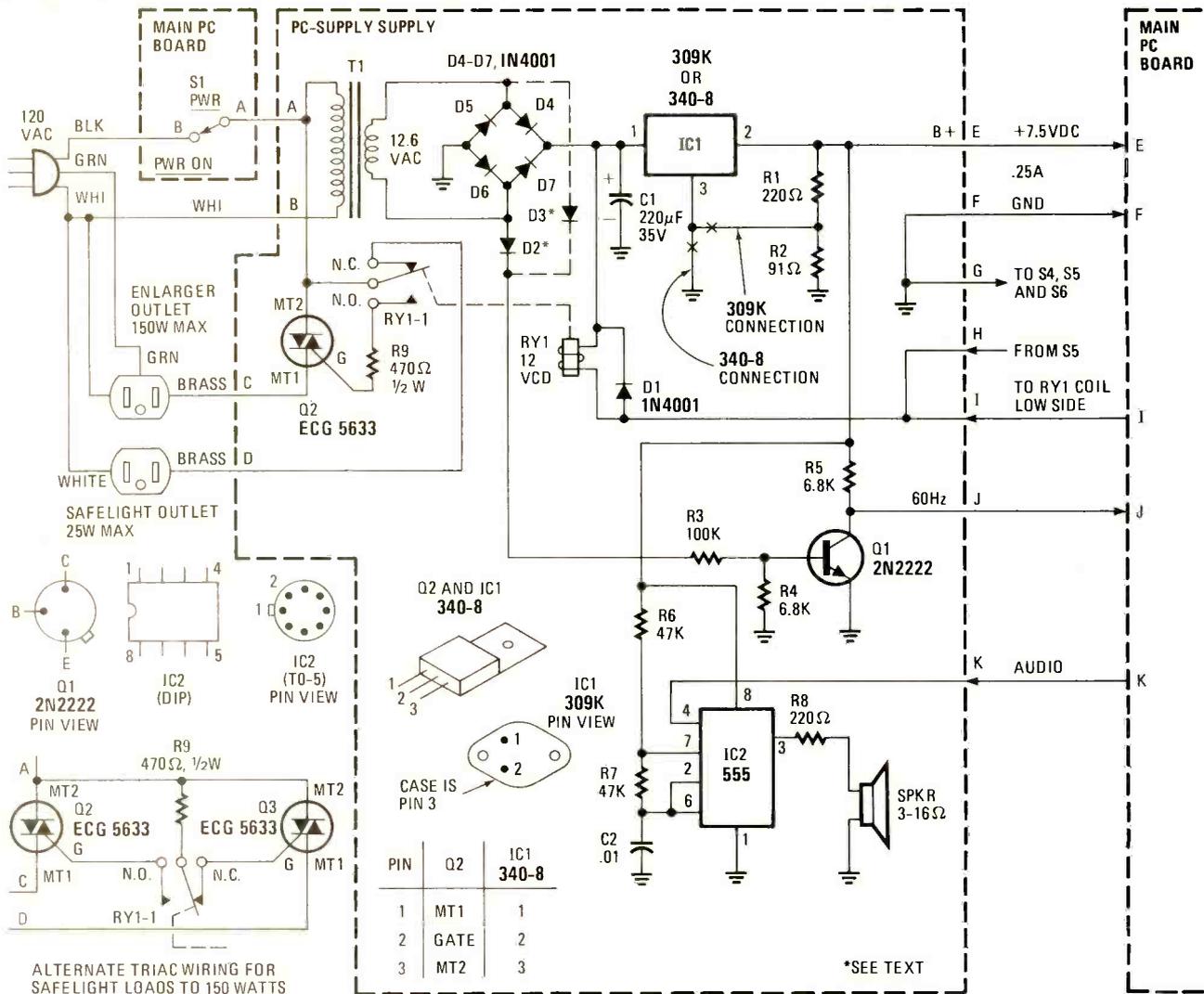


FIG. 4 (above)—POWER-SUPPLY CIRCUIT also contains the audio circuit that develops 1-second pulses.

FIG. 5 (left)—COMPONENTS SIDE of the main circuit board. Note the size marked.

FIG. 6 (bottom left)—FOIL PATTERN on the other side of the two-sided board.

nut on each screw to secure the speaker and solder the two speaker connections to their pads. Refer to Fig. 11 for details. Set the board aside.

Continue with the main board. Sockets are highly recommended for all IC's, and imperative for the calculator IC. The displays are installed in Molex *Soldercon* sockets. When using these sockets, do not press them directly against the board unless you are sure that they will not short to foil patterns running between them. All pushbuttons, rocker switches, LED's and displays go on one side, and the remaining parts and jumpers on the other. Mount components in this sequence: resistors, diodes, transistors, jumpers, capacitors and IC1-16's sockets. On the other side, mount the display's sockets and the three LED's. The LED's mentioned in the parts list were selected for their small diameter, .085 inch, and pleasing appearance. Their lead length, however, is only 0.25 inch. To raise the

## POWER SUPPLY PARTS LIST

All resistors 1/4 watt, 10%

R1, R8—220 ohms

R2—91 ohms

R3—100,000 ohms

R4, R5—6800 ohms

R6, R7—47,000 ohms

C1—220  $\mu$ F, 35 volts, electrolytic

C2—.01  $\mu$ F

Q1—2N222, RS-2031 (Radio Shack) or any NPN silicon transistor with a beta between 50 and 150

Q2—200-volt, 10-amp triac. Sylvania ECG 5633 or equal

Q3—Optional, same as Q2. See text.

IC1—309K or 340-8 voltage regulator

IC2—555 timer

D1, D4—7—1N4001, Radio Shack 276-1101 or any 25-volt, 1-amp silicon diode

D2, D3—Silicon diode, see text.

RY1—Relay, SPDT contacts, 12-VDC coil. Guardian 1345-1C-12D, Essex 64-902 or Cornell-Dubilier 603-12V

T1—Transformer, 120 volts to 12.6 volts, 300 mA. Radio Shack 273-1385 or equal

Miscellaneous—Speaker, 3—16 ohms, 2—2 1/2 inches. Power cord, 8 feet, No. 18, 3 conductors. Strain relief.

tip of the LED's to the same height above the board as the 7-segment displays (0.6 inch), solder solid-wire extensions to the LED leads or use larger LED's. Finish by installing the switches. Do not install the IC's or displays at this time. Set the board aside.

The case can be easily made as shown in Figs. 10 and 11, or purchased ready-to-use. Strip about 18 inches of outer jacket from the line cord and install the cord through the side of the case with a strain


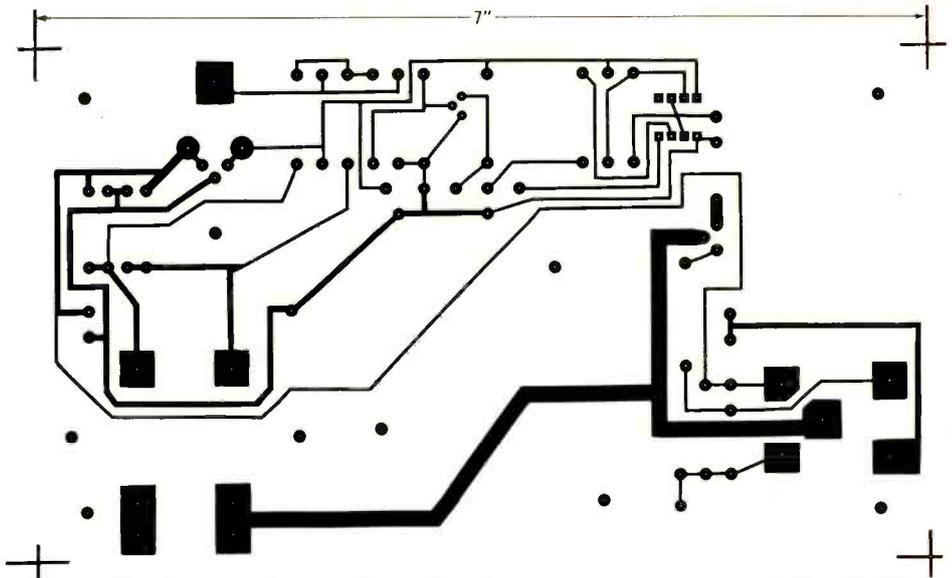


FIG. 7—THE POWER SUPPLY CIRCUIT BOARD is single-sided. Again, be sure to note the dimension across the top as this board is not drawn actual size.

relief. The duplex outlet will have 2 silvery screws in a silvery metal strip on its cold side, and a brass-colored metal strip with either 2 silver or 2 brass-colored screws on the hot side. Break the thin brass strip connecting the 2 screws on the hot side to isolate them from each other. Leave the 2 screws on the cold side in common with each other. Shorten the green and white leads on the line cord from 18 to 6 inches. Connect the green wire to the green screw on the outlet, and the white wire to one of the cold screws. Connect one end of the remaining 12 inches of white wire to the other cold screw, and the other end to one side of T1's primary (hole B in Fig. 9). Connect


one end of an 18-inch wire to each of the remaining holes on the power supply board. The wires to holes A and C should be No. 18 gauge. The remaining ones can be No. 24 or 26. Temporarily connect the wire from hole A to the black wire in the line cord. Interconnecting wires should be stranded.

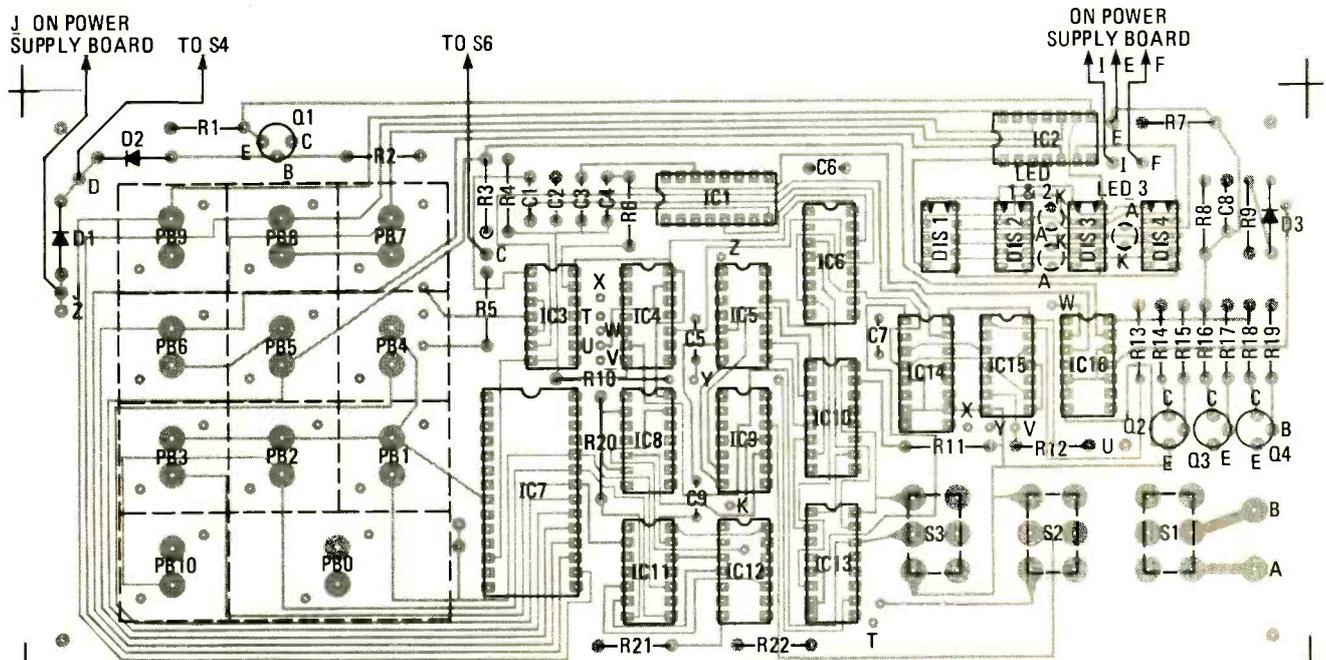Attach the board to the rear half of the case as shown in Fig. 11. Mount it so the transformer is toward the bottom of the case (when mounted on a wall). The outlets can be on either the right or left side to suit your darkroom's layout. Connect the No. 18 wire from the triac (hole C on the power supply board) to one of the unused hot screws on the outlet sock-





NOTE: HOLES A-A TO K-K ARE JUMPED EITHER TO POWER SUPPLY BOARD OR TO CABINET-MOUNTED COMPONENTS. HOLES T-T TO Z-Z ARE JUMPED TO EACH OTHER ON REAR SIDE OF BOARD.

FIG. 8—PARTS PLACEMENT ON THE MAIN CIRCUIT BOARD. Note that the keyboard mounts directly to this board too. As indicated, jumpers connect this board to the power supply board.

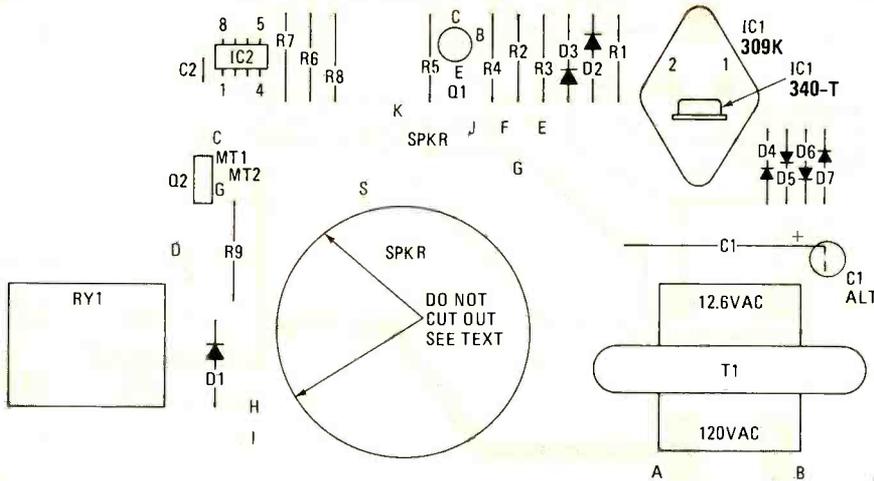

**FIG. 9—PARTS PLACEMENT ON THE POWER-SUPPLY BOARD. Note that the speaker and audio circuit components are also placed on this board.**

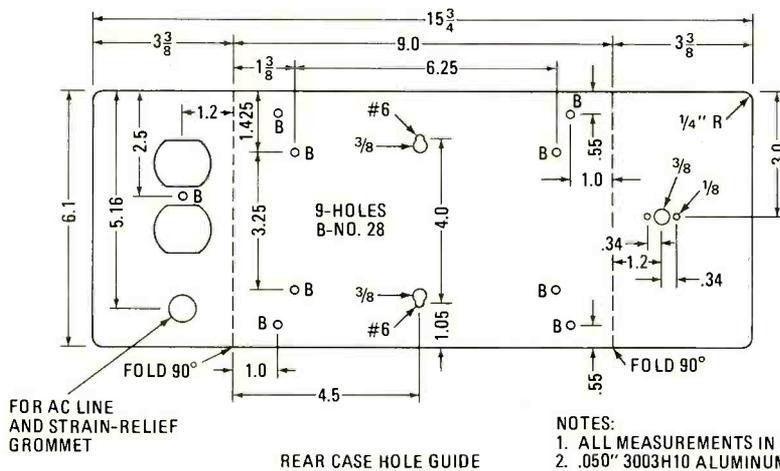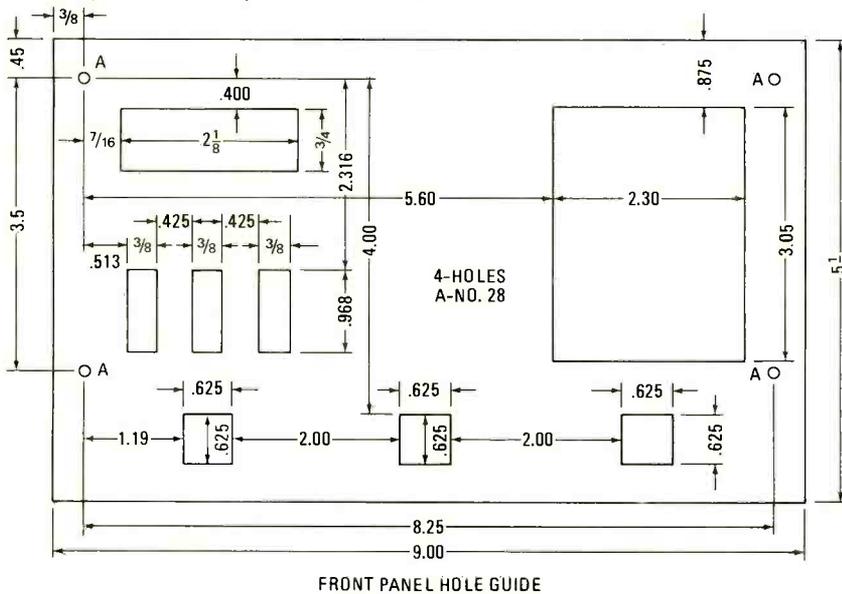

- NOTES:  
 1. ALL MEASUREMENTS IN INCHES  
 2. .050" 3003H10 ALUMINUM FRONT  
 3. .050" 3003H10 ALUMINUM REAR

**FIG. 10—FOLLOW THESE GUIDES FOR MAKING HOLES in both the front and rear panels of the case. Be sure to follow the listed dimensions accurately.**

START/STOP switch with two 4-40 × 1/4 screws. Make sure the ground terminal is in intimate contact with bare metal on the inside of the case.

Verify that the clearance between the foil side of the board and the case is adequate, and plug a 15-watt lamp into the socket connected to hole D, the safe-light socket. Plug the line cord into the 120-volt power line. A steady tone should be heard and the lamp should light. Grounding IC2-4 should turn the tone off. Measure +7.5 to +8.5 volts DC at hole E, and 30 to 70 percent of this voltage at hole J. Vary R4 if outside the 30 to 70 percent range. Ground hole H or I and verify that the lamp goes off. Move the lamp to the other outlet and verify that it lights when hole H or I are grounded.

Interconnect the main and power supply boards and the front panel switches and remote START/STOP jack as shown in Figs. 3 and 4. Remove the temporary connection between the line cord's black wire and T1's primary, and make the permanent connections shown in Figs. 3 or 4. Epoxy the red filter in place over the cutout in the panel for viewing the displays. This should be one of the very first things done when assembly initially starts. Connect main board to front panel as shown in Fig. 11.

### Testing

With all the IC's and displays removed from the main board, power the unit. Verify that the AC power switch works, and that the FOCUS switch activates the relay. Verify that B+ is present on each of the IC's power pins as shown in the table in Fig. 3. Shut power off and install the calculator IC, the four readouts and IC2. The displays, when power is reapplied, will usually show one, but occasionally two, zeroes in the right position(s). A decimal point will show if the TIME switch is in the SEC position, and a colon if in the MIN/SEC position. The overflow LED and audio will be on. Enter [9], [8], [7], [6] and verify that these digits show on the display. If odd characters appear, look for solder bridges near the display sockets, using a loupe of about 10 power. If none of the numbers appear on the display, check orientation of IC7 in its socket, the voltage at IC7-15 and that IC7-12 is at ground. If these tests pass, measure the voltage at IC7 pins 6, 7 and 8. The voltage at these pins should be high only when a pushbutton is pressed or a switch inside IC8 or IC11 is closed. If high at this time, either one of the pushbuttons is defective, or a solder splash exists somewhere, probably near IC8 or IC11's sockets. After getting the correct results, turn the unit off and then on to clear the display. Enter [5], [4], [3], [2] and verify the display. Again, momentarily turn off the unit, then enter and verify the [1], [0] entry. Turn the unit off and install the remaining IC's, being careful to minimize touching the leads to prevent static elec-

et, and the wire from hole D to the remaining unused hot screw. Secure the duplex receptacle outlet to the case with a single 6-32 × 3/8 screw in its center hole. Either scrape the paint from below the head of this screw or use a star washer

under the head to cut through the paint and into bare metal. It is imperative that the head of this screw be in excellent electrical contact with the case for safety. Mount the phono-type jack used in conjunction with a foot switch as a remote

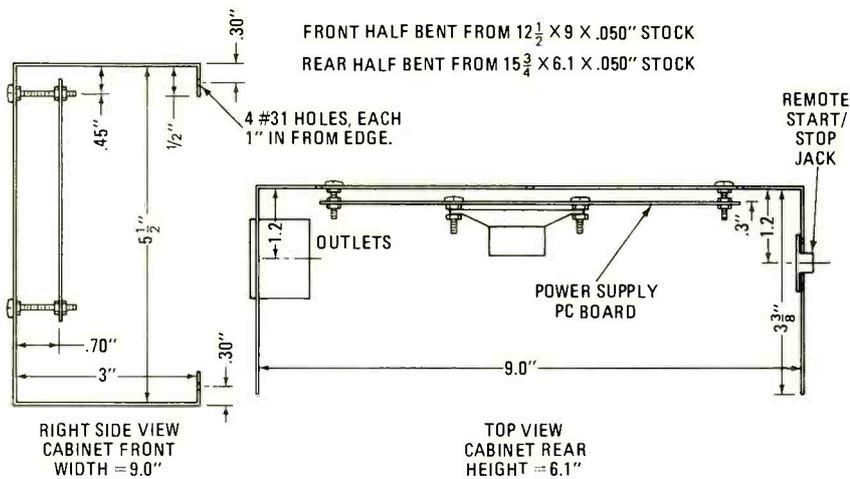


FIG. 11—CASE BENDING INSTRUCTIONS for the builder who wants to make his own case. The detail at the right shows how the speaker is positioned and mounted inside the case.

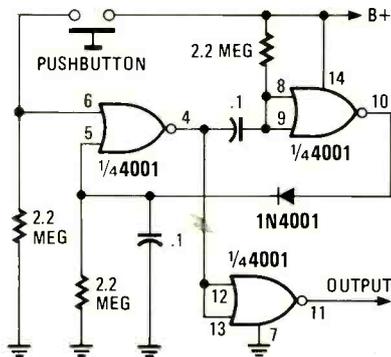


FIG. 12—SIMPLE TEST CIRCUIT produces a single bounce-free output each time you push the switch.

tricity damage. Before applying power to the unit, double check the orientation of the IC's. Apply power and verify that the AUDIO switch works. Enter any 5 digits. When the fifth one is entered, the overflow LED should light. Clear the display using the CLEAR button (one zero will remain). With the TIME switch in the MIN/SEC position, enter any 2 digits and press the START button.

About 0.5 second later, the relay will energize and the timing cycle will begin. Allow it to complete, and verify that the selected time reappears at completion. Enter 2 new numbers and reinitiate the cycle. Interrupt it with a single push of the PAUSE button. A second push should allow the cycle to continue. Interrupt it again, this time with the START/STOP button. The time last entered should reappear in the display.

Enter 1, 1, 0 (1 minute and 10 seconds) and start the cycle. Verify that the display jumps from 1:00 to :59.

Move the TIME switch to the SECONDS position, enter any number and verify operation. The flickering of the display in the SECONDS mode is normal. It occurs because during the computation period, the calculator IC blanks its segment and digit outputs until a valid final answer is produced.

The audio signal produces one beep for each second selected on the minutes/

seconds range. In the seconds range, there may be one additional beep more than the number of whole seconds selected, depending upon the size of the fractional seconds entered. For example, an entry of 2.2 will give 2 beeps, and an entry of 2.4 will give 3 beeps. An entry of 2.3 will give 2 solid beeps and maybe a half-hearted third one also, depending upon the speed of your particular calculator IC and the position of its internal oscillator when you happened to start the cycle.

Most discrepancies will be due to construction errors such as miswiring, bad soldering, etc., or defective IC's. I have had difficulties when using 4017's manufactured by MITEL Semiconductor whose part identification prefix is SIL. Usually, one of the 10 outputs refuses to go high. If the failed output is unused, the IC is OK to use since usually the good outputs go high at the correct time. Integrated circuits IC6 and IC10 can be interchanged as can be many other pairs of IC's.

Several innocent-looking capacitors are vital to proper operation. Capacitor C3, if too small or open, will cause timing accuracies to be off as much as 20% or cause the decrementing to look erratic, and make the unit sensitive to line transients. If line transients are suspected of causing large jumps in the display's contents, try increasing C3 to 0.1  $\mu$ F, adding no more than 0.1  $\mu$ F from the collector of Q1 on the power supply board to ground, and/or adding capacitance across the secondary or primary of T1.

Capacitor C4, if too small or open, will cause difficulty in entering numbers, self-starting while entering numbers, or premature ending of the timing cycle. If C6 is too small, it could cause 41 to be subtracted at undesired times.

Calculator IC's aren't designed for a 10-Hz counting rate. To make this unit operate reliably at this rate, IC7's internal clock was speeded up by reducing R21 to 75K from the manufacturers' recommended 470K. My prototypes operated

properly with three IC's manufactured at widely different times. If R21 is too small, the internal clock will harmlessly stop, while if too large, the timing interval on the SECONDS range will be about double the desired value.

For difficult problems, wire the test circuit in Fig. 12, which produces a single bounce-free output each time the push-button is pressed. Break the connection between holes J and J, and connect the test circuit output to hole J on the main board. You can now single-step the timer through its sequences, remembering that 6 pulses are required to produce a single output from IC1-5.

When using a scope to look at the outputs of IC7 or most other points in the circuit, connect the scope's external trigger input to D1 (a convenient test point can be made by inserting a bare loop of wire in the holes adjacent to IC7-10 and IC7-11). Adjust the controls so triggering is on the positive polarity. Connect the vertical input to D1 and adjust the horizontal gain and centering until D1 is high between the first and second vertical lines on the scope's graticule (assuming 10 major divisions and 11 vertical lines). Move the vertical input to D9, IC7-16. If the horizontal controls are properly set, the trace should be high between the ninth and tenth vertical lines. (If your scope's external trigger input is capacitively coupled, add a 100K resistor from D1 to ground.) As an example of using this setup, suppose that pressing the keys would not enter numbers in the display. Suspecting that either KP, KN or KO is always high or continuously being pulsed high, you scope these points. If you noted that KO was high between the fourth and fifth vertical lines, the D4 time slot, you should suspect everything associated with the Minus function (IC8-10, IC8-11 and the drive circuits to IC8-12). Similarly, if 41 isn't being subtracted at whole-minute intervals, enter the numbers 2, 0, 0 and make sure that IC4-11 is low in the D8 and D9 time slots, IC15-4 is high during the D8 time slot, IC15-3 is high during the D9 time slot, IC15-11 is high during the D8 and D9 time slots, etc. Ignore signals occurring during D1 to D4.

Fasten the halves of the case to each other with four sheet metal screws. The timer is ready for use.

### Parts substitution

Although the only custom parts are the cabinet and PC boards, several parts are difficult to obtain. For example, Datane-tics has a minimum billing of \$25, and GI's Los Angeles-area distributors have minimums of \$10. But since the calculator IC is not a heavy-demand item, distributors don't stock it and are reluctant to order the necessary quantity from the factory.

The remaining items should all be readily available from R-E's advertisers  
*continued on page 60*

# VIDEO MODULATORS

*If you are into VTR's, TV games, home computers and TV modulator must be used to feed modulated RF to*


**FRED BLECHMAN K6UGT**



VD-1 by Ramsey




ATARI model CA-010410

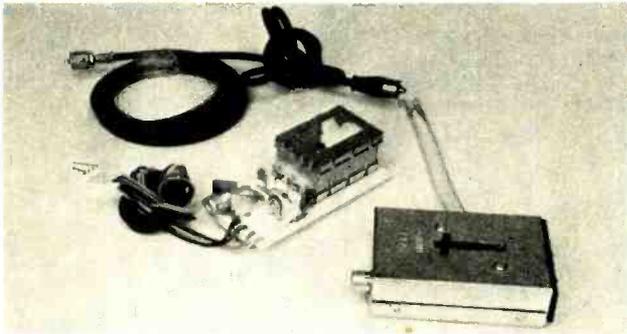


SUP "R" MOD II, cables and switch included



MODEL E & P

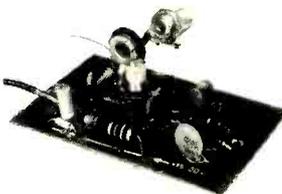

RF-1 RF modulator

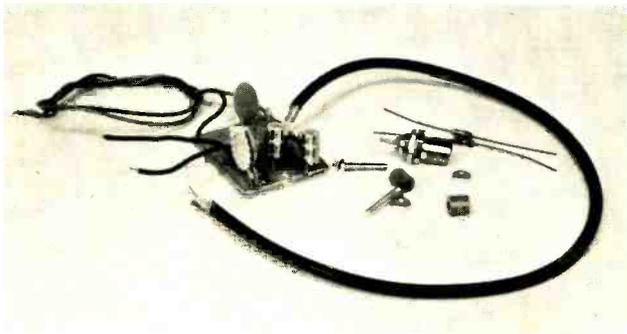

RFVM-1 sold by Vamp and Quest Electronics

IN THE LAST TWO YEARS FOUR "NEW" ELECTRONIC PRODUCTS have been introduced into the consumer marketplace—video games, video cassette recorders, video cameras and home computers. While these products have been available in some form for several years, their design finally became practical enough for consumer acceptance. Coincidentally, each product uses a video display for its output. A TV screen is essential for playing a video game or watching a video recorder, and most home computers use a video display for the readout, although printers can also be used. Video cameras, long used for closed-circuit security and surveillance systems, are growing in popularity now that video cassette recorders are available for making home movies, and, of course, cameras also use a video display.

Two basic methods make the video signal visible on a picture tube. The most efficient method is to feed the video output of a game, camera, video recorder or computer directly into the video amplifier of a video monitor or TV set. Since most TV sets require rewiring to provide direct access to the video amplifier (and those with a hot chassis can create a dangerous shock hazard), video monitors have generally been used. However, when home video games became popular, it was obvious that the public would not care to buy a special monitor to play the games. Therefore, an old video camera technique was revived—generating an RF signal on an unused TV channel and modulating it with the video signal! By connecting the modulated RF carrier to the antenna terminals of a standard TV set, you could watch the game by simply tuning to the unused channel.

In the beginning, video game manufacturers, to avoid interfering with VHF signals, created carriers in the high UHF band. Shielding problems, signal instability with temperature variation and other design considerations caused the shift to VHF carriers modulated by the video signal. Several million video games were sold (some for as little as \$25) complete with built-in video-modulated RF oscillators. The Federal Communications Commission (FCC) then cracked down on the manufacturers, requiring them to test units to rigorous specifications before type approval was issued, in order to try minimizing the spurious radiations being generated to neighboring TV sets—even to other sets in the home!

With technological advances taking place in the game field, microprocessors and dedicated integrated circuits (IC's) became commonplace among experimenters. Home computers suddenly blossomed from garage and basement labs to full-blown manufacturing plants. Experimenters and hobbyists found an increasing need for some means to couple the video output of their devices to a display. Video monitors have remained a low-production item and are therefore high-priced. TV set manufacturers have not recognized the sales advantage of adding a switch and jack to existing designs to allow direct video input. Therefore, there has been a steadily increasing

# turn your TV into a video monitor

cameras in security and surveillance systems, a video TV set used as monitor. Here's what modulators are about.

market for a separate video-modulated VHF oscillator that allows the owner of a video game, camera, recorder or home computer to use the device with a standard TV set.

These VHF oscillators have many different names: RF modulator, VHF modulator, RF oscillator, video-to-TV interface, video-to-RF modulator, etc., but in this article we will use the general term of "video modulator," even though this is technically incorrect. (The device is *not* modulating the video—it is being modulated *by* the video!) Some manufacturers have sensed the need for this device among hobbyists and experimenters, and the Comparison Chart shows 14 video modulator sources. Many of these devices (and maybe others) are available at computer shops.

Figure 1 shows a simplified block diagram for a typical video



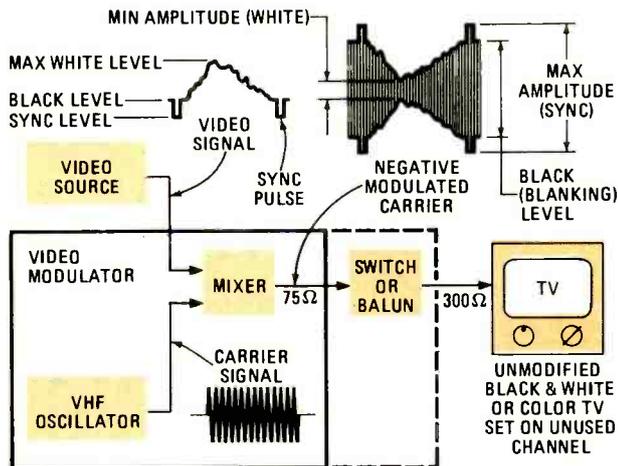


FIG. 1—BLOCK DIAGRAM OF VIDEO MODULATOR.


modulator. The video signal from the camera, computer, recorder or game should be the standard NTSC (National Television System Committee) format used in the United States, Japan, Canada and Mexico. This means that the picture carrier is modulated so a *decrease* in scene brightness causes an *increase* in output power. This is known as *negative* modulation polarity. With negative modulation polarity, the picture content may vary the transmitter output power from 15% for white level to 75% for black at the blanking level. The horizontal sync pulse rides atop the blanking pulse—extending into the blacker-than-black level at 100%. The tunable VHF oscillator generates a sinewave on a locally unused TV channel; this sinewave signal becomes the carrier. In the mixer, the video signal amplitude-modulates the VHF carrier with *negative* modulation polarity. This modulated VHF carrier connects to the antenna terminals

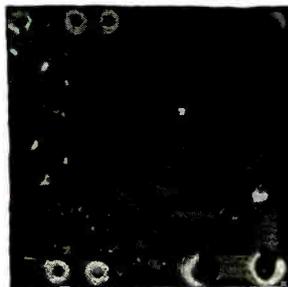

TV-1 video to TV interface

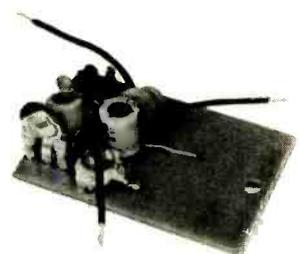

PXV-2A Pixe-Verter

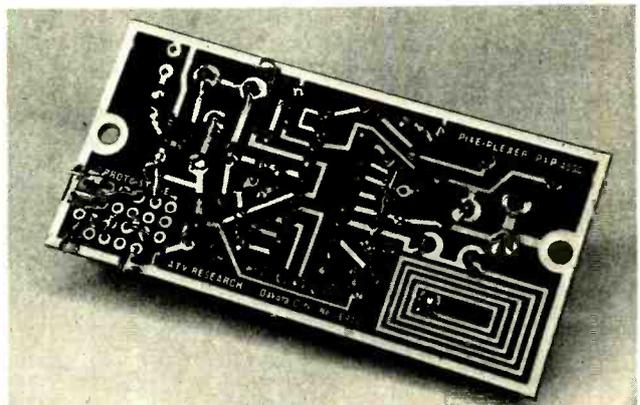


PXP-4500 Pixe-Plexer from ATV Research



Model 1-7 RF modulator



E & P video modulator

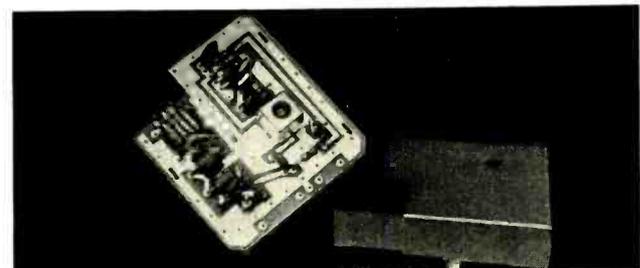

VIDEO CUBE 5500-R from Delta Electronics

COMPARISON CHART - VIDEO MODULATORS

MANUFACTURER OR DISTRIBUTOR	MODEL	PRICE (\$)		OUTPUT CHANNEL NO.			SUPPLY VOLTAGE (DC)	VIDEO INPUT CONTROL	RF-SHIELDED	INPUT CONNECTOR	OUTPUT CONNECTOR	PERFORMANCE					SIZE (CM.)			SOFTWARE			SHIPPING AND REMARKS							
		KIT	ASSEMBLED	2	3	4						5	6	MIN. VIDEO INPUT (PEAK-TO-PEAK)	RF REJECTION	VIDEO CAMERA	VIDEO RECORDER	MICROCOMPUTER	LENGTH	WIDTH	HEIGHT	DOCUMENTATION		SCHEMATIC	USE DIRECTIONS	PRECAUTIONS				
																											1	2	3	4
ADVANCED COMPUTER PRODUCTS P.O. BOX 17329 IRVINE, CA 92713	U1001 RF MODULATOR WITH AUDIO	—	7.95	✓	✓			9	N	Y	N	①	②	P	G	G	P	8	5.5	2.5	P	N	N	N						SHIPPING: 5% + \$50 INSUR. CAL. RES. ADD 6% TAX. OUTPUT INVERTED. SEE TEXT.
ADVANCED VIDEO PRODUCTS 5835 HERMA SAN JOSE, CA 95123	RF-1 RF MODULATOR	12.00	—	✓	✓	✓	✓	9-20	Y	N	N	N	.4	G	E	E	G	8.3	5.2	2.5	G	Y	Y	N						SHIPPING: C.O.D. CHARGE. CAL. RES. ADD 6% TAX. TUNING WAND INCLUDED.
ATV RESEARCH 13TH AND BROADWAY DAKOTA CITY, NE 68731	PXV-2A PIXE-VERTER	8.50	—	✓	✓	✓	✓	-5 TO -6.5	Y	N	N	N	2	F	G	G	F	5.1	3.2	2.0	E	Y	Y	Y						SHIPPING: POSTPAID. NEGATIVE SUPPLY VOLTAGE REQUIRED.
	PXP-4500 PIXE-PLEXER	24.50	—	✓	✓	✓	✓	15	N	N	N	N	④	G	G	G	G	7.7	3.8	2.3	E	Y	Y	Y						SHIPPING: POSTPAID AUDIO INCLUDED.
CALIFORNIA INDUSTRIAL P.O. BOX 3097K TORRANCE, CA 90503	CA-010410 ATARI RF MODULATOR	—	13.95	✓	✓			1.5-12	N	Y	N	①	.8	F	E	E	G/F	6.5	3.2	2.8	P	Y	N	N						SHIPPING: \$1 FOR ORDERS UNDER \$15. CAL. RES. ADD 6% TAX. WILL OPERATE ON PEN CELL. 15 FT. COAX & RF CONNECTOR INCLUDED.
DELTA ELECTRONICS 7 OAKLAND ST. AMESBURY, MA 01913	5500R VIDEO-CUBE	13.95	—	✓	✓			5-12	N	Y	N	N	4	P	F	F	P	6.3	5.6	2.8	G	Y	Y	Y						SHIPPING: POSTPAID. MASS. RES. ADD SALES TAX. MUST BE TAILORED TO CIRCUIT - SEE TEXT.
ELECTRONIC SYSTEMS P.O. BOX 212 BURLINGAME, CA 94010	NO. 107 RF MODULATOR	13.50	—	✓	✓			5VDC OR 12VAC CT	N	N	N	N	2	G	E	E	F	6	6	1.5	F	Y	N	N						SHIPPING: POSTPAID WHEN PAYMENT SENT WITH ORDER. CAL. RES. ADD 6% TAX. PC BOARD ALONE: \$7.60.
FORMULA INTERNATIONAL, INC. 12603 CRENSHAW BLVD. HAWTHORNE, CA 90250	VHF MODULATOR (E&P)*	—	4.50	✓				5-6.5	N	Y	N	①	②	②	③	③	③	6	3.8	2.4	P	N	Y	N						SHIPPING: 10% OUTSIDE CAL. CAL. RES. ADD 6% TAX. MIN. ORDER: \$10. OUTPUT INVERTED - SEE TEXT.
BILL GDDBOU ELECTRONICS OAKLAND AIRPORT CA 94614	RF MODULATOR (E&P)*	—	7.50	✓				5-6.5	N	Y	N	Y	②	②	③	③	③	6	3.8	2.4					NO DOCUMENTATION RECEIVED WITH UNIT					SHIPPING: \$.50. CAL. RES. ADD 6% TAX. OUTPUT INVERTED - SEE TEXT.
JADE COMPUTER PRODUCTS 5351 WEST 144TH ST. LAWNOALE, CA 90260	TV-1 VIDEO-TO-TELEVISION INTERFACE	8.95	—	✓	✓	✓	✓	5-12	Y	N	N	N	.25	G	E	E	G	3.5	3.5	1.5	E	Y	Y	Y						SHIPPING: \$1.25. CAL. RES. ADD 6% TAX. (MADE BY UHF ASSOCIATES) SMALLEST UNIT. COAX INCLUDED.
M & R ENTERPRISES P.O. BOX 61011 SUNNYVALE, CA 94088	SUP "R" MOD II TV INTERFACE	—	29.95	✓				12	Y	Y	①	①	2	G	G	G	G	8.2	3.9	2.5	E	Y	Y	Y						SHIPPING: \$1. CAL. RES. ADD 6% TAX. TV SWITCH & COAX INCLUDED.
QUEST ELECTRONICS P.O. BOX 4430E SANTA CLARA, CA 95054	VIDEO MODULATOR (TV-1)	8.95	—	✓	✓	✓	✓	5-12	Y	N	N	N	.25	E	E	E	G	3.5	3.5	1.5	E	Y	Y	Y						SHIPPING: POSTPAID. CAL. RES. ADD 6% TAX. SEE JADE MODEL TV-1 FOR TEXT. COAX INCLUDED.
	VIDEO MODULATOR (RFVM-1)	8.95	—	✓	✓	✓	✓	5	Y	N	N	⑤	.8	G	E	E	F	4.5	3.3	2	E	Y	Y	Y						SHIPPING: POSTPAID. CAL. RES. ADD 6% TAX. SEE VAMP MODEL RFVM-1 FOR TEXT. MOUNTING HARDWARE, COAX & CONNECTOR INCLUDED.
RAMSEY ELECTRONICS P.O. BOX 4072 ROCHESTER, NY 14610	VD-1 VIDEO-TO-RF MODULATOR	6.95	—	✓	✓	✓		5-10	N	N	N	N	.5	F	G	G	F	4.6	2.6	2.5	G	Y	Y	N						SHIPPING: \$.75 FOR ORDERS UNDER \$10. N.Y. RES. ADD 7% TAX. LEAST EXPENSIVE KIT.
UHF ASSOCIATES P.O. BOX 24 JENNER, CA 95450	TVS-100	⑥	⑥	✓	✓			15-20	Y	Y	①	①	1	G	E	E	G	16	5	2	⑥	⑥	⑥	⑥						⑥ AUDIO INCLUDED.
VAMP, INC. P.O. BOX 29315 LOS ANGELES, CA 90029	RFVM-1 RF-TO-VIDEO MODULATOR	8.95	—	✓	✓	✓	✓	5	Y	N	N	⑤	.8	G	E	E	F	4.5	3.3	2.0	E	Y	Y	Y						SHIPPING: \$1 FOR ORDERS UNDER \$15. CAL. RES. ADD 6% TAX. MOUNTING HARDWARE, COAX & CONNECTOR INCLUDED.

NOTES: E = EXCELLENT G = GOOD F = FAIR P = POOR Y = YES N = NO \*E&P STAMPED ON CASE IS ONLY IDENTIFICATION  
 ① RCA PHONO JACK ② NOT TESTED - SEE TEXT. ③ UNIT WILL NOT WORK WITH NTSC VIDEO - SEE TEXT. ④ VARIES WITH INTERFACE CIRCUIT.  
 ⑤ F-59 CONNECTOR SUPPLIED. ⑥ INFORMATION NOT AVAILABLE. WRITE COMPANY FOR SPECIFICATIONS, PRICE AND AVAILABILITY.

of a standard black-and-white or color TV set. When the TV set is tuned to the VHF carrier frequency, the information contained on the video signal is displayed conventionally. For most units tested, a TV antenna switch or a balun transformer (75 ohms to 300 ohms) is needed for connection to the TV antenna terminals.

### Evaluating the modulators

Bob Buckner, an electronics consultant, built all the kit units reported on, and did the majority of the data compilation. He and I did the comparative testing together. Gene Hill, co-owner of UHF Associates, provided most of the units for building and testing, with the understanding that the "chips fall where they may" in the evaluations. (As it turned out, the two UHF Associates units were outstanding, and the reader will have to take my word that my objectivity was not influenced by the cooperation of UHF Associates!)

Twelve different video modulator designs were examined for this article, although some were available from more than one source. Each design was different in circuitry, layout and components, although some similarities existed. Two sources distribute the E & P unit: Formula International, Inc., and Godbout Electronics. Although this was the least expensive assembled unit, it appears to be wired for a *positive-sync*, video input signal, since we could not receive anything except a *negative* picture that would not synchronize with the TV. Inverting the input video signal with a properly biased transistor circuit would probably allow this unit to be used with a standard TV set. However, this was not tried.

Figure 2 shows the schematic of the UHF Associates *model*

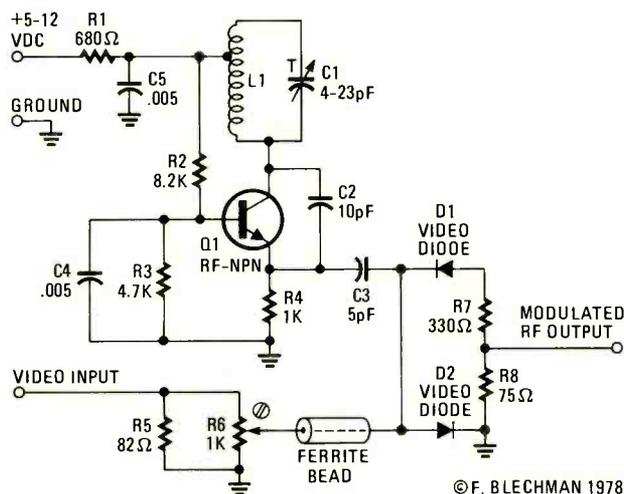


FIG.2—UHF ASSOCIATES MODEL TV-1 schematic diagram.

TV-1 modulator, distributed by Jade Computer Products and Quest. The VHF frequency is generated by a tuned Hartley oscillator circuit. Resistors R2, R3 and R4 bias the transistor, with tapped printed-circuit inductor L1 and trimmer capacitor C1 forming the tank circuit. Adjusting C1 determines the frequency. Capacitor C2 provides positive feedback from the tank circuit to the emitter at Q1. Capacitor C4 provides an RF ground for the base of Q1. Bypass capacitor C5, together with resistor R1, filters the radio frequencies generated in the tank circuit to prevent radiation from the power-supply lines.

The video signal enters the parallel combination of resistors R5 and R6; this combination closely matches the 75-ohm impedance of most video cables. Resistor R6 is a small screwdriver-adjusted potentiometer that is used to control the video input level to mixer diodes D1 and D2. These diodes are operated in their nonlinear region to mix the video signal with the VHF carrier. With no video input, the VHF carrier, which is loosely coupled to the mixer by capacitor C3, passes through D1 to voltage divider R7-R8. The output impedance is 75 ohms, to match standard video coaxial cable. As the video signal leaves video level control R6, it encounters the ferrite bead; this bead

blocks any RF on the video-input line, yet passes the video signal on to diodes D1 and D2. This video signal effectively biases the diodes, allowing them to conduct or block the carrier signal, thus modulating the carrier. For example, as the video signal amplitude goes positive, D2 is forward-biased toward ground, so the carrier amplitude is decreased. However, as the video signal goes *negative*, and grows even *more* negative to the sync level, D2 cuts off and the maximum carrier amplitude (minus the diode voltage drop) passes through D1 to R7-R8. Therefore, white-level video signals yield the lowest VHF carrier output, and sync pulses are the highest, as shown in Fig. 1!

### Comparison chart

The sources, prices and shipping information shown in the Comparison Chart were correct as of early March, 1978. The output channels and supply voltages are those specified in manufacturer's literature. Some units might be tunable beyond the specified channels. The supply voltages are all positive, except for ATV's *Pixe-Verter*, which requires a negative voltage. The video input on those units designated in the chart with a "Y" (for "Yes") consists of a small potentiometer, usually with a screwdriver slot for adjustment. Most units do not have video input or VHF output connectors, this being left up to the user's discretion to suit a particular application. Those units that *do* have connectors use standard RCA phono jacks, except for the Vamp unit, which has one F-59-type RF connector supplied with the kit.

The performance parameters were judged based on comparisons with other units. The peak-to-peak video voltage was measured using an oscilloscope, with the "minimum" standard being that point below which the picture quality was noticeably affected. For those units with a listed voltage range, the test was conducted at the minimum voltage.

Since a video modulator might be operated in or near a computer terminal, each modulator was used to display a color signal while near a Radio-Shack TRS-80 computer, and the interference from the computer was evaluated. In many cases, the interference was hardly noticeable, even though most units were unshielded and clip leads were used for making some connections. Probably if shielded wire and connectors are used and a metal enclosure is placed around each unit, the RF interference from the computer would not be a problem.

The most difficult judgment involved was that of picture quality using a black-and-white video camera and a color TV video signal. The camera was an FS 11 from Advanced Video, and all the negative-sync-output modulators provided good to excellent results, except for the *Videocube*. The *Videocube* requires special matching, depending on the mating circuits, and the results could probably be improved by further refinements.

The color video source was the video output of an RCA *SelectaVision* video cassette recorder, and most units provided a surprisingly good picture. In some cases, jockeying of video input level and supply voltage was required; once tuned properly, however, the color and contrast were good. Again, the exceptions were the positive-sync units, which were unusable with a standard video signal.

The test that really "separated the men from the boys" was when we tried to receive a video signal from a computer through the TV front end! The Radio Shack TRS-80 computer was used with each video modulator and displayed on a Midland *model 15-023* 12-inch black-and-white TV set. The computer produces 16 lines at 64 characters-per-line, and the results were compared with a direct video connection to the TRS-80 12-inch black-and-white video monitor. Under no conditions in our tests could a video modulator duplicate the clarity that was obtained by this direct connection to the video monitor. This is not really surprising when you consider that the effective video bandpass of even a good TV receiver is no more than 4.0 MHz, while the video monitor is rated at 5.5-MHz maximum bandwidth.

Next month we'll continue this discussion and then take a detailed look at the products of each manufacturer as listed in the comparison chart.

R-E

# Radio-Electronics Tests ReVox Model B-760 FM Tuner



CIRCLE 102 ON FREE INFORMATION CARD

1

**LEN FELDMAN**  
CONTRIBUTING HI-FI EDITOR

ANYONE READING THE PUBLISHED SPECIFICATIONS of the *model B-760* stereo FM tuner manufactured by Studer ReVox America, Inc. (1819 Broadway, Nashville, TN 37203), and familiar with the new U.S. tuner measurement standards as adopted by the IHF and the IEEE, will immediately realize that the manufacturer's specs are not written in accordance with the approved standards (as of this writing). We realized that this would make it difficult to compare published claims with actual measured performance, but we also felt that it was appropriate to measure this fine tuner in exactly the same way that we measure other tuners. This, as we came to learn, was particularly important in distortion measurements where 40-kHz deviation signals resulted in one distortion reading, while full 75-kHz deviation yielded another.

The front panel of the *model B-760* is shown in Fig. 1. The left side of the front panel contains a POWER on-off switch, with a superimposed indicator light and phone jack just below. A switch immediately to the right of these controls is used for introducing optional Dolby noise reduction (our unit was not equipped with this extra circuit module), and a light above this switch illuminates when the Dolby unit is activated. The volume control just below is then used for varying the headphone output level. The selected-station frequency is displayed digitally above two meters (a signal-strength meter and a center-of-channel meter). Pushbuttons below the meters are used to store frequencies in the system's memory bank, introduce a station blank for any given memory pushbutton, add or cancel a fixed 25-kHz to the tuned-to frequency that is displayed and select manual tuning, which then permits you to use the conventional rotary tuning knob in the usual fashion. As you turn this knob, displayed frequencies move up or down in 50-

kHz increments.

The 15 numbered pushbuttons to the right of the tuning knob are used to store favorite station frequencies. While in the manual mode, if you tune to a station that you wish to retain, just press the STORE IN MEMORY pushbutton and the numbered station selector pushbutton desired; from then on, pressing that particular numbered pushbutton instantly tunes to the selected frequency.

To the right of the 15 memory buttons are a stereo indicator, a SEPARATION switch for maximum or high-blend stereo reception and a MONO override pushbutton. A companion switch selects interstation muting or interstereo muting (this switch allows only stereo signals to come through). A muting indicator light is located above this switch, while below is another pushbutton that overrides both forms of muting.

Hidden secondary controls are located behind the upper bezel showing the trade name and model number; this bezel swings down to disclose the controls. Figure 2 shows the group of switches at the left of this area, including slide switches for selecting de-emphasis (75 or



2

50  $\mu$ s as well as 25  $\mu$ s if an optional Dolby unit is installed) and a MEMORY MODE switch. In the READ ONLY mode of this switch, new information cannot be programmed into the tuner (to prevent accidental cancellation of previously stored frequencies), while in the READ WRITE mode, frequencies can be programmed into any of the 15 memory locations. Three

tiny rotary controls at the right (see Fig. 3) are used to adjust the stereo-only and interstation muting thresholds and to adjust output level



3

from one of the tuner's sets of outputs.

The left-hand side of the rear panel (shown in Fig. 4) contains vertical and horizontal scope-connection jacks for observing multi-




4

path, fixed-level and variable-level output jacks and a DIN multipin connector. A voltage selector knob chooses the correct power-line operating voltage, and a separate line cord is provided to match either foreign or domestic power requirements. To the right of these controls is a receptacle that accepts a supplied 300-ohm plug to which a 300-ohm transmission line can be connected; next to this plug is a coaxial connector for a 75-ohm transmission line from antenna to tuner.

## Circuit highlights and construction

Figure 5 shows an internal view of the *model B-760* tuner with the internal shields removed. The complexity of the layout is due to the fact

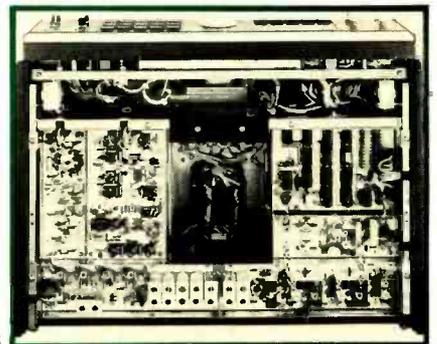

5

that it contains 65 IC's, 63 transistors, 2 diode matrices (91 diodes), 42 diodes, 19 varactor

## MANUFACTURER'S PUBLISHED SPECIFICATIONS:

**Usable Sensitivity** (for 40-kHz deviation, 46-dB S/N): mono, 2.0  $\mu$ V (11.2 dBf); stereo, 20  $\mu$ V (31.2 dBf). **AM Suppression:** 70 dB. **Selectivity** (referred to 300-kHz separation and 40-kHz deviation): 80 dB. **Capture Ratio:** 0.9 dB. **IF Rejection:** 110 dB. **Image Rejection:** 106 dB. **Frequency Response:** 30 Hz to 15 kHz,  $\pm$  1 dB. **Harmonic Distortion** (mono and stereo, L = R): 0.15%. **S/N Ratio:** 75 dB. **Stereo Separation** (40-kHz deviation, 1 kHz): 42 dB. **Subcarrier Suppression:** 65 dB. **Output Level:** 1.16 V (400 Hz). **Power Requirements:** 100, 120, 140, 200, 220 or 240 V, 50 to 60 Hz, 40 watts. **Dimensions:** 17 1/4" W  $\times$  5.94" H  $\times$  13 1/8" D. **Weight:** 26 lbs., 7 oz. **Suggested Retail Price:** \$1145.

(variable-capacitance) diodes and 3 bridge rectifiers. Of particular interest to those not familiar with a frequency-synthesized, digital readout tuner is the circuit design used for these functions.

The electronic storage of station frequencies and their addresses is accomplished by a 16-bit by 12-bit CMOS random access memory (RAM). The stored information is retained in RAM as long as the unit remains connected to the power outlet, and in the event of a power failure, replaceable alkaline batteries (stored behind the tilt-down front bezel) can be used so there is no loss of information. Extremely low current consumption (less than 10  $\mu$ A) makes storage in RAM possible for over a year from the battery supply.

The front end of the tuner contains two broadband amplifying stages, followed by six tuned filters and a symmetrical push-pull mixer stage. Eighteen dual-varicap diodes are used for tuning all tuned circuits including the local oscillator. The IF section is designed as a phase-linear toroid filter in a separate screened compartments and is completely passive. An IC-equipped broadband limiter features six amplifying stages. An automatic-gain control circuit allows the signal-strength meter to display input-signal values logarithmically, so that meaningful readings are possible from a few microvolts to more than 100 mV. The FM detector is a digital demodulator type that uses a line-demodulating principle. A phase-locked-loop circuit is used in the multiplex decoder section and, unlike most of these circuits, discrete parts were used for the phase-locked loop (not an IC). Interference frequencies above 53 kHz are suppressed through the use of a phase-linear 100-kHz low-pass filter, a bandpass filter (23 kHz to 53 kHz) and separate 114-kHz and 130-kHz rejection filters plus a 19-kHz pilot tone rejection filter.

### Lab measurements


Table 1 summarizes our lab measurements, which were taken in accordance with IHF measurement standards; they therefore do not readily lend themselves to comparison with the manufacturer's currently published specifications. The 50-dB quieting value was exceptionally good in both mono and stereo, as were the ultimate signal-to-noise ratios obtained for a 65-dB input signal at 100% modulation. Image, IF and spurious rejection measurements were limited by our test equipment, which can only read these figures up to 100 dB (hence, the "+" notation after each one).

We encountered difficulties when we began to measure harmonic distortion at the three prescribed test frequencies in mono and stereo. As long as we used the DIN values of 40-kHz deviation, distortion readings were quite low; but as deviation was increased to meet U.S. standards, the readings began to rise over the last few kHz of modulation. The distortion figures shown in parentheses are those obtained using  $\pm$ 40-kHz modulation, while the higher figures are those obtained using  $\pm$ 75-kHz modulation. Although the high-deviation results were not bad, they would have been much better if the design had been adjusted for U.S. modulation extremes. The significance of this difference is of little importance if you are listening to a station that carefully monitors its modulation depths, but, as most people know, many stations not only reach but sometimes even exceed the 100% modulation limits. It is common practice for many popular and rock music stations to use high compression levels (decreasing dynamic range) and, at the same

TABLE 1		
RADIO-ELECTRONICS PRODUCT TEST REPORT		
Manufacturer: Studer/ReVox		Model: B-760
FM PERFORMANCE MEASUREMENTS		
<b>SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE</b>	<b>R-E Measurement</b>	<b>R-E Evaluation</b>
IHF sensitivity, mono: ( $\mu$ V) (dBf)	2.0 (11.2)	Very good
Sensitivity, stereo ( $\mu$ V) (dBf)	7.0 (22.1)	Very good
50-dB quieting signal, mono ( $\mu$ V) (dBf)	2.1 (11.6)	Excellent
50-dB quieting signal, stereo ( $\mu$ V) (dBf)	26.0 (33.5)	Excellent
Maximum S/N ratio, mono (dB)	84	Superb
Maximum S/N ratio, stereo (dB)	75	Superb
Capture ratio (dB)	0.9	Superb
AM suppression (dB)	70	Superb
Image rejection (dB)	100+	Superb
IF rejection (dB)	100+	Superb
Spurious rejection (dB)	100+	Superb
Alternate channel selectivity (dB)	85	Excellent
<b>FIDELITY AND DISTORTION MEASUREMENTS</b>		
Frequency response, 50 Hz to 15 kHz ( $\pm$ dB)	1.0	Very good
Harmonic distortion, 1 kHz, mono (%)	0.26 (0.14)	Fair, see text
Harmonic distortion, 1 kHz, stereo (%)	0.28 (0.14)	Good, see text
Harmonic distortion, 100 Hz, mono (%)	0.3 (0.15)	Fair, see text
Harmonic distortion, 100 Hz, stereo (%)	0.4 (0.18)	Fair, see text
Harmonic distortion, 6 kHz, mono (%)	0.20 (0.16)	Good, see text
Harmonic distortion, 6 kHz, stereo (%)	0.22 (0.16)	Very good, see text
Distortion at 50-dB quieting, mono (%)	2.8	Fair
Distortion at 50-dB quieting, stereo (%)	0.7	Good
<b>STEREO PERFORMANCE MEASUREMENTS</b>		
Stereo threshold ( $\mu$ V) (dBf)	7-100 (22.1-45.2)	Excellent
Separation, 1 kHz (dB)	42	Excellent
Separation, 100 Hz (dB)	40	Excellent
Separation, 10 kHz (dB)	34	Excellent
<b>MISCELLANEOUS MEASUREMENTS</b>		
Muting threshold ( $\mu$ V) (dBf)	4-30 (17.2-34.7)	Excellent
Dial calibration accuracy ( $\pm$ kHz at MHz)	"Perfect"	Superb
<b>EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION</b>		
Control layout		Excellent
Ease of tuning		Superb
Accuracy of meters or other tuning aids		Excellent
Usefulness of other controls		Excellent
Construction and internal layout		Superb
Ease of servicing		Very good
Evaluation of extra features, if any		Excellent
<b>OVERALL FM PERFORMANCE RATING</b>		Very good, see text

time, push modulation to the limit so that they will be the "loudest station on the dial" as you traverse the FM frequency band.

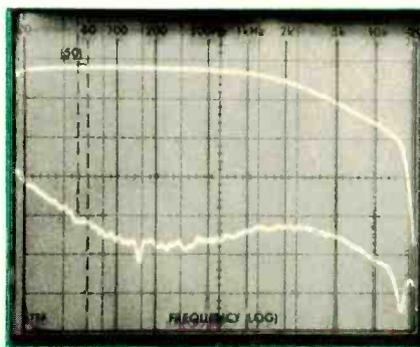Stereo separation was very good, and as claimed. Figure 6 is a scope photo showing a continuous plot of separation and frequency



response (including 75- $\mu$ s de-emphasis). Vertical divisions in Fig. 6 are equal to 10 dB of amplitude difference. The frequency response of the desired channel (shown by the upper trace) was well within 1 dB of the prescribed

curve from 30 Hz to 15 kHz.

The variable muting and variable stereo-only threshold controls cover a wide range and enable users to take proper advantage of these features regardless of signal conditions in their areas.

### Summary

An overall product analysis is given in Table 2, together with our summary comments.

As indicated, the sound quality was excellent, with background noise on strong-signal stations pushed so far down as to be inaudible both in mono and stereo. Construction details (not apparent in the photos) include totally modular design, chrome-plated shield plates and zinc castings for the front-panel side sections and light alloy profiles to complete the subdued-looking front panel and its hinged bezel. Rear-panel connections are recessed so that plugs never interfere with a back wall or surface against which the unit is to be mounted.

Many of you may be familiar with ReVox's superb open-reel tape decks that, although they are often purchased for home use, are regarded generally to be of true professional

## B-760 UPDATE

After we completed our lab measurements, we advised the U. S. headquarters of Studer ReVox in Nashville of our findings regarding harmonic distortion readings when we applied full (U.S. standard) modulation to the prototype unit supplied to our lab.

The company immediately sent a *Telex* to the European headquarters, and has since been advised that this early prototype was typical of detector bandwidth requirements in Europe, where stations are often crowded even more closely together than in the U.S. Studer ReVox also reported that modifications incorporated in *model B-760* units being shipped to the U.S. have resulted in a lowering of the THD figures so that their present published specification will read 0.1% THD (for 40-kHz modulation) as compared with 0.15% THD as first specified. Units presently in production are typically running 0.05% distortion for 40-kHz deviation and around 0.1% for a full  $\pm 75$  kHz modulation, such as is practiced in the U.S. The manufacturers appreciated our bringing this matter to their attention, and we, in turn, thanked them for their prompt response and action. If their currently reported distortion measurements prove to be the case with units now being shipped to the U.S. (and that would mean all units, since our measurements were conducted upon a first available prototype), this would negate our only criticism of this excellent tuner.

### TABLE 2

## RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Studer/ReVox

Model: B-760

### OVERALL PRODUCT ANALYSIS

Retail price	\$1145
Price category	High
Price/performance ratio	Very good
Styling and appearance	Excellent
Sound quality	Excellent
Mechanical performance	Superb

**Comments:** Compared with previously tested frequency-synthesized, crystal-controlled digital readout FM stereo tuners, this latest entry from Studer ReVox is something of a bargain. Of the other two popular models currently available (Sherwood's *model Micro/CPU 100* and Lux's *model 5T50*), the former has nonvolatile memory for four favorite stations, while the latter "remembers" up to seven. The ReVox model (selling for considerably less) stores in its memory up to 15 of your favorite FM stations and will, like other frequency-synthesized tuners on the market, guarantee tuning accuracy (and, hence, lowest distortion) that is governed only by the accuracy of the reference crystal—in this case, 0.005%, or 5 parts-per-million. An additional (if not obviously) advantage is that the ReVox model can be tuned in increments of as little as 25 kHz. This means that it will not only take care of European FM station frequency assignments (these can be as little as 50 kHz apart from each other in certain countries); but if you want to use a wireless FM microphone with this tuner, its tuned-to frequency does not have to be a multiple of 100 kHz, or 200 kHz, and you would still be able to tune to it with great precision and low distortion. The one design flaw was that the IF-detector section could not handle U.S. high-modulation levels, as explained in the text. Even so, the measured distortion levels were, in most cases, lower than the inherent distortion of the program sources (and modulation practices) of many FM and stereo FM stations in the U.S. We believe that once ReVox is aware of this problem, a quick fix will be found, since at lower modulation levels (up to 70% of U.S. standards), distortion is as low as one could expect from an otherwise excellent tuner.

quality and ruggedness. It appears that much of the same design philosophy has been applied to the *model B-760* tuner, and it should enjoy good acceptance from those audiophiles who really care about the quality of their FM equipment. If there had not been a small problem in measuring distortion, our overall pro-

duct rating might have been an "excellent" or even a "superb." Under the present circumstances (which may well be modified by the manufacturer) we can only assign a "very good" to this product, taking due account of its price and other remarkable performance and convenience features.

R-E

# Shure V15 Type IV Phono Cartridge

LEN FELDMAN

CONTRIBUTING HI-FI EDITOR


SHURE BROTHERS' LATEST CONTRIBUTION TO phono cartridge science is the *model V15 Type IV*, a pickup that introduces several new design features that, altogether, significantly improve its trackability—the ability of the stylus to stay in contact with both walls of a record groove at extremely light tracking forces. The *model V15 Type IV* is shown in Fig. 1.

The effective stylus mass in the *model V15 Type IV* has been lowered to 0.29 milligram, a reduction of approximately 12% compared with Shure's *model V15 Type III* cartridge.

This reduction was accomplished by using a telescoped shank structure and a lightweight, high-energy magnet. The *model V15 Type IV* also incorporates a two-function bearing system that Shure claims has been independently optimized for low and high frequencies. Another feature of the stylus assembly is its hyperelliptical nude diamond tip.

Very low-frequency record warps (between 0.5 Hz and 8 Hz) can result in changes in the distance between the cartridge and the record. These changes can cause groove skipping, cartridge bottoming, signal wow and even amplifier or speaker overload. The *model V15 Type IV* cartridge features a built-in, viscous-

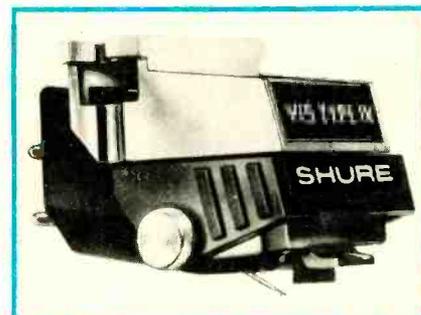damped dynamic stabilizer. Because it is viscous-damped, the stabilizer also resists sudden warp-caused changes in motion, thereby maintaining a proper vertical tracking angle and



CIRCLE 103 ON FREE INFORMATION CARD

### MANUFACTURER'S PUBLISHED SPECIFICATIONS:

**Frequency Response:** 10 Hz to 25,000 Hz. **Trackability** (at 1-gram tracking force, mounted in SME tone arm): 29 cm-per-second at 400 Hz; 42 cm-per-second at 1 kHz; 47 cm-per-second at 5 kHz; 37 cm-per-second at 10 kHz. **Output Voltage** (at 1 kHz, 5 cm-per-second peak recorded velocity): 4.0 mV-per-channel. **Channel Balance:** within 2.0 dB. **Channel Separation:** minimum, 25 dB at 1 kHz; 15 dB at 10 kHz. **Optimum Load:** 47,000 ohms in parallel with 200-pF to 300-pF capacitance per channel. **Inductance:** 500 mH. **DC Resistance:** 1380 ohms. **Tracking Force Range:** 0.75 gram to 1.25 grams. **Force Exerted by Dynamic Stabilizer** (added to arm tracking force setting): 0.5 gram. **Mounting Centers:** 12.7 mm (standard, 0.5 inch). **Net Weight:** 6.4 grams. **Suggested Retail Price:** \$150.

stylus tracking force.

Static charges on a record can attract the cartridge to the record surface, again changing the arm-to-record distance, vertical tracking angle and stylus tracking force. Static electricity also discharges through the stylus and amplifying system and is often heard as rapid pops and clicks. The *model V15 Type IV* deals with this problem by having a group of over


10,000 electrically conductive fibers in the dynamic stabilizer. This brush-like arrangement sweeps the record grooves, picks up the static electricity and discharges it through the cartridge ground terminal. The fibers also sweep the record grooves free of dust, and are ultra-fine with an approximate diameter of 7.6 microns (0.0003 inch).

Three types of replacement stylus assemblies are available for the *model V15 Type IV* cartridge. The *model VN45HE* is a hyperelliptical nude diamond-tip stylus assembly, which is the exact replacement for the stylus assembly supplied with the original cartridge. It is identified by a black grip and a black nameplate. The *model VN4G* stylus assembly features a 0.0006-inch-radius spherical (conical) nude diamond tip, and is identified by a black grip and a gray nameplate. For playing monophonic 78 RPM records, a biradial (elliptical) nude diamond tip is provided in the *model VN478E* replacement stylus assembly. This tip has radial dimensions of 0.005 inch by 0.0025 inch, and will track at forces between 3/4 gram and 1 1/4 grams.
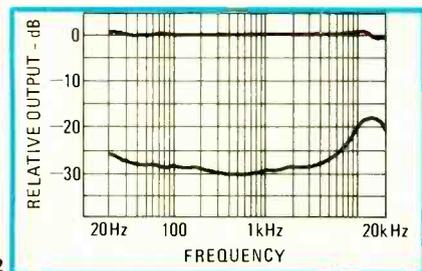
### Laboratory measurements

Results of our laboratory measurements of the *model V15 Type IV* cartridge are summarized in Table 1. Two types of test records were used to measure cartridge frequency response. The first record, STR-100 (manufactured by CBS Records) offers constant velocity signals up to 500 Hz, at which point the cut switches to constant velocity (5 cm-per-second). The second record, CBS STR-130, is recorded using the standard RIAA recording curve. We translated the first results (from the STR-100) below 500 Hz to the equivalent of constant velocity so that a flat response curve could be presented. For the STR-130 tests, we used a laboratory preamplifier that has an accuracy of better than  $\pm 0.2$  dB over the entire RIAA range from 20 Hz to 20,000 Hz. We suspect that the small deviations in these test records are probably greater than any deviation from the flat response of the cartridge itself, and so we averaged the two results to plot the final response curve, (the upper trace in Fig. 2). Shure Brothers, in their own production-line testing, used a frequency-response envelope that is only  $\pm 1$  dB wide to around 8 kHz, increasing to around  $\pm 2.5$  dB at 20,000 Hz. This "limit envelope" is shown in Fig. 3. Note that in Fig. 2, our test sample performed considerably better than the limits permitted by Shure, with variations less than  $\pm 1$  dB from 20 Hz to 20 kHz.

The lower curve of Fig. 2 shows the separation between channels obtained over the entire audio range; again, this separation far exceeded Shure's minimum specifications at the two test



frequencies, 1 kHz and 10 kHz.

### Summary

The overall product analysis, together with our summary comments, is in Table 2.

**TABLE 1**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**


Manufacturer: **Shure Brothers Inc.**

Model: **V15 Type IV**

### PHONOGRAPH CARTRIDGE MEASUREMENTS

	R-E Measurements	R-E Evaluation
<b>FREQUENCY RESPONSE (Hz-kHz, <math>\pm</math> dB)</b>	20-20, 1.0 See Fig. 3	<b>Superb</b>
<b>STEREO SEPARATION</b>		
Separation, 1 kHz (dB)	29.0	<b>Excellent</b>
Separation, 10 kHz (dB)	18.0	<b>Excellent</b>
Separation, 30 kHz (dB)	N/A	<b>N/A</b>
<b>CHANNEL BALANCE, 1 kHz (dB)</b>	0.5	<b>Superb</b>
<b>TRACKABILITY MEASUREMENTS</b>		
Stylus velocity at 1 kHz (cm-per-second)	43	<b>Superb</b>
Stylus velocity at 10 kHz (cm-per-second)	37	<b>Superb</b>
<b>COMPONENT MATCHING CHARACTERISTICS</b>		
Output level, 1 kHz, 3.54 cm-per-second (mV)	3.0	
Optimum load impedance (ohms)	47,000 (200 to 300 pF)	
Tracking force range	0.75 to 1.25 grams	
Cartridge weight (grams)	6.4	
<b>OVERALL PHONO CARTRIDGE RATING</b>		<b>Superb</b>

As with any phono cartridge, the final test is in the listening. Therefore, Shure has developed a test record containing instrumental selections (orchestral bells, flute and harp) of increasing intensity so that you can check trackability under practical musical listening conditions. The record also contains a series of subaudible tones superimposed upon music; this allows you to determine system resonance quite easily. This test record also shows how effective the dynamic stabilizer of the *model V15 Type IV* is in reducing the effects of arm/cartridge resonance, since it is possible to play these bands with and without the stabilizer for comparison. The record (Shure *TTR-115*) is available as a bonus to purchasers of the *model V15 Type IV* cartridge. Needless to say, the *model V15 Type IV* was able to track the most heavily recorded passages of this disc with clar-

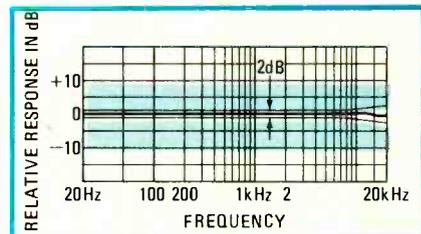

ity and extremely good musical definition. Nor could we find any other "obstacle course" records that were beyond the capability of this cartridge. For serious-minded audiophiles who want the very best musical performance from their precious discs, the relatively high-priced *model V15 Type IV* cartridge will prove to be well worth its cost.

**TABLE 2**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer: **Shure Brothers, Inc.**

Model: **V15 Type IV**

### OVERALL PRODUCT ANALYSIS


Retail price	<b>\$150</b>
Price category	<b>High</b>
Price/performance ratio	<b>Excellent</b>
Styling and appearance	<b>Excellent</b>
Sound quality	<b>Superb</b>
Mechanical performance	<b>Excellent</b>

**Comments:** We wonder why Shure Brothers calls their newest and most expensive cartridge the *model V15 Type IV*. This seems to suggest a relatively minor updating from the well-accepted *model V15 Type III*. Actually, the *model V15 Type IV* represents a quantum leap in engineering, performance features and concepts over the earlier *model V15 Type III*. Shure has managed to take into account many of the problems that plague the home user of a phono system and not just designed a cartridge that performs well under ideal test conditions.

The *model V15 Type IV* achieves the sought-after straight-line frequency response that totally eliminates that peaked high-end shrillness encountered with many other cartridges. This may take some getting used to, since many are conditioned to expect such false high-end response from their records. Proper cartridge loading was made easier, too, since, unlike other Shure models, 200 pF of capacitance (not difficult to obtain with a few feet of audio cable combined with arm-lead and whatever other stray capacitance is "built in" to most systems) smooths out any slight upper-resonance peaks.

Our listening tests convinced us that the clean sound of the highs was also due, in part, to the lower tracing distortion made possible by the new, hyperelliptical diamond stylus tip shape. This shape not only maintains good contact with high-frequency undulations in the record groove, but also maintains that contact over a greater area of the groove wall than do conventional elliptical tips. The dynamic stabilizer, coupled with the graphite fiber destaticizer, really works—its audible benefits are easily discerned, especially on seriously warped discs.

# Scanners will never be the same

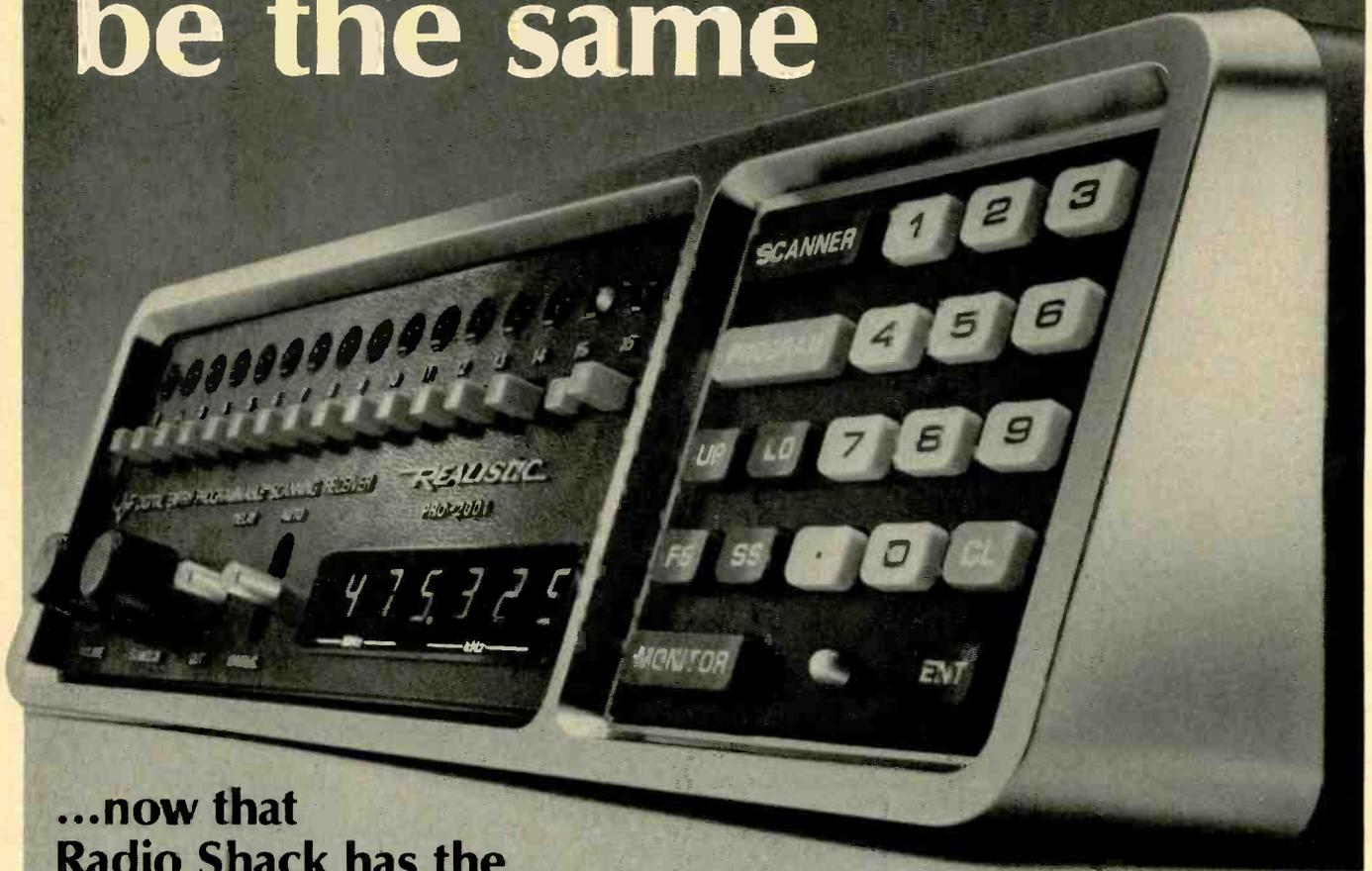

## ...now that Radio Shack has the amazing new Realistic 2001 with built-in microprocessor!


The PRO-2001 makes possible continuous, automatic reception of six UHF and VHF bands for all kinds of action — police, fire, Ham, weather, mobile telephone, railroad communications and more. And with its microprocessor you can program it for any 16 of 16,650 frequencies, without buying crystals!

Enter familiar area frequencies. Use the digital keyboard to punch-in actual frequencies for monitoring, storing or exploring — no codes or switches to slow you down. A special ENTER button reduces accidental entries. Digital readout shows which frequencies are being scanned, monitored or programmed into the memory. And you can monitor any frequency without entering it into the

scanner — it's like having a seventeenth channel for even greater versatility!

Search for "unknown" frequencies. The 2001's powerful search capability lets you find new, often unpublicized channels. Just enter lower and upper limits (they can even be in different bands) and select the search speed. The rest is automatic!

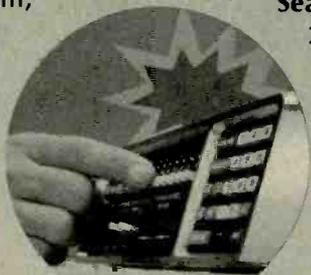"Traditional" deluxe scanner features. LED channel indicators and individual lockout buttons. Automatic or manual scan. Switchable scan delay. High-speed skipper circuit. Built-in speaker, jacks for recorder, headphone, external speaker. With power cables for home or mobile use. The Realistic® 2001 — a revolution in action radio. About \$400.\*



Mobile use in some states and localities may be unlawful or require a permit — check with local authorities.



### FREE! New '79 Catalog

Come in for your copy and see what's *really* new in electronics. Bigger than ever! 176 pages, over 100 in full color. 2000 exclusive items.

\*Price may vary at individual stores and dealers.

SOLD ONLY WHERE YOU SEE THIS SIGN:

# Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102  
OVER 7000 LOCATIONS IN NINE COUNTRIES

# Forest Belt tells...

## What You Need To Know About SPECIAL SIGNAL GENERATORS

TO FIND OUT WHAT'S WRONG with a TV, hi-fi stereo system, or any other receiver, we must know where the circuitry fails to process its signal correctly. Spot the stage that messes up or blocks a signal, and you're more than halfway to curing the problem.

Two procedures have long served troubleshooters: signal tracing and signal injection. Both are intensely practical; both are fast; both are dependable—when you're sure of the signal being fed into the set.

That's where today's special signal generators come in handy. They produce specific, definite input signals, sometimes for the front end of a receiver, sometimes for a particular section. In either case, you can be sure of what you're dealing with as you diagnose troubles, and this confidence speeds repairs. You cannot always be that certain when you depend on station signals for testing.

A few generators today have evolved into multipurpose instruments that justify the term "analyzer" (which indeed several are called). This month's Special Section introduces you to some of these unique instruments, and tries to guide you in taking advantage of the new efficient troubleshooting they can provide. This issue we cover stereo troubleshooting. Next month TV.

# Want To Fix Radios? Think Stereo

*It takes a particular breed of signal generator to service quality radios. For FM stereo, you can use special-purpose analyzers or take advantage of some of the features of your TV sweep generator.*

IT'S GOOD SOMETIMES TO REVISIT THE SO-called "ordinary instruments." Like radios, for instance. Who thinks much about radios these days? Yet there are plenty of them around that need—and are worth—repairing.

Radios fall into four categories:

1. Inexpensive models, which are seldom worth bothering to fix. You can't work on them without charging a sensible fee, and that may be as much or more than a new set costs. Consider these sets as "throwaways."

2. Quite a few AM/FM clock radios and table models are good enough (and cost enough) to be worth making minor repairs. If you are familiar with these sets, they are easy to troubleshoot. A share of their troubles falls among clocks or switches that you typically replace rather than repair. Some table models are stereo.

3. Autosound has become a hot item in the electronics field. A truly elegant car stereo system now costs more than a TV set, even more than color TV in some cases. And in no way is a car stereo owner going to throw *that* away! Some technician will be asked to repair it whenever it doesn't sound right or goes on the blink. Besides that, a great many auto stereo systems are sold and installed by electronics dealers with service facilities. Many underdash and in-dash systems far outperform those available from the car manufacturer. (Indeed, car dealers are dipping into this quality autosound sales market by installing—or having an expert install—systems not provided by the car manufacturer.)

4. Home stereophonic and quadriphonic systems almost invariably include an AM/FM (or FM-only) tuner or receiver. In many systems, this is the prime music source. It has to be sold, installed and serviced periodically. There are few complaints about repair fees on these

<sup>1</sup> Forest Belt wrote six books on *1-2-3-4 Servicing*, published by Howard W. Sams & Co., Inc., Indianapolis, IN 46206. Forest also teaches basic *Easi-Way Servicing*, an advanced version, in his Training Workshops. If you'd like to see us devote one whole special section to the principles of *Easi-Way Servicing*, drop us a note.

systems, as long as the repair work is top-notch.

Radio servicing is not yesterday's orphan. It is today's strong, profitable business. You deal with stereo sets, in most cases. And that's no "bubble-gum-and-baling-wire" kind of servicing; it's right up there full of advanced technology.

"Never did like TV sets," one oldtime service tech told me a while back. No need for him to; he makes a respectable living fixing radios. He's good. He knows AM/FM/stereo sets inside out. From table models to hi-fi component receivers, radios are his specialty.

"I didn't think much of transistors, either," he continued. "But you learn what you need to." Watching him work, you'd think solid-state never bothered him at all.

What about IC's? "No problem," he answered. Just like that. Then, after a pause, he admitted, "Well, I have my share of dogs, but I'm learning to trust



Sound Technology model 1000A

my judgment with integrated circuits."

So, if you haven't given radios a serious look lately, it's time you did. New technology has been used in them just as in TV sets. And high-grade instruments make the servicing just as definite a process. Haphazard work has no place in troubleshooting stereo radios. They're not difficult to fix, but neither are they simple gadgets that you can repair by guesswork alone.

#### What it takes

As with any electronics servicing, you

first need a no-hesitation way to move directly toward an accurate diagnosis. If you don't have your own logical troubleshooting system, consider the method I call *Easi-Way*. This method is a refinement of *1-2-3-4 Servicing* (see box).

Additionally, you need to know what's in all those sections, stages and circuits, and how they should act normally.

Highly important today, precisely because technology has spread so rapidly into ordinary radios, are special test instruments. Chief among those designed for radio servicing is a multiplex generator. The complex nature of an FM stereo signal dictates that an instrument duplicate dependably the signals and combinations required for testing and adjusting. Just because much of the multiplex circuitry now resides in an IC does not eliminate the need for a distinct test signal. In fact, as you'll see presently, IC servicing makes a good generator absolutely necessary. Without one, you can only guess at what's actually happening in a faulty radio (or in a working radio, for that matter).

Not that there are many choices. Only a few manufacturers build generators now for servicing stereo radios. Table 1 lists those models for which we've been able to obtain information. These multiplex generators each produces a composite stereo signal that contains pilot, L + R and L - R sideband signals. The composite signal can be used alone to test multiplex sections directly, or can be frequency-modulated on an FM-band station frequency so that you can feed it through the RF and IF stages. This latter mode tests the operation of the whole receiver, from antenna terminals to speakers.

Three of the generators listed in Table 1 provide sweep alignment for FM receivers. However, each unit does this differently. The Heathkit *model 1G-5237*, for example, provides a sweep at the generator's 100-MHz RF center frequency. The sweep width is variable to 750 kHz, which is sufficient to let you assess the 250-kHz bandwidth needed in the RF and IF stages of an FM stereo receiver. A

5.35-MHz crystal oscillator supplies a fixed RF signal at 10.7 MHz, so that you can "mark" the IF sweep-response curve or prealign the IF adjustments. Moreover, its 17th through 20th harmonics occur at 90.95 MHz, 96.30 MHz, 101.65 MHz and 107.00 MHz. These signals let you check operation and dial calibration in the front end.

On the other hand, Sencore's *model SG165* provides a sweep signal for IF alignment only. A 10.7-MHz center frequency is swept 500 kHz wide, which is quite sufficient for testing full bandwidth (a function of the IF strip anyway, not of the RF section). A 10.7-MHz marker identifies where the precise center of the IF passband should be.

The Sencore generator offers an extra feature for working with AM/FM sets. It furnishes front-end signals at 535 kHz–1635 kHz for AM broadcast receivers. And fixed RF signals at 262 kHz and 455 kHz allow quick, accurate IF alignment in either auto or home receivers that pick up AM broadcasts.

Sound Technology's *model 1000A* provides a unique alignment method. It uses what they call a "dual-sweep" signal. The usual 60-Hz sinewave signal, which frequency-modulates the generator's RF center signal *and* drives the oscilloscope's horizontal amplifier during sweep alignment, is in this case itself modulated with a 10-kHz signal. The result is an unusual scope display that conveys a quantity of information in addition to just bandwidth. Intermodulation distortion, for example, in the whole RF/IF/demodulator system can be calculated directly from the scope display. Also, discriminator alignment can be perfected for minimum distortion, a highly desirable technique for quality hi-fi and autosound stereo receivers.

Of course, all these instruments include the regular composite multiplex signal, similar to the *Leader model LSG-231*. Alignment of RF and IF sections can also be managed with an ordinary RF signal generator, although you cannot easily verify the bandwidth or discriminator symmetry by using single-signal alignment. For correct multiplex alignment, however, you must provide a stereo multiplex signal.

### Alignment troubleshooting

Communications technicians long ago learned a fast way to diagnose transmitter/receiver faults: alignment. Some TV technicians use this technique for color TV servicing and, of course, in the RF and IF sections of TV receivers.

You feed in an alignment test signal, and trace its effects with an oscilloscope or other appropriate instrument. Along the way, you proceed with alignment. Any stage that does not respond to adjustment, or does not produce the proper effect, must be defective. This combination of injection, tracing and aligning

TABLE 1—Stereo Generators

	FM Freq. (MHz)	Pilot Signal (kHz)	SCA Signal (kHz)	Audio Signals (Hz)	RF Output (mV)	Composite Output (V)	Sweep Width ( $\pm$ kHz)	Sweep Base for Scope	RF Markers (MHz)	AM Freq. (kHz)
<b>Heathkit IG-5237</b>	100 (var. $\pm 2$ )	19 38	65 or 67	400 1000 5000	n.a.	n.a.	750 (var.)	Yes <sup>1</sup>	10.7 90.95 96.30 101.65 107.00	
<b>Leader LSG-231</b>	100 (var. $\pm 1$ )	19	67	1000	0.1 –10	0–1				
<b>Sencore SG165</b>	86–110 tunable	19	67	400, sine- and square wave	FM, 0.1; AM, 100	0–2.5	500 (at 10.7-MHz only)	No		525–1625 tunable
<b>Sound Technology 1000A</b>	88–108 tunable	19	67	1000	0–30	0–5	600 <sup>2</sup> (var.)	Yes		

**Notes:**

- <sup>1</sup> Through composite signal jack.
- <sup>2</sup> Patented dual-sweep system—see text.

n.a. = information not available.  
var. = variable.

pinpoints just about any defect. At the very least, it helps you diagnose the faulty section and localize the defective stage very quickly.

Let's see how this concept works in the *Pioneer model TX-8500* stereo tuner. This chassis incorporates some of the very latest IC's. It is important to note how this troubleshooting technique uncovers a defective IC as easily as any other component.

For a signal source, we use here the *Sound Technology model 1000A*. You thus gain some familiarity with the dual-sweep signal. For viewing, a *Gould model*

*OS-1100* triggered oscilloscope is used.

Figure 1 is a block diagram of the tuner's sections and stages. Note that a great deal of the tuner's functions are handled inside IC's. All the more reason to approach the system logically.

Using the *model 1000A*, feed a modulated FM signal into the antenna terminals, using a 300-ohm matching transformer. Feed in enough RF to create a signal at the mixer that is large enough to observe on your oscilloscope. For the first steps in our example, the input level is 30,000  $\mu$ V.

Equipment interconnections are the

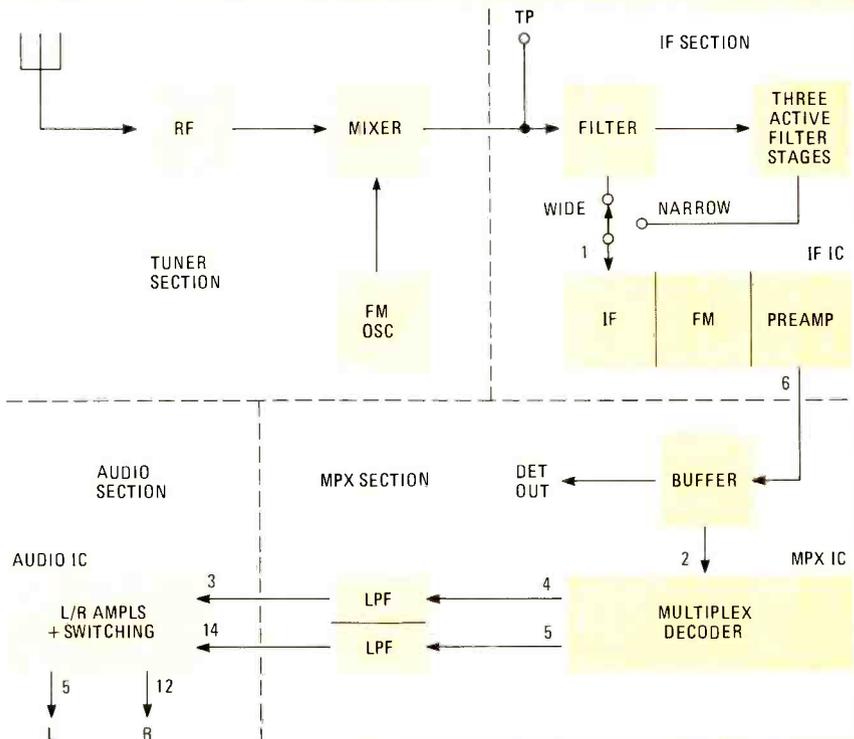


FIG. 1—EVEN WHEN A STEREO FM RADIO is not composed mainly of IC's, as this one is, it must have the stages shown here.

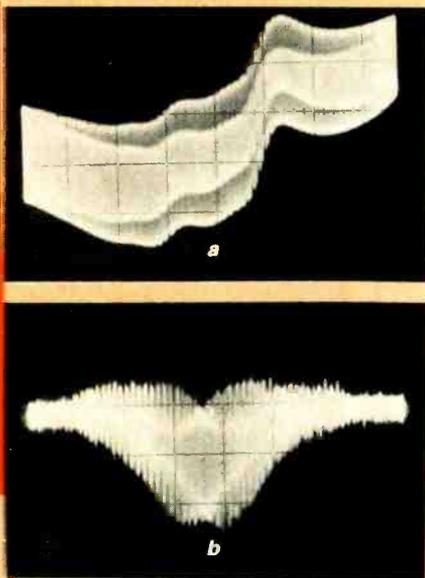


FIG. 2—SWEEP SIGNAL without demodulator probes shows (a) front-end amplification and tunability, and (b) the result of IF filters that determine selectivity and bandwidth.

same as for any sweep alignment. A 60-Hz output from the generator goes to the oscillator's horizontal amplifier. Switch a triggered scope to its X-Y mode of operation. In the *model OS-1100*, this converts Channel 1 into an X-axis or a horizontal channel; in some scopes, the triggered amplifier becomes the X-axis input channel. In this case, the vertical (Y-axis) input goes to Channel 2, and through a cable from the generator. A regular 1:1 scope probe, connected to a jack on the generator, can be used as a test cable for the receiver.

Turn everything on, and give the instrument a few minutes to warm up. Adjust the scope's X-axis input knob to produce a trace that does not overscan the screen. Set the stereo tuner dial and the generator RF output at the same frequency. The *model 1000A* must be set for dual sweep, and its sweep width must be at maximum (about 600 kHz).

Find your first test point; the tuner output is usually handy. Clip the test probe to the high side of the IF feed line, and the common clip to ground. Turn the

scope's Y-axis sensitivity control fairly high. You can expect a twisted-looking RF trace to appear, with an amplitude as much as 100 mV, maybe a bit less. Swing the tuning of either the tuner or the generator back and forth until you center this curve on the scope trace.

Figure 2-a shows how this dual-sweep trace is likely to look when you check out the tuner's RF section—consisting of the RF amplifier, oscillator and mixer. There is slight (or no) RF signal; if you are unable to tune this sweep curve (move it back and forth by dialing the tuner or generator) this signifies trouble right in the front end. Troubleshoot these stages before you proceed. And *only* when they prove OK are you ready to go on to the IF section.

The *model 1000A* tuner has a narrow bandwidth for weak-signal stations. One filter allows the usual 250 kHz+ bandwidth; the extra filters, when they're switched into the signal path, cut the bandwidth to a sharply skirted, barely 250-kHz bandpass signal. In either mode, the filters determine the IF selectivity. So, your next step is to verify that the filters pass the IF signal properly.

Move your test probe to the output of the filters. In this receiver, a good test point is at the input to the IF amplifier. This is at pin 1 of this particular IC, which is beyond the filter stages.

Filters are passive elements. What active transistors there are in the narrow-band filter stages achieve mainly impedance matching. Therefore, in either mode, there is a signal drop across the filter system. Don't expect more than perhaps 20 mV of signal just past the filters. If there are any tuned circuits between the front end and the IF amplifier, peak them now.

Change the scope sensitivity so that you can observe such a small signal (see Fig. 2-b). The bandwidth-limiting effect of the filters is clearly visible. (If you've never seen a trace like this before, don't worry. It's a result of the unique dual-sweep signal from this *model 1000A* generator. Without it (that is, using a regular stereo signal) you would not be able to see

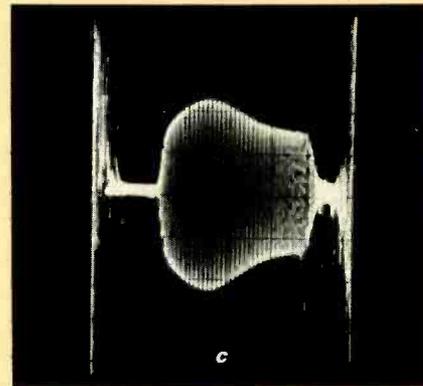
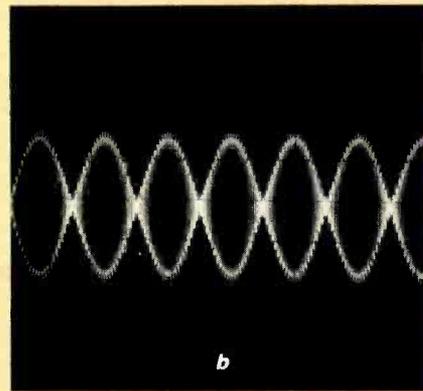
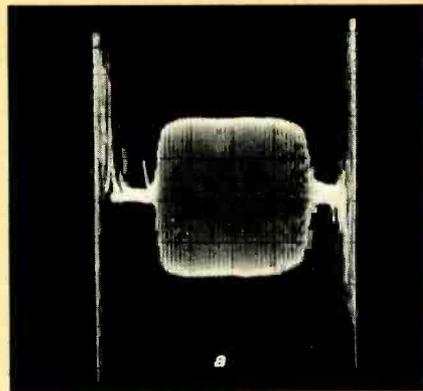


FIG. 4—DUAL-SWEEP PRESENTS unfamiliar but informative response curve (a) at the output of IC that demodulates FM signals. The signal at (b) results at same point when standard stereo signal is fed in. The trace at (c) shows how a slightly misadjusted FM detector can seriously alter the dual-sweep curve, creating considerable IM distortion.

so definitely the effects of the filters.)

All okay so far? You're ready to move on now to the IF section. Only two things can go wrong with the IC: It can develop an internal short that fouls up DC voltages both inside and out, and the same defect will probably also block or upset the signal operation. Or, the IC can mess up signals even without showing DC symptoms.

Obviously, a signal test is your quickest means of verifying that the IF integrated circuit is operative. The diagram of internal functions for this IC is shown in Fig. 3. The input to the IC is at pin 1, and you've already proved the signal is OK there.

This IC performs many functions: It amplifies the IF signal, demodulates the

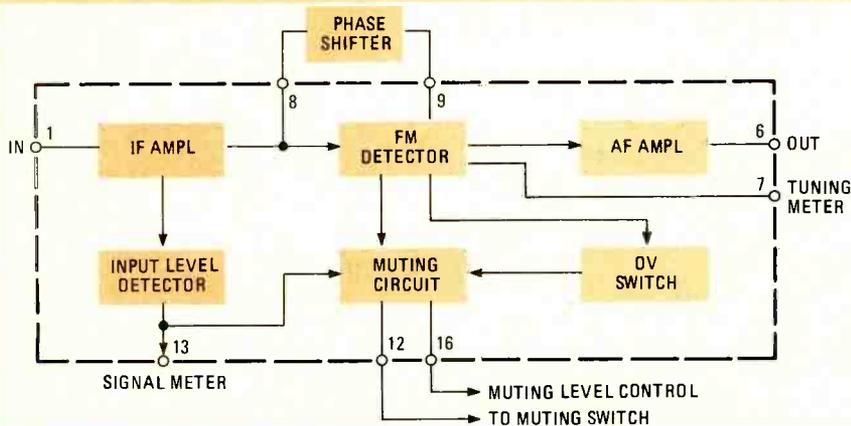


FIG. 3—THIS NEW IC CONTAINS almost everything needed to amplify IF, demodulate FM and amplify composite stereo signals—plus it offers several peripheral functions.

FM signal (the dual-sweep waveform, in this case), and adds some amplification to the recovered signal. Because certain peripheral operations originate here, you should check this IC if one of these is malfunctioning. First, however, you should make a signal check at output pin 6. Figure 4-a shows the demodulated version of the dual-sweep signal.

If you feed a stereo signal into the tuner from the generator, you observe a signal composed mainly of L - R sidebands at this point. Figure 4-b shows this kind of output from the IF integrated circuit. The signal has been demodulated by a quadrature detector in the IC (note the outboard phase-shift stage).

It is important to remember that as you use your scope to trace through the receiver stages, you should keep reducing the generator output to just the proper degree for a clean trace. The best generator RF level for every test can be found by reducing the generator output until the trace begins to look "grassy" or noisy, then by increasing the level just enough to clean up the display. The generator-output setting for all the traces shown in Fig. 4 is about 3000  $\mu$ V; this setting can vary with different receiver models.

One strong advantage of the dual-sweep signal shows up at this test point. You can spot instantly any misalignment of the FM sound detector. Any humps (Fig. 4-c) in the bandpass display can be attributed to defective demodulation. *Very carefully*, realign first one slug, then the other, inside the detector tuning coil (Fig. 5). A perfectly flat top and bottom for this waveform display indicate absolute minimum intermodulation distortion, which is the worst product of even a slight detector misalignment. You could not detect subtle misadjustments with a stereo pattern, nor with the usual S-curve method of detector alignment.

With IF and demodulation all taken care of, you can now turn your attention to the multiplex section. A buffer amplifier (Fig. 1) feeds a composite stereo signal (or, in our example, the dual-sweep signal) to the detector output jack and to the multiplex decoder IC.

Again, the construction of the IC itself

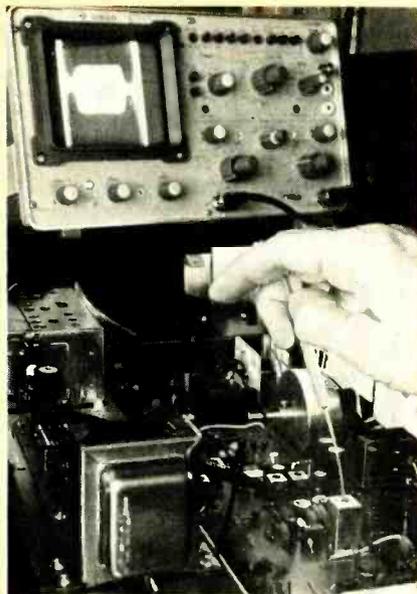


FIG. 5.—TO CORRECT FAULTY DUAL-SWEEP curve in Fig. 4-c, realign FM sound-detector coil at end of IF strip, while observing curve.

(Fig. 6) tells you what your troubleshooting approach should be. Verify that the signal arrives at IC pin 2 for the input. Then, check that pins 4 and 5 generate the demodulated L and R signals.

At this point, you may feel more comfortable switching to a stereo signal from the generator. But first, look at the dual-sweep signal once more at both output pins of the multiplex IC. The two traces should look exactly alike and bear the same amplitude. If so, it proves that the multiplex IC is not altering the overall frequency response. The 10-kHz modulation that is part of the dual-sweep signal has come through properly and without attenuation. The frequency response from 60 Hz to 10 kHz is essentially flat; no tilt has occurred.

#### Troubleshooting by stereo signal

Changing to a stereo test signal requires some alterations in the equipment connections. Leave the generator feeding between 300  $\mu$ V and 1000  $\mu$ V of RF signal into the tuner's 300-ohm antenna input. Set the generator function switch to stereo, the internal signal to L - R or

multiplex, and the modulation level to about 80 percent ( $\pm$  60 kHz).

Move the receiver test probe to Channel 1 of the oscilloscope. The sweep cable from the generator is left disconnected. Set the scope back to triggered operation, and set the scope timebase at 0.2 ms-per-division if the generator's internal audio is 1000 Hz, or at 0.5 ms-per-division if the audio is 400 Hz.

Clip the test probe to multiplex IC pin 2 to monitor the input. Make sure the receiver and generator are tuned to the same frequency. You should find between 0.5 volt and 1.0 volt at this point, depending on the modulation percentage at the generator. (In our demonstration setup, an 80-percent generator modulation results in 0.8 volt of signal input to the multiplex IC.) Figure 7-a shows how an L - R signal looks at this point.

Now, to check multiplex decoding, move the test probe to pin 4 or pin 5 of the IC. These pins should produce exactly equal signal amplitudes, about the same as the input level. The signals should also look alike (you can't check phase with this simple a setup, but it isn't necessary.) Figure 7-b shows how the decoded stereo signal looks.

If the signal is missing or distorted at this juncture, you know that you have to troubleshoot in the vicinity of the IC. Verify that all DC voltages are what they should be on each pin of the IC. If they are not, check whether the voltage change is caused externally or by the IC.

Then, examine the small components around the IC, particularly electrolytic capacitors. Some capacitors are there to introduce phase shifts, others to bypass unwanted signals (your scope can check this), and others to couple signals. In addition, leaky capacitors can upset DC voltages.

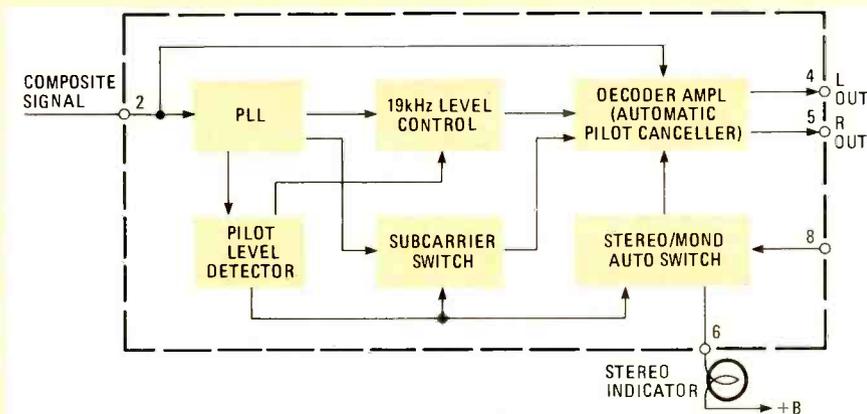


FIG. 6.—SINGLE IC OFTEN PERFORMS all stereo multiplex decoding functions; needs only external low-pass filters following, to eliminate L - R sideband products.

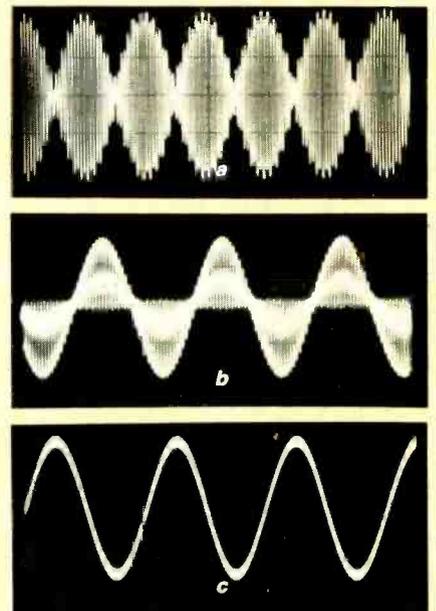


FIG. 7.—WAVEFORMS TAKEN FROM PINS of stereo IC of Fig. 6. (a) Input from FM detector; (b) decoded stereo; and (c) audio signal after sideband products are filtered out.

Finally, if the DC voltage checks OK and none of the components around the IC are bad, but a signal still doesn't show up as it should at the output pins, suspect the IC itself. One last hint: Make sure a defective low-pass filter is not loading down the IC output. Disconnecting the filters will show.

Next in your troubleshooting sequence, verify that the low-pass filters do what they should. You can move the test probe to the input pins of the amplifier IC, and clip alternately to pin 3 and pin 14. Two things happen to the signal. First, the sideband components are removed, leaving only the 1000-Hz sine-wave modulation (Fig. 7-c). Second, the filters pull down the amplitude (leaving in our demonstration only 0.2 volt peak-to-peak).

**TABLE 2—TV Sweep Generators for FM Radio Alignment**

	Frequency (MHz)	Markers Included
<b>Eico 369</b>	3-220, continuous	Tunable
<b>Leader LSW-333</b>	TV VHF/UHF 10.7 83-113	No
<b>Viz WR-514A</b>	TV VHF .05-50, 88-108	For TV only

Pins 5 and 12 are the output pins for the audio IC. The output usually runs between 2 volts and 3 volts peak-to-peak. At this point when you've checked this, the whole audio section of this stereo tuner has been tested. Again, watch out for small parts associated with the IC; any one of them could lead you to think that the IC is bad. But if they are all definitely OK and the voltages supplying the IC are normal, any other trouble must be blamed on the IC itself.

**Serious misalignment**

So far you have used a step-by-step, align-as-you-go method to troubleshoot an entire FM tuner. A special signal generator supplies the signals, which you track with your scope. The dual-sweep

technique offers obvious advantages but calls for an expensive instrument. What if you don't own this particular generator?


You can use this trace-and-align technique with any generator you do have. Some TV alignment generators cover FM frequencies. Table 2 lists some sweep generators that will work for this purpose.

A useful alternative has been included in the Sencore *model SG165* and the Heathkit *model IG-5237* stereo generators. Either of these generators can be used to perform plain sweep alignment of the IF signals and sound detector. The Heathkit unit lets you sweep-align both RF and IF sections, while the Sencore generator provides sweep only for the IF section. Either will do; remember that bandwidth and selectivity are determined in the IF strip and its filters, not in the front end.

The *Viz model WR-50C* RF generator offers something still different—it incorporates sweep outputs at 455 kHz and at 10.7 MHz. Moreover, an external crystal socket lets you plug in a 10.7-MHz crystal, giving a tightly controlled unmodulated RF source; the 20-mV output is ample enough to drive an IF strip.

It is not unusual to encounter an FM receiver that has been tampered with by its owner. Serious hi-fi buffs ordinarily know better than to try to fool around with coils in an expensive tuner. But you do encounter serious misalignment problems (sometimes caused by a technician who either doesn't have a proper signal generator or who has not been taught correct alignment procedure). In such cases, you need a fast way to adjust the alignment nearly right. When coils are far from their proper settings, you may be at a loss to correct them by just observing a sweep curve.

Begin with an accurate 10.7-MHz signal source. The Sencore *model SG165* has a crystal-controlled, unmodulated 10.7-MHz oscillator. The Heathkit *model IG-5237* has an IF marker output, held tightly at 10.7 MHz by a 5.35-MHz crystal; the output is sufficient to drive the IF's and limiters in most receivers. The Leader *model LSG-16* RF generator has

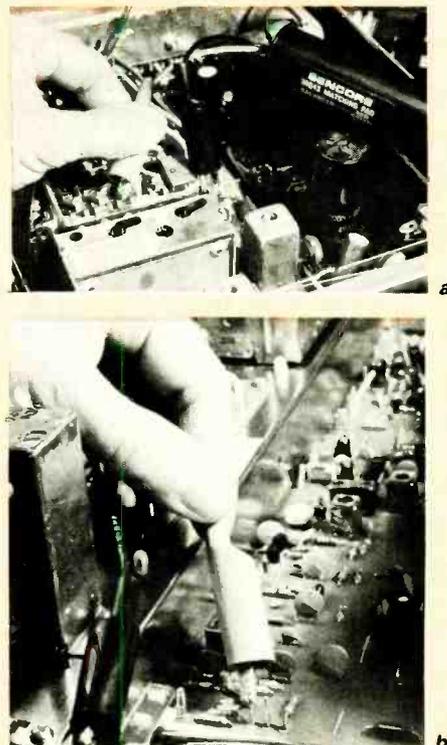

**FIG. 8.—INJECTION POINTS FOR IF single-frequency or sweep alignment: (a) on mixer tuning capacitor; and (b) at IF input link.**

a crystal feature similar to that of the *Viz model WR-50C*.

If crystal control is lacking, any good RF generator will do (see Table 3) if you do two things to insure pinpoint accuracy—which is particularly important with FM stereo demodulators.

1. Turn the generator on for at least an hour's warmup before alignment.
2. Check the output at 10.7 MHz with a frequency counter, and refine it precisely whenever you are ready to make the final sound-detector adjustment.

(The Hickok *model 257* RF generator has a counter output jack, which lets you leave the counter connected for monitoring.)

After selecting a precise source of 10.7-MHz unmodulated RF, feed this signal into the FM tuner mixer. Figure 8 shows two handy points: Clip the generator-output lead to the mixer tuning capacitor, or where the tuner feeds the IF strip on the main chassis board. In a car receiver, you can often clip the lead to the mixer-coil terminal, if it is easier to reach.

Find the electrolytic capacitor that bridges the balancing resistors in the sound detector. Connect a high-impedance DC voltmeter probe at the positive (+) end of the capacitor and the common lead to ground. This is your alignment indicator; if the receiver has a signal-strength meter for FM, you can use that. (Do not confuse this meter with a centering-type tuning meter. They are not similar.)

Rock the generator-output level control up and down to find a signal strength

**TABLE 3—RF Generators for FM Alignment<sup>1</sup>**

	Model	Frequency (MHz)	Output (mV)	Audio (Hz)	Built-in Calibrator
<b>B&amp;K/Precision</b>	E200D	0.1-54	100	400	Yes
<b>Eico</b>	330	0.1-54	300	400	
<b>Heathkit</b>	IG-42	0.1-30	100	400	
<b>Hickok</b>	257	0.1-54	100	1000	Yes
<b>Leader</b>	LSG-16	0.1-100	n.a.	1000	
<b>Viz</b>	WR-50C	0.085-40	50	600	Yes <sup>2</sup>
<b>Wavetek</b>	3001				

**Notes:**

<sup>1</sup> AM only; use without modulation.

<sup>2</sup> Also has 455-kHz and 10.7-MHz sweeps.

that does not saturate the indicator reading. Noise in the set causes a certain residual no-signal reading on the voltmeter. Set the generator output to make the meter read about halfway between this no-signal voltage and the level at which injecting more signal no longer raises the DC voltage reading. As you bring the IF strip into alignment, you may have to reduce the RF signal to keep this "halfway-between" reading. Otherwise, saturation prevents you from knowing whether your adjustments are improving anything or not.

Start with the last IF can. Adjust first the top slug, then the bottom slug for a maximum meter reading. Work your way back to the first IF coil, peaking the top slug first, then the bottom slug. Go through the whole IF strip at least twice, or until no further improvement can be made.

Do not tamper with the top slug (the secondary) of the sound-detector transformer yet. However, you can peak the bottom slug. You will probably have to revise this setting later, but this procedure presets it to nearly correct.

Now, to set the top slug of the detector, change your meter connection. Connect the probe to the resistor that is in series with the sound output (center tap) of the detector transformer. Be sure the coupling capacitor (if there is one) doesn't get between the transformer and your DC test probe.

Rock the top slug back and forth until you find an exact zero voltage. If the transformer and the diodes are OK, the voltage will swing sharply positive and

negative from 0 as you rock the secondary adjustment. You may have to jump back and forth between this adjustment and the bottom slug (change the DC meter connection each time). The two slugs do interact. A little patience (and work) will find the proper zero setting.

### Sweeping IF signals

Now, with the IF coils peaked, you are ready to inspect bandwidth. This demonstration is carried out for you with the Sencore *model SG165*, on a stereo receiver that does not use filters in the IF section. With filters, you seldom find more than one or two IF coils to adjust—typically between the mixer section and the IF strip. However, you generally find a sound-detector coil that may need adjusting.

Use a sweep generator set to 10.7 MHz, and connect the sweep RF to the same mixer or IF point used for your preliminary IF alignment (Fig. 8). Note that with the Sencore *model SG165*, you must use an oscilloscope that has a line-sweep function *inside* the scope, because the *model SG165* does not have a sweep-base output to connect to an oscilloscope. Hence, with this generator, you cannot use the X-Y mode of your triggered scope, and any triggered-sweep operation is impossible. We used the Sencore *model PS163* scope for our test; several other scopes, especially recurrent-sweep scopes, have a line-sweep mode.

The Heathkit *model IG-5237* and the Sound Technology *model 1000A* both have a 60-Hz sweep-base signal to feed a scope. The *model IG-5237* provides it via the composite signal jack, when you set the function switch for RF sweep. All the TV/FM sweep generators listed in Table 2 have a sweep-base output right on the front panel, ready to connect to the horizontal (X-axis) input of any oscilloscope.

This next step is important. Many technicians overlook it and become frustrated trying to set up a sweep trace in an FM receiver.

Disconnect the averaging capacitor that bridges the two balancing resistors in the sound detector. This is the same capacitor to which you clipped your DC voltmeter earlier. For sweep alignment, disconnect the positive (+) end of the capacitor; just leave it dangling. Then, connect your oscilloscope 10:1 probe to the point from which you disconnected the capacitor. This places the probe at the cathode end of the diode pair, and an up-direction sweep display on the scope screen. Set the scope input for 0.5 volt-division.

The Sencore *model SG165* generator uses post-injection markers; the scope probe therefore goes to a jack on the generator, and another test cable goes from the front panel of the instrument to the scope's vertical (Y-axis) input. To connect the probe inside the receiver, follow the same procedure.



Heathkit model IG-5237

Adjust the generator output to provide just enough signal so that a sweep display doesn't show a lot of "grass" or noise. Don't overdrive the receiver IF strip because this would show a false response. Also keep the markers as small as you can; with post-injection, they won't distort the curve but they can spread out and become confusing.

Now, use IF adjustments to bring about a flat-topped sweep response. Do not turn any single slug very much; pre-setting made them all fairly close. Watch the three markers, if you're using the Sencore generator. These markers are at 10.6 MHz, 10.7 MHz and 10.8 MHz. The curve should not turn down for skirting until its flat top is beyond the 10.6-MHz and 10.8-MHz markers.

Figure 9-a shows a typical IF response after preadjustment but before sweep touchup. The curve is slightly off-side. The IF cans must be touched up. Otherwise, bandwidth and tuning will not be symmetrical, and stereo recovery may not be dependable—particularly on any marginally distant station.

You will find that in each IF can, one core affects the tilt of the top of the response curve. The other core slides one end or the other of the curve under or out from under the markers. Very little adjustment is needed to place the properly shaped curve, evenly under all three markers, as shown in Fig. 9-b. Also adjust the bottom (primary) slug in the detector transformer.

The flat top of the curve should extend a bit beyond the two outer markers, to give a solid 250-kHz response. Be careful not to extend the top too far, or adjacent-frequency stations will try to capture each others' places on the dial!

Finally, you're ready to adjust the detector coil. Disconnect the scope and reconnect the capacitor you unhooked earlier. Now, find the resistor that comes from the center tap of the detector-coil secondary. This resistor is the sound-output point that precedes any coupling capacitor. Connect your scope probe there.

You may have to increase the scope's vertical-input sensitivity. Otherwise, the S-curve display may be too flat. You may also have to turn down the markers; if they are too large, they may confuse you as to where the center of the curve is.

Now, adjust the top slug of the detector-transformer sound so that the 10.7-

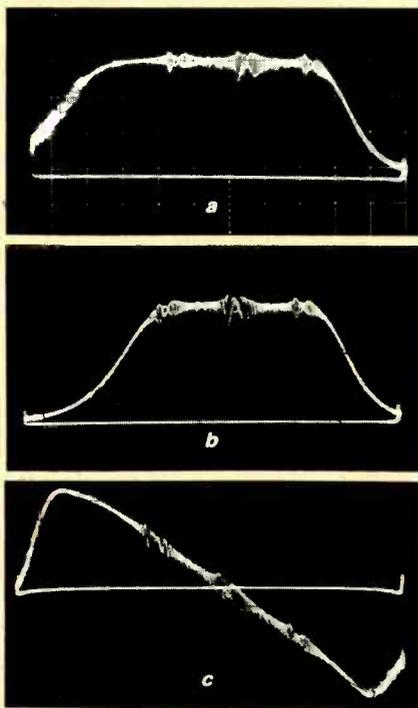


FIG. 9.—SWEEP-ALIGNMENT CURVES: (a) off-center from markers and too wide; (b) curve moved into position, with correct shape; and (c) detector S-curve set up symmetrically around markers, with 10.7 MHz at exact center.

### A Methodical Troubleshooting System

Basically, *Easi-Way Servicing*<sup>1</sup> comprises five steps. A brief description of each step gives some idea of how timesaving and direct this troubleshooting technique is.

**Step 1: Analyze the Functions** in an instrument. Consider a hi-fi system, for example. Operate the equipment and decide whether the trouble lies in a turntable, a tape or cassette deck, in the tuner function, or in the receiver's amplifier. You cannot afford to waste time hunting defects in the wrong equipment. This may seem an obvious point, but it often happens. The trick is to establish specific tests that let you analyze each function more or less independently of all others.

**Step 2: Diagnose the Section** that operates incorrectly or not at all. In a stereo tuner, it might be the RF section, the IF section, the demodulator, or the multiplex section. In a stereo or quadriphonic amplifier, the malfunction could occur in the preamp section, power supply, voltage amplifiers, tone control, or power amplifier; any of these could be at fault, and you can multiply by two (or four for quadriphonic operation). Diagnose *which* section, and you're way ahead of the game. Naturally, your aim is to focus troubleshooting attention only in the section actually containing the fault. That makes sense, but it's not always the way it happens. Again, the secret rests in specific procedures that prove your diagnosis.


**Step 3: Localize the Stage** that's bad within the section you diagnosed. I define a stage as a transistor, FET, diode, (or tube) plus its components and wiring.

An IC and its associated components can form a stage. Or an IC can be a whole section. A stage usually processes a signal; some stages process DC voltages (or voltage changes). The fact is, your tests for localizing a bad stage depend largely on what components are in the stage and what they should accomplish. But (a) you have only a few of these stages to test because of steps 1 and 2; (b) the tests are common and seldom complicated; and (c) you save a lot of other testing once you know which stage is bad.

**Step 4: Isolate the Circuit** that is causing the stage malfunction. Circuits are contained within a stage. Signal circuits include input coupling, output coupling, decoupling or bypass, feedback and tuned circuits. The DC circuits include the collector, base and emitter-supply circuits; bias dividers; and supply branches, etc. In DC-coupled stages, signal and DC circuits involve the same components; but you can test them either as DC-handling or as signal-handling circuits. And, of course, you only have a few circuits to test.

**Step 5: Pinpoint the Component** at fault, which is the ultimate goal. Obviously, the whole concept involves avoiding having to troubleshoot functions, sections, stages, or circuits that are really OK. All five servicing steps described here point you logically in that direction.

If you're an old-timer and successful, you probably already use all these steps. But it doesn't hurt to review good techniques. These steps are a godsend to technicians who were never taught a direct, straight-moving troubleshooting procedure. **R-E**

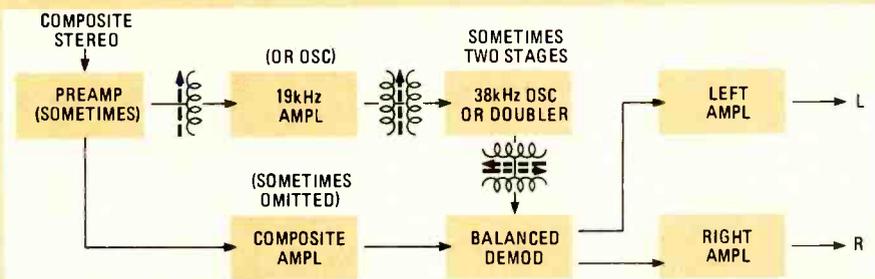

**FIG. 10.—STAGES IN NON-IC MULTIPLEX SECTION** actually work similar to IC types, but several adjustments are needed to keep them in alignment.

MHz marker is exactly centered on the S-curve. Touch up the bottom slug to make the S-curve symmetrical. Figure 9-c shows the symmetrical S-curve that you're trying for. (*Do not* make any other IF adjustments.)

Work back and forth between the top and bottom slugs. The bottom slug should cause the shoulders of the S-curve to be symmetrical and equidistant from the center marker. The top slug slides the whole curve back and forth around the center marker.

Disconnect the generator and the scope. You know if the IF section is not only operative but in tip-top alignment. Naturally, any nontunable coils you find along the way will alert you to troubleshoot the associated stage. Check the transistor first, then other components. Open bypass capacitors can make a coil tune more broadly than expected, distort the sweep curve to an impossible degree, and make coil-tuning seem erratic. Yet, you might not spot this trouble when you go through the set with an unmodulated IF signal. Nor is a faulty coil uncommon; ordinarily, it will fail completely to tune.

#### Stereo multiplex alignment

Integrated circuits in modern stereo receivers leave little adjustment either necessary or possible. But there are still many older receivers around that you may have to service. As with the rest of the receiver, alignment makes a fine troubleshooting technique.

Figure 10 shows the stages you can expect to see in the multiplex section of most stereo receivers. Without a multiplex IC such as that shown in Fig. 6, the balanced-detector system is the most used. The main differences lie in how the pilot signal from the station (or generator) develops a 38-kHz injection signal


for recovering the L - R, which then combines with L + R to form the original L and R signals. Some pilot signals lock a 19-kHz oscillator, which then is doubled to 38 kHz. In other sets, the pilot signal is amplified and then locks a 38-kHz oscillator. In either case, a 38-kHz signal goes to a balanced demodulator.

A composite stereo signal is sometimes amplified before being applied to the balanced demodulator, sometimes not.


To troubleshoot, start by aligning the 19-kHz and 38-kHz coils. Connect a 10:1 scope probe at the output of the last coil, the one that feeds the balanced demodulator. You'll find a handy clip-on point at the input end of either diode in the demodulator. Figure 11-a shows the 38-kHz sinewave that is present there. The scope timebase was set for 20  $\mu$ s-per-division; the vertical input was set for 5 volts-per-division, or whatever voltage it takes for a sizable display.

Peak all the transformers for maximum amplitude of the 38-kHz signal. This is not their final adjustment, but indicates whether any of them are defective. If one transformer fails to tune, investigate the stage around it as described. If there's no 38-kHz signal, use your scope to trace through this branch of the section to discover the reason.

Connect your scope probe to the center

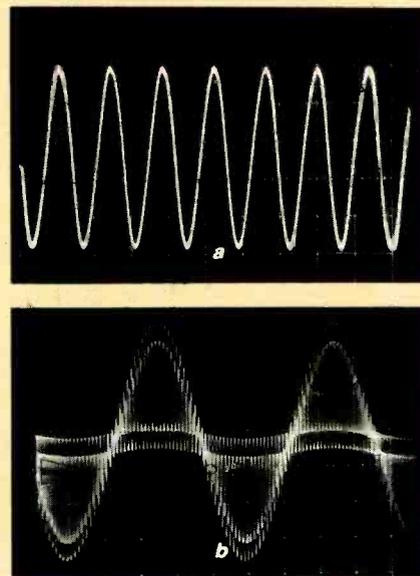

**FIG. 11.—PLAIN RF SIGNAL (a)** at 38 kHz injects carrier signal into balanced demodulator to beat against L - R sidebands and recover (b) L - R signal for stereo FM reception.

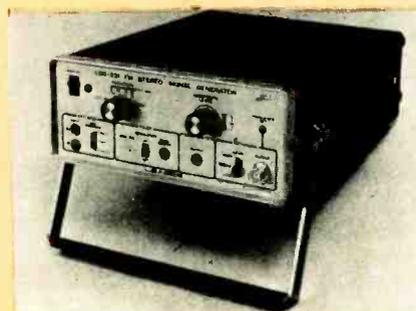

Leader model LSG-231

input point of the balanced demodulator. Set the generator to modulate only one side—say, the left side. The composite stereo waveform at the input to the demodulator is distinctive (Fig. 11-b). If it's missing or unduly weak, which means its amplitude is less than at the input of the section, trace backward until you find where the waveform reappears or shows normal amplitude.

A major criterion for good multiplex alignment is *separation*: When you feed a left-side-only signal into the stereo receiver, does any audio signal appear in the right-side amplifiers and vice-versa (of course)?

One easy way to check this is to first measure the output of both amplifiers using a monophonic signal, balancing them equally (which also proves that the amplifier part of the stereo receiver is working), and then switch to a stereo input with only one side modulated.

The meters on the Sencore model SG165 generator are already calibrated in decibels for comparing separation. Connect the meters to the left and right amplifier outputs. You are still feeding a stereo-modulated RF signal into the receiver's front end.

Turn the left-side modulation on and the right-side modulation off. Crank up the amplifier volume until the left-side meter indicates about three-fourths of full-scale. Then, very carefully tweak each transformer in the multiplex section. Try for a *maximum* left-side output, but with *minimum* reading on the right-side



Sencore model SG165



FIG. 12.—SENCORE MODEL SG165 METERS are calibrated to show exact amount (in decibels) of separation in stereo recovery system of FM radio.

meter.

You'll find it necessary to compromise. You will also discover that these adjustments are extremely critical, and that there is some interaction between trans-

formers. These are the same coils you peaked earlier, but those were rough adjustments. Now you are settling the phase right down to the very best obtainable for the demodulator. Perfect phase results in the best possible separation.

When the left-side output is at maximum and the right-side output is at minimum, set the amplifier volume so that the meter on the left reads exactly full-scale. The decibel scale will show that this establishes a zero-decibel reference. The meter on the right then indicates the decibel difference, the amount of separation. Figure 12 shows a stereo tuner exhibiting 25 dB of separation.

Switch the left-side modulation off and turn on the right-side modulation. Adjust the volume for a full-scale reading on the right-hand meter. The meter on the left should indicate the same low separation achieved with the opposite mode. If the two sides are unbalanced—that is, if separation is greater in one direction than in the other—you must refine the final adjustment, the balanced demodulator transformer. Also you must check the potentiometer separation control, if the set has one.

Finally, separation in both directions should meet the radio manufacturer's specification. Naturally, as you go along, defects can simply prevent you from accomplishing the necessary alignment. Once you are accustomed to making alignments tests, you can diagnose a set quicker this way than it takes to read about it. R-E

### Low-priced programmable TV game IC's introduced

"A winner for next Christmas," says R. C. Norwood, general manager of General Instruments Consumer Products Line, referring to the company's new low-priced programmable (LPP) game set. Norwood indicated that the product has already received an enthusiastic response from such manufacturers (among others) as Radofin and General Electronics.

The LPP system "offers the consumer a large number of game combinations with cartridge flexibility at a console price one-



LOW-COST PROGRAMMABLE TV GAME built using new IC's from General Instrument. The game is not microprocessor based. Instead of the cartridges containing ROM memory, each cartridge contains a dedicated game IC.

half of that of the programmables currently in the market place." All cartridges provide realistic sound, on-screen scoring and are tailored to both U. S. and European TV standards.

The LPP uses an AY-3-8615 color video processor IC in the game console. Cartridges currently available are: the 8610 *Supersport* (20 games); the 8675 *Motorcycle* (8 games); and the 8603 *Road Race Set* (3 games). In the planning stage are three other cartridges: *Shooting Gallery* (12 games); *Wipeout* (24 games); and *Wartare* (10 games).

### 1978-1979 SCTE officers and directors

The Society of Cable Television Engineers, Inc. (SCTE) has announced its slate of officers and regional directors for 1978-1979. They are as follows:

President, Bob Bilodeau (serving to end of 1978 only); eastern vice president, Harold Null; western vice president, Gay Kleycamp; secretary, Judith Scharf; and treasurer, Ed Horowitz.

Regional directors are Frank Bias, Glenn Chambers, Bill Ellis, Jim Grabenstein, John Morovich, Bruce Uerling, and John Weeks.

### Moratorium asked on microwave installations in NY area

Because of increased public concern over the possible adverse long-term effects of microwave radiation, New York City's

Board of Standards and Appeals has asked Mayor Edward Koch to declare a temporary moratorium on constructing or installing microwave facilities in the area until "satisfactory guidelines" have been established. To date, no studies have been made concerning the long-term effects of such facilities.

The Board's request arose partly out of a recent decision to deny permission to construct a 180-foot microwave transmission tower in Staten Island. This tower would have formed part of an overall U.S. Coast Guard maritime traffic plan for New York Harbor. If the moratorium is approved, this would be the first time any major metropolitan area in the U.S. has taken such an action to determine health and safety standards for microwave radiation.

### Robert Villont announces his candidacy for NESDA president

At a recent meeting of the Washington State Electronics Council, NESDA senior vice president, Robert (Bob) Villont announced that he would seek the presidency of NESDA. In his speech, Villont expressed his main concern was increased NESDA membership, but also stressed that the national office should strive to practice what it preaches to the membership—namely, service to the customer. Washington and Oregon groups have endorsed Villont and pledged continued support in implementing his campaign plans, if he is elected. R-E

# Reducing CB Interference



*Many television interference complaints are caused by the second and third harmonics from CB transceivers. A special test instrument has been developed so technicians can easily measure interference components.*

ED PILLER, W2KPO

JIM SMITH PUSHES THE MICROPHONE button on his CB base station to communicate with a friend on the other side of town. Thirty seconds later, he receives a phone call from an irate neighbor telling him that he's wiping out his favorite football game on Channel 5. How many times (in one form or another) is this scene repeated across the United States? Judging from information provided by the FCC, over 100,000 formal complaints of CB-caused interference are now being received a year. However, for every documented complaint, there may be 50 or more cases that are unreported. Apparently the problem has reached tremendous proportions.

The FCC has cracked down through rules requiring harmonics and spurious radiations from new CB transmitters to be a minimum of 60 dB down from the power output of 3 watts to 4 watts. Furthermore, since many home entertainment receivers may be as much at fault as poorly designed transceivers, Senator Goldwater and Congressman Vanik have introduced bills into Congress that would require RF interference-suppression devices to be incorporated in home receivers at the time of manufacture. In addition, local town boards in some cases have levied fines for interference and have imposed ordinances on antenna structures. Many of these cases are now being tried in the courts since they usurp some of the FCC's jurisdictional powers.

I faced some of these problems from 1951 through 1966 while operating a 1-kW SSB amateur transmitter on the 21-MHz and 29-MHz bands from a 50-foot tower in a suburban area. A situation developed that even when I was out of town, interference complaints were received against my

nonoperational station. This was primarily due to the fact that my antenna was the most prominent one in the area. Accordingly, it was the most logical place (in the minds of some) from which these interfering signals could originate. There is a wealth of information available on the causes and cures for RF interference from cases studied in the amateur radio service, and some of the major items will be discussed in this article.

## Causes of interference

In seeking to cure interference problems, it is important to diagnose the cause. Suppression techniques can be applied only when the interference path has been located. Generally, interference can be caused by harmonics and other spurious frequencies generated in the CB transceiver itself. It can also be generated through overload and audio rectification in the home entertainment device that is caused by faulty design. It can also be the result of other outside phenomena completely unrelated to the communication devices.

Interference in the home TV set can be caused by front-end overload from a local signal due to inadequate rejection ahead of the first RF stage. During the overloading process, interfering frequencies are generated within the receiver itself. They can also be induced by a strong RF signal being rectified in a particularly sensitive portion of a solid-state or vacuum-tube circuit. Low-level audio circuits are especially vulnerable to this. Interference signals have also been known to enter directly through the power lines, which can act as a receiving antenna and conduct the signal to the affected receiver.

Other sources of interference that may be blamed on the CB'er are completely unrelated to his operations; i.e., corona and noise generated by local power lines and oil burner ignition systems; or line noise caused by vacuum cleaners, electric razors, washing machines, light dimmers, fluorescent lighting and other appliances. Automobile ignition systems, diathermy machines and industrial equipment have also been known to cause interference problems. Improperly adjusted power microphones can cause badly distorted signals as well as spurious products that could affect adjacent-channel CB's and other home-receiving devices. Emissions from the public service, broadcast, amateur and land-mobile bands can also interfere.

In tracking down the interference, it is important to determine a pattern: When does it occur? How often? What are its symptoms? Can voices or call signals be identified? Does the visual or aerial interference occur in accordance with a ranging voice modulation?

Once it is determined that the interference is caused by a local transmitter, a receiver capable of tuning from 2 MHz to 30 MHz could help identify the cause in most cases. Other receivers tuning the 30- to 54-MHz and 144- through 170-MHz frequencies could also identify emissions in other bands that could cause interference. Observing the interference signal on the home set, while listening to it on its fundamental frequency, would be the surest way of identification.

## Measurements and tests

In making interference measurements to determine its sources and causes, it is important to make sure that your own CB system is relatively

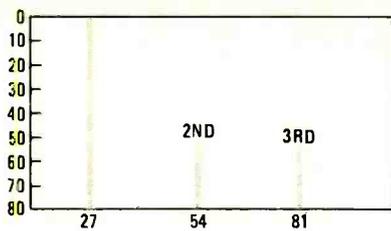


FIG. 1—SPECTRUM ANALYSIS of fundamental, second and third harmonic frequencies.

free from radiating spurious signals. This, of course, can be established by setting up the receiver in a laboratory and making tests with a good spectrum analyzer. The resulting test data would appear on the cathode ray tube of the analyzer. Figure 1 shows the fundamental frequency of 27 MHz and the second and third harmonics at 54 MHz and 81 MHz. The second and third harmonics are normally considered to be a major source of CB interference and should be at least 60 dB down from the fundamental frequency.

Unfortunately, the above lab setup requires very expensive equipment that is normally not available to the average service technician. Leader Instruments Corporation, recognizing this problem, has introduced the *model LHM-950* CB harmonic meter system. This instrument includes a calibrated tunable voltmeter and a directional coupler (*model LC-32*) at a cost of \$334.95. When used with a 50-ohm dummy load, such as the Leader *model LPM-880S*, a complete test system is available for harmonic measurements. (See Fig. 2). Once the test setup is completed, suitable adjustments can be made to harmonic traps within the transceiver.\* The effectiveness of add-on low-pass filters in the RF output line can also be determined.

Interference caused by radiation of the second and third harmonics can easily be detected on a home TV set. The second harmonic normally appears on Channel 2, and the third harmonic on Channel 5 or Channel 6.

It is important to note that while the FCC regulations require that harmonic suppression be a minimum of 60 dB, this value may not be adequate under certain conditions. For example, a fringe-area receiver picking up a weak TV signal could be wiped out by the second or third harmonic of a local CB set even though the interfering harmonic is suppressed more than 60 dB.

Figure 3 shows the block diagram of the *model LHM-950*. A signal is coupled from the output of the transceiver via a directional coupler (see Fig. 2) to the input of the *model*

\*CB transceiver adjustments should only be performed by a technician having a valid first-class or second-class FCC radio-telephone license.

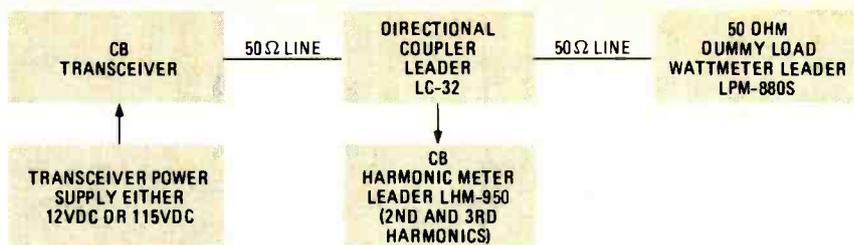


FIG. 2—TEST SYSTEM for harmonic measurements.

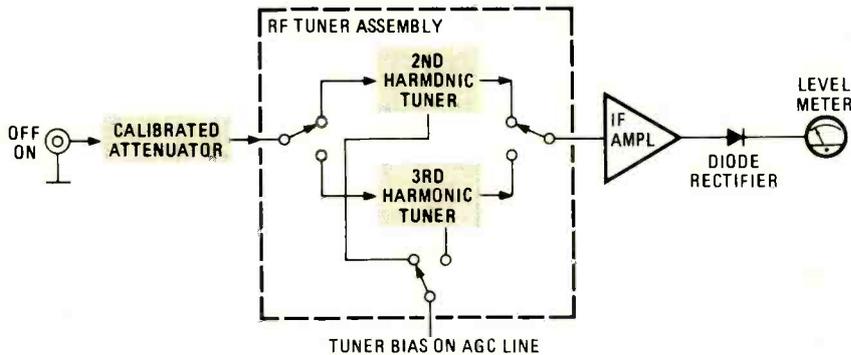


FIG. 3—INTERNAL CONSTRUCTION, *model LHM-950* harmonic meter.

*LHM-950*. A calibrated attenuator feeds the signal through an RF tuner, which then converts it to a 45.75-MHz IF signal. The IF is thereby amplified and rectified. The DC output signal of the rectifier is fed to a calibrated meter. The attenuator is adjusted to bring the reading on-scale, and the second-harmonic tuning is peaked. A reading is then obtained in dBμ (dB above 1 μV). When applied to a calibration curve, a dB reading below the fundamental signal can be obtained. The third harmonic is measured similarly.

### Curing interference

The cure for radio-frequency interference can be very simple or extremely involved and complicated. The simple remedies should be tried first. A good low-pass filter, designed to operate at the output connector of the CB set, should be installed if the measured harmonics do not meet the 60-dB requirement. If interference is still being received on the TV set, a high-pass filter, mounted as close as possible to the tuner, should be installed. This filter attenuates signals below 54 MHz and prevent spurious interference from being generated by an overload condition at the TV set front-end. If interference still persists, the CB set output should be connected to a shielded 50-ohm dummy load. If interference is still present, perhaps it is being conducted through the power line or radiated directly from the set itself. A power-line RF could cure the first problem; the second may require extensive grounding and shielding at the CB set.

It is a good idea to substitute another CB set for the one under test and determine if the interference persists. Some CB sets have been known

to generate spurious frequencies in the RF-amplifier chain that are not harmonically related to the output frequency. In addition, you can substitute a second TV set to observe if the interference signal disappears. If this is the case, then the fault lies in the TV set rather than in the CB unit.


### Summary

RF interference from a CB set can be reduced by applying appropriate measures at the set itself, the affected receiver or in both. A logical system would include trying filters at each place and substituting a different transmitter and receiver in each case. The path of interference should be determined and measures applied to eliminate it. Additional RF interference information can be obtained by contacting the A.R.R.L. or the FCC. In many cases, RF interference filters may be supplied free of charge from the home entertainment equipment manufacturer. R-E

A complete RFI (Radio Frequency Interference) packet containing extensive information can be obtained at no cost. Just send a large self-addressed manila envelope with forty-six cents (\$.46) postage to the A.R.R.L., 225 Main Street, Newington, CT 06311, and request the information.

To obtain the new FCC booklet on "How to Identify and Resolve Radio-TV Interference Problems," send a check for \$1.50 (payable to the Superintendent of Documents) to the Consumer Information Center, Dept. 051F, Pueblo, CO 81009.

for an  
experience  
in electronics,

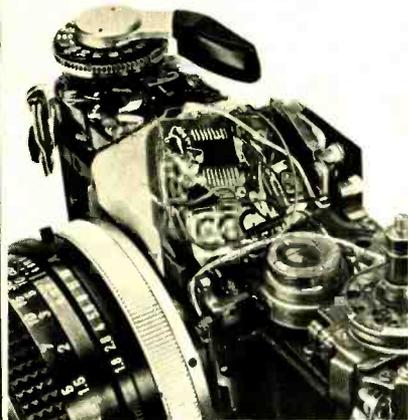

## get into cameras

Improve your income by acquiring additional skills as a camera repair technician. Increasing use of electronics in cameras is creating still more opportunities for camera repair specialists. Take advantage.

### Performance Training

National Camera developed the first comprehensive technical training for camera repair technicians in the '50's. More practicing technicians have received training from us than from any other single source. Now this better-than-ever professional program is as close to you as your mailbox. Learn at home!

### Complete Package

You get texts, tools, practice equipment — a complete program including the latest additions in photographic electronics — not available anywhere else.

### Free catalog

Find out about great training programs in camera repair technology. You can learn at home, keeping your present job, or at our one-year resident school in Colorful Colorado. For free information, use the card in this publication or write us today.



Technical Training Division, Dept. GBD  
2000 West Union Ave.,  
Englewood, Colorado 80110

Accredited member: NHSC, NATTS

CIRCLE 15 ON FREE INFORMATION CARD

### FLYBACK SUBSTITUTE

*Help! I need a replacement for the flyback in an Ambassador color TV, model 2914. The part number seems to be A29056-A, but it's not listed in Sams or any other sources I could think of.—S. G., Tucson, AZ.*

I've been crisscrossing references until I'm blue in the face! With no direct substitute yet. This is a brand name that was made by 10 different companies. From the type of part number, it could be a Nivico. A random check of Sams Photofacts turned up a Nivico 7208, and the flyback number is A29056-A. However, no substitute is listed for it either.

You might try obtaining one from JVC, America Inc., 58-75 Queens-Midtown Expwy, Maspeth, NY 11378. Check Sams 1035-2 to see if the circuit looks like yours. Good luck!

### TOO MUCH RIPPLE

*There's far too much ripple in the DC power supply of this GE model JA chassis. I've checked and replaced the filter capacitors; this didn't help much. What else could cause this?—A. K., Elmhurst, NY.*

There's really only one thing left. Check the filter choke. It may have developed an internal short across the windings but not to ground!

(Feedback: "Bingo!")

R-E

## You Can Count On DAVIS!



### NEW CTR-2A 500 MHz & 1 GHz COUNTERS

NOW WITH  
PERIOD MEASUREMENT (Optional)  
AND BUILT-IN PREAMP

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler & Preamp
- Period 1us to 1 sec. (optional)
- TCXO Std.  $\pm 2$  ppm
- Input Diode Protected
- 12V-DC Operation (optional)
- Oven Crystal  $\pm .5$  ppm (optional)
- Selectible Gate Times .1 sec. & 1 sec.

500 MHz kit CTR-2A-500K	\$249.95
500 MHz assembled CTR-2A-500A	349.95
1 GHz kit CTR-2A-1000K	399.95
1 GHz assembled CTR-2A-1000A	549.95

#### OPTIONS:

(02) Oven Crystal	\$49.95
(03) 43" LED	10.00
(04) 12 V-DC	10.00
(05) 10 sec. Time Base	10.00
(06) Period Option	15.00



DAVIS ELECTRONICS  
636 Sheridan Drive  
Tonawanda, NY 14150  
716/874-5848



CIRCLE 71 ON FREE INFORMATION CARD

## TUNER SUB \$19.95

Since all tuner subs that we know of are modified TV Tuners, we decided to market an excellent performing yet very low cost sub for the technician who has to get all he can for his money... a "Poor Boy's Sub" for only \$19.95.

This was not an easy task since cabinets, knobs and controls would push the price far above \$19.95... We searched for a tuner that needed no cabinet and no controls... one that the tech could scrounge the knobs from most any old TV...

It took over two years but we finally found it. The gain is excellent... Battery drain is very low (only 18 mls). It's self biasing so there is no R.F. gain control to fiddle with... It works equally well on tube or transistor sets... b/w or color... and is as easy to use as starting a fight with your wife (well, almost). All you need do is hook the set's IF cable to the "Poor Boy" and view the picture... That's it... no set up controls to confuse you.

We compared the "Poor Boy" with other subs costing over twice the price and found it to work just as well on all the comparison tests we made... and often a lot easier to use... Even though instructions aren't needed... you get those too.

The "Poor Boy" is small enough to easily hold in one hand... no wires or controls dangling around. It comes completely wired and tested including batteries and ready to use. Send a check for only \$19.95, and we even pay the shipping (how about that?) or we will ship COD.

Try it for 10 days... If not completely satisfied... return for full refund.

CALL TOLL FREE 1-800-433-7124

### TEXAS TUNER SERVICE

4210 N.E. 28TH STREET,  
FORT WORTH, TEXAS 76117

Master Charge and Visa accepted

CIRCLE 76 ON FREE INFORMATION CARD



## Our new Bearcat® 250!

has all the fantastic space age features of our super popular Bearcat® 210, but now we've added:

- 50 synthesized crystalless channels
- User selectable scanning speeds
- Priority channel
- Digital time clock—accurate to seconds
- Automatic or user controlled squelch
- Search Direction—Search "up" or "down" for quicker return to desired frequencies
- Transmission activity counter—tells you how busy each frequency has been
- Search & Store—Will find and "remember" up to 64 active frequencies for later recall
- Direct channel select—Advance directly to a channel without stepping through interim channels
- Non volatile memory—No batteries required to retain memory, even when scanner is unplugged
- Auxiliary—On/Off control of equipment (tape deck, alarms, lights, etc.) when transmissions occur on programmed channels

To reserve your space-age Bearcat® 250 and receive your order priority number for spring-summer delivery, send \$389.00 plus \$5.00 for U.S. U.P.S. shipping. Foreign orders invited at slightly higher cost. Visa and Master Charge card holders may call toll free 800-521-4414 to order. Outside the U.S. and Michigan dial 313-994-4441. To order by mail or for a free catalog completely describing the fantastic crystalless Bearcat® 250 write: COMMUNICATIONS ELECTRONICS, Box 1002—Dept. 10, Ann Arbor, Michigan 48106 U.S.A.

©1978 Communications Electronics

CIRCLE 68 ON FREE INFORMATION CARD



# ADVANCING the state of the art



in automatic percussion units... the **PROGRAMMABLE DRUM SET** features: score editing, bridges, intro's, external sync to sequencers foot controls, memory save switch & much more.

Enter scores in seconds - **NO PROGRAMMING KNOWLEDGE IS REQUIRED!**

High Fidelity describes the 3750 as "an easy project... fun to do and yields delightful results... an excellent educational tool and versatile aid to the musician who can't afford a live rhythm section."

#3750 ..... \$84.95... (+\$3 shipping)

Another Great Kit from: **RAIA**  
8 F 1020 WEST WILSHIRE BLVD. OKLAHOMA CITY, OK 73118

- Send Programmable Drum Set Kit (\$84.95+ shipping enclosed)  
 TELL ME MORE... Send the instruction manual first (\$2.00 refundable upon kit purchase)

name: \_\_\_\_\_

address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

SEND FREE CATALOG

CIRCLE 18 ON FREE INFORMATION CARD

## NEW EICO 480 TRIGGERED SWEEP 10 MHz SCOPE

100% Solid State • Includes 10:1 Probe

More Professional scope performance for your money! DC to 10 MHz bandwidth, AC and DC coupling, 11 position calibrated attenuator, 10 mV/cm sensitivity, push-button operation. Outstanding features: Built-in TV Sync Separator; Digitally controlled trigger circuits; reference baseline display; calibrated 21 step sweep speed; Fully regulated power supply; Custom Bezel for standard camera mounting. **Assembled \$425.00**

### FREE '78 EICO CATALOG

Check reader service card or send 50c for first class mail. See your local EICO Dealer or call (516) 681-9300, 9:00 a.m.-5:00 p.m. EST. Major credit cards accepted.

EICO-108 New South Rd. Hicksville, N.Y. 11801



CIRCLE 64 ON FREE INFORMATION CARD

## DIGITAL DARKROOM TIMER

continued from page 37

and local parts houses. Most of the IC's are part of Sylvania's ECG series (just add the ECG prefix to the 4-digit designation given in the parts list), and probably part of RCA's SK series. Do not use Motorola's HEP series because even though they designate their CMOS gates with a 4-digit number between 4000 and 4099, their numbers, in no case, correspond to the industry standard numbers given in the parts list. That is, HEP4001 is not the same as CD4001, ECG4001 or the part specified for IC3 and IC15.

### Repeatability, accuracy and short-time limits

The repeatability of any selected interval is about 7.8 ms, the period of the digit-scan frequency. This occurs because operation of the EQUALS key is not synchronized with IC7's internal clock.

The uncompensated accuracy of any interval is a constant dependent upon: 1) line-frequency accuracy; 2) the difference between the relay's pull-in and drop-out time; 3) the phase shift across the transformer (which may delay the triac's turn-on if the relay energizes while the line voltage is close to zero); 4) an extra delay of 0.2 second in IC7 the first time the Equals function is activated. The first



## You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ...and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2850, and you can purchase in sections to spread costs out...or have two-year time payments. Combine the incomparable quality of Schober components with your talent...and produce a far better organ than you can buy!

Thousands of others have, ever since 1955.

You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.) Why not clip it right now, before you forget?

The Schober Organ Corp., Dept. RE-177  
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE 56 ON FREE INFORMATION CARD

## THERM DIGITAL HEAT SENSORS



\*THERM I: 3 digit .3" LED display; 5AA alkaline batteries; 15-20 hour continuous operation; battery recharger and NiCads optional.

\*THERM II: 3 digit .5" LCD display, 9v alkaline battery; 125 hour continuous operation.

\*MINI-THERM: plugs directly into DVM for reading on DVM display; 9v alkaline battery; 125 hour continuous operation.

- Rugged, handheld aluminum case.
- Accuracy .2% ± 1 LSD.
- Resolution: 1° F, K, or C.
- Probe: Comes with 5' teflon cable (replaceable)
- Range: -50°C (-58°F) to +150°C (302°F)
- Battery-operated.

(415) 941-2764  
P.O.Box 4477 Mtn. View CA 94040



CIRCLE 63 ON FREE INFORMATION CARD

three factors will not produce more than about 12 ms of error. The 0.2-second error is compensated for by delaying the relay pull-in by using IC6-7 as the source of the signal to latch IC3. As a result, the accuracy is about 30 ms in the seconds range, and 100 ms in the minutes/seconds range. Though repeatability is much more important than accuracy, if you need high accuracy at short intervals, shunt R2 with any silicon diode, anode to Q1's base, and experimentally add sufficient capacitance from Q1's base to ground to achieve the required accuracy. Start with about 5  $\mu$ F.


If you print in color, avoid using intervals less than about 0.5 second with incandescent-lamp enlargers because during the warmup and cooling period of the lamp, which could be close to 0.1 second long, the color temperature of the lamp will be too low compared with the steady-state value. This will produce reddish color shifts if printing from a slide, and a cyan shift is produced if printing from a negative. **R-E**

**A**

**HIGH BLOOD PRESSURE.**  
**Treat it...and live.**

The National High Blood Pressure Education Program,  
U.S. Department of Health, Education, and Welfare.

## Bugbooks® & Bugworks®

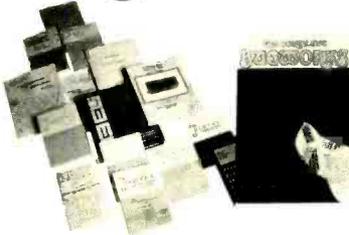

In E&L's Complete Bugworks Catalog, you'll find everything you need to master the world of electronics. And to start, check out the Bugbooks. 23 Volumes of the most comprehensive & authoritative tutorials in electronics today, from basic circuit design to advanced Microcomputer experiments.

They're all in the works—the Complete Bugworks.

Send for your free copy today.




**E&L INSTRUMENTS, INC.**  
61 First Street, Derby, Conn. 06418  
(203) 735-8774 Telex No. 96 3536

TM

**CIRCLE 28 ON FREE INFORMATION CARD**
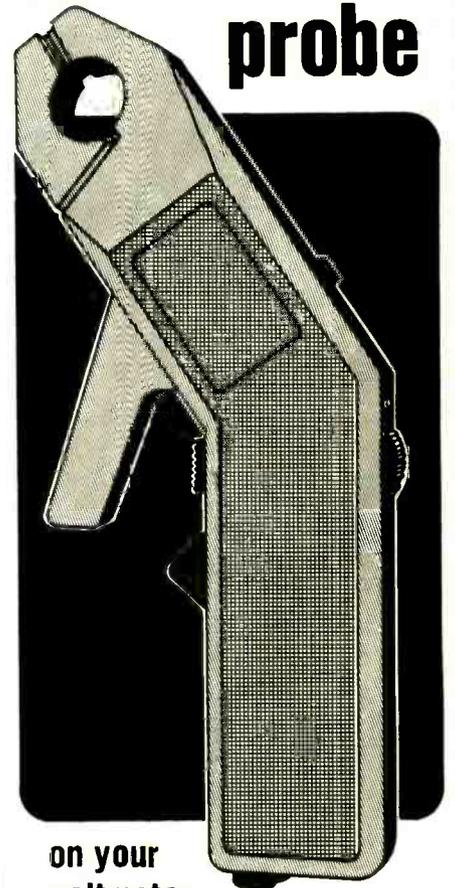
# NOW! Measure dc, ac and ac-on-dc current with the F.W. Bell Current Gun™ probe



on your  
voltmeter,  
multimeter or scope.

This new clamp-on probe lets you read from 0 to 1 kHz and from 0 to 200 A, accurately, safely, quickly. No disturbing the circuit or insulation. Clamps over conductors up to 3/4" dia.

Write for full specs today.



A Subsidiary of  
The Arnold Engineering Company

4949 Freeway Drive East Columbus, Ohio 43229  
Phone: (614) 888-7501 TWX: 810-337-2851

**CIRCLE 37 ON FREE INFORMATION CARD**

# HOLD IT! Anywhere you want it.

PanaVise tilts, turns, rotates. One quick turn of the control knob and you securely position your work exactly where you want it. Holds firmly but gently the most delicate electronic parts and P. C. boards.

Whether you're into building home electronics, trouble shooting, or professional servicing... you'll wonder how you got along without this modestly priced "extra hand."

Model 396 Wide Opening PanaVise shown. An ingenious variety of other interchangeable bases, holders and accessories also available. See your electronics distributor, or write for FREE brochure.

**PANAVISE®** Dept. CE2  
5224 Chakemco St., South Gate, CA 90280




**CIRCLE 49 ON FREE INFORMATION CARD**

# JUST \$495 GETS YOU THIS DUAL TRACE GOULD SCOPE PLUS TWO X10 PROBES.

You know that's a great price. Especially when you consider the outstanding performance you get with this Gould OS245A oscilloscope.

And you get clear, bright displays. 5mV/div. sensitivity and exceptionally versatile trigger performance. It's ideal for TV or general electronic service work; perfect for hobbyists and educational institutions. You can rely on Gould to live up to these specs:

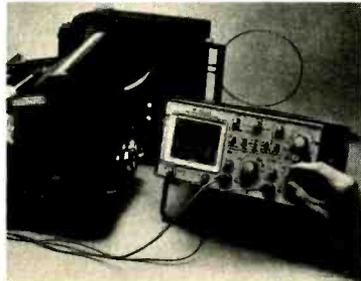- DC to 10 MHz; dual trace
- Trigger performance in excess of 15 MHz
- TV trigger facilitates solid synchronization with TV signals



- Portable; weighs just 11 lbs.
- Carries full two year warranty on all parts and labor excluding normal calibration, fuses and minor maintenance. **Just one phone call gets you action.**

Don't miss out on this bargain. Pick up the phone now and call us toll-free at 800-325-6400. (In Missouri call 800-342-6600). We'll rush you free literature and ordering information on the OS245A as well as other Gould oscilloscopes applicable to your needs. Gould Inc., Instrument Systems Division, 3631 Perkins Avenue, Cleveland, Ohio 44114.



CIRCLE 62 ON FREE INFORMATION CARD

## NEGATIVE PICTURE, NO SYNC

The picture goes negative and loses sync on this Sears model 562.10420 chassis. The brightness control behaves like automatic-gain control. I checked the AGC circuit but didn't find anything. Where to now?—G. E., Belleville, IL.

Go right back to the automatic-gain control (AGC) and clamp it with a bias box at about +1.9 volts. If this clears up the problem, then follow through the AGC stage very carefully. These symptoms could indicate leaky transistors.

(Feedback: "That solved it. The AGC keyer and amplifier transistors were both very leaky. Thanks for the help!")

## DOUBLE PICTURES

I'm a student trying to fix this Sanyo model 21V65. It has double pictures or double horizontal foldover. Changing the tubes brought no results.—J. S., Virginia Beach, VA.

This is most apt to be a horizontal oscillator/AFC problem. Remove the AFC by grounding it, then see if you can adjust the horizontal-hold control so that only one straight-sided picture appears on the screen. If you can, the oscillator is able to run on-frequency. Put the AFC back in. If the picture goes out of sync, the problem is in the AFC, with the most likely cause being the dual-diode unit. Make sure that this unit is perfectly balanced. R-E

## BEST IN NEW ELECTRONICS BOOKS!

- The Handbook of Telephones & Accessories. 432 p., 215 il. \$9.95
- Install Electronic in Cars, Boats, Planes, Trucks & RV's. 364 p. \$7.95
- The BASIC Cookbook. 140 p. \$4.95
- How to Repair Video Games. 270 p., 182 il. \$7.95
- Beginner's Gde.—Designing/Building Trans. Radios. 140 p. \$4.95
- 101 Practical Uses for Propane Torches. 140 p., 98 il. \$3.95
- Towers' International FET Selector. 140 p. \$4.95
- How to Design/Build Electr. Instrumentation. 420 p., 210 il. \$9.95
- Automotive Air Conditioning Handbook. 280., 157 il. \$6.95
- How to Repair Movie & Slide Projectors. 304 p., 270 il. \$7.95
- Close-Up Circuit TV Install., Mainten., & Repair. 304 p., 220 il. \$8.95
- Understanding Sound, Video & Film Recording. 140 p., 74 il. \$5.95
- Build-It Book of Solar Heating/Propag. Forecasting. 196 p. \$6.95
- Hdbk. of Solar Flare Monitoring/Propag. Forecasting. 196 p. \$6.95
- 57 Practical Programs & Games in BASIC. 210 p., 611 il. \$7.95
- Beginner's Guide to Microprocessors. 182 p., 106 il. \$5.95
- Hearing Aid Handbook. 432 p., 224 il. \$8.95
- CMDS Databook. 280 p., 270 il. \$6.95
- Master DP-AMP Applications Handbook. 476 p., 320 il. \$9.95
- Miniprocessors: From Calculators to Computers. 196 p., 67 il. \$5.95
- Complete Hdbk. of Public Address Sound Systems. 272 p. \$7.95
- Modern Transistor Radios. 64 p., 112 il. \$2.50
- Microwave Oven Service & Repair. 420 p., 210 il. \$9.95
- IC Function Locator. 224 p. \$5.95
- Hdbk. of Marine Electronic/Electrical Systems. 546 p., 338 il. \$9.95
- Solid-State Motor Controls. 322 p., 162 il. \$8.95
- Master Handbook of Ham Radio Circuits. 392 p., 301 il. \$8.95
- How to Completely Secure Your Home. 224 p., 162 il. \$5.95
- Towers' International Transistor Selector. 200 p., 179 il. \$6.95
- Ham Radio Incentive Licensing Guide. 154 p., 70 il. \$4.95
- Programming Microprocessors. 280 p., 102 il. \$6.95
- The "Compiler" Book—Build Super Calculators/Minicomputer Hardware with Calculator Chips. 322 p., 227 il. \$7.95
- Master Transistor/IC Substitution Handbook. 518 p., 165 il. \$7.95
- Modern Crystal Radios (Make and Use Series). 64 p., 101 il. \$2.50
- Home-Brew HF/VHF Antenna Handbook. 210 p., 143 il. \$5.95
- CBR's Handy Manual of SSB. 80 p., 42 il. \$2.25
- Beginner's Gde.—Making Electronic Gadgets. 140 p., 113 il. \$4.95
- Modern Digital Communications. 308 p., 122 il. \$6.95
- Microprocessor Progr.—Computer Hobbyists. 378 p., 219 il. \$8.95
- Illus. Dict.—Broadcast—CATV—Telecommunications. 420 p. \$8.95
- Linear IC Applications Handbook. 280 p., 183 il. \$6.95
- Build-It Book of Optoelectronic Projects. 238 p., 175 il. \$5.95
- Photo Guide to AM/FM Stereo Repair. 288 p., 281 il. \$6.95
- Servicing Medical & Bioelectronic Equipment. 350 p., 165 il. \$8.95
- How to Use AF & RF Signal Generators. 238 p., 162 il. \$5.95
- Model Railroad Electronics. 308 p., 218 il. \$5.95
- The ABC Book of Hi-Fi/Audio Projects. 182 p., 131 il. \$4.95
- Complete Hdbk. of Electrical/House Wiring. 476 p., 197 il. \$8.95
- 88 Practical Op Amp Circuits You Can Build. 140 p., 120 il. \$4.95
- How to Build Metal/Treasure Locators. 140 p., 60 il. \$3.95
- Home Audio Systems Schematic/Servicing Manuals, each 200 p. \$5.95
- Vol. 1 Caphart, Zenith.  Vol. 2 Channel Master, Coronado, Hitachi.  Vol. 3 Automatic Radio, Admiral, Midland, Sharp.

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Clip entire ad to order. 100% guaranteed or your money refunded.

TAB BOOKS DEPT RE-88  
BLUE RIDGE SUMMIT, PA. 17214

CIRCLE 23 ON FREE INFORMATION CARD



## PTS 8001 Component Analyzer

Solid state component tester works in or out of circuit. Simple hook-up to any standard oscilloscope. High, medium and low range switch for matching the impedance to the component being tested.  
Dealer Net \$54.95

See the Yellow Pages for the PTS Servicenter Nearest You or Contact:



**PTS ELECTRONICS, INC.**

P.O. Box 272 Bloomington, IN 47401 812-824-9331

CIRCLE 40 ON FREE INFORMATION CARD

## MATHEMATICS ELECTRONICS ENGINEERING MATHEMATICS ADVANCED MATHEMATICS

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually enjoy doing it!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

**The INDIANA  
HOME STUDY INSTITUTE**

P.O. BOX 1189

PANAMA CITY, FLA 32401

CIRCLE 12 ON FREE INFORMATION CARD



## endeco soldering & desoldering equipment

### SOLDERING IRONS



Pencil style. Safety light. Two heats — 20w and 40w. 6 tips. Unbreakable handle. 2 and 3 wire neoprene cords.

### DESOLDERING IRONS



Pencil style. Safety light. Some operate at 40w, 11de at 20w. 8 tip sizes. 2 and 3 wire neoprene cords.

### SOLDERING & DESOLDERING KITS



Everything needed to solder or desolder or both. All in a handy lifetime metal box with hasp.

See your distributor or write...

## Enterprise Development Corp.

5127 E. 65th St. • Indianapolis IN 46220  
PHONE (317) 251-1231

CIRCLE 6 ON FREE INFORMATION CARD



ELF II by  
NETRONICS

As featured  
in POPULAR  
ELECTRONICS

Shown with  
optional 4k Memory Boards,  
GIANT BOARD™ and Kluge Board.

## HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!

Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits—the very first night—even if you've never used a computer before!

## ELF II featuring RCA COSMAC microprocessor/mini COMPUTER

**\$99.95**

Stop reading about computers and get your hands on one! ELF II is an outstanding trainer for anyone who needs to use a computer to maximize his or her personal effectiveness. But ELF II isn't just a trainer. Expanded, it can become the heart of a powerful computer system capable of solving sophisticated business, industrial, scientific and personal finance problems. ELF II also includes the new Pixie Graphics chip that lets you display any 256 byte segment of memory on a video monitor or TV screen. Easy instructions get you started right away, even if you've never used a computer before. ELF II can be assembled in a single evening and you'll still have time to run programs including games, video graphics, etc. before going to bed!

### Learning Breakthrough! A Short Course On Microprocessor And Computer Programming

Written For Anyone! Minimal Background Needed!

Why spend a small fortune on a personal computer without knowing how to use its advanced capabilities? We'll teach you how to make ELF II respond to your needs, without waiting for someone to develop the software. You learn, in non-technical language, each of ELF II's 31 instructions so you'll understand everything ELF II can do...and how to get ELF II to do it. It's your chance to master an advanced personal computer quickly and painlessly, even if you've never used a computer before!

#### SPECIFICATIONS

ELF II features an RCA COSMAC COS/MOS 8-bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hex keyboard, two digit hex output display, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through PC board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen.

#### EXPANSION OPTIONS

ELF II GIANT BOARD™ with cassette I/O, RS 232-C/TTY I/O, 8-bit P I/O, decoders for 14 separate I/O instructions and a system monitor/editor • 4k Static RAM. Addressable to any 4k page to 64k • Prototype (Kluge) Board accepts up to 36 IC's • Gold plated 86-pin connector • Expansion Power Supply (Not required unless adding 4k RAM) • All of the above PC boards plug directly into ELF II's expansion bus.

#### ELF II TINY BASIC

Commands include SAVE, LOAD, ±, ×, ÷, ( ), 26 variables A-Z, LET, IF/THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, RCM, CLEAR, LIST, RUN, PLDT, PEEK, POKE. Comes fully documented. (4k memory required.)

#### SEND TODAY!

NETRONICS R&D LTD., Dept. RE8 (203) 354-9375  
333 Litchfield Road, New Milford, CT 06776

YES! I want to run programs at home and have enclosed:  \$99.95 plus \$3 p&h for RCA COSMAC ELF II kit  \$4.95 for power supply, required for ELF II kit  \$5.00 for RCA 1802 User's Manual.

\$4.95 for Short Course on Microprocessor & Computer Programming.  
 ELF II connects to the video input of your TV set. If you prefer to connect ELF II to your antenna terminals instead, enclose \$8.95 for RF Modulator.  
 \$39.95 plus \$2 p&h for ELF II GIANT BOARD™ kit  
 4k Static RAM kit, \$89.95 ea. plus \$3 p&h  
 \$17.00 plus \$1 p&h for Prototype (Kluge) Board  
 \$34.95 plus \$2 p&h for Expansion Power Supply kit  
 Gold plated 86-pin connectors at \$5.70 ea.  
 \$64.95 plus \$2 p&h for ASCII Keyboard kit.  
 \$14.95 for ELF II TINY BASIC cassette.  
 I want my ELF II wired and tested with the power transformer, RCA 1802 User's Manual and Short Course on Microprocessor & Computer Programming for \$149.95 plus \$3 p&h.

Total enclosed (Conn. res. add tax) \$ \_\_\_\_\_  Check here if you are enclosing Money Order or Cashier's Check to expedite shipment.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Dealer Inquiries Invited!

CIRCLE 53 ON FREE INFORMATION CARD

## 8080 A demonstration program for the 8253 timer.

C. TITUS, M. DEJONG, D. LARSEN, P. RONY and J. TITUS\*

IN A PREVIOUS COLUMN, WE INTRODUCED the characteristics of the Intel 8253 programmable interval timer, a 24-pin IC that is very useful in counting and timing operations.

This month's column describes a demonstration program that illustrates the various modes of operation of the timer.

The details of the test circuit are shown in Fig. 1. Although an oscilloscope is handy to monitor the output signal, OUTO, from counter No. 0, we have found it just as useful to use a single 7490

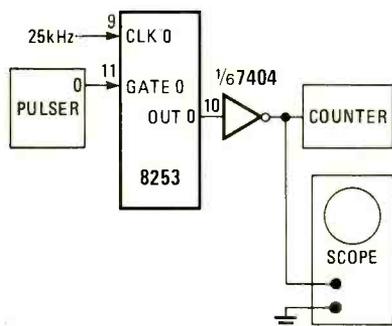


FIG. 1

decade counter IC to detect negative-edge transitions at output signal OUTO. The 25-kHz input clock frequency, which has a period,  $\tau$ , of 40  $\mu$ s, is the input at CLK0.

Before you use the 8253 IC, you must understand the nature of output signal OUTO as a function of the IC's six different modes of operation: mode 0 through mode 5. Intel literature<sup>1</sup> is somewhat confusing in this area, so the diagrams have been simplified by omitting all signals except for the OUTO signal. This permits you to simultaneously compare all six operation modes, as shown in Fig. 2. Note that modes 0 and 1 provide a negative monostable clock pulse of duration NT; mode 2 provides a series of negative clock pulses of pulse width  $\tau$  and period NT; mode 3 provides essentially a

squarewave of period NT; and modes 4 and 5 provide a single strobe pulse of pulse width  $\tau$  at a time NT after a trigger pulse has been applied to counter No. 0. Quantity N is a 16-bit timing byte initially loaded into counter No. 0. In our demonstration program, the timing byte is 000 000<sub>8</sub>, which corresponds to the decimal number 65,536. At this point, there are two possible actions input GATE0 can take:

1. GATE0 functions as a *gating* input; when at logic 0, pulses that are input at CLK0 do not reach counter No. 0 and no counting occurs. This type of behavior occurs with mode 0, mode 2, mode 3 and mode 4.
2. GATE0 functions as a *trigger/reset*

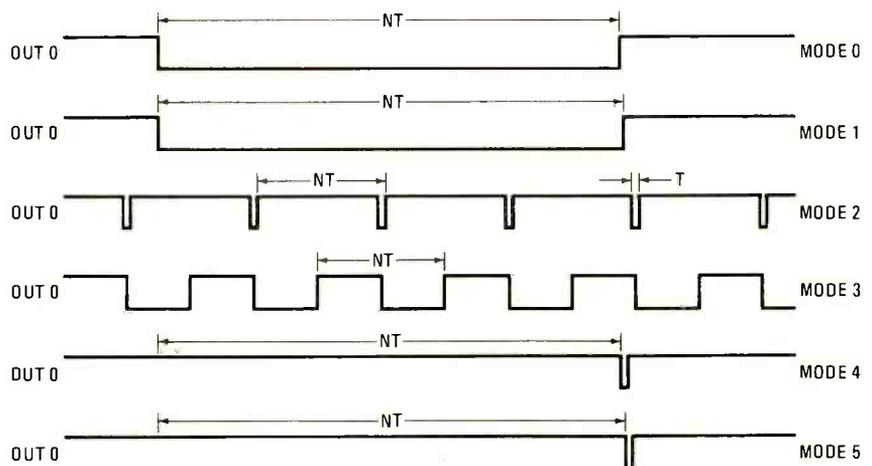


FIG. 2

input; a positive-edge transition at GATE0 resets counter No. 0 and initiates counting. Each time there is a positive edge at GATE0, counter No. 0 is reset. This type of behavior occurs with mode 1, mode 2, mode 3 and mode 5.

These different actions can best be observed with the aid of a counter and a value of NT in the range of 3 to 10 seconds. In this case, the value of N is 65,536 and  $\tau$  is 40  $\mu$ s; so  $NT = (65,536)(40 \times 10^{-6}) = 2.62$  seconds.

The program that we use to test the 8253 IC is shown in Table 1. Note that a memory-mapped I/O (Input/Output) is used, in which the control register has an address of 200 003<sub>8</sub> and counter No. 0 has

an address of 200 000<sub>8</sub>. The program is quite simple. First output the control word, 060<sub>8</sub> (mode 0), into the control register. Next, successively load the LO and HI counter bytes, both of which are 000<sub>8</sub>, into counter No. 0. Finally, enter a wait loop.

When you execute this program, output signal OUTO goes immediately to logic 0 and remains there for NT seconds, after which it returns to logic 1. You can repeat this behavior only by executing the program a second time starting at memory address 003 000<sub>8</sub>.

If you change the control word at location 003 001 to 062<sub>8</sub> (mode 1), start the execution of the program and press the pulser shown in Fig. 1, you will also observe a negative pulse with a duration of 2.62 seconds. If you fail to press the pulser, however, and thus do not apply a positive edge at GATE0, you will observe no monostable pulse. On the other hand,

repeatedly pressing and releasing the GATE0 pulse at time intervals of less than 2.62 seconds can prolong the monostable pulse indefinitely. In this way, you are able to produce a *retriggerable monostable multivibrator* input.

The control word of 064<sub>8</sub> lets you observe the mode 2 behavior shown in Fig. 2. Repeatedly generating positive edges at GATE0 at time intervals of less than 2.62 seconds repeatedly resets counter No. 0 and prevents the short negative clock pulses from appearing. You can accomplish the same purpose by allowing GATE0 to remain at logic 0 after you have applied a positive edge. The GATE0 input thus exhibits both gating and trigger/reset behavior.

\*This article is reprinted courtesy of American Laboratories.

Dr. DeJong is head of the Department of Mathematics/Physics at the School of the Ozarks. Dr. Rony, Department of Chemical Engineering, and Mr. Larsen, Department of Chemistry, are with the Virginia Polytechnic Institute and State University. Dr. C. Titus and Mr. J. Titus are with Tychon, Inc.

**TABLE 1—DEMONSTRATION PROGRAM for the 8253 interval timer. The control word at address 003 001 is changed to demonstrate the behavior of the different modes of operation.**

Address	Instruction	Label	Mnemonic	Comment
003 000	076	TIMER,	MVIA	/Move control word into accumulator
003 001	060		060	/Mode control word
003 002	062		STA	/Store it within control register
003 003	003		003	/in 8253 interval timer chip
003 004	200		200	
003 005	076		MVIA	/Move LO counter byte into accumulator
003 006	000		000	/LO counter byte
003 007	062		STA	/Store LO byte in counter #0
003 010	000		000	
003 011	200		200	
003 012	076		MVIA	/Move HI counter byte to accumulator
003 013	000		000	/HI counter byte
003 014	062		STA	/Store HI byte in counter #0
003 015	000		000	
003 016	200		200	
003 017	303		JMP	/Wait
003 020	017		017	
003 021	003		003	

The mode 3 behavior (control word of 066<sub>8</sub>) is similar to that for mode 2, except that a nearly symmetrical squarewave is produced. Deviations from symmetry occur when the counter byte is an odd number, and are most evident when the counter byte is very small.

In mode 4 (control word of 070<sub>8</sub>), the positive edge of the  $\overline{WR}$  pulse, which is applied at pin 23 of the timer when you execute the STA instruction at 003 014, initiates counting that produces a nega-

tive clock pulse of pulse width  $\tau$ . The time duration between the positive edge and the pulse is 2.62 seconds. The GATEO input acts as a gating input, with a logic 0 inhibiting the counting process.

Finally, in mode 5 (control word of 072<sub>8</sub>), a positive edge at GATEO initiates counting. Repeatedly generating positive edges at GATEO at less than 2.62-second time intervals repeatedly resets counter No. 0 and prevents the appearance of the single negative clock pulse.

It should be noted that in all modes, counter action begins on the first negative clock transition after  $\overline{WR}$  (pin 23) or GATEO goes to logic 1; and that  $\overline{WR}$  can initiate counting in all modes except mode 1 and mode 5.


Although in many 8253 timer applications, the primary purpose is to generate the proper output signal at OUT0 (as shown in Fig. 2), you can also read the contents of the 16-bit counter *without affecting the counting operation*. By inputting a control word of 000<sub>8</sub>, 100<sub>8</sub>, or 200<sub>8</sub>, you can latch the 16-bit count of either counter No. 0, counter No. 1, or counter No. 2, respectively. You can then read the two bytes into the 8080A IC, with the LO counter byte first and the HI counter byte second.

To discuss complex counter applications in any detail is beyond the scope of this article. However, a 16-bit frequency counter has been described elsewhere,<sup>2</sup> and a scheme has been proposed<sup>3</sup> for measuring the half-life of a radioactive substance. **R-E**

**REFERENCES:**

1. *Intel Data Catalog*, 1977, Intel Corp., 3065 Bowers Ave., Santa Clara, CA 95051.
2. Lynne, P., "Implementing an LSI Frequency Counter," *Byte* 2 (11), 146 (1977).
3. DeJong, M. L., private communication. (Professor DeJong will implement a number of counting schemes in a physics laboratory, and would be interested in corresponding with others who have similar interests.)

# ok® wire wrapping center ok®

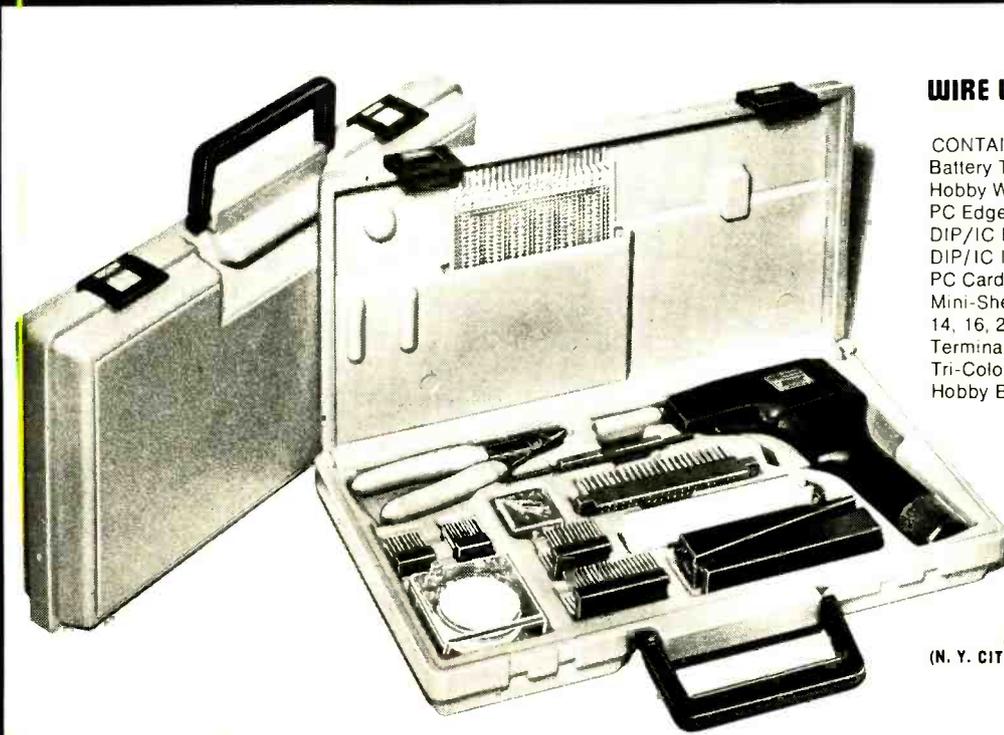

**WIRE WRAPPING KIT WK-5**

- CONTAINS:
- Battery Tool BW-630
  - Hobby Wrap Tool WSU-30 M
  - PC Edge Connector CON-1
  - DIP/IC Extractor Tool EX-1
  - DIP/IC Insertion Tool INS-1416
  - PC Card Guides & Brackets TRS-2
  - Mini-Shear with Safety Clip SP-152
  - 14, 16, 24 and 40 DIP Sockets
  - Terminals WWT-1
  - Tri-Color Wire Dispenser WD-30-TRI
  - Hobby Board H-PCB-1

**\$74.95**

ADD \$1.00 FOR SHIPPING  
(N. Y. CITY AND STATE RESIDENTS ADD TAX)

**OK MACHINE & TOOL CORPORATION**

3455 Conner St., Bronx, N.Y. 10475 (212) 994-6600 / Telex 125091

# hobby corner

## Build an inexpensive expanded-scale voltmeter to monitor AC line voltage.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

FEW THINGS ARE MORE FRUSTRATING TO those of us who know something about electricity than the hot weather "brown-out." This occurs when the power company reduces the voltage in an attempt to make the supply go around. There were brownouts during the past several summers, and it is possible the situation will become worse before it gets better. Not only is it frustrating when the usually reliable AC voltage is cut by 5%, 10% or more, it is potentially *harmful* to your home appliances.

If you reduce the input voltage to a motor, the result is that the operating temperature rises. Reduce it enough and the temperature becomes so high that it burns the insulation off the coil wires, and that's the end of the motor.

Most motors can operate at a 10% or greater voltage reduction with no more effect than just running a little warmer than usual. The amount of undervoltage a given motor can tolerate safely depends upon its design and its load (i.e., how hard it is working).

Thus, you can see that there is no magic voltage figure that applies equally to all motors. If you have a motor that operates at or near its maximum load, it may be the first to go while others are seemingly unaffected.

On the other hand, it is not good for any motor to operate at higher than normal temperatures. Such operation over a period of time, whether all at once or broken up into many intervals, shortens the life of a motor. You don't want a motor to operate that way unless it must.

There are two things you can do: Raise the voltage or turn the motor off. The former can be a very expensive operation but sometimes it is necessary.

It is much more practical to turn the motor off or not start it up when the voltage drops. Do not use your washing machine or dryer until later; postpone using your power saw; and turn off a nonessential fan or air conditioner.

However, you have to know at the time when the voltage is down—reading about it later won't help. Of course, you could hook your VOM or VTVM to the power line but you do use them for other things. Not even a 150-VAC panel meter is the


easiest instrument to read accurately. What you should have is a line-voltage monitor and now is the time to build it.

### AC line monitor

The problem with a VOM or a panel meter is that the scale graduations are very small and set close together. Sometimes they are marked in units of 5 volts or even 10 volts, which does not make for very accurate readings. If the meter scale went from a low of 100 volts to a high of 125 volts, for example, you could read it much more easily.

That's just what an expanded-scale meter is: the bottom of the scale is left off or highly compressed, and the top is expanded to fill all or most of the space.

Figure 1 shows both an expanded-scale meter and the method for attaching it to the power line. I *strongly recommend*

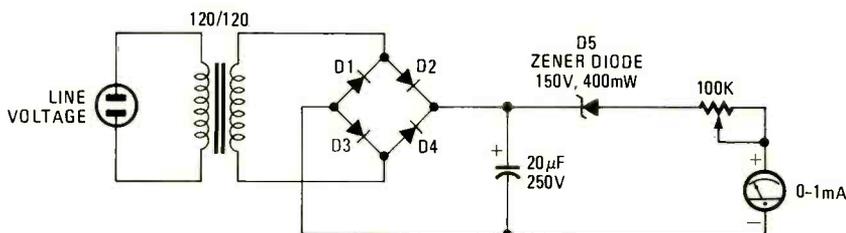

D1, 2, 3, 4 - SILICON DIODES, 50mA, 250 PRV (1N4004 OR EQUIVALENT)

FIG. 1

using an isolating transformer. If you do not own or cannot find an inexpensive transformer with a secondary winding close to 120 volts AC, you can use two small filament transformers placed back-to-back, as seen in Fig. 2. These transformers can be 5, 6.3, or 12.6 volts, or almost anything as long as they are the same. They can also be the smallest transformers you can find since very little power is drawn from them.

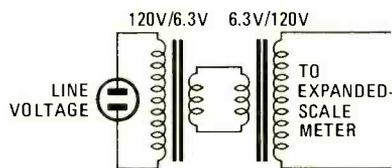


FIG. 2

### How it works

Here's how the meter operates: Diodes D1 through D4 rectify the AC voltage to DC voltage, and the capacitor smooths out most of the ripple. The Zener diode, D5, doesn't allow any appreciable amount of current through until its Zener voltage is reached, thereby effectively eliminating the bottom part of the scale. The potentiometer is used to set the meter during calibration. Any milliammeter with a scale from 0 to 1 can be used but choose one that comes apart easily so that you can change the scale markings.

Obviously, what the circuit is doing is measuring any change in a DC voltage that is caused by a change in the AC line voltage. The reason for this roundabout method of checking is to avoid a complex AC circuit that functions no better than this one.

### Calibration

To calibrate the expanded-scale voltmeter requires a variable AC voltage source and a way to measure it. The most

convenient variable AC source comes from an adjustable-voltage autotransformer (known also as a *Variac*) if you can borrow one. Figure 3 shows how to connect this transformer. The AC meter across the *Variac* output can be any accurate VOM, VTVM, DMM, etc.

First, set the transformer to put out 120 volts (or the normal voltage in your area) and adjust the potentiometer until the expanded-scale voltmeter reads about three-quarters full-scale. Do not change the potentiometer after making this adjustment. Mark "120" on the face of the scale right under the needle of your expanded-scale voltmeter.

Next, change the variable-voltage transformer to another voltage and mark that on your new meter. Continue changing and marking until there are as many gradations as you will need. Now your

expanded-scale voltmeter is ready to connect to the power line.

### Substitute variable-voltage supply

Here are a couple of ways to perform the calibration if you can't locate a variable-voltage transformer. One method requires an old model-train transformer (from back in the days when these trains

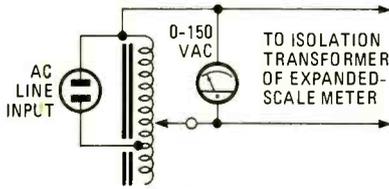


FIG. 3

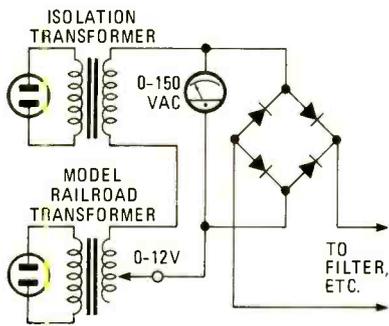


FIG. 4

ran on AC). Connect the secondary in series with the secondary of the isolation transformer (see Fig. 4).

The variable AC output (usually from 0 to 12 volts or 16 volts) will either add to or subtract from the output of the isolation transformer. Perform the calibration up or down (as needed) and then switch the output leads of the train transformer. This will cause the total output to vary in the other direction and you can complete the calibration. (Incidentally, that train transformer is a handy item to have around the workbench.)

You can also use several filament transformers, although this is a less convenient method. Connect them as shown in Fig. 5

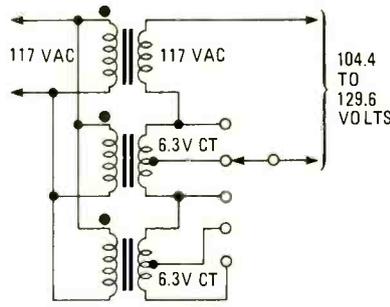


FIG. 5

to obtain various fixed points on the scale. Reversing one or more secondaries will provide additional points. Assuming you have a 117-volt AC line, the combination shown in Fig. 5 will yield outputs of 104.4, 107.55, 110.7, 117, 120.15, 123.3, 126.45 and 129.6 volts. [For voltages


below 117, you must reverse the phase (connections) to the primary winding of the 117-volt isolation transformer.] Of course, other filament voltages will yield other results.

### The Zener diode

The useful range of your expanded-scale voltmeter will depend upon both the exact voltage of the Zener diode and the internal resistance of the meter. In my setup, a 145-volt Zener produces a range of 95 volts to 125 volts. Of course, the top and bottom readings also vary with how the calibration potentiometer is set; for example, I can easily change mine to read from 105 volts to 135 volts.

You can actually tailor your expanded-scale voltmeter to your specific needs. Lowering the Zener voltage by 5 volts or 10 volts expands the range (compresses the scale—the gradations are closer together). Using a Zener with a higher voltage rating causes just the opposite effect (it expands the scale more), but if the Zener voltage exceeds the DC voltage applied, the meter will not register.

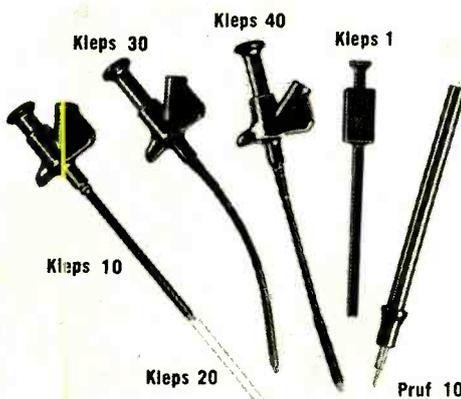It is easy to adjust the Zener voltage in the circuit. When Zener diodes are placed in series, their voltages add (just like resistors). So, five 30-volt diodes in series act just like a 150-volt unit. Thus, you can place smaller Zener diodes of assorted values in series to obtain any value you need. R-E



## Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. \$1.39
  - Kleps 20.** Same, but 7" long. \$1.49
  - Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79
  - Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 3/4" long. \$2.59
  - Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$ .99
  - Prof 10** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$ .89
- All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:  
**RYE INDUSTRIES INC.**

133 Spencer Place, Mamaroneck, N.Y. 10543  
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 59 ON FREE INFORMATION CARD



## Accuracy like a VTVM... Convenience like a VOM...

NEW BATTERY-OPERATED FET  
SOLID-STATE VOLT-OHMMETER #116

Easy-to-build KIT

**\$41.85** =116K

Factory-Wired & Tested


**\$56.12** =116W

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 megohms input on DC, 1 megohm on AC
- 500-times more sensitive than a standard 20,000 ohms-per-volt VOM
- Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 0-1.2, 12, 120, 1200V; 4 DC voltage ranges: 0-1.2, 12, 120, 1200V; 4 Resistance ranges: 0-1K, 0-100K, 0-10 meg., 0-1000 meg.; 4DB ranges: -24 to +56DB.

Sensitive easy-to-read 4 1/2" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5 3/4" H x 6 3/4" W x 2 7/8" D. 3 lbs.

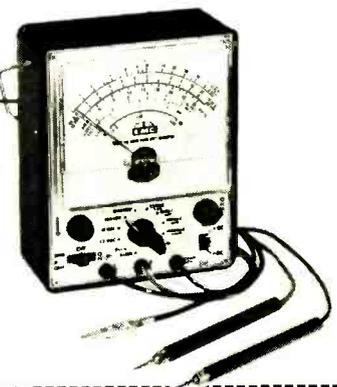

Send FREE catalog of complete EMC line and name of nearest distributor. RE-8

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

# EMC

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York, N.Y. 10012

AUGUST 1978

# ANNOUNCING ... A New CREI Program: Minicomputer & Microprocessor Technology Including A Microprocessor Laboratory

Now you can learn at home  
the new technology that is  
revolutionizing electronics

The microprocessor has ushered in the age of microtechnology and electronics will never again be the same. The microprocessor has made possible the placing of an entire computer on a silicon chip one quarter inch square. The microprocessor "miracle chip" is in the process of changing the world. Soon all technical personnel in electronics will have to understand and work with the microprocessor. It is invading virtually every area of electronics. And it is profoundly affecting your electronics career.

### **Brand New Program**

CREI has a brand new program to help you learn how to work effectively with this revolutionary electronics development. CREI's new program in Minicomputer and Microprocessor Technology is designed to prepare you for this field by giving you the education and practical experience you need.

The program provides solid preparation in electronics engineering technology with a specialization in minicomputers and microprocessors. In addition, it includes a microprocessor laboratory which features a fully programmable microcomputer which utilizes the Motorola 6802 microprocessor chip. This is an extremely important element of your program.

### **Programming Essential**

As you may well know, you must learn how to *program* the microprocessor in order to design, service or troubleshoot microprocessor electronic systems. There is only one effective way to learn this all-important skill of programming, and that is by actually *doing it*. CREI's new program gives you this opportunity as you work with the exciting microprocessor laboratory.

### **Programming Is Easy**

With CREI's new program, learning the skill of programming is simple. Within a few hours you'll be programming the microprocessor and in a short time you'll learn how to program it in three languages: BASIC, assembly and machine languages. In addition, you will learn how to interface the microprocessor with other systems and to test and debug specialized programs.

# Preparation at Home

## Wide Choice of Programs

Please note, however, that CREI's new program is only one of 16 state-of-the-art programs in advanced electronic technology offered by CREI. So even if you choose not to specialize in micro-processor technology, CREI has an advanced electronics program to meet your needs.

With CREI, you may choose from any of the following areas of specialization in advanced electronics:

- Microprocessor Technology
- Computer Engineering
- Communications Engineering
- Digital Communications
- Electronic Systems
- Automatic Controls
- Industrial Electronics
- Television Engineering
- Microwave Engineering
- Cable Television
- Radar and Sonar
- Nuclear Instrumentation
- Satellite Communications
- Aeronautical and Navigational
- Solid State Theory
- Nuclear Engineering

## Unique Lab Program

An exclusive option available with CREI programs in electronic engineering technology is CREI's unique Electronic Design Laboratory program. It gives you actual experience in designing practical electronic circuits. It also helps you to understand the theories of advanced electronics and gives you extensive experience in such areas as tests and measurements, breadboarding, prototype construction, circuit operation and behavior, characteristics of electronics components and how to apply integrated circuits. Only CREI offers this unique Lab Program.

## Practical Engineering

CREI programs give you a practical engineering knowledge of electronics. That is, each part of your training is planned for your "use on the job." By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.


## Free Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog. This fully illustrated, 56 page book describes in detail the programs, equipment and services of CREI.

## Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.
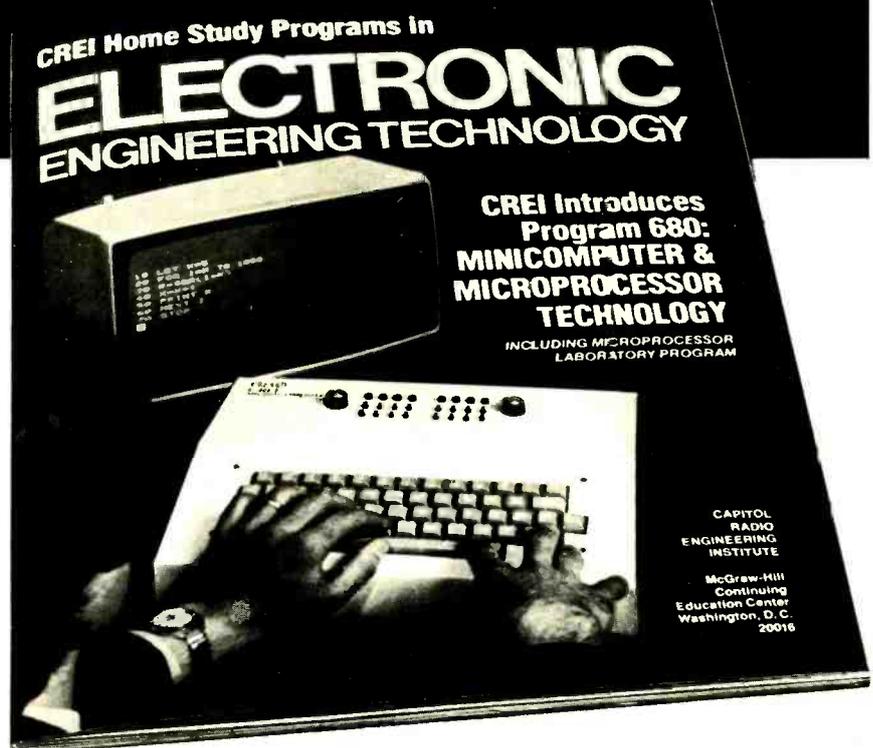
# Send for this FREE Book describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

# CREI CAPITOL RADIO ENGINEERING INSTITUTE

McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue Northwest  
Washington, D.C. 20016

Accredited Member National Home Study Council

## GI Bill

*CREI programs are approved for training of veterans and servicemen under the G.I. Bill.*



# state of solid state

*An in-depth look at a temperature transducer and precision voltage reference all on one IC. Plus a look at some new developments.*

KARL SAVON, SEMICONDUCTOR EDITOR

CONTAINED WITHIN THE DATA SHEET FOR the REF-02 +5-volt precision voltage reference are the terms, *regulator* and *thermometer*. The REF-02 is a bandgap reference that uses the predictable temperature characteristics of silicon-diffused junctions to create a stable voltage. It does not use a constant-starting point such as a Zener, but much the opposite. It takes the temperature-variable junctions of two silicon transistors and sets them against each other to produce a near-zero temperature coefficient.

There is also a temperature-dependent output available at a terminal on the package. An accurate thermometer can be constructed by combining the reference and temperature-dependent outputs in an external operational amplifier. The thermometer can be calibrated directly in degrees Fahrenheit, Celsius or Kelvin, and can have a linear scale factor that can be adjusted by choosing different resistor values. Typical scale factors are from 10 mV/°C to 100 mV/°C. Measuring the output voltage on a digital voltmeter then gives direct temperature readings.

The thermometer has another unique feature. It can be calibrated accurately at a single temperature, which can be room temperature. Although it requires an accurate 100-mV source as part of the calibration procedure, repeated adjustments at two known temperatures, such as the boiling and freezing points of water, do not have to be made.

The REF-02 circuit is shown in Fig. 1. The circuit does not have many inputs and outputs and fits easily in an eight-pin TO-99 case. Included are an input terminal for the power supply; an output for the precisely regulated voltage; a terminal marked TEMP, which is the temperature-dependent voltage; a trim terminal, and ground (three terminals are not connected).

You could not tell from a cursory glance that the heart of the circuit is just two transistors. Transistors Q1 and Q2 have been proportioned in current and area so that the current density in Q1 is one-sixteenth of the current density in Q2. The emitter area of Q1 is four times that of Q2, which means if both transistors carried identical currents, the current density in Q1 would be one-fourth

that of Q2. In addition, collector resistors R3 and R4 scale the currents in Q1 and Q2 in the ratio of 1:4. The product of the two factors gives a 16:1 current-density ratio.

First with respect to the constants,  $k$  is Boltzmann's constant, which is a physical constant equal to  $1.3804 \times 10^{-23}$  joule/°K, and  $T$  is the absolute temperature of the junction in degrees Kelvin. Celsius temperatures are converted to Kelvin by adding 273. Kelvin and Celsius degrees represent identical temperature increments, but  $-273^\circ\text{C}$  or  $0^\circ\text{K}$  is known as absolute zero. The  $q$  term is the charge on

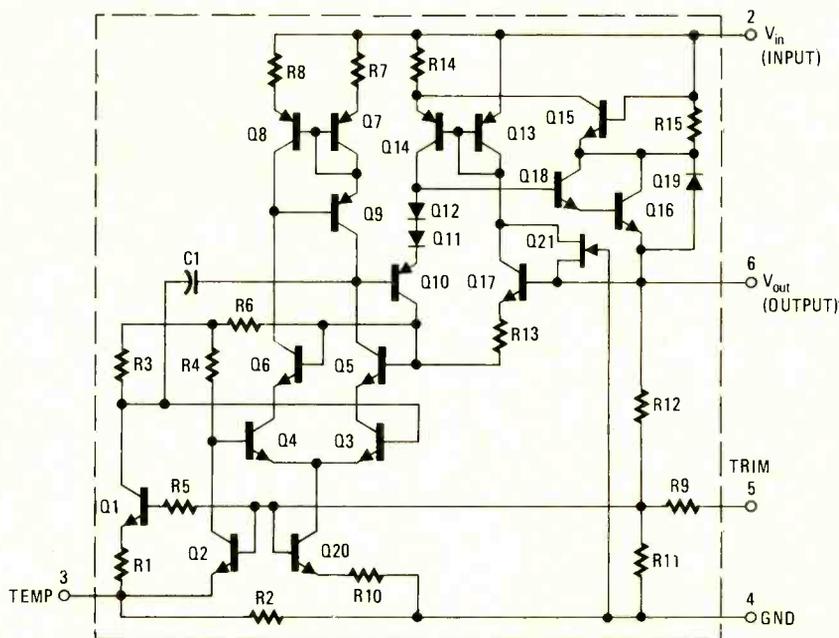


FIG. 1

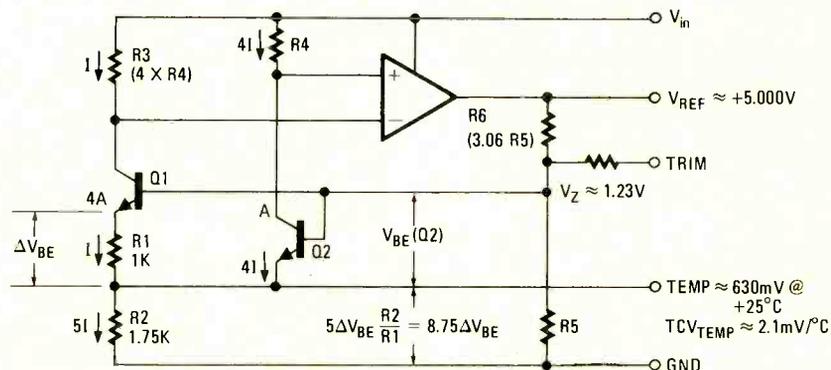


FIG. 2


The diode equation relates the base-to-emitter voltage of a diode or transistor to its temperature and current. One form of the diode equation is  $V_{be} = kT/q \ln I_c/I_s$ . Here's a good opportunity to exercise the natural logarithm function on that gift scientific calculator!

an electron equal to  $1.6021 \times 10^{-19}$  coulomb,  $I_c$  is the diode or transistor collector current, and  $I_s$  is the saturation current.

At first, it might seem that the voltage across a silicon junction increases directly as temperature because of term  $T$  at the

beginning of the equation. However, the saturation current is itself highly dependent on temperature, and, in fact, the temperature coefficient of the junction is negative. The coefficient is in the order of  $-2.1 \text{ mV}/^\circ\text{C}$ , with its precise value determined by the manufacturing process.

Even though the equation appears to show that  $V_{be}$  would be zero at 0 degrees Kelvin, the temperature-dependent  $I_s$ -term decreases toward zero at a rapid rate. If absolute zero is approached as a limit, the 1.23-volt bandgap voltage of silicon results. Another approach is to take the  $-2.1 \text{ mV}/^\circ\text{C}$  coefficient and determine what happens at absolute zero. The junction voltage would be the room-temperature voltage, or around 0.6 volt, plus the increase that results from the 293 (273 + 25)-degree drop in temperature, or  $298 \times 2.1 \times 10^{-3} = 0.628$  volt. The bandgap voltage is therefore about 1.23 volts. It turns out that if this voltage is generated by adding two terms by the method described in following paragraphs, a zero coefficient voltage is theoretically produced.

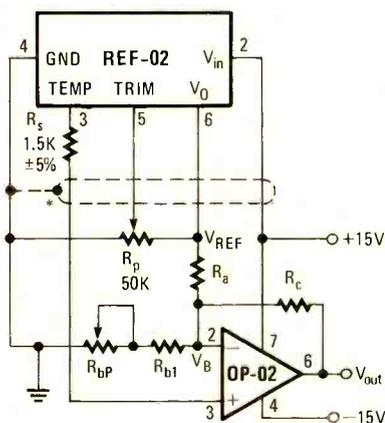

\*UP TO 10 FEET OF SHIELDED 4-CONDUCTOR CABLE.

FIG. 3

The diode equation becomes very interesting when you compare the voltage across two diode junctions with different current densities. Recall that when you take the difference between the logarithms of two numbers, the result is the same as the logarithm of the ratio between the numbers:  $\ln A - \ln B = \ln A/B$ . Substitute numbers for A and B and verify it on your calculator. If the voltage between two junctions is calculated by subtraction, the equation now looks very much the same as before, except that the  $\ln$  term operates on the ratio of the current densities in the two junctions:  $\Delta V_{be} = kT/q \ln J_1/J_2$ . You may have seen this expression before to describe the input to a differential amplifier that produces specific currents in the two input transistors. The  $kT/q$  term at room temperature calculates to about 26 mV. To double the current in a transistor, it takes  $26 \ln 2$ , or about 18 mV. A

significant change in the equation is that because it was created by subtracting two equations with  $I_s$ -terms, the temperature-variable saturation current has dropped out. Now, the temperature coefficient is entirely due to the T-term in the numerator and has a positive sign.

In summary, the temperature variation of a single transistor junction has a negative temperature coefficient, while the difference in voltage between two semiconductor junctions with different current densities has a positive temperature coefficient.

In Fig. 2, the components associated with the internal operational amplifier function are replaced with an amplifier

symbol, but essential feedback and gain determining resistors are retained.


As mentioned previously, the current density in Q1 and Q2 are in the ratio of 16:1. We can now calculate the differential voltage between the base-emitter junctions from the diode equation. The current in Q1 and Q2 is maintained in a 4:1 ratio by the 4:1 ratio of the collector resistors. Negative feedback around the operational amplifier requires that the input voltage at the inverting and noninverting inputs be identical; so the current through R3 in the Q2 collector must be four times as great as the current through R3 in the Q1 collector.

continued on page 76

## Everything you ever want to know about Personal Computers . . .

# \$1.00

Postage Paid in U.S. and Canada

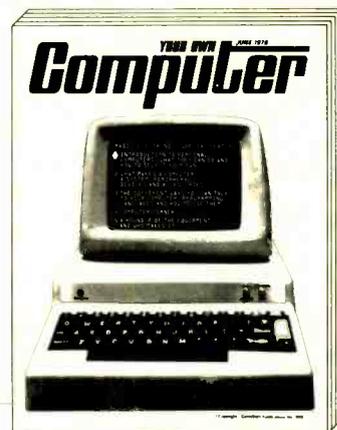

Here it is—everything you need to know about the state of the art, just as it appeared in the big, colorful special section of the June, 1978 RADIO-ELECTRONICS—"Your Own Computer."

This complete, colorful, 32-page reprint of that first-in-the-field special feature tells you *everything* you want to know, including: An Introduction to Personal Computers—what they can do and how to select your own; What Makes a Computer System—peripheral devices and accessories; The Different Ways You Can Talk To Your Computer—programming languages and how to use them; a special edition of Computer Corner; and, A Roundup of the Equipment, the most complete Who-Makes-It Computer Manufacturer Listing you can find!

We've reprinted this giant special section of RADIO-ELECTRONICS for your convenience. Every serious experimenter and technician will want this vital information at home *and* in the office, lab or workshop, where you can refer to it when you need it. At this very special low, low price of just \$1.00, you can afford to have your own copy of "Your Own Computer" everywhere you go—and give some to friends, too.

Don't delay. We're ordering a big reprint of this very popular feature section, but we're expecting a big demand, too. For your convenience, use the coupon below to order your own reprints of the single most authoritative, most colorful, most comprehensive report on today's Personal Computers, the 32-page reprint of RADIO-ELECTRONICS' "Your Own Computer," for just \$1.00. Do it today.

**Ms. Nancy Estrada**  
17 Slate Lane, Central Islip, New York 11722

Please send me \_\_\_\_\_ copies @ \$1.00, Total \$\_\_\_\_\_ of your 32-page reprint of RADIO-ELECTRONICS' "Your Own Computer" special report. My check or money order is enclosed. New York State residents must include State Sales Tax.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# service clinic

## Pulse-width modulated DC power supplies and how to troubleshoot them.

JACK DARR, SERVICE EDITOR

WE'RE CONTINUALLY DISCOVERING NEW uses for known circuits. Pulse-width modulation (PWM) has been around for some time. Actually, the basic principle has been used for DC voltage regulation in TV sets. If I'm not mistaken, Sony's model KV-1722 was the first chassis to use a PWM circuit.

The basis of a PWM circuit is a controllable switch, to which a DC voltage supply (rectified and filtered) is fed from the AC line. This switch is normally off. Sony uses a gate-controlled switch (GCS) that behaves similar to a silicon controlled rectifier, but it can be turned on or off by control pulses to create a series of pulses; you'd probably call this circuit a chopper. Figure 1 is the block diagram of a basic PWM circuit.

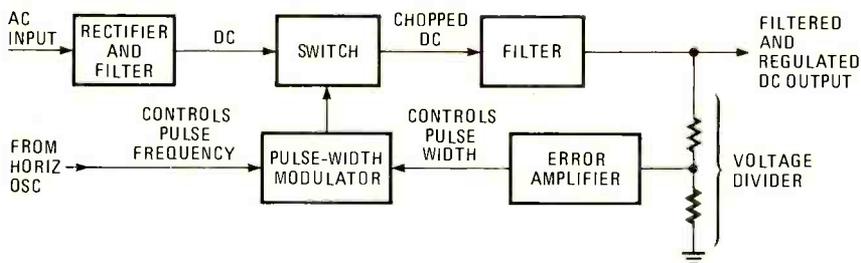


FIG. 1

Let's see how this circuit behaves. As you should know, the DC output voltage of a power supply is developed from the charge in the filter capacitors. All that the power supply does is recharge the capacitors at regular intervals, when the load current discharges them. Therefore, there's a given amount of charge (energy) in the capacitors, and the voltage will remain fairly constant under normal current drain. In the PWM circuit, the chopped DC power supply simply feeds in pulses containing just enough energy to recharge the capacitors and hold the voltage constant.

Now, if the load current increases, more energy is being taken out than is being fed in and the output voltage drops. If the current decreases, less energy is removed and the voltage goes up. In either case, an error amplifier senses the change in load voltage. This stage controls the action of a switching-pulse generator. This is the stage that turns the

GCS on or off. The error amplifier controls the pulse width of the modulator. In the Sony circuit, this is a monostable multivibrator. If the output voltage goes down, the pulses become wider; when the output voltage goes up, the pulses grow narrower.

If the output pulse becomes narrower, there is less total energy in it. A smaller amount of energy is sent to the filter capacitors, their charge decreases, and the output voltage goes back down to normal. A wider pulse sends more charge into the capacitors, with the result that the voltage goes up to normal. Remember, this all takes place within a very short period of time, the regulation action is almost instantaneous. Figure 2 shows the difference between the normal

that the GCS is actually off most of the time. With the 30% duty cycle, the GCS is off 70% of the time! This greatly reduces the power that is dissipated by the GCS.

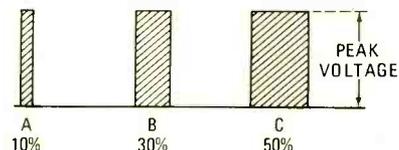


FIG. 2

There are other advantages, some of which have been used before in a different way. First, the basic ripple frequency isn't 60 Hz–120 Hz, but 15,750 Hz. The DC voltage is gated at the horizontal frequency. So, filter capacitors and chokes can be made smaller for the same filtering efficiency. However, both capacitors and chokes must be able to handle a fairly high ripple current at high frequencies. Only low-loss capacitors can be used in order to withstand the dielectric heating. Chokes must be high-Q types and able to withstand heavy RF current. So, do not use stock electrolytic capacitors or chokes for replacements.

This is the same problem we've been experiencing on flyback-derived DC voltage supplies. Stock sinewave diodes don't work well because they draw too much reverse current with a spike pulse. Only the fast-recovery diodes operate properly. The correct diodes, transistors and capacitors must be used, or "the cure will be worse than the disease."

Servicing these power supplies requires even more extensive use of the scope than in the old type of power supplies. You must use the scope to trace the control pulses through their circuits, and make sure they go to the right place, with the correct waveform! On a recent TV I found a nice squarewave where the schematic called for a sharp sawtooth waveform. Eventually, I found that two small capacitors contained in the sawtooth-shaper circuitry were open. Replacing them brought back the sawtooth waveforms and normal operation of the power supply. These are just some more circuits where "the VOM isn't enough!"

Although PWM circuits look fairly complex at first, they aren't really. Each stage has a definite function, and if you check each stage methodically to make sure they are doing their job properly, it

continued on page 78

# NEW for Professional Technicians

## Forest Belt's TRAINING WORKSHOPS 1978

- THREE-DAY
- INTENSIVE
- UP-TO-DATE
- PERSONAL
- UNIQUE
- Includes lodging
- Breakfasts, lunches, and coffee breaks during WORKSHOPS
- Grand AWARDS BANQUET
- FREE Extra SEMINAR

### ADVANCED VIDEO SERVICING

Featuring VCRs, Digital Controls, VIR . . .  
and much more

Intensive Forest Belt teaching techniques and exclusive, proven training aids bring you right up-to-date in the troubleshooting and repair of today's video equipment for home or industry.

Special emphasis on solid-state and integrated circuits. See new IF and color alignment methods you probably never thought of. Learn about Vertical Interval Reference (VIR) automatic color control in newly introduced TV receivers. Understand digital and solid-state tuning systems. Participate in live equipment demonstrations. Sit in on the industry's first look at practical, **Easi-Way™** repair of video cassette recorders.

DON'T BE LEFT BEHIND in your own industry! Be the one technician in your region who not only keeps up but stays AHEAD of new technology and servicing methods. ENROLL NOW to be sure you do not miss this vital and unique Advanced Video Servicing WORKSHOP.

FREE Price and Profit SEMINAR Tuesday evening.

**September** Hospitality Inn East  
**11-13 (Communications)** Interstate 70 at Post Road  
**or 18-20 (Video)** Indianapolis, INDIANA

Centrally placed for convenient travel from anywhere in the mainland U.S. Also timed earlier in the year, in case you should not be away from your shop during the pre-Christmas season. You can attend in time to prepare you for the year-end service rush and the new sets being sold.

Comfortable, pleasant accommodations: two people to a room (two beds). Indoor pool. Shopping downtown by freeway. Bring your spouse if you wish, at the nominal No-WORKSHOP fee (she joins the WORKSHOP group for breakfasts and lunches). If you prefer to room with a specific other WORKSHOP attendee, tell us.

Enrollments close August 4, 1978, or when capacity is reached.  
Per Workshop **\$495**



### ADVANCED COMMUNICATIONS SERVICING

Featuring FM Two-Way, PLL, Single Sideband . . .  
and much more

Here, too, intensive Forest Belt teaching methods and exclusive, tested learning aids assure you up-to-the-minute training in troubleshooting and maintaining communications systems.

Special emphasis on solid-state and integrated circuits. Observe professional alignment and tuneup methods. Deal profitably with Business and Land Mobile Radio—and the growing General Mobile Radio on UHF wavelengths. Learn of new developments in Marine and Aircraft Radio. Study the latest phase-locked loops, including their digital programming. Take part in live equipment demonstrations. See **Easi-Way™** techniques applied to communications.

GROW AS A REAL EXPERT in your specialty. Grab this exceptional opportunity to polish up your diagnosis and repair skills. Become familiar with new technology and money-saving instruments. ENROLL NOW in Advanced Communications . . . a giant step beyond our popular CB Servicing WORKSHOPS.

FREE Math and Formulas SEMINAR Tuesday evening.

**November** South Seas Plantation  
**6-10 (Communications)** Captiva Island, FLORIDA  
**or 13-17 (Video)** (near Sanibel and Ft. Myers)

For technicians who could use a bit of get-away time as part of this unique training package. Two days of consulting or on-your-own follow each WORKSHOP. Make your own airline reservations, well in advance; but we take care of placing you in our luxury cottage lodging.

Exceptional resort accommodations: four people (two bedrooms, four beds, two baths) or six people (three bedrooms, six beds, three baths) in fancy beach cottages. Bring your spouse, if you wish, at the nominal No-WORKSHOP fee (she joins the WORKSHOP group for breakfasts and lunches). If you prefer to share a room with a specific other WORKSHOP attendee, tell us. Cottages have kitchen facilities. An unusual winter-season bargain.

Enrollments close Sept. 15, 1978, or when capacity is reached.  
Per Workshop **\$595**

----- FIRST COME, FIRST SERVED ----- ENROLLMENT DEADLINES ABOVE -----

Yes, enroll me promptly for TRAINING WORKSHOP at right.  Advanced Communications Servicing  Advanced Video Servicing

I enclose check or money order for \$\_\_\_\_\_ U.S. dollars.

- \$495 per WORKSHOP in Indianapolis
- \$595 per WORKSHOP in Florida
- \$175 for spouse
- \$250 for spouse (includes lodging, same meals as for WORKSHOP enrollee)
- \$475 for CB Service WORKSHOP (same as 1977, and includes lodging) at Indianapolis August 21-23, 1978.

Name \_\_\_\_\_ Age \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_ Phone \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

NOTE: You need 2 years electronics training or experience to gain proper benefit from these Advanced TRAINING WORKSHOPS. NOT FOR BEGINNERS.

Mail to: Forest Belt's TRAINING WORKSHOPS, Box 68120, Indianapolis IN 46268

CIRCLE 30 ON FREE INFORMATION CARD

**STATE OF SOLID STATE**  
continued from page 73

The differential voltage between the two emitter junctions appears across R1 and is  $26 \ln 16$ , or 72 mV. A positive temperature coefficient of 2.1 mV/°C is produced by amplifying 72 mV by a factor of 8.75 up to 0.63 volt.

The current through R2 is the sum of I and 4I or 5I, already an amplification of five times the current through R1. Resistors R2 and R1 are in the ratio of 1.75K to 1K. The total gain is  $(4 + 1) \times 1.75 = 8.75$ . Then, to determine the constant reference, just add the junction voltage of a silicon transistor with its negative 2.1-

mV coefficient. The base-emitter junction of Q2 increases the voltage across R2 by the required junction potential to the constant 1.23-volt bandgap voltage. To get the rest of the way up to the 5-volt output of the REF-02 at the base of Q1 and Q2, the voltage is amplified by the ratio of R6 and R5, at which point  $V_{REF}$  is  $1.23 \times (3.06 + 1) = 1.23 \times 4.06 = 5$  volts.

Now, combine the constant output and the variable temperature coefficient output of the REF-02 to construct the thermometer (see Fig. 3). The REF-02 acts as the temperature sensor and may be located remotely by using a shielded cable with the additional precaution of

reducing the capacitance loading pin 3 by isolating resistor R<sub>s</sub>.

The TEMP output is directly connected to the noninverting op-amp input, and a portion of  $V_{REF}$  is summed with a portion of the amplifier output at the inverting op-amp input. As usual, the feedback amplifier forces the inverting and noninverting inputs to be essentially equal. Thus, it is possible to solve the conditions relating the output voltage to the two inputs. An output must be created that can be controlled in temperature coefficient by using a portion of  $V_{TEMP}$ , and that can be shifted in DC value by using a portion of  $V_{REF}$ .

Since the inverting input must equal  $V_{TEMP}$ , the sum of the contributions to the inverting input voltage on pin 2 of the op-amp from  $V_{OUT}$  and  $V_{REF}$  must also be equal to  $V_{TEMP}$ . Superposition is the method used. First, assume  $V_{OUT}$  is zero by shorting it to ground and calculate what part of  $V_{REF}$  gets to pin 2. At this point,  $R_b$ , the sum of the fixed resistor  $R_{b1}$  and the variable resistor  $R_{bp}$  are in parallel with  $R_c$ ;  $V_{REF}$  is therefore divided by the ratio  $(R_b || R_c) / (R_a + R_b || R_c)$ .

Similarly, with  $V_{REF}$  shorted to ground, the portion of  $V_{OUT}$  transferred to pin 2 is  $(R_a || R_b) / (R_c + R_a || R_b)$ .

Working out the equation for  $V_{OUT}$  yields the expression:  $V_{OUT} = AV_{TEMP} + BV_{REF}$ , where A is equal to  $1 + (R_c / R_a || R_b)$  and B is equal to  $R_c / R_a$ .

**burglar-fire alarm catalog**  
**FREE!**



**MORE THAN 900 PRODUCTS**

**detectors, controls, sounders, locks, tools**

**EVERYTHING NEEDED TO PROTECT HOME, BUSINESS, INSTITUTION**

Huge selection of high quality professional alarm products. 64 fact-filled pages with detailed specs, diagrams, technical notes.

Products range from basic switches, controls, bells, sirens to most sophisticated detectors — radar, modulated or passive infrared, microwave, ultrasonics, ion, data links using pulse code multiplex, FSK radio, automatic phone dialers, leased line connections and display panels. Full selection of tools, relays, wire, foil, terminals, books.

**WRITE FOR FREE CATALOG TODAY!**

(Outside U.S., send \$1.00)



**mountain west alarm**  
box 10780 • phoenix, az 85064

(602) 263-8831

**CIRCLE 13 ON FREE INFORMATION CARD**

"THE ORIGINAL"

**Personal Computing™ 78**

**Good by ATLANTIC CITY**

**HELLO PHILADELPHIA**

**The Largest Personal Computing Show Ever Held**

**ONLY MAJOR EAST COAST SHOW IN '78**

August 25, 26, 27th at the Philadelphia Civic Center

300 + Booths  
80 Hours of Free Seminars  
Art Show  
Music Festival  
Banquet

THREE FULL DAYS OF FUN

As of May 11, 1978 the following companies have selected their booth locations. Over 200 exhibitors expected at the only Major East Coast Personal Computing Show of the year.

INTERFACE AGE MAGAZINE HEATH COMPANY BYTE MAGAZINE MICROAGE ITHACA AUDIO ARTEC ELECTRONICS COMPUTER MART OF NEW JERSEY SUMMAGRAPHS PERSONAL COMPUTER CORP. TELPAR VECTOR ELECTRONICS BITS BOOKS SOUTHWEST TECHNICAL PRODUCTS (SWTP) CROMEMCO TECHNICAL DESIGN LABS HAYDEN BOOKS DIGITAL EQUIPMENT CORP OSBORNE & ASSOCIATES OHIO SCIENTIFIC INSTRUMENTS RAMSEY ELECTRONICS MIDWEST SCIENTIFIC INSTRUMENTS COMPUTER MART OF PENNSYLVANIA ADVANCED COMPUTER PRODUCTS PAGE SELECTIONS PROCESSOR TECHNOLOGY THE DIGITAL GROUP CREATIVE COMPUTING MAGAZINE RADIO SHACK ALPHA MICRO SYSTEMS TECHNICAL SYSTEMS CONSULTANTS NORTHERN VALLEY SYSTEMS COMPUTER RETAILING E & L INSTRUMENTS (SHORTLESS & RAWSON) NORTH STAR MARKETLINE COMPUTER RESOURCES NBC IMPORTS E BERG PUBLICATIONS EXTENSYS DILITHIUM PRESS EXPANDOR MICROSETTE NATIONAL MULTIPLEX JADE COMPUTER EMPORIUM NEWMAN COMPUTER EXCHANGE MICRO TECHNOLOGY UNLIMITED MICRO COMPUTER DEVICES RADIO ELECTRONICS MAGAZINE PARASITIC ENGINEERING COMPUTER ENTERPRISES ARRL COMPUTER TEXTILE BASIC BUSINESS SYSTEMS MICRO COMPUTER PRODUCTS S D SALES COMPUTALKER COMPUCOLOR TECHNICO POLYMORPHIC SYSTEMS WILLIAM ELECTRONICS MODULAR SYSTEMS INC ENCLOSURE DYNAMICS MICROPOLIS RICO ENTERPRISES OBJECTIVE DESIGNS SYBEX ELECTRONIC CONTROL TECHNOLOGY APPLE COMPUTER MANCHESTER EQUIPMENT

**DAYTIME EVENTS** • New Products • Demonstrations • Personal Computing College • Exhibits • Art Show • Join Clubs at The Club Booth • User Group Meetings

**EVENING EVENTS** • User Group Meetings • Parties • Music Festival • Banquet, Saturday, August 26, featuring Dr. Adam Osborne, Chris Morgan, Editor of Byte and more. Stay over and enjoy the evening events

Deluxe hotel accommodations with rates starting at \$24 single \$31 double with free shuttle bus to and from Philadelphia Civic Center. Bring the family • Visit Historic Philadelphia • Have an unforgettable Philadelphia experience, pre-register before August 10th and save time and money (20%)

RADIO-ELECTRONICS

Send \_\_\_\_\_ 3 Day Registrations @ \$8 each, \$10 at Door

Send \_\_\_\_\_ Banquet Tickets @ \$17.50 each.

Total Enclosed \_\_\_\_\_

Send Hotel information.

Hold my registration and Banquet Tickets for pick-up at the convention.

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

PHONE \_\_\_\_\_

Send To:  
**PERSONAL COMPUTING 78**  
Rt. 1 Box 242 • Mays Landing, N.J. 08330

RE

It is also known that  $V_{TEMP}$  follows the relationship,  $0.632 + 2.1 \times 10^{-3}(T - 25)$ , where T is in degrees Celsius. If, for example, you want to calibrate the thermometer to read degrees Celsius directly, and need a scale factor of 0.01 so that 0 degrees produces a 0-volt output and -55 degrees Celsius produces a -0.55-volt output, plug these two temperatures into the above equation and solve for the respective values of  $V_{TEMP}$ . You now have two values of  $V_{TEMP}$ , you know what  $V_{OUT}$  should be at those temperatures and you know that  $V_{REF}$  is 5.000V. Now plug these into the equation for  $V_{OUT}$  and solve for A and B. For these numbers, you get  $A = 4.762$  and  $B = 0.47$ . If you put these numbers back into the equation for  $V_{OUT}$ , the result is  $V_{OUT} = 0.01 T$ .

The final accuracy of the circuit depends on the op-amp and the version of the REF-02 reference used. It varies from 0.5% with the REF-02A and OP-02A to 0.9% with the REF-02C and OP-02C. The first combination works over the -55° to +125°C range and has a temperature error of under 0.625 degree at the high limit. The second combination, designed for operation from 0° to 70°C, calculates to a similar maximum temperature error of 0.63 degree. Deviations in the linear characteristic are also specified by linearity and offset errors. Offset error can be eliminated by using

*continued on page 98*

## Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

**WERSI**



Wersi Electronics, Inc.  
Dept. 42,  
1720 Hempstead Road  
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 1 ON FREE INFORMATION CARD

# You can be sure

more times in more circuits in more places  
than with any other multimeters on the market today

Each Sencore DVM is backed with 15 Megohm input impedance for one third less circuit loading on every measurement. That means 50% higher accuracy than other DVMs.

**DVM38 \$395**

**3½ DIGIT .1% DCV ACCURACY  
AUTO-RANGING DVM**

A "prime" standard at your fingertips for measurements you can trust. Auto-ranging for extended low-level range and ease of operation. 15 Megohm input impedance assures .1% reading accuracy is maintained in solid state circuits. Highly sensitive, yet fully protected to 2000 VDC overloads. Hi-Lo Power Ohms circuit simplifies in-circuit resistance measurements.

**DVM37 New \$268**

**3½ DIGIT .1% DCV ACCURACY  
PORTABLE DVM**

Prime standard .1% accuracy on the bench or in the field for less than \$250. The DVM37 is the most accurate portable DVM you can buy, with 15 Megohm input impedance for 50% more accuracy. Includes automatic features—Auto Zero, Polarity, Decimal, Overrange. Fully protected inside to over 2000V on all functions, including Ohms, and protected outside with super-rugged case. Full ranges for every test. Fingertip "Push-On" switch in probe saves batteries as power is applied only when needed.



New DVM37



DVM32

In stock at your favorite local  
Sencore Full Line Distributor.

CIRCLE 22 ON FREE INFORMATION CARD

**DVM32 \$225**

**3½ DIGIT .5% DCV ACCURACY  
PORTABLE DIGITAL MULTIMETER**

Bench and field master for digital accuracy measurements anywhere. 0.5% DCV accuracy, backed with 15 Megohm input impedance. Exclusive battery-saving Auto-Display turns the display on automatically when you make a measurement. 2000V input protection on all functions and ranges—including Ohms.

**DVM36 \$158**

**3½ DIGIT .5% DCV ACCURACY  
POCKET PORTABLE DVM**

Pocket portable lab accurate performance that fits every budget with highest performance-to-price benefits of any meter. .5% DCV accuracy, backed with 15 Megohm input impedance for lowest circuit loading. Full protection to 1000 V on all functions and ranges—including ohms. Drop-proof case. Battery-saving "Push On" button in probe.

**DVM35 \$134**

**3 DIGIT 1% DCV ACCURACY  
POCKET PORTABLE DVM**

Fast, direct reading digital accuracy for the man on the go. Same features as DVM36, except 3-digit, 1% DCV accuracy, backed by 15 Megohm input impedance that is ten times more accurate than analog meters.



DVM38



DVM36

**SENCORE**

DIGITAL MULTIMETER SPECIALISTS

3200 SE SENCORE DRIVE SIOUX FALLS SD 57107 16051 339 0100

INTERNATIONAL FM-2400CH

# FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.



Frequency stability:  $\pm 0.0005\%$  from  $+50^\circ$  to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm 0.00025\%$  from  $+25^\circ$  to  $+125^\circ$  (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

<b>FM-2400CH</b> (meter only) Cat. No. 035320 .....	<b>\$595.00</b>
<b>RF crystals</b> (with temperature correction) .....	<b>24.90 ea.</b>
<b>RF crystals</b> (less temperature correction) .....	<b>18.90 ea.</b>
<b>IF crystals</b> .....	<b>catalog price</b>

Write for catalog

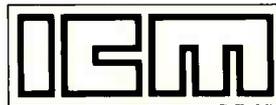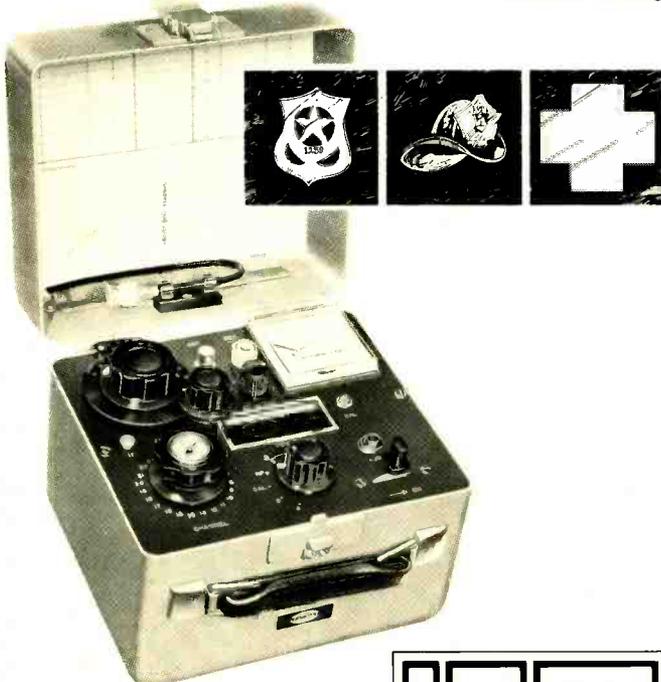

INTERNATIONAL CRYSTAL MFG. CO., INC.  
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 65 ON FREE INFORMATION CARD

## SERVICE CLINIC *continued from page 74*

# For faster service

# USE ZIP CODE

# on all mail


won't take long to find the cause of the problem. Here's one general-purpose hint: If the entire power supply seems to be out, although the DC input voltage from the rectifiers is normal, look around the *horizontal oscillator* stages. You will see that the entire operation of this circuit depends on the presence of horizontal pulses at the input of the PWM modulator stage. Most of these stages have what is called a starter circuit. This feeds a small pulse of DC voltage to the horizontal oscillator to get it started. Once the oscillator starts, the output stage begins and the normal DC power supply starts up. Remember, this all takes place practically instantly. All the oscillator needs is a starting boost. However, if the horizontal oscillator transistor is bad, or there are faults in the oscillator that make it run off-frequency, you can use external DC power supplies to troubleshoot if necessary.

R-E

### DON'T MISS IT

Next month's issue of **Radio-Electronics** will tell you how to build a digital capacitance meter and also how to repair antique radios. Plus much, much more!

## Where's the screwdriver?

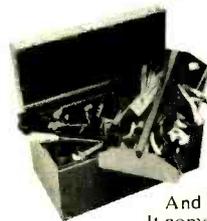

In a tool box, tools and parts are everywhere. They're hard to find. They get lost. (And they get dirty.)

With a Platt tool case, that wouldn't happen. It's designed so you'll know where everything is. Smaller tools are in individual pockets in our patented one-piece pallet. Larger tools and parts are in compartments. And papers and order book are in lid pockets. (Everything is neat and clean.)

And Platt's tool case helps you look more professional. It comes in handsome, lightweight, durable ABS Thermoplastic. Or rich looking vinyl reinforced by ABS Thermoplastic. What's more, it also has a 5 year guarantee.

Contact us for complete information on Platt's full line of tool cases and your nearest distributor.

Pat. No. 3,880,285

# platt

Cases for business and industry.

2301 S. Prairie Ave., Chicago, Ill. 60616 (312) 225-6670




CIRCLE 67 ON FREE INFORMATION CARD
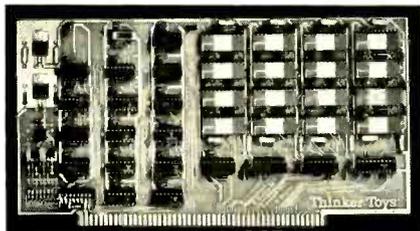
# new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

**8K DYNAMIC MEMORY**, *Econoram III 8K*, uses memory-refresh system called *SynchroFresh*. The board is designed to be used with S-100 microcomputers. The 8K memories use one-half the power of static boards and do not interrupt CPU operations or timing. *SynchroFresh* circuitry



uses the S-100 bus's natural timing and monitors the microprocessor's machine states using T4 states for refresh. Completely assembled, tested and warranted *Econoram III 8K X 8* sells for \$149.—**Thinker Toys**, 1201 10th St., Berkeley, CA 94710.

**CIRCLE 104 ON FREE INFORMATION CARD**

**MINIPRINTER**, model *MP-44*, is a 5- X 7-dot matrix printer for use with any microcomputer using TTL logic levels. It makes permanent copies on electrosensitive paper at speeds up to 88 characters-per-second, 44 characters-per-line. Both printer and paper supply are board-mounted for interfacing to microcomputer, which



then uses an 8-bit parallel output port to control motor and print. Software can be easily implemented in any computer language, and examples of assembly-language coding for the 6800 and 8080 microprocessors are provided. Coding for the 6800 allows unit to be operated immediately from the model *Micro-80 I/O* bus. Price: \$257.—**Electronic Product Associates, Inc.**, 1157 Vega St., San Diego, CA 92110.


**CIRCLE 105 ON FREE INFORMATION CARD**

**THIN-FILM FUSED RESISTOR**, *Melt-Ohm*, has dual-layer metal/organic thin-film structure. Unit generates sufficient heat during overload conditions to break resistance elements, thus opening the circuit. The *Melt-Ohm* resistor creates an

open circuit at about 400°C; it is noncombustible, functions precisely and accurately, and has excellent fusing characteristics. Specifications: Power, ¼ watt; range, 10-10,000 ohms; ±5% tolerance; TCR, ±100 PPM/°C.—**Susumu Co., Ltd.**, Tosh-Jo Co., 140 Main St., Metuchen, NJ 08840.

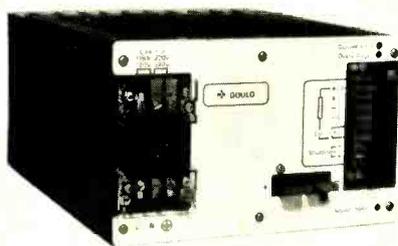**CIRCLE 106 ON FREE INFORMATION CARD**

**CUSTOMIZED SWITCHING POWER SUPPLIES** are available for special engineering requirements needing features or operating characteristics not found in standard catalog units. Power supplies are customized by either reprogramming off-the-shelf catalog units; by placing standard units into rack assemblies having control or sequential logic; or by redesigning units to incorporate changes and modifications required by




the special application; i.e., providing an 8.2-volt, 60-amp output to a standard 500-watt model (shown). Inquiries welcome.—**Gould, Inc.**, Electronic Components Div., 4601 North Arden Dr., El Monte, CA 91731.

**CIRCLE 107 ON FREE INFORMATION CARD**


**CRYSTAL-LESS SCANNER**, *Bearcat 250*, provides 50-channel monitoring and automatic search, store and recall capabilities. Solid-state circuitry includes non-volatile memory and allows pushbutton frequency programming in five bands: low and high VHF, UHF, "T" band and ham frequencies between 146 MHz and 148 MHz. Other features include a digital clock, priority channel, count feature that displays the number of times any frequency has been received, selective scan- and search-speed control, lockout (to remove unwanted frequencies during scan and search); antenna, external antenna jack and crystal filter. Front-mounted speaker has bright LED



# ACCURACY MADE EASY

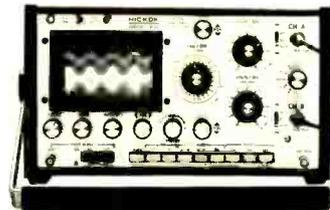

DUAL TRACE MODEL 532 - 30 MHz

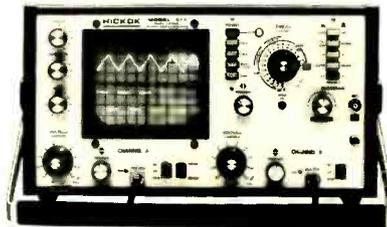

DUAL TRACE MODEL 517 - 15 MHz  
USABLE TO 27 MHz



SINGLE TRACE MODEL 515 - 15 MHz

Put Hickok Scope reliability on your side and get things done easier, faster, better and with complete assurance that you're doing them right.

Economically priced Hickok push-button-triggered Scopes are quick and easy to set up and use. A color-coded front panel speeds up and simplifies operation. Triggering is practically fool-proof, well in excess of the MHz rating. And excellent pulse responses virtually eliminate overshoot and ringing.

Call your nearby Hickok distributor and set up a demonstration today. See for yourself how a modestly priced Hickok single or dual trace 15 MHz, or dual trace 30 MHz, Scope will save you time and exasperation.

If you're outside of Ohio, call us toll free at 800-321-4664 for the name of your nearest Hickok distributor.

# HICKOK


the value innovator

INSTRUMENTATION & CONTROLS DIVISION  
THE HICKOK ELECTRICAL INSTRUMENT CO.  
10514 Dupont Avenue • Cleveland, Ohio 44108  
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 10 ON FREE INFORMATION CARD

AUGUST 1978  
79

# Grandfather's Clock Was Never Like This!

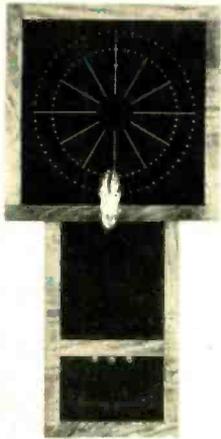

CL7402

If you love contemporary design and yet appreciate the more traditional, here's the perfect clock for you! Amelect has created their own version of the ever popular grandfather clock. Not only

do the electronic eyes around the modern clock face light up displaying each second, minute, and hour, but our grandfather model includes a very novel and exciting electronic pendulum. There's even a shelf for displaying your prized treasures!

The upper section of the clock is 9 $\frac{3}{4}$ " square with an overall length of 19 $\frac{1}{4}$ " all encased in beautiful, hand crafted hardwoods. Select from solid walnut, maple, mahogany, or cherry. This clock is covered by a 1 year warranty on material and workmanship.

As shown on R-E April '78 front cover and described by Fred Blechman.

Available completely assembled or in kit form.

CL7402	Assembled .....	\$95.00
CL7402	Kit with Cabinet .....	71.50
CL7402	Kit less Cabinet.....	56.25
	Shipping and Handling .....	3.50

To order write or call 219-297-3320  
Indiana residents include 4% Sales Tax

# AMELECT

INCORPORATED

P.O. Box 367 - 106 S. Newton St.  
GOODLAND, INDIANA 47948

Allow 3 to 4 weeks for delivery

CIRCLE 70 ON FREE INFORMATION CARD

## For faster service

## USE ZIP CODE

## on all mail

1  
out of  
2 who  
have it  
don't  
know  
it...

Do you?

21 million Americans have high blood pressure. But 50 percent of those who have it, don't know it.

When blood pressure goes higher than it should, and stays high, it sets the stage for heart attack or stroke.

Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association



display and comes with mounting bracket. Price: \$399.95.—**Electra Co.**, Div. Masco Corp. of Indiana, 300 E. County Line Rd. So., Cumberland, IN 46229.

CIRCLE 108 ON FREE INFORMATION CARD


**COLOR-BAR GENERATOR**, model LCG-396, provides signals for TV alignment and performance tests as well as patterns for adjusting VTR, MATV and CATV systems. Pushbutton on/off control of chroma and luminance. Both fixed and variable output levels are provided. The unit can generate 8 precision color bars as well as dot, crosshatch, center-line single crosshatch and four color rasters. Also featured are a composite video output, two RF channels, scope trig-



ger output and full protection against ambient temperatures. The model LCG-396 sells for \$899.95.—**Leader Instruments Corp.**, 151 Dupont St., Plainview, NY 11803.

CIRCLE 109 ON FREE INFORMATION CARD

**S-100 BUS-COMPATIBLE MUSIC BOARD**, model 6, generates music, sound effects, Morse code, touch-tone synthesis and more. Fully assembled unit features selectable output port address decoding, latched 6-bit D/A converter, audio amplifier, speaker, volume control and phono jack for connection to home audio system. Glass-epoxy PC board has plated-through holes, gold-plated fingers and high-quality components. User's

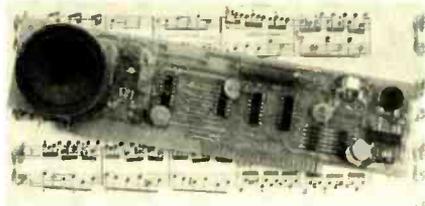

manual (provided with the model 6) contains BASIC and 8080 assembly language programs. The model 6 Music Board is available through computer stores and costs \$59.95.—**Newtech Computer Systems, Inc.**, 131 Joralemon St., Brooklyn, NY 11201.

CIRCLE 110 ON FREE INFORMATION CARD

**PROGRAMMABLE CLOCKS**, model 3300S, model 3300H, are designed for auto, marine and aircraft-navigation applications, and come in two time-display formats: Hour/minute/second (model 3300S) and hour/minute/.01 minute (model 3300H). Both models contain the following features: 6-digit LED display; advance-retard control for fine adjustment of timebase frequency; a countdown timer that counts to zero and back up; auxiliary timer for use as a stopwatch, alarm; and split and remote/split run. Options include a rechargeable NiCad battery pack; a multiple timebase for timing in hour/minute/.01 minute, minute/second/.01 second, or minute/.001 minute; a periodic interval timer to sound beeper at selected intervals; an external alarm jack; and an AC adapter.

Specifications include: accuracy—.001% crystal-controlled, or better than 0.01 minute-per-day; operating temperature—32°F; power re-



quirements—11.0–14.5 VDC, 0.05–0.5 amp. Clock measures 2 1/4 X 7 1/4 X 6 1/4 inches, and weighs 2 1/2 lbs. Prices: *models 3300S and 3300H*, \$329. Options: NiCad battery pack, \$30; multiple timebase (*model 3300H only*) \$15; periodic interval timer, \$15; external alarm jack, \$15; AC adapter, \$20.—**Custom Control Systems**, 21 E. Canon Perdido St., Santa Barbara, CA 93101.

**CIRCLE 111 ON FREE INFORMATION CARD**

**CB BASE STATION**, *model D201A*, is an SSB/AM unit that features tube circuitry and a selectable crystal-controlled or fully tunable receiver; a 4-watt AM output; and a 12-watt PEP SSB output. Controls include an S/R/F power/SWR meter; mike gain; RF gain; squelch; clarifier; switchable noise blanker and limiter; and *model Astatic GPD104* mike. Specifications: adjacent



channel rejection, 8 dB+; SSB sensitivity, .1  $\mu$ V; AM sensitivity, .35  $\mu$ V. Unit measures 2 1/2 W X 7 1/2 H X 13 inches D. Suggested list price, \$995.—**TRAM/Diamond-Corp.**, Box 187, Lower Bay Rd., Winnisquam, NH 03289.

**CIRCLE 112 ON FREE INFORMATION CARD**

**MOBILE TRANSCEIVER**, *model PTR-130K*, is a miniaturized unit that provides 100-Hz resolution from 100 kHz to 30 MHz in all modes; frequencies are pushbutton-selectable. The 100-Hz frequency synthesizer contains an RF compressor that increases output by 12 dB, plus cascaded mechanical filters for high-quality selectivity. Unit



measures 6 1/2 X 2 1/2 X 8 inches. Estimated retail price, \$650—\$700.—**Palomar Electronics Corp.**, 665 Oppen St., Escondido, CA 92025.

**CIRCLE 113 ON FREE INFORMATION CARD**


**DATA CASSETTES**, *Series CDC-1, CDC-2, CDC-3 and Series DDC-20, DDC-40, DDC-60*, are designed specially for use in hobby and small-business computers. *Series CDC* cassettes come loaded in one-, two- and three-minute lengths and use high-quality computer shells, polyolefin slip sheets, machined guide rollers, stainless steel pins, oversized pressure pads and hubs, and extra-short leaders. The *Series DDC* line of cassettes are loaded with high-density calendared ferric-oxide tape, ideal for most computer applications. Suggested retail prices: *Series CDC*, \$4.95—\$6.35; *Series DDC*, \$4.50—



\$5.50.—**Avdex Corp.**, 2280 Grand Ave., Baldwin, NY 11510.

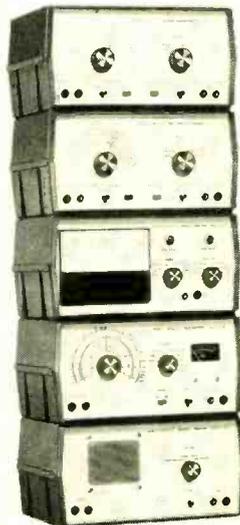**CIRCLE 115 ON FREE INFORMATION CARD**

**TEST INSTRUMENT KITS**, *Series 5280*, comprise a test bench "primer" for electronics beginners. The *model IT-5283* Signal Tracer provides AF/RF tracing; acts as an audible volt/ohmmeter; reads resistance from 0 to 5 megohms; and can serve as substitute speaker for radio/TV servicing. The *model IM-5284* Multimeter measures AC/DC voltage to 1000 volts, DC current to 1000 mA, and provides 4 impedance ranges to 100 megohms. The *model IG-5280* RF Oscillator has an RF output from 310 kHz to 110 MHz and harmonics can be read to 220 MHz. The *model IG-5282* Audio Generator has sinewave and squarewave output capability and a switchable range from 10 Hz to 100 kHz. The *model IB-5281* RCL Bridge provides separate resistance, inductance and capacitance ranges.



Each unit operates from two 9-volt batteries (plus one C-cell for the *model IM-5284*), or from the *model IPA-5280-1* power supply, which has 5 outputs for simultaneous operation of the instruments. Kits are priced at \$37.95 each; the *model IPA-5280-1* power supply costs \$24.95. Free catalog available.—**Heath Co.**, Dept. 350-500, Benton Harbor, MI 49022.

**CIRCLE 50 ON FREE INFORMATION CARD**

**BROCHURE** describes new General Electric GAP (Guaranteed Active Parts) program for service technicians to order replacement TV parts by phone. Contains map of U.S. with listing of toll-free "800" numbers. Master Charge or BankAmericard/Visa can be used to order parts. Parts obsolescence is eliminated with the GAP program—GAP parts may be returned for full credit if they do not remain active. All requests for the brochure must be made on company letterhead.—**General Electric**, Room 1102, 45 E. 17th St., New York, NY 10003.

**CIRCLE 117 ON FREE INFORMATION CARD**

# Measure resistance to .01 $\Omega$ ...



at a price that has no resistance at all.

- 3 1/2 digit bright LED display
- 100 $\mu$  V, .01 $\Omega$  resolution
- 0.5% accuracy typical
- Autozeroing
- Completely overload protected on all 29 ranges
- RFI shielded for use in RF fields
- 100% overrange reading
- Selectable high-/low-power ohms
- Full range of optional accessories available

At \$119.95, the 2810 is a "best buy" among DMM's currently available. Its 10 ohms range allows you to check the low contact resistance of switches, relays, breaker points or connectors. Poor solder connections can also be spotted. Place your order now... contact your local distributor for immediate delivery.

**BK PRECISION**

**DYNASCAN CORPORATION**

6460 West Cortland Avenue  
Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Ontario  
Intl. Sis. Empire Exp., 270 Newtown Rd.  
Plainview, LI, NY 11803

**CIRCLE 69 ON FREE INFORMATION CARD**





**TELEPHONE** bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEVEY LABORATORIES**, Box 547-R, Pennsboro, WV 26415

**UNLOCK** your future. Become professional locksmith by spare time homestudy. \$13 in an hour possible. All tools, equipment included. **Facts FREE**. Send name. **LOCKSMITHING INSTITUTE** (homestudy), Dept. 1339-088, NJ 07424

**FOR SALE**

**FREE** catalog. IC's, Semi's. **CORNET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US Inquiries.

**RADIO & TV** tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, Calif. 92105

**BUILD YOUR OWN TV CAMERA!**  
Ideal for home & business

THE ECONOMIC ANSWER TO HOME MONITORING OF NURSERIES, ENTRANCES, DRIVEWAYS, BUSINESS and INDUSTRIAL SURVEILLANCE. KIT FOR AMATEUR TV PLUS HUNDREDS OF OTHER APPLICATIONS. MODEL XT-1A, SERIES D - KIT FORM SIBS ASSEMBLED. \$275. SEND STATE WORKS ON ANY TV SET. ORIGINAL SOUND KIT \$29.95. PHONE OR WRITE for catalog. Dial 402-367-3771

BOX 453-RE **ATV Research** DAKOTA CITY, NE 68731

**SEEKING** Japanese transistors for CB, TV, stereo repair? Request complete list. Compare 1 to 9 prices: 25C710 .45, 25C517 3.95, 25C799 3.60, 25C1306 2.90, 25C1678 2.25, 7A7205P 2.90, BA521 2.90, SG613 5.95. See our full page ad in the Market Center of this issue. **FUJII-SVEA ENTERPRISE**, Dept. RE, PO Box 40325, Cincinnati, OH 45240

**TS-510A** signal generator, 10-420 MHz, \$250.00. Send stamp for test equipment catalog. E. **FRENCH**, Box 249, Aurora, IL 60507

**YES, YOU CAN BUILD AN ELECTRONIC ORGAN**

That has a PIPE ORGAN SOUND

With **DEVTRONIX** easy to build assemblies. Own the ultimate in organ design & sound at 1/2 the cost of commercial organs.

Several models to choose from.

**BROCHURE AND DEMO RECORD \$1.00**

**Deutronix** ORGANS, INC. Dept. B 5872 Amapola Dr. San Jose, CA 95129

**PRINTED** circuit boards from camera-ready artwork. Free details. **CM Circuits**, 22 Maple Avenue, Lackawanna, NY 14218

**BREATHE BETTER AIR WITH AMAZING NEGATIVE ION GENERATOR KITS AND ASSEMBLED UNITS**

Scientists have long known that negative ions can be beneficial to man's health. These tiny but potent, atmospheric particles abound in nature. Now, through the magic of science, you can duplicate this delightful phenomenon in the privacy and convenience of your own home or office.

Room/Portable Units Ion Testers Accessories

**DEALERS WANTED**

**GOLDEN ENTERPRISES** P.O. Box 1282-RE Glendale, Arizona 85311

(Please send \$1.00 for fascinating details)

**TUBES**, receiving and industrial, semiconductors, factory boxed, low prices, free price list. **TRANSELETRONIC INC.**, 1365 - 39th Street, Brooklyn, NY 11218 212-633-2800

**PRINTED CIRCUIT**

Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.

Send stamp & address label for flyer

**TRUMBULL**  
833 Balra Dr., El Cerrito, CA 94530

**SUMMER special!** Complete cartrivision television recorder electronic assembly. (See previous issues.) \$11.50 plus \$3.50 S & H. Master Charge, BankAmericard. **M.E.C.**, 369, Madison, AL 35758

**VERSATILE LOGIC ANALYZER**

**DATA DOMAIN, WAVE-SHAPE, AND MAP MODE**  
16 BITS x 16 MODES  
POS, MID OR NEGATIVE TIME DISPLAY - 10 MHz  
0.9999 CLK OR EVENT DELAY. MANY MORE FEATURES. WRITE FOR MORE INFORMATION.

**lab ci nce** PO BOX 1972 BOULDER, CO 80306

VLA-1000 \$575.00

**RECORDS-TAPES!** Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-0878, New Rochelle, NY 10801

**PHONE RECORDING CALL ADAPTER**

Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Tape becomes a permanent record. Don't depend on your memory to recall important details of business and personal calls. Easily installed. No extra monthly phone chgs. **FCC Approved**

**AMAZING ELECTRONIC MICRO MINI MIKE**

World's smallest, solid state, self contained with 1.5V Merc. Bat. fern. Picks up most sounds and transmits without wires up to 300 ft. thru FM Radio. Tuneable. Use as mike, ampl., alarm & alert system, baby sitter, bell line, etc. **Mike \$18.95**, Phone Call Adapter \$24.50\* (plus \$1.00 ea. for pstg. & hlg.) Cal. res: add tax. Free data Mail Order, BIA, M/C, card's o.k. Qty. disc. avail. **AMC Sales**, Dept. 19, 3335 Lubec St., Box 928, Downey, CA 90241.

2-1/4 x 3/4 x 1/2"

**Same day shipment.** First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

**INTEGRATED CIRCUITS**

**7400TTL** 74LS00N 41 LM340T-15 110  
7400N 17 74LS00N 25 LM340T-18 110  
7404N 17 74LS04N 25 LM340T-19 110  
7409N 23 74LS04N 25 LM340T-20 110  
7410N 17 74LS10N 25 LM340T-21 110  
7414N 83 74LS14N 51 LM340T-22 110  
7420N 83 74LS20N 51 LM340T-23 110  
7422N 139 74LS22N 51 LM340T-24 110  
7430N 20 74LS30N 39 LM340T-25 110  
7442N 60 74LS42N 39 LM340T-26 110  
7445N 89 74LS45N 51 LM340T-27 110  
7447N 60 74LS47N 39 LM340T-28 110  
7448N 89 74LS48N 51 LM340T-29 110  
7450N 25 74LS50N 39 LM340T-30 110  
7474N 49 74LS74N 39 LM340T-31 110  
7480N 89 74LS80N 51 LM340T-32 110  
7489N 206 74LS89N 51 LM340T-33 110  
7490N 43 74LS90N 39 LM340T-34 110  
7492N 43 74LS92N 39 LM340T-35 110  
7493N 43 74LS93N 39 LM340T-36 110  
7494N 43 74LS94N 39 LM340T-37 110  
74100N 90 74LS100N 51 LM340T-38 110  
74101N 90 74LS101N 51 LM340T-39 110  
74102N 134 **LINEAR**  
74120N 59 CA3045 90 LM2112 7.50  
74125N 39 CA3045 90 LM2112 7.50  
74145N 59 CA3081 90 LM2112 7.50  
74150N 59 CA3081 90 LM2112 7.50  
74151N 59 CA3081 90 LM2112 7.50  
74152N 59 CA3081 90 LM2112 7.50  
74461N 59 CA3081 90 LM2112 7.50  
74462

# FREE PROBES FREE PROBES FREE PROBES

COPIES \$695.00

NLS MS-215 DUAL TRACE MINISCOPE \$395.00

**1c SALE**

**LM3A 3 dig 1% DC** ..... \$125.  
**LM3.5A 3 1/2 dig .5% DC** ..... \$147.  
**LM40A 4 dig .1% DC** ..... \$190.  
**LM4A 4 dig .03% DC** ..... \$227.

Rechargeable batteries and charger included  
 Measures DC Volts, AC Volts, Ohms and Current  
 Automatic polarity, overload and overtemp indication  
 Rechargeable batteries and charger included  
 Measures DC Volts, AC Volts, Ohms and Current  
 Automatic polarity, overload and overtemp indication  
 No adjustment and no full-scale ohms adjustment  
 Battery operated - NiCad batteries; also AC line operation.  
 Large LED display for easy reading without interpolation  
 Size: 1.9" H x 2.7" W x 4" D  
 Parts & labor guaranteed 1 year  
 Tilt stand option ..... \$ 3.50  
 Leather case ..... \$18.00

Purchase any of the LM series Meters and buy the LEATHER CASE for 1c

**MS-15 MINISCOPE** \$289

With Rechargeable Batteries & Charger Unit

15 megahertz bandwidth.  
 External and internal trigger.  
 Time base - 1 microsec. to 100 sec.  
 Settings - 3.  
 Battery or line power.  
 Automatic sweep.  
 Power consumption - 10 watts.  
 Voltage range - 100V to 10V.  
 Frequency range - 10 Hz to 15 MHz.  
 Dimensions: 6.4" W x 7.5" D, 3 pounds.  
 Lifetime guaranteed 1 year.  
 Includes carrying case.

**MS-215 Dual Trace Version of MS-15 \$395.00**

**3 LEVEL GOLD WIRE WRAP SOCKETS**

	1-24	25-49	50-99	100-249	250-999	1K-5K
1/2 pin	41	38	35	31	23	17
1/4 pin	39	38	36	32	23	17
1/8 pin	42	39	35	30	23	17

18 pin \$3.50 54 44 37 30 23 17  
 20 pin \$4.00 54 44 37 30 23 17  
 25 pin \$5.00 70 44 37 30 23 17  
 28 pin \$6.00 85 80 70 44 37 30 23 17  
 32 pin \$7.00 90 85 80 70 44 37 30 23 17  
 36 pin \$8.00 94 78 68 68 58  
 40 pin \$9.00 100 90 84 75 71  
 44 pin \$10.00 140 80 84 75 71  
 48 pin \$11.00 140 80 84 75 71  
 52 pin \$12.00 140 80 84 75 71

SOCKETS PURCHASED IN MULTIPLES OF 50 PER TYPE MAY BE COMBINED FOR BETTER PRICES.

All sockets are 0.100" pitch, closed entry, end & side stackable. 2 level. Solder Tail on Profile. Tin Socket. 200 Plugs available. CALL FOR QUOTATION

**SALE S-100 BUS EDGE CONNECTORS SALE**

**S100-WWG 50/100 Cont. 125 ctrs. 3 LEVEL WIRE WRAP .025" sq. posts on 250 spaced rows. GOLD plated.**  
 1-4 5-9 10-24  
 \$4.00 \$3.75 \$3.50

**S100-WVN 50/100 Cont. 125 ctrs. 3 LEVEL WIRE WRAP .025" sq. posts on 250 spaced rows. NASGLO tin-nickel plated.**  
 1-4 5-9 10-24  
 \$3.50 \$3.25 \$3.00

**S100-STG 50/100 Cont. 125 ctrs. DIP SOLDER TAIL on 250 spaced rows for VECTOR and IMASI motherboards GOLD plated.**  
 1-4 5-9 10-24  
 \$4.00 \$3.75 \$3.50

**S100-STN 50/100 Cont. 125 ctrs. DIP SOLDER-TAIL on 250 spaced rows for VECTOR and IMASI motherboards NASGLO tin-nickel plated.**  
 1-4 5-9 10-24  
 \$3.50 \$3.25 \$3.00

**RGB1G 50/100 Cont. 125 ctrs. DIP SOLDER TAIL on 140 spaced rows for ALTAIR motherboards GOLD plated.**  
 \$5.00

**R681-3 50/100 Cont. 125 ctrs. PIERCED SOLDER EYELET tails. GOLD \$7.35**

**Other Popular Edge Connectors**

**R644 G 22/44 Cont. 156 ctrs. PIERCED SOLDER EYELET tails. GOLD plated.**  
 1-4 5-9 10-24  
 \$3.00 \$2.75 \$2.50

**R644-3 22/44 Cont. 156 ctrs. WIRE WRAP tails. GOLD \$4.71**

ATTN: OEM'S and Dealers, many other connectors available call or quotation.

**8803 MOTHER BOARD FOR S100 BUS MICRO-COMPUTERS**

Kit includes 12 1/2" x 10" cabinet for +5, +12, -12 buses and 150 spaced mounting spacers.  
 Wiring side shown. Component side bare epoxy glass with white markings for component locations.  
 10 epoxy glass board with 2 ounce copper solder plated and 038 diameter holes for leads.  
 Solder mask with solder windows on critical circuits to avoid accidental short circuits.  
 Mounts 11 receptacles with 100 contacts (2 rows) on 125 centers with 250 mil spacing.  
 Vector part number 8803-2, or mounts 10 receptacles plus interconnections to smaller mother board for expansion.  
 Includes etched circuits and resistors for option of active, pull-up, or floating terminations.  
 Large buses: +5V and GND (10 AMP), ±12V or 15V (1 AMP). Current ratings are per MIL-STD-275 with 100% rise.  
 Fits in Vector rack enclosures.  
 Fits in NASGLO 8800 microcomputer as expansion board.

**Price: \$29.50**

**Vector Plugboards**

**8800V**  
 Universal Microcomputer/processor plugboard, use with S-100 bus. Complete with heat sink & hardware. 5" x 10" x 1/16"

1-4	5-9	10-24
\$19.95	\$17.95	\$15.95

Same as 8800V except plain, less power buses & heat sink.

1-4	5-9	10-24
\$14.95	\$13.46	\$11.96

**8801-1**

Hi-Density Dual-In-Line Plugboard for Wire Wrap with Power & Grd. Bus Epoxy Glass 1/16" 44 pin con. spaced .156

1-4	5-9	10-24
\$36.82	\$31.97	\$29.81

**3677 9.6" x 4.5"**  
 \$10.90

**3677-2 6.5" x 4.5"**  
 \$9.74

**3682 9.6" x 4.5"**  
 \$10.97

**3682-2 6.5" x 4.5"**  
 \$9.81

**3662 6.5" x 4.5"**  
 \$7.65

**3662-2 9.6" x 4.5"**  
 \$11.45

**3690-12 CARD EXTENDER**  
 Card Extender has 100 contacts-50 per side on .125 centers-Attached connector-is compatible with S-100 Bus Systems..... \$25.00  
 3690 6.5" 22/44 pin .158 ctrs. Extenders..... \$12.00

Gen. Purpose D.I.P. Boards with Bus Pattern for Solder or Wire Wrap. Epoxy Glass 1/16" 44 pin con. spaced .156

P pattern plugboards for IC's Epoxy Glass 1/16" 44 pin con. spaced .156

**1/16" Vector BOARD**  
 .042 dia holes on 0.1 spacing for IC's

Phenolic

PART NO.	SIZE	1 - 9	10 - 19
64P44XXX	4.5x6.5"	\$1.49	1.34
169P44XXX	4.5x17"	\$3.51	3.16

Epoxy Glass

PART NO.	SIZE	\$1.70	1.53
64P44	4.5x6.5"	\$2.10	1.89
169P44	4.5x17"	\$4.30	3.87
169P84	8.5x17"	\$7.65	6.89

**ELIT-WRAP**

Wrap insulated wire on .025" square posts  
**FOUR TIMES FASTER**  
 (vs. regular manual wire-wrap tools)

**P180**  
 with two 100' spools of 28 ga. wire  
**\$24.50**

**P180-4T**  
 includes charger, wire  
**\$75.00**

**SLIT-N-WRAP WIRE**  
 NO 28 GAUGE INSULATED WIRE, 100' SPOOLS

W28-2: 28 Pgs. 3. Green W28-2: 28 Pgs. 3. Clear W28-2: 28 Pgs. 3. Red W28-2: 28 Pgs. 3. Blue

**2708 8K 450 ns**

**EPROM FACTORY PRIME \$10.00 EA.**  
 25 + Call For Price

**14 & 16 PIN GOLD 3 LEVEL WIRE WRAP SOCKETS**

14 - G3 100 for \$30.00  
 16-G3 100 for \$30.00  
 50 of each for \$32.00

Sockets are End & Side stackable, closed entry.

**LIQUID CRYSTAL DIGITAL CLOCK-CALENDAR**

For Auto, Home, Office  
 Small in size (2x2 1/2 x 1 1/2)  
 Push button for seconds release for date.  
 Locks month anywhere with either 3M double-tape or VELCRO included.

**MODELS AVAILABLE:**  
 CD-101, portable model runs on self-contained batteries for better than a year.  
 CD-102, runs on 12 Volt system and is back-lighted.  
 CD-101 or LCD-102 your choice.

**\$34.95**  
 Clear case stand for \$2.00

**LEDU 10A 151 \$72. SPECIAL**

Perfectly balanced, fluorescent lighting with precision magnifier lens. For print, technical & hobbyist. Has on cast protective shade. Int. 3 diode lenses. 42" reach.

**\$44.95**

with 19" high/adjust lamp insured \$45.35  
 color: Gray or Black  
 Choke: 2000 or 2500

**SC-5 With Rechargeable Batteries & Charger Unit \$195**

Features include: • By using the new NLS SC-5 Prescaler, the range of the FM-7 Frequency Meter, which is 10 Hz to 50 MHz, may be extended to 512 MHz (the upper VHF & UHF frequency bands). • The FM-7 utilizes an LED readout, providing 7-digit resolution. • The FM-7 can be calibrated to an accuracy of 0.0001%. • The SC-5 is accurate to one part per million. • Each unit has 30 millivolts sensitivity, is battery powered and has a charger unit included. • Dimensions of each are 1.9" H x 2.7" W x 3.9" D. • The units may be obtained separately or as a "Frequency Duo." • Parts & Labor guaranteed 1 year.  
 Tilt stand option ..... \$ 3.50  
 Leather case ..... \$18.00

**MICRO-KLIP**  
 for .042 dia. holes (all boards on this page)  
 T42-1 pkg. 100 \$ 1.50  
 T42-1 pkg. 1000 \$ 11.00  
 P-149 hand installing tool \$ 2.03

**8" LED ALARM CLOCK**

12 hr. LED Alarm Clock uses 3 1/2" digit 8" LED Display with AM/PM indicators and colors. Direct drive. PIN to PIN interface with **87996A** I.C. Just add switches, AC Supply, Alarm. Display and I.C. only.

**\$7.95 or 2/\$15.00**

**Price Breakthrough! \$17.50**

**MA1003 CAR CLOCK**

Bright Green Fluorescent Display Crystal Time Base Assembled, just add switches and 12 VDC.

**SPECIAL**  
 14CS2 100 for \$14.00  
 16CS2 100 for \$16.00  
 14 pin CS2 100 for \$21.00  
 16 pin CS2 8 for \$21.00

These low cost DIP sockets will accept both standard width plugs and chips.  
 For use with chips, the sockets offer a low profile height of only .125" above the board. These sockets are end stackable.

**Vector WRAP POST**  
 .042 dia. holes (boards on this page)  
 1/2" pkg. 100 \$ 2.28  
 1/2" pkg. 1000 \$ 14.00  
 P-149 hand installing tool \$ 2.80

**PRIORITY ONE ELECTRONICS**

4911R West Rosecrans, Hawthorne, CA 90250

Terms: VISA, MC, BAC, check, Money Order, C.O.D., U.S. Funds Only. CA residents add 6% sales tax. Minimum order \$10.00. Orders less than \$75.00 include 10% shipping and handling, excess refunded. Just in case please include your phone no. "Sorry, no over the counter sales"

Prices subject to change without notice.

Send for our latest brochure. phone orders welcome (213) 973-4876 OEM and Institutional Inquiries Invited.

**24 PIN DIP PLUGS WITH COVERS**  
 3 / \$1.00  
 40 / \$10.00

# FREE PROBES FREE PROBES FREE PROBES


# ELECTRONIC SUPERMARKET

Phone Orders:  
(617) 532-2323  
BA, MC or AE

P.O. Box 619 Dept. R-8 Lynnfield, Massachusetts 01940
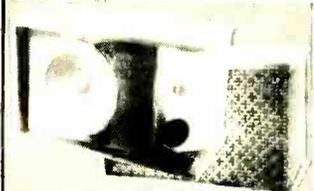
## SPEAKER KITS


These unique systems were designed for direct dispersion of the high frequencies and wide dispersion of the low tones. Cabinet measures 17 x 10 1/2 x 9 1/2 deep. Kit includes: 2-cabinets; 2-8" woofers; 2-4" dome tweeters; crossovers; grill cloth & instructions. Assembled systems deliver freq. resp of 30 to 20,000 Hz. Buy the complete kit or just the cabinets!  
COMPLETE KIT - Order No. 7ZU70242 Sh. Wt. 35 Lbs. .... \$49.50/pair  
CABINETS Only ..... 70B70200 Sh. Wt. 25 Lbs. .... \$25.00/pair



- 12" DIAGONAL
- NEW CRT INSTALLED
- RECONDITIONED
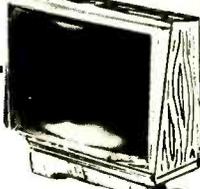
## Video Monitor

Used checked-out monitors outfitted with brand new 12" CRT. Solid state monitors will display 80 characters x 16 lines. Std. comp. video signal input, SO-239 connector. 115VAC. Qty. Ltd. Great for your CCTV or Micro Computer!  
Sh. Wt. 40 Lbs. .... 8A30200 ..... \$98.88 each



**SPECIAL INTRODUCTORY OFFER - TRY US OUT!**  
TAKE 10% OFF ANY ORDER OVER \$10.00!

## VIDEO GAME PARTS

A complete video game except the TV interface. Includes: 2 joystick controls; 12V @ 200ma xformer; two 7-segment 0.5" LED displays; LS and CD CMOS chips; 555 timers; 2' 8 ohm speaker; 3-lead 12V regulator; large control panel & case, & more! Wt. 5 Lbs.  
#8GV80028 ..... \$7.88

## PAY PHONES Touch-Tone®

Reconditioned touch-tone® pay telephone. Complete, in beige or black - state choice. Quantity is limited. What a conversation piece! Wt. 45 Lbs.  
#8C30273 ..... \$69.88 each

"AA" NICADS - "8-pack"  
10V @ 500 mA, or as single cells. 8 oz.  
8V20305 ..... \$8.00/pack

Pay phones, speakers, parts? There's much more in our **FREE CATALOG!** Circle us on the free information card!

Terms: Add postage. No C.O.D.'s. Phone Orders BA-MC-AE: (617) 532-2323.

CIRCLE 73 ON FREE INFORMATION CARD

1 out of 2 who have it don't know it...

Do you?

21 million Americans have high blood pressure. But 50 percent of those who have it, don't know it. When blood pressure goes higher than it should, and stays high, it sets the stage for heart attack or stroke. Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association




## ENGINEERS, SCIENTISTS, HOBBYISTS, GADGETEERS:

"This Month" catalog is published 7 times a year. Each 32 page issue is updated and filled with hundreds of unique, hard-to-find special buys of industrial-electronic, scientific, CCTV, optical and electro-mechanical products.

Our 44th year!

Free Catalog

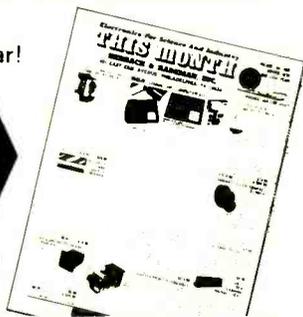Reduced facsimile of one of our 8 1/2" x 11" catalogues



**HERBACH & RADEMAN, INC.**  
401 East Erie Avenue  
Philadelphia, Penna. 19134

PHONE (215) 426-1700

NAME \_\_\_\_\_  
COMPANY \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY, STATE, ZIP \_\_\_\_\_  
 HOME  BUSINESS

## ONE OF OUR UNIQUE PRODUCTS

HIGH TORQUE REVERSIBLE 6 OR 12V. PM FIELD MOTOR \$9.95

This beautiful, chrome finished, high efficiency field motor was originally designed as a "pedal assist" drive motor for bicycles. It will find many applications in mechanical drives where high starting torque is needed. Can also serve as a low power DC generator.



SPECIFY CAT. NO. 21K139 6/\$54.00 12/\$96.00

CIRCLE 79 ON FREE INFORMATION CARD

## UNIVERSAL 4Kx8 MEMORY BOARD KIT

\$69.95  
32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin bus, may be used with F-8 & KIM

## EXPANDABLE F8 CPU BOARD KIT

\$99.00  
featuring Fairbug PSU, 1K of static ram, RS 232 interface, documentation, 64 BYTE regs. er

## C/MOS (DIODE CLAMPED)

4001	18	4016	29	4027	37	4053	1	10
4002	18	4017	90	4028	80	4055	1	25
4006	95	4018	90	4029	95	4066	7	0
4007	18	4019	37	4030	33	4071	18	18
4009	37	4020	90	4035	97	4076	97	97
4010	37	4021	90	4042	65	4510	22	22
4011	18	4022	90	4046	135	74010	92	92
4012	18	4023	18	4047	150	74193	95	95
4013	29	4024	95	4048	34	34	34	34
4015	74	4025	18	4050	34	34	34	34

2708 BK EPROM (450 m)	\$ 7.75
2532 STATIC SHIFT REG	\$ 1.95
2513 CHARACTER GEN	\$ 6.75
2518 HEX 32 BIT SR	\$ 2.20
2102-1 (1480n)	\$ .99
2102-1 (1480n)	\$ 1.25
MM5270 4Kx1 DYN	\$ 3.45
MK 4008P	\$ 1.95
2101-1-25K x 4 STATIC	\$ 5.50
2111-1-25K x 4 STATIC	\$ 3.45
2112-1-25K x 4 STATIC	\$ 2.75
2114-4K STATIC RAM (450n)	\$ 8.50
5280/2107 8K DYNAMIC RAM	\$ 4.25
2504 400L	\$ 3.95
5204 4K PROM	\$ 4.95
82523	\$ 1.95
AY-5103 UART	\$ 4.95
8703C TELETYPE 3 STAGE	\$ 13.50
BINARY 8 BIT A/D CONVERTER	\$ 9.50
8080A	\$ 9.50

AP BOARDS USED FOR SOLDERLESS BREADBOARDING

264L - 128 FIVE-TIE POINT TERMINALS	\$12.50
212R - POWER BOARD	\$ 2.50
2248L - 96 FIVE-TIE POINT TERMINALS	\$10.00
209R - POWER BOARD	\$ 2.25

IC TEST CLIPS  
TC-14 - \$4.50 TC-16 - \$4.75

CTS 206-8 eight position dip switch	\$1.60
CFS 206-4 four position dip switch	\$1.45
LIGHT ACTIVATED SCR'S TO-18, 200V 1A	\$ 1.10

SILICON SOLAR CELLS  
2 1/2" diameter .4V at 500 mA \$4.00

FND 359 C.C. 4" x 50	LED READOUTS
FCS 8024 4 digit	DL-704 C.A. 3" x 75
C.C. 8" display	\$5.95 DL-747 C.A. 6" x 11.25
FND 503 C.C. 5" x 85	FND 800 C.C. 8" x 11.95
FND 510 C.A. 5" x 85	FND 807 C.A. 8" x 11.95
DL-704-3" C.C. x 75	

## PRINTED CIRCUIT BOARD

4 1/2" x 6 1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched \$60 ea 5/52 60

## 7 WATT LD-65 LASER DIODE IR \$8.95

2N 3820 P FET	\$ 45
2N 5457 N FET	\$ 45
2N2646 UJT	\$ 45
ER 900 TRIGGER DIODES	4 \$1.00
2N 6028 PROG UJT	\$ 65

MINIATURE MULTI-TURN TRIM POTS 100, 1K, 2K, 5K, 10K, 25K, 50K, 100K, 200K, 500K, 1Meg, 2Meg, \$75 each 3/52.00

## CHARGED COUPLE DEVICES

CCD 321 AH2-512 audio analog S.R. .... \$95.00  
CCD 201C 100x100 Image Sensor ..... \$95.00  
CCD 202C 100x100 Image Sensor ..... \$145.00

## VERIFAX PC BOARD

\$4.00  
This board is a 1/16" single sided paper epoxy board, 4 1/2" x 6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8,16 or LSI DIP IC's with buses for power supply connector.

## FP 100 PHOTO TRANS

RED, YELLOW, GREEN or AMBER	\$ 50
LARGE LED'S 2V	\$ 6/51.00
TL-118 OPTO-ISOLATOR	\$ 75
MOLEX PINS	100/\$1.00
	1000/\$8.00

## 10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12.2, 100, 150 or 200V

1 WATT ZENERS - 3.3, 4.7, 5.6, 9.1, 10, 12, 15, 18, or 22V \$7.51.00

## MC6860 MODEM CHIP

\$9.95

## MCM 6571A 7 x 9 character gen.

\$10.75

## Silicon Power Rectifiers

PRV 1A	3A	12A	50A	125A	240A
100 06 14	30	80	370	700	5.00
200 07 20	35	1.15	4.25	6.50	
400 09 25	50	1.40	6.50	9.50	
600 11 30	70	1.80	8.50	12.50	
800 15 35	90	2.30	10.50	16.00	
1000 20 45	110	2.75	12.50	20.00	

## SAD 1024 "REDUCED 1024 stage analog" "Bucket Brigade" shift register.

\$18.95

(N 4148 (N 914) 15/\$1.50

## REGULATORS

309K	\$ .95	340K-12.15	
723	\$ .50	or 24V	\$ .95
LM 376	\$ .60	340T 5, 6, 8, 12	
320K-5.1	\$ 1.00	15, 18 or 24V	\$ .95
or 15V		78 MG	\$1.35
320T-5.1	\$ .95	79 MG	\$1.35
or 24V			

## TRANSISTOR SPECIALS

2N6233-NPN SWITCHING POWER	\$ 1.95
MRF-8004-CBF RF Transistor NPN	\$ 1.50
2N3772 NPN Si TO-18	\$ .75
2N1546 PNP GE TO-3	\$ .75
2N4908 PNP Si TO-3	\$ 1.00
2N5086 NPN Si TO-3 Darlington	\$ 1.70
2N5086 PNP Si TO-92	4 \$ 1.00
2N3137 NPN Si RF	\$ .85
2N3919 NPN Si TO-3 RF	\$ 1.50
2N1420 NPN Si TO-18	3/\$ 1.00
2N3767 NPN Si TO-66	\$ .70
2N2222 NPN Si TO-18	5/\$ 1.00
2N3055 NPN Si TO-3	\$ .50
2N3904 NPN Si TO-92	5/\$ 1.00
2N3906 PNP Si TO-92	5/\$ 1.00
2N5296 NPN Si TO-220	\$ .50
2N6109 PNP Si TO-220	\$ .55
2N3638 PNP Si TO-5	5/\$ 1.00
MPSA 13 NPN SIL	4/\$ 1.00

## TTL IC SERIES

7400-13	7445-65	74151-61
7401-13	7446-68	74153-61
7402-13	7447-58	74154-94
7403-13	7448-68	74155-94
7404-15	7450-15	74157-55
7405-13	7472-25	74161-55
7406-16	7473-28	74163-55
7407-20	7474-28	74164-85
7408-18	7476-45	74165-95
7409-18	7476-30	74170-168
7410-13	7480-31	74173-120
7411-18	7483-65	74174-95
7412-13	7485-87	74175-85
7413-19	7486-65	74176-75
7414-60	7490-42	74177-75
7416-22	7491-58	74180-65
7417-15	7492-43	74181-190
7420-13	7493-43	74190-100
7425-25	7494-67	74191-100
7426-22	7495-65	74192-79
7427-19	7496-65	74193-79
7430-13	74107-28	74194-80
7432-22	74121-29	75325-150
7437-21	74122-38	74196-86
7438-21	74123-45	74219-35
7440-13	74125-40	74367-65
7441-70	74126-40	75491-50
7442-37	74150-94	75492-50

## DATA CASSETTES

\$ .95

## 44 Pin Solder Tail .156" Connector

\$1.95

MM 5387AA new clock chip which will directly drive LEO's 12/24 hrs., 1 supply & alarm \$5.95

## NO. 30 WIRE WRAP WIRE SINGLE STRAND

100' \$1.40

## ALCO MINIATURE TOGGLE SWITCHES

MTA 106 SPDT \$ .95

MTA 206 DPDT \$ 1.70

MSD 206 P.DPDT CENTER OFF \$ 1.85

LEVER SWITCH \$ 1.85

## Full Wave Bridges

PRV	2A	6A	25A
100	1.50	1.25	2.00
200	.75	1.50	3.00
400	.35	1.50	4.00
600	1.20	1.75	4.00

## DIP SOCKETS

8 PIN	17	24 PIN	.35
14 PIN	20	28 PIN	.40
16 PIN	22	40 PIN	.60
18 PIN	25		

## SANKEN AUDIO POWER AMPS

5i 1010 G 10 WATTS	\$ 7.80
5i 1020 G 20 WATTS	\$15.70
5i 1050 G 50 WATTS	\$28.50

## TANTALUM CAPACITORS


22UF 35V 5 S1 00	68UF 35V 4 S1 00
47UF 35V 5 S1 00	100UF 10V \$ .25
68UF 35V 5 S1 00	22UF 25V \$ .40
1UF 35V 5 S1 00	15UF 35V 3/\$1.00
2.2UF 20V5 S1 00	30UF 6V 5/\$1.00
3.3UF 35V 4 S1 00	47UF 20V \$ .35
4.7UF 15V 5 S1 00	68UF 15V \$ .50

## 74LS SERIES

74LS00	20	74LS132	70
74LS01	21	74LS138	70
74LS02	21	74LS139	70
74LS04	23	74LS151	85
74LS05	24	74LS153	85
74LS08	24	74LS155	85
74LS09	23	74LS156	82
74LS10	20	74LS157	62
74LS11	20	74LS158	62
74LS12	20	74LS160	80
74LS13	40	74LS161	80
74LS14	80	74LS162	80
74LS15	25	74LS163	80
74LS20	22	74LS166	80
74LS21	22	74LS169	80
74LS22	22	74LS170	150
74LS24	30	74LS173	100
74LS27	35	74LS174	75
74LS28	37	74LS175	75
74LS30	37	74LS181	200
74LS32	32	74LS190	90
74LS33	30	74LS191	90
74LS34	35	74LS192	90
74LS40	25	74LS193	90
74LS41	35	74LS195	90
74LS42	35	74LS196	75
74LS43	25	74LS197	100
74LS45	25	74LS198	100
74LS47	35	74LS250	70
74LS49	35	74LS251	70
74LS50			

# 600 MHZ. FREQUENCY COUNTER ±0.1 PPM TCXO

## OPTO-8000.1

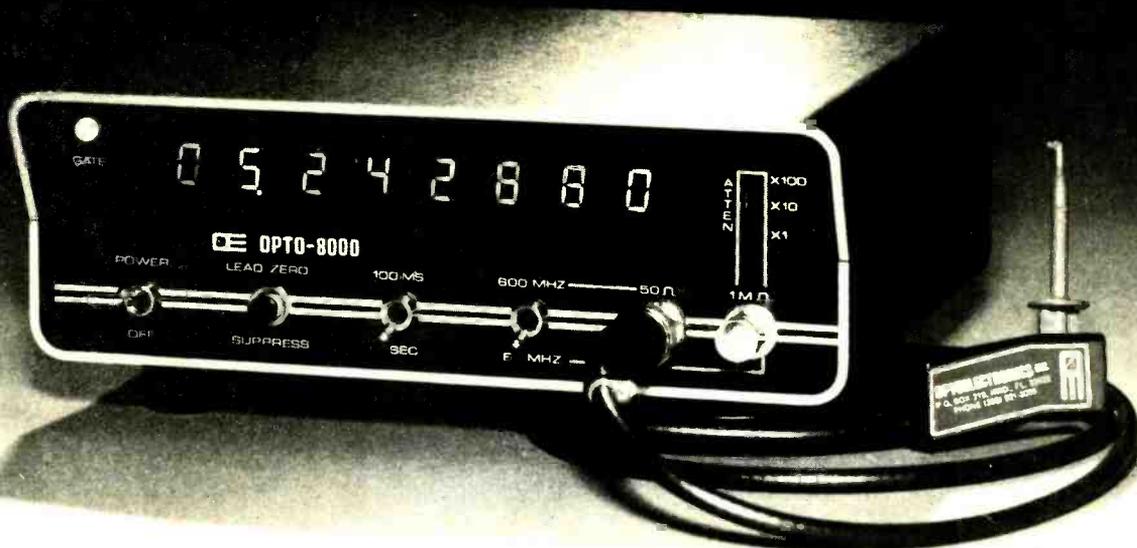

This new instrument has taken a giant step in front of the multitude of counters now available. The Opto-8000.1 boasts a combination of features and specifications not found in units costing several times its price. Accuracy of  $\pm 0.1$  PPM or better — *Guaranteed* — with a factory-adjusted, sealed TCXO (Temperature Compensated Xtal Oscillator). **Even kits require no adjustment for guaranteed accuracy!** Built-in, selectable-step attenuator, rugged and attractive, black anodized aluminum case (.090" thick aluminum) with tilt bail. 50 Ohm and 1 Megohm inputs, both with amplifier circuits for super sensitivity and both diode/overload protected. Front panel includes "Lead Zero Blanking Control" and a gate period indicator LED. AC and DC power cords with plugs included.

#### SPECIFICATIONS:

Time Base—TCXO  $\pm 0.1$  PPM GUARANTEED!  
 Frequency Range—10 Hz to 600 MHz  
 Resolution—1 Hz to 60 MHz; 10 Hz to 600 MHz  
 Decimal Point—Automatic  
 All IC's socketed (kits and factory-wired)  
 Display—8 digit LED  
 Gate Times—1 second and 1/10 second  
 Selectable Input Attenuation—X1, X10, X100  
 Input Connectors Type —BNC  
 Approximate Size—3" h x 7½" w x 6½" d  
 Approximate Weight—2½ pounds  
 Cabinet—black anodized aluminum (.090" thickness)  
 Input Power—9-15 VDC, 115 VAC 50/60 Hz  
 or internal batteries  
 OPTO-8000.1 Factory Wired **\$299.95**  
 OPTO-8000.1K Kit **\$249.95**

#### ACCESSORIES:

Battery-Pack Option—Internal Ni-Cad Batteries and charging unit **\$19.95**  
 Probes: P-100—DC Probe, may also be used with scope **\$13.95**  
 P-101—LO-Pass Probe, very useful at audio frequencies **\$16.95**  
 P-102—High Impedance Probe, ideal general purpose usage **\$16.95**  
 VHF RF Pick-Up Antenna-Rubber Duck w/BNC #Duck-4H **\$12.50**  
 Right Angle BNC adapter #RA-BNC **\$ 2.95**

#### FC-50 — Opto-8000 Conversion Kits:

Owners of FC-50 counters with #PSL-650 Prescaler can use this kit to convert their units to the Opto-8000 style case, including most of the features.

FC-50 — Opto-8000	<b>Kit \$59.95</b>
*FC-50 — Opto-8000F	<b>Factory Update \$99.95</b>
FC-50 — Opto-8000.1 (w/TCXO)	<b>Kit \$109.95</b>
*FC-50 — Opto-8000.1F	<b>Factory Update \$149.95</b>

\*Units returned for factory update must be completely assembled and operational

**TERMS:** Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: \$1.00. Personal checks must clear before merchandise is shipped.



### OPTOELECTRONICS, INC.

5821 NE 14 Avenue  
 Ft. Lauderdale, FL 33334  
 Phones: (305) 771-2050 771-2051  
 Phone orders accepted 6 days, until 7 p.m.



CIRCLE 16 ON FREE INFORMATION CARD

**NO-ETCH**  
Duplicate or make additions to modifications of Any Etched Board. Ideal for point-to-point or wire wrap breadboards. Complete set of (3) tools IP6003 \$25.00 ppd. A.F. Stahler Co., P.O. Box 354R, Cupertino, CA 95014 - (408) 252-4219.



## FREE KIT Catalog

STOP! Take a minute & let us send our latest kit catalog. If you like, send us the name & address of a friend who may also be interested and we'll include to you our booklet "How to build electronic thermometer".

contains TEST & EXPERIMENTER'S EQUIP.

**DAGE** SCIENTIFIC INSTRUMENTS  
BOX 1054R LIVERMORE CA 94550

## NEW! 1978 MICROCOMPUTER CATALOG

Giant, information-packed catalog lists 1,000's of mini-micro computer products, plus books & periodicals for professionals & beginners alike.

**NCE/Compumart**


Dept REA Box 8610 Ann Arbor, Mi 48107

**FREE**  
Norm. \$1.00

**PICTURE TUBE MACHINE**  
We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFR.

For complete details send name, address, zip to:

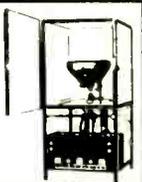**LAKESIDE INDUSTRIES**  
3520 W. Fullerton Ave.  
Chicago, Ill. 60647  
Phone: 312-342-3399



## AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices. Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog \$1. Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.

**B&K** test equipment. Free catalog. Free shipping. Dinosaur discounts. **SPACETRON-DH**, 948 Prospect, Elmhurst, IL 60126

**BLITZ ZOINK ZATT: UNSCRAMBLE** these fascinating police communications with our **CODE-BREAKER** and keep informed. Tunes all scramble frequencies. works with all scanners, and is factory built and guaranteed.

**\$34.95PP. UNSCRAMBLER KIT:** Latest Technology, 2 1/2 X 2 1/2 X 1/2 inch. complete instructions, only \$19.95PP. Thousands of satisfied customers. Catalog 50¢. Order from **KRYSTAL KITS**, BOX 445, BENTONVILLE, ARK. 72712. COD orders. 501-273-5340.



**SELLING** rider manuals, single volumes, sets, older Sams' Photofacts, Supreme. **Beitman**, Box 46, Highland Park, IL 60035

## NOTICE: RECORD RATERS WANTED

(No experience required) Each month you will receive nationally released albums to rate. **THERE IS NO EXTRA CHARGE** for the LP's you receive. You pay a small membership fee which covers all costs of the LP's. We pay postage. In return for your opinion, build your LP collection "First come basis". For application write: **EARS, DEPT RX** Box 10245, 5521 Center St., Milwaukee, WI 53210.

© 1975

**NAME** brand test equipment. Up to 50% discount. Free catalog and price list. **SALEN ELECTRONICS**, P.O. Box 82, Skokie, IL 60076

# Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS... New BARGAINS!  
**FREE UPON REQUEST!** Send today for FREE copy of NEW CATALOG WS-78. Address: Dept. RE

**FAIR RADIO SALES**  
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

**TAPE** head cleaner. 8 oz. — \$2.30. Includes postage and handling. Write: "CLEANER," Box 176, Whitewater, WI 53190. 800-558-9572 except WI

**COMPUTER**, peripheral, technical reports; project supplies; kits. Send \$1 for **THE CPU HOBBYIST**, Box 738-RE, College Park, MD 20740

## ATTENTION Audio Synthesis Experimenters

A FABULOUS FIRST: Motion Detector ICs. Converts motion to a voltage which triggers internal alarm circuitry. May be programmed for certain changes in light (motion). Includes on-chip musical sequence generator.

WHILE THEY LAST. MDC \$5.95

**PREMIUM OP AMP:** BB-3500 from BURR BROWN. Features: LOW NOISE, DRIFT, LOW INPUT BIAS. 15 kHz, 20V P-P output (1v/uS slew rate) and more. Regularly sells for up to \$36.00 each! EXCLUSIVE... only 99¢ ea. \$155.00

**SERIAL ANALOG DELAY:** 1024 stages, identical to SAD 1024A. \$16.95

**AUDIO SYNTHESIS LITERATURE:** "Tech Notes" featuring circuits, ideas, new products, parts sources, construction aids, calibration methods & more. Our own P. & D newsletter. Tech Notes. 12 issues \$17.50

**HYBRID ACTIVE FILTER:** Identical to the AF-100 ICA DIP Package. D.C. to 10 kHz, 4 on board op amps, state-variable filter. Simult. HP, BP, LP & notch outputs \$6.95 ea.

**SYNTHESIZER VCO module:** Sawtooth ± 15V, 10V P-P, 10Hz-10kHz sync in, trig out 1.5" square, 100" grid. \$24.50 ea.

**BIFET & BIMOS op amps:** TL071, LF351, CA3140. \$9c ea.

We have a lot of exciting bargains which aren't advertised, so write for our FREE FLYER TODAY!

(603) 382-5179  
**CFR ASSOCIATES**  
Box F  
Newton NH 03858

# B&K PRECISION OSCILLOSCOPES

## NEW 15MHz portable 3" dual-trace scope

- 15MHz bandwidth with smooth roll-off; usable response extends beyond 30MHz
- 2mV/div. vertical sensitivity
- Operates on 117VAC, 234 VAC, 12VDC or optional internal battery pack
- Fully regulated high- and low-voltage supplies
- Algebraic addition and subtraction of Channel A and B input signals
- Nineteen calibrated sweep ranges cover 0.5 microsecond to 0.5 second
- TTL Compatible Z-axis input
- Compact size; measures only 5.5 x 8.25 x 14.3"
- Includes two slim-body 10:1 direct probes and accessory tips
- Built-in sync separators



MODEL 1432



### Dual-Trace 5" -15MHz Triggered Sweep

- 24nSEC rise time permits display of high-speed square wave pulses
- Dual trace display • Individual vertical sensitivity and positioning controls • Large 8 x 10cm rectangular viewing area • Front-panel Vectorscope operation with matched-sensitivity inputs • 19 calibrated sweep ranges • Intensity modulation (Z-axis) input for time or frequency markers • Internal calibration source • 100% solid state (except CRT)
- Compact, lightweight and rugged
- Protective carrying case and accessory probes


Model 1472C-P



### 3" -5MHz Solid State Oscilloscope

- High sensitivity • CB modulation monitor • Ultra compact and lightweight (weighs only 8 1/2 lbs); goes anywhere
- Vertical sensitivity 10mV/division • New high brightness CRT and smoked-glass graticule • Can be externally triggered
- Protective carrying case and accessory probes.


Model 1403A-P

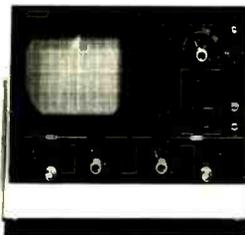

### Dual-Trace 5" -10MHz Triggered Sweep

- Usable deflection to 15MHz • 35nSEC rise time permits accurate display of high-speed square wave pulses • Large 8 x 10cm rectangular viewing area
- Front-panel Vectorscope operation with matched-sensitivity inputs
- TTL compatible intensity modulation (Z-axis) input for time or frequency markers and character displays
- Internal calibration source
- 100% solid state (except CRT)
- Compact, light-weight and rugged
- Protective carrying case and accessory probes

Model 1471B-P

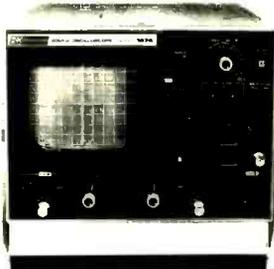

### Dual-Trace 5" -30 MHz Triggered Scope

- 11.7 nS rise time • 30 MHz dual trace operation • Internal signal delay line • 21 position sweep switch • Intensity modulation compatible for 5V p-p • Illuminated graticule • Internal 0.5 V p-p ± 1% calibration source • 100% solid state (except CRT)
- X-Y Vectorscope capability • High performance/cost ratio
- Protective carrying case and accessory probes

Model 1474-P

Before you buy, check our prices...

Call TOLL FREE (800) 645-9518

N.Y. State call (516) 752-0050

**FORDHAM**

YOUR ONE STOP DISCOUNT CENTER

Send for new 1978 catalog of over 3,000 items... 164 pages of test equipment, CB, tools, tubes, components and electronic supplies.

RADIO SUPPLY CO. INC  
855R Conklin St  
Farmingdale, N.Y. 11735

Mastercharge, BankAmericard, VISA and C.O.D.'s accepted

ADD \$3.00 TO COVER SHIPPING, HANDLING & INSURANCE N.Y. Res. add approx. sales tax.



more than  
20,000 different  
components

**RECTIFIERS**  
10 For For  
1N4001 .60 5.00  
1N4002 .70 6.00  
1N4003 .80 7.00  
1N4004 .90 8.00  
1N4005 1.00 9.00  
1N4006 1.10 10.00  
1N4007 1.20 11.00

**VOLT. REG**

LM340K-5	1.70
LM340K-6	1.70
LM340K-8	1.70
LM340K-12	1.70
LM340K-15	1.70
LM340K-18	1.70
LM340K-24	1.70
LM340T-5	1.50
LM340T-6	1.50
LM340T-8	1.50
LM340T-12	1.50
LM340T-15	1.50
LM340T-18	1.50
LM340T-24	1.50

**5400 SERIES**

5400	1.00
5404	1.25
5410	1.00
5426	1.25
5473	1.50
5475	1.50
5486	1.90
5493	2.00
54100	1.80
54LS04	1.00

**OEM SPECIALS**

1N34	.25	2N2905A	.30	2N3903	.16
1N60	.25	2N2906	.25	2N3904	.16
		2N2906A	.30	2N3905	.16
1N270	.25	2N2907	.25	2N3906	.16
1N914	.10	2N2907A	.30	2N3954A	3.75
2N173	.75	2N2913	.75	2N3955	2.45
2N404	1.75	2N2914	1.20	2N3957	1.25
2N173	1.75	2N3019	1.00	2N3958	1.20
2N443	2.50	2N3053	.30	2N4037	.60
2N508A	.45	2N3054	.70	2N4093	.85
2N718	.25	2N3055	.75	2N4124	.16
2N930	.25	2N3227	1.00	2N4126	.16
2N956	.30	2N3274	3.40	2N4141	.20
2N1302	1.25	2N3250	.50	2N4142	.20
2N1305	.75	2N3251	.50	2N4143	.20
2N1540	.90	2N3252	.50	2N4200A	.45
2N1544	.80	2N3253	.50	2N4234	.95
2N1560	2.80	2N3254	.17	2N4400	.16
2N1605	1.75	2N3414	.17	2N4401	.16
2N1613	.50	2N3416	.19	2N4402	.16
2N1711	.50	2N3417	.20	2N4403	.20
2N2102	.70	2N3442	1.85	2N4403	.20
2N2160	.70	2N3553	1.50	2N4409	.16
2N2218	.25	2N3563	.20	2N4410	.16
2N2218A	.30	2N3565	.20	2N4441	1.00
2N2219	.25	2N3638	.20	2N4442	1.15
2N2219A	.30	2N3642	.20	2N4443	1.35
2N2221	.25	2N3643	.20	2N4852	.55
2N2221A	.30	2N3645	.20	2N5061	.30
2N2222	.25	2N3646	.14	2N5064	.50
2N2222A	.30	2N3731	3.75	2N5130	.20
2N2270	.40	2N3740	1.00	2N5138	.15
2N2369	.25	2N3771	1.75	2N5296	.50
2N2484	.32	2N3772	1.90	2N5306	.20
2N2712	.18	2N3773	3.00	2N5400	.40
2N2904	.25	2N3819	.40	2N5401	.50
2N2904A	.30	2N3823	.70	2N5457	.35
2N2905	.25	2N3866	1.25	2N5458	.30

**7400 TTL**

7400	.18	7442	1.08	74107	.49
7401	.21	7448	1.15	74121	.55
7402	.21	7450	.26	74122	.49
7404	.24	7451	.27	74123	1.05
7405	.24	7453	.27	74125	.60
7407	.45	7454	.41	74126	.81
7408	.25	7460	.22	74132	3.00
7409	.25	7472	.39	74141	1.15
7410	.20	7473	.45	74150	1.10
7411	.30	7474	.45	74151	1.25
7413	.85	7475	.80	74153	1.35
7416	.43	7482	1.75	74154	1.54
7417	.43	7483	1.15	74157	1.30
7420	.21	7485	1.12	74161	1.45
7422	1.50	7486	.45	74164	1.65
7425	.43	7489	2.49	74165	1.65
7427	.37	7490	.69	74166	1.70
7428	.35	7491	1.20	74174	1.95
7430	.26	7492	.82	74175	1.95
7432	.31	7493	.82	74180	1.05
7437	.47	7494	.91	74181	3.55
7438	.40	7495	.91	74191	1.50
7440	.21	7496	.91	74195	1.00
7441	1.10	74100	1.25	74197	1.00

PARTIAL LISTING — WRITE FOR FREE CATALOG

CIRCLE 38 ON FREE INFORMATION CARD

**JAPANESE TRANSISTORS**

2SA484	2.44	2SC482	1.40	2SC1226A	.85	2SD170	1.50
2SA495	.60	2SC495	.85	2SC1237	4.00	2SD180	2.50
2SA497	1.44	2SC517	3.60	2SC1239	3.50	2SD188	2.70
2SA634	1.00	2SC634A	.60	2SC1306	3.50	2SD234	.85
2SA636	1.25	2SC710	.49	2SC1307	4.75	2SD235	.85
2SA673	.70	2SC711	.49	2SC1377	4.80	2SD313	1.05
2SA678	.65	2SC735	.48	2SC1383	.50	2SD314	1.50
2SA682	1.49	2SC756A	2.40	2SC1448	1.00	2SD315	1.20
2SA683	.60	2SC778	3.50	2SC1449	.85	2SD358	1.10
2SA699	1.30	2SC781	2.50	2SC1678	2.00	2SD360	1.05
2SA699A	1.45	2SC789	1.00	2SC1728	1.85	2SD427	2.55
2SA733	.49	2SC798	3.95	2SC1760	1.60	2SD525	1.50
2SA777	.99	2SC799	3.25	2SC1816	3.50	2SK19	1.25
2SB54	.49	2SC1000	.49	2SC1908	.49	2SK30A	.75
2SB56	.95	2SC1013	.95	2SC1909	3.75	2SK33	.90
2SB186	.49	2SC1014	.95	2SC1957	1.00	2SK55	1.00
2SB187	.55	2SC1017	1.20	2SC1973	.90		
2SB324	.60	2SC1018	1.00	2SC1975	3.50	3SK22Y	2.20
2SB370	65	2SC1061	1.25	2SC2028	3.80	3SK40	2.30
2SB405	.60	2SC1079	3.95	2SC2029	3.40	3SK45	2.20
2SB415	.65	2SC1096	.80	2SC2091	2.50	3SK49	2.20
2SB461	1.60	2SC1098	3.00	2SC2092	3.25		
2SB463	1.40	2SC1115	3.00				
2SB507	1.40	2SC1170B	4.95	2SD72	.80	4004	3.00
2SC371	.49	2SC1172	5.25	2SD77	1.50	4005	3.00
2SC372	.49	2SC1173	.75	2SD88	4.80	40081	1.50
2SC481	1.50	2SC1209	.75	2SD118	3.00	40082	3.00

**JAPANESE CIRCUITS**

AN136	2.90	LA4400FS	3.40	TA7055P	3.00	UPC20C	3.75
AN214	3.35	LA4400FR	3.40	TA7060P	1.40	UPC41C	2.80
AN239	6.50	LD3120	2.40	TA7061P	1.50	UPC563H2	8.00
AN241	2.40	M5115PR	7.80	TA7063P	1.50	UPC566H	1.25
AN315	3.50	PLLO1A	13.50	TA7075P	3.75	UPC575C	2.60
BA511	3.00	PLLO2A	8.50	TA7089P	2.90	UPC595C	2.90
BA521	3.40	PLLO2A-G	8.50	TA7120P	1.50	UPC1001H2	3.50
HA1202	2.20	SG613	6.75	TA7150P	3.75	UPC1008C	5.75
HA1306	4.90	STK011	7.50	TA7153P	6.90	UPC1020H	3.25
HA1308	4.50	STK015	6.50	TA7203P	4.25	UPC1025H	3.50
HA1322	4.20	STK032	14.20	TA7204P	3.70	UPC1168H	4.50
LA1201	4.25	STK050	24.50	TA7205P	3.60	UPD277C	4.50
LA4031P	3.20	STK066	11.35	UH1C003	6.50	UPD857C	15.50
LA4032P	4.20	STK415	8.50	UH1C004	6.50	UPD858C	9.50
LA4051P	3.20	TA7045M	3.25	UPC16C	2.50	UPD861C	18.50

**CHECK OUR NEW LOWER PRICES**



**NEW-TONE  
ELECTRONICS**

PO Box 1738A Bloomfield, N.J. 07003  
Phone (201) 748-6171, 6172, 6173

**FORDHAM BEST BUYS**

**BK PRECISION 3 1/2-Digit Portable DMM**  
• Overhead Protected • Battery or AC operation • 3" high LED Display • Auto Zeroing Model 2800  
comes complete with test leads, operating manual and spare fuse  
**\$85**

**EICO 3 1/2 Digit DMM Kit \$65.00**  
• Flashing Over-Range Indicator • Auto Polarity • Overload Protected  
Model 270 wired Reg. \$80.00

**Weller Xcelite Service Master Attache Style Tool Kit \$39.95**  
Model 995M  
**Tool Cases \$239.50**  
MODEL TC 100/ST Reg. \$283.00  
**Roll Kit \$13.95**  
Model 99PR

**WAHL NEW ISO-TIP "Quick Charge" \$27.95 \$26.95**  
12 units 3 or more  
• Model 7500 Cordless Soldering Iron \$17.95  
• Model 5800 Thermal Spot Circuit Tester \$22.50

**NLS 15 MHz Mini Oscilloscope \$246.50**  
Model MS-15  
• Battery or line operation  
• Automatic and line sync modes  
• Power consumption less than 15 W  
• Vertical Gain 0.01 to 50 volts/div 12 setting  
• External or internal trigger  
NOW AVAILABLE MS 215 Reg. \$395.00  
(Dual Trace Version of MS-15) \$349.95

**RCA Color Generator \$59.95**  
MODEL WR 508  
Reg. \$89.50

**ESQ QT Sockets & Bus Strips**

QT type	#holes	price
QT 595	590	12.50
QT 596	bus strip	2.50
QT 475	470	10.00
QT 478	bus strip	2.25
QT 355	350	8.50
QT 358	bus strip	2.00
QT 185	180	4.75
QT 125	120	3.35
QT 85	80	3.25
QT 75	70	3.00

**BSR Record Changer Accessories \$24.95**  
Model BSR-129

**ESQ Logic Probe \$40.00**  
Model LP-1  
• Compact, circuit powered  
• Multi-family compatibility DTL/TTL/HTL/CMOS  
• Detects pulses as short as 50 nsec

**LEADER Instruments Core 20 MHz. Dual Trace \$615.96**  
Model L 80-500  
• Add, subtract modes on CH 1 & CH 2  
• Front panel X-Y operation  
• 17.5 nsec rise time  
Reg. \$769.95  
with accessories

**Econo-Lamp \$14.95**  
Model XL-339A  
Coin's Red, yellow, blue, black, oyster white U.L. listed

**The Hobby Wrap Wire Wrapping Tool \$32.00**  
Model BW-630  
• Battery Operated (not included)  
• Wraps 30 AWG wire onto std DIP sockets (025")  
• Complete with built-in bit and sleeve

**Logic Monitor \$67.50**  
Model LM-1  
• Automatically displays static and dynamic logic • Works with DTL, HTL, TTL and CMOS • 16 LED display  
• Circuit powered design

**Transistor Tester \$22.00**  
Model 100  
• 9 volt battery included  
• Movable base pin conforms to TO-5, TO-18 and small "in-line" leads  
• Tests transistors in or out of circuit • Operates on contact  
• Clear speaker tone, no visual observations to make

**Magnifier LAMP \$42.50**  
Model MG 10A  
Precision ground and polished magnification lens. Uses 2W 19 Cooline fluorescent

**Call TOLL FREE (800) 645-9518**  
FREE 1978 Catalog  
Before you buy test equipment, any make or model, check our prices  
Master Charge • BankAmericard • C.D.S. accepted  
**FORDHAM**  
855 Conklin St. Farmingdale, N.Y. 11735  
New York State residents add approx sales tax  
Add \$3.00 for shipping and insurance (continental USA only)

**Voltage Spike Protector \$7.95**  
Model GESP-752  
Limits voltage transients that might damage equipment. Plugs into any 120 volt grounded AC

**Vector Complete line available**  
**520 MHz Frequency Counter \$382.50**  
Model 1850  
Reg. \$450.00

**20 K ohm/v VOM Multimeter \$17.95**  
S Reg. \$29.95  
with mirrored scale.

CIRCLE 75 ON FREE INFORMATION CARD

# BULLET ELECTRONICS

P. O. BOX 19442R Dallas, Texas  
(214) 823-3240 75219

## 8 GOOD REASONS TO BUY FROM BULLET:

1. We are an established company, in business since 1976.
2. Mail order is our only business. Full Time.
3. Components & un assembled kits may be returned for full refund.
4. Full retail service on any kit we sell.
5. Our customers are important. We are always available for help.

6. Quality Merchandise No Junk!
7. We sell it like it is! Parts are as described.
8. We try harder - We want your business from now on.

**THE SMALL PRINT**  
No COD's All orders add  
C.O.D.'s MO 5% for shipping  
MC/VISA & handling  
TX residence Orders over \$50  
add 5% Sales tax (10% discount  
for orders under \$25) address  
Orders under add 10% for  
handling

### MOBILE CLOCK CALENDAR KIT

Seems like everybody sells digital clock kits, however we have the only low cost DIGITAL CLOCK / CALENDAR for mobile operation. We provide quality printed circuit boards and step-by-step instructions, parts overlays and schematics. This clock has many features and we supply all the parts but a small resistor: Fantastic for car, boat or Van.  
• Integral Timebase (0.1% ACC)  
• 5 W x 2 1/2" LCD  
• Large 4 DIGIT LED display with AM/PM indicators  
• Flashing color at 1/2 Hz rate  
• Special noise and overvoltage protection for mobile use  
• Auxiliary output will drive relay or TRIAC to control external equipment

23.50 NO CASE  
12 VAC XFMR for 110 VAC  
1.50  
24 Hour format add  
2.00

### MG-01 ELECTRONIC GRANDFATHER CLOCK

While we are talking about clocks check out the MINI GRAND FATHER CLOCK Revisited in April 1978 RADIO ELECTRONICS. We have the only kit in the world with all the below listed features. The biggest problem is to describe how unique and fascinating this timepiece really is! The LED "Swinging" Pendulum and Matching Tick-Tock Sound are available only on our clock. In addition the electronic "bell" notes each hour (ie 3 times for 3 o'clock). Housed in the optional Solid Hardwood Case, the unit makes a beautiful addition to any room.  
• 1/2 4 DIGIT LED READOUT  
• Adjustable tone & duration on chime  
• Simulated swinging LED Pendulum  
• All CMOS Construction  
• Quality printed boards  
• All electronics switches + and XFMR included  
39.95 KIT 59.95 ASEMB

Optional Solid Hardwood Case for MG-01 Clock over 10 inches high. Great! Ruby SOLID WOOD 19.95

WE STOCK A COMPLETE LINE OF QUALITY LOW COST PANEL METERS. SEND FOR FREE CATALOG TODAY.

## ULTRASONIC SENDER RECEIVER KIT U02

**TOTAL SECURITY!** Completely invisible ultrasonic (23KHZ) sound beam works like a photoelectric beam but is unaffected by light, heat or noise. Separate Transmitter and Receiver can be used from 6 inches to 25 feet! A solid object breaking the beam causes an output to go low that will sink up to 150 MA to Drive a Relay, TRIAC, etc. Complete electronics are provided. Works on 12VDC (unregulated) and draws less than 100 MA. Useful for burglar alarms, object counters, automatic door openers, automatic door bells, electronic rat traps! and more.  
• Complete Kit LESS CASES 21.50  
• Control entry delay and Alarm Timeout Circuit 3.95 will source or sink up to 200 MA CC.

**10 WATT WARBLE ALARM KIT** 2.50  
It's hard to believe this little gem puts out 10 Watts of alternating dual tone screams. A real great attention getter. Great for alarms, games, toys, etc.  
with PC Board speaker not included  
Requires 12VDC @ 1A

**OTHER GREAT KITS!** We have 15A power supplies, C.D.I.'s, D.V.P.'s, mini mobile clocks, clock timers, sound circuits and many more. It's all in our latest catalog. FREE ON REQUEST

**PARTS** (many more listed in catalog)

MC1468R	5A positive Voltage Reg.	House	1.75
MC1351P	FM IF and Sound System	House	.50
CA3011	Wideband IF Amp IC	House	.50
MM5375	6 Digit Alarm Clock Chip		2.95
555	Timer & Pulse Gen Chip		.49
741	Op-amp 8 pin MINI DIP		.20
LM3900	QUAD OP AMP		.45
723	Pos Voltage Reg DIP		.65
725	Ultra low noise high gain Op amp	House	.99
NE565A	PLL DIP		.50
TCA430	Quad Audio Oscillator Dip		.69

MJ500, MJ1000	Matched Pair 8A Darlingtons	Pair/3.00
IN4148	Switching Diodes	25/1.00
2N3569	NPN Silicon Switching	6/1.00
2N2712	NPN Small Signal	8/1.00
2N4343	P Channel FET	4/1.00
2N6028	Programmable Unijunction	2/1.00
2N6111	PNP Med Power	3/1.00
	30W 10220	

**ZENER GRAB BAG:** A very nice assortment of 10 different voltage zeners between 2.7v and 30VDC in 400 MW, 5W and 1W. All are prime units but most have Mfg's numbers. We supply a cross reference sheet to standard numbers.  
SPECIAL PRICE 10 pieces 1.00

**CAPS**

922	100VDC Mylar	8/1.00
92	50VDC Mylar	6/1.00
15md	400VDC Mylar	4/1.00
1md	35V Tant Axial	6/1.00
47md	35V Tant Axial	6/1.00
2.2md	20V Dip Tant	4/1.00
22md	20V Dip Tant	4/1.00
33md	10V Dip Tant	4/1.00
220md	25V Alum. Axial	7/1.00
500md	35V Alum. Axial	5/1.00
1100md	35V Alum. Axial	4/1.00

**HEATSHRINK TUBING**  
A very good Assortment of 3/32", 1/8", 3/16", & 1/4" in 8 inch lengths 12 pieces total included.  
This item FREE with purchase of 15.00 or more

Miniature 7k pot w/switch PC Mount or panel mount 1/8" shaft	49
Black plastic knob for above	FREE
LIMITED QTY Computer Grade FILTER CAP	2 X 5's 9500 mfd@75V 2.95 or 4.9 95
SPECIAL SALE TIL 912 LED Common Anode 7 Segment Readout	3.00
Terminator Strip	2.95 or 4.9 95
3 Pin Socket	while they last 6/3.00

For faster service USE ZIP CODE on all mail

**LOWEST prices.** CPU's: 3001 \$14, 3002 \$9, 3003 \$10, 8035 \$21, 8035-8 \$16, 8080A 2μs \$7.85, 8080A-1 1.3μs \$11, 8080A-2 1.5μs \$8.95, 8085 1.3μs \$18, 8085A-2 .8μs \$29.95, 8748-4 2.5μs \$49.95, 8748-8 5μs \$45.95, PACE 16 bit \$38; PROM's: 2716 \$39.95, 3621-1 50ns \$5.95, 8755 EPROM \$65; RAM's: 1103A .95, 2114 \$11.15, 2115-2 45ns \$6, 2116 \$49, 2117-4 \$52, 2125A 45ns \$5.95, 3106A \$3.20, 5101L CMOS \$8; 8080/8085 Back up: 8155 \$17, 8156 \$18, 8251 \$10, 8253 \$22, 8255 \$8, 8257 \$15, 8259 \$16, 8275 \$75, 8279 \$17, 8741 \$72; Terms: Money order or certified check. California residents add 6% tax. **BYTE ELECTRONICS**, Box 8603-R, San Jose, CA 95155

## BUSINESS OPPORTUNITIES

**MECHANICALLY** inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

## HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-H, Box 248, Walnut Creek, CA 94597.**

## ULTRA MINI WIRELESS MICROPHONE

Amazing new model features both ultra-miniature size & a battery saving on-off switch. Picks up & transmits sounds without wires up to 300 ft. through any FM radio. Use as remote mike, intercom, baby sitter, alert/airmail syst, hot line etc. Great at parties. FCC appd. Compl. w. batt. Money back guar. Only \$19.95 + \$1.50 post-hd. Mass. Res. add tax. Order Today. M/C, COD ok  
**MLI INDUSTRIES, Dept. RE**  
50 HUNT ST., WATERTOWN, MASS. 02172



## DATA BOOK SALE

Through September 15th.

- AMB0203 8080A/9080A MOS Microprocessor Hand Book.** Detailed descriptions of the 8080A and associated CPU components. **\$4.95**
- AMB0205 MOS/LSI Data Book.** Static RAM's dynamic 4K RAM's, 2K EROM, shift registers, FIFO memories and complete microprocessor and support circuits. **\$3.95**
- AMB0206 Linear and Interface Data Book.** Comparators, data conversion products. Line drivers/receivers, MOS memory and microprocessor interface, Op Amps, Voltage Regulators etc. **\$4.95**
- FSB0104 Fairchild Bipolar Memory Data Book.** Bipolar memories, ECL static memories, TTL static memories, TTL dynamic memories and macrologic. **\$1.95**
- FSB0105 Macrologic Bipolar Microprocessor Data Book.** Microprogramming for implementing as many system functions as possible in one centralized logic block. **\$2.95**
- FSB0112 Fairchild Hybrid.** Custom and standard product as well as reliability and design considerations. **\$0.95**
- LCC4041 T.I. Power Semiconductor Data Book.** 816 pages germanium and silicon power transistors, SCR's, Triacs, darlington's, Silicon power high voltage and low voltage types etc. **\$5.95**
- UNB0400 Uniretro Semiconductor Data Book.** 500 pages on rectifiers, fullwave bridges, transient voltage suppressors, zeners, programmable unijunction transistors, etc. **\$3.95**
- SIB0304 Siliconix FET Data Book.** Complete data on selecting the right FET for your application, characteristics and PCB board layout. **\$2.50**
- SIB0305 VMOS Power FET's.** Technical information, application and design aids, characteristics and device I application selection for this latest in technology. **\$1.50**
- FSB0103 Fairchild Power Data Book.** Basic parameter and data information as well as information on technology, safe operating area, reliability etc. **\$1.95**
- SIB0303 Siliconix High Speed CMOS Analog Switches.** Complete data and applications **\$2.95**

## NEW TEXAS INSTRUMENTS DATA BOOKS NOW AVAILABLE

- LCC4162 TTL Supplement**  
The most recent TTL functions are included in this supplement to the 2nd edition of the TTL Data Book. **\$1.95**
- LCC4330 The Interface Circuits Data Book**  
Complete information including line drivers, receivers, memory drivers, sense amplifiers and peripheral drivers **\$4.75**
- LCC4350 The Voltage Regulator Handbook**  
Encompasses the total power supply design and aids in selection of regulator I.C.'s and associated components **\$2.50**
- LCC4380 The MOS Memory Data Book**  
Complete data, selection + interchangeability guide to Static and Dynamic RAM's, ROM's, EPROM's, CCD, Shift Registers + UART **\$2.50**

## The TTL Data Book

The brand new edition of the TTL data book (832 pages), provides the most complete, up to date information available, combining the contents of the popular first edition, and the 1974 TTL Supplement, plus data on 124 new circuits. The contents include: detailed specification on over 900 T.I. device types including standard TTL and high technology schottky clamped TTL. Pin assignment drawings of all TTL types including bipolar memories and microprocessors. Complete line of T.I. C. Sockets and interconnection panels. Stock No. LCC4112 **\$4.95**

## NEW DATA BOOKS Now available

- GSB0100 Zener, Transistor and Transzorb Catalogue.** Discrete devices and pertinent data and complete device characterization **\$3.95**
- RAB0606 Raytheon Selection Guide.** A full line condensed quick reference source on all Raytheon components **\$1.00**



P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over-the-counter sales.  
12 Mercer Rd., Natick, Mass. 01760  
Behind Zayres on Rte. 9  
Telephone Orders & Enquires (617) 879-0077

IN CANADA 3 LOCATIONS

5651 Ferrier St. 44 Fasken Dr., Unit 25  
Montreal, Quebec Rexdale, Ontario  
Tel. (514) 735-6425 Tel. (416) 675-3311

Baxter Centre  
1050 Baxter Road  
Ottawa, Ontario  
Tel. (613) 820-9471

MINIMUM ORDER \$10.00 • ADD \$2.00 TO COVER POSTAGE & HANDLING • Canadian customers add 30% for exchange and handling. All federal and provincial taxes extra.  
Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.

CIRCLE 77 ON FREE INFORMATION CARD

# SUMMER MADNESS SALE

## Active Electronic Sales Corp.

### TTL HIGH SPEED PLASTIC DUAL-IN-LINE I.C.'s

Stock level	Part No.	Price
46000	74H00	.16
1300	74H01	.16
11600	74H02	.16
8900	74H03	.16
51000	74H04	.17
9000	74H05	.17
1500	74H08	.22
17000	74H10	.16
4400	74H11	.22
1000	74H12	.16

Stock level	Part No.	Price
4000	74H15	.17
12000	74H20	.16
6000	74H22	.16
2000	74H30	.18
24000	74H40	.16
3000	74H50	.16
2000	74H51	.17
1000	74H52	.17
6000	74H53	.17
1000	74H54	.18

Stock level	Part No.	Price
2000	74H55	.18
3000	74H60	.18
2000	74H61	.18
2000	74H62	.18
2000	74H64	.16
6000	74H65	.16
1000	74H71	.35
2000	74H72	.31
2000	74H73	.49
24000	74H74	.24

Stock level	Part No.	Price
1200	74H76	.55
1000	74H78	.55
1500	74H87	2.75
1000	74H101	.35
1000	74H102	.35
1000	74H103	.50
2000	74H106	.45
1000	74H108	.49
3000	74H113	.24
2000	74H114	.24
1200	74H183	2.25


### TTL PLASTIC DUAL-IN-LINE I.C.'s

Stock level	Part No.	Price
36000	7400	.09
22000	7404	.09
6800	7423	.07
13000	7425	.12
43000	7437	.09
57000	7438	.09
22000	7443	.15
38000	7445	.19
23000	7454	.07
32000	7460	.07
41000	7472	.12

Stock level	Part No.	Price
15000	7480	.19
26000	7482	.15
56000	7491	.19
45000	74150	.39
69000	74151	.29
12000	74152	.89
90000	74153	.29
33000	74154	.49
2900	74155	.29
23000	74156	.19
42000	74157	.29

Stock level	Part No.	Price
41000	74162	.34
90000	74174	.39
21000	74175	.39
11000	74180	.34
13000	74181	.79
31000	74182	.29
30000	74190	.34
48000	74191	.34
16000	74194	.34
56000	74195	.29
8000	74199	.69
33000	74283	.49

### Dual In-line Sockets

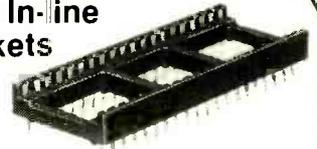

- PLUGGABLE SOCKET FOR IC PACKAGES WITH LEADS
- LOW COST - NO GOLD IS USED IN THE RECEPTACLE OR NEEDED ON THE LEADS
- HIGH RELIABILITY GAS-TIGHT JOINT FOR "GOOD AS GOLD" PERFORMANCE
- COMPACT - LOW PROFILE DESIGN
- NO WICKING WHEN SOLDERED TO PC BOARD
- FLAMMABILITY RATING - UL 94V-0

Stock level	Contacts	Price
185,000	8 PIN	.11
245,000	14 PIN	.13
190,000	16 PIN	.15
29,000	18 PIN	.19
80,500	22 PIN	.27
60,000	24 PIN	.28
30,000	28 PIN	.36
65,000	40 PIN	.48

### NEW 1978 CATALOGUE

Our new and expanded comprehensive 1978 catalogue (144 pages), listing complete descriptions, illustrations and monolithic pricing on over 10,000 items is available on request.

- Subject to prior sale
- Prices valid only till September 15th, 1978

• Standard 1978 catalogue prices on the above devices will once again take effect September 15th, 1978.

### MICROPROCESSOR CHIPS

#### CPU's

Stock level	Part No.	Price
7100	8080A	7.95
5500	6800	9.95

#### UV EPROM

Stock level	Part No.	Price
11900	2708	8.99

#### MOS STATIC RAM's

Stock level	Part No.	Price
13500	2114 4K 450NS	9.95
84600	2102LFPC 1K 350NS (Low power)	1.19

#### MOS DYNAMIC RAM's

Stock level	Part No.	Price
7200	4060/9060 4K 300NS	3.95
2800	416 16K 250NS	19.95

#### UART's

Stock level	Part No.	Price
16500	AY5-1013A	4.95
12300	AY3-1015	5.95

### INTERFACE SUPPORT CIRCUITS

Stock level	Part No.	Price
8300	8212	1.98
3500	8214	4.95
25200	8216	1.98
3300	8224	2.75
2400	8226	1.98
3100	8228	4.75
1400	8238	4.75
5700	8251	5.95
1100	8253	14.95
2700	8255	5.95
1000	8257	9.95
840	8259	14.95
4500	6810	3.95
8000	6820	4.95
9600	6850	5.95
1500	6852	5.95

### BRAND NEW 1978 IC MASTER

Complete integrated circuit data selector. New 1978 edition (2200 pages) is twice as big as last year. Master guide to the latest I.C.'s including microprocessors and consumer circuits.

Free quarterly updates.



**\$24.95**  
Lowest price available



P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over-the-counter sales.  
12 Mercer Rd. Natick, Mass. 01760  
Behind Zayres on Rte. 9  
Telephone Orders & Enquires (617) 879-0077

IN CANADA 3 LOCATIONS

5651 Ferrier St. Montreal, Quebec Tel. (514) 735-6425  
44 Fasken Dr. Unit 25 Rexdale, Ontario Tel. (416) 675-3311  
Baxter Centre 1050 Baxter Road Ottawa, Ontario Tel. (613) 820-9471

MINIMUM ORDER \$10.00 • ADD \$2.00 TO COVER POSTAGE & HANDLING • Canadian customers add 30% for exchange and handling. All federal and provincial taxes extra.  
Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.

# 4-for-1 SALE!

Top Quality J.I.L. 4-in-1  
IN-DASH  
AM-FM CAR STEREO with  
CASSETTE or 8-TRACK  
PLUS 40-CHANNEL CB!

**\$14900**  
WHILE SUPPLY  
LASTS



From J.I.L., a leader in car entertainment centers... a modular, compact, first quality 4-in-1 unit at a price you might pay for a radio only! Get stereo high-fidelity FM Radio, AM Radio, Cassette or 8-track, and CB all for on low price. Tens of thousands sold nationally. Order while supplies last.

- #853/102 In-Dash Combination 8-Track Stereo, AM/FM/Stereo Radio and 40-Channel Digital Touch-Tuning AM-CB. Features LO/DX switch, Stereo light, 8-track program lights, CB standby switch, LED channel readout. Plus many other features  
-while supply lasts only... **\$149.00**
- #610/102 In Dash Combination Stereo Cassette Player, AM/FM/Stereo Radio and 40-Channel Digital Touch-Tuning AM-CB. Features cassette eject/FF button, CB selector, CB standby switch Plus many other features  
-while supply lasts only... **\$159.00**
- #202-SSB Single Sideband 40-Channel CB featuring Digital Touch-Tuning AM-SSB CB for 120 effective channels with greater clarity and reach. All functions right on the mike. A top-notch unit. Choose SSB instead of standard 40-channel CB with #853 or #610 above.  
Please add ..... **\$50.00**

## ACCESSORIES

- AM/FM/CB Retractable Antenna (mounts like reg. car antenna)  
List \$39.95 ..... **NOW \$29.95**
- 5 1/4" Full-tone Coaxial Speakers  
20 oz. magnets.  
List 39.95 pr. .... **NOW \$19.95**
- 6" x 9" Full-tone Coaxial Speakers  
10 oz. magnets each  
List \$69.95 pr. .... **NOW \$29.95 pr.**
- Field Strength/SWR Meter to test Ant.  
List \$29.95 ..... **NOW \$19.95**

**CLIP AD AND ATTACH TO LETTER**  
Pa. Res. Add 6% Sales Tax.

**LESLIE PAUL INC.** 0300  
"DISCOUNT MAIL ORDER!"  
70 James Way, Southampton, Pa. 18966  
Phone Orders Call (215) 322-8599

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
BankAmericard/Visa/Master Charge.  
Card # \_\_\_\_\_ Exp. Date \_\_\_\_\_

CIRCLE 72 ON FREE INFORMATION CARD

## DIGITAL CASSETTE TAPE C-60



- \* without B.O.T., E.O.T.
- \* 60 minutes recording time
- \* Write enable tap
- \* ANSI Notch
- \* ANSI support plane

FOR DIGITAL  
COMPUTER RECORDING  
All these tapes made in U.S.A.  
Never Recorded—Reg. \$6.80 each  
**OUR PRICE 3 for \$5.00**



TYPE TIL 305 LED  
5X7 ALPHANUMERIC  
DISPLAY  
~~\$3.80~~ EACH

- 0.300-Inch-High Character
  - High Luminous Intensity
  - Low Power Requirements
  - Wide Viewing Angle
  - 5 X 7 Array with X-Y Select and Decimal
  - Compatible with USASCII & EBCDIC Codes
- SPECIAL SALE**  
4 for \$9.90

## THE MOST POPULAR MM5314 CLOCK KIT

- Features:
- \* 12/24 Hours Display
  - \* 50/60 Hz Input
  - \* 6 Digits Bright Orange Readouts



Kit includes plastic case, MM 5314 I.C. One set transistor drivers, P.C. Board, gas discharge displays, all other electronic parts and transformer. Catalog no. DC-8SP  
**SPECIAL PRICE**  
**\$16.95 PER KIT**

## 9 STEPS LED LEVEL INDICATOR KIT



for most stereo amplifiers  
This new project works as a pair of VU meter to indicate the output level of your amplifier from -20dB to +3dB. Kit includes all LED, transistors, electronic components, P.C. Board and instructions.  
Easy to build and fun to see.  
**ONLY \$9.90 EA.**

## 60W + 60W



OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8Ω. Power supply is 24 - 36V AC or DC. Complete unit

only \$37.50 ea.  
Power transformer \$7.50 ea.

## RCA 2N3055



NPN power transistor.  
100V 115 watt  
15 amp  
**2 for \$1.80**

## COMPUTER GRADE CAPACITORS



All capacitors are Brand New U.S. made in standard size

5600MFD	60V	\$2.20 EA.
8500MFD	35V	\$2.75 EA.
9000MFD	50V	\$3.25 EA.
4200MFD	150V	\$2.50 EA.
3000MFD	15V	\$1.50 EA.
11000MFD	35V	\$3.20 EA.
14500MFD	40V	\$3.40 EA.
20000MFD	55V	\$3.50 EA.
23000MFD	20V	\$3.00 EA.
58000MFD	20V	\$3.20 EA.
100,000MFD	6V	\$2.50 EA.



## VHF MODULATOR

(Size of a Match Box)

This unit converts the video signal to RF signal. Ideal for computer terminal or TV games.

Video input: 1V DC RF  
output: 1.5MV  
Preset at 61.25 MHz  
(channel 3)  
Frq. adjustable ± 3 MHz  
Power Supply 5~8V DC 10 MA  
**\$4.50 EACH**

## DIP SWITCHES



(On-Off Contacts)

4 positions	\$1.50
5 positions	\$1.60
6 positions	\$1.70
7 positions	\$1.70
8 positions	\$1.80
10 positions	\$2.00

## PHOTO RESISTOR C.D.S.



This U.S. made photo resistor is packed in a clear glass case with a dia. of 1/2". Max. range 50K 0  
**80¢ ea.**

## PHOTO RESISTOR C.D.S.



Dual 50K in one cell with 3 leads mini size with 1/4" dia. Ideal for light control device.

**SPECIAL**  
**3 for \$1.00**

## MERCURY SWITCH



The switch is a light bulb type SPST with a drop of mercury inside. Ideal for alarm control, or a motion device switch. Small size like a 6V light bulb.  
**60¢ ea.**

CIRCLE 42 ON FREE INFORMATION CARD

## SUPER 15 WATT AUDIO AMP KIT



**ONLY \$23.50 each**

Uses STK-015 Hybrid Power Amp

Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power 1/2dB response from 20-100,000 Hz. This amplifier has QUASI-Complimentary class B output. Output max is watt (10 watt RMS) at 4Ω.

## 30MHZ FREQUENCY COUNTER KIT



Only ~~\$59.50~~ **\$53.50**

Model 250-30A

Includes all parts, PC Board and Transformer

Take advantage of this new state-of-the-art counter featuring the many benefits of custom LSI circuitry. This new technology approach to instrumentation yields enhanced performance, smaller physical size, drastically reduced power consumption (portable battery operation is now practical), dependability, easy assembly and revolutionary lower pricing!

- 0.5" red LED 6 digits display
- Resolution: 1 Hz at 1 sec. 10 Hz at 1/10 sec.
- Sensitivity: 10 Mv RMS to 30 Hz
- Internal power supply: 5.2V at 1 amp regulated
- Input connector: BNC type
- Input power required: 117V AC 50/60 Hz
- Diode protected for over voltage input



## FM WIRELESS MIC KIT

**\$6.95 EACH KIT**

This new model FM wireless MIC kit uses 3 high freq. transistors, works in the FM range (88-108 MHz). It transmits the sound wave fidelity clearly over long distances (up to 250 ft.). Kit comes with all electronic parts, P.C. Board and mini microphone!

## SOUND ACTIVATED SWITCH



All parts completed on a PC Board. SCR will turn on relay, buzzer or trigger other circuit for 2-10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V-9V D.C. \$1.75 ea./2 for \$3.00

**Sub-Mini Size Condenser Microphone \$2.50 each**  
FET Transistor Built-in



## FLUORESCENT LIGHT DRIVER KIT

12V DC POWERED

Lights up 8-15 Watt Fluorescent Light Tubes

Ideal for camper, outdoor Auto or Boat

Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

**ONLY \$5.50 PER KIT**



## MANY SOUND DECISIONS!

Solid state sound indicator operating voltage 6V DC 30mA. Small size approximately 3/8" x 1 1/4".

Model EB2116 (Continuous)  
Model EB2126 (Slow Pulse)  
Model EB2136 (Fast Pulse)



\$3.60 EACH



Slow pulse



Fast pulse

## 1Watt AUDIO AMP

All parts are pre assembled on a mini PC Board  
Supply Voltage 6-9V D.C.  
**SPECIAL PRICE \$1.95 ea.**



## "FISHER" 30 WATT STEREO AMP (15W X 2)

Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board, Power supply ± 16V DC (not included). Power band with (KF 1% ± 3dB). Voltage gain 33dB. 20Hz-20KHz.

**Super Buy Only \$22.50 each kit**



## 5W AUDIO AMP KIT

2 LM 380 with Volume Control  
Power Supply 6-18V DC  
**only \$5.00 ea.**



## TIMER KIT

Time Controlled from 1-100sec. Ideal to be used as timer delay unit for burglar alarm, photo service, and other purposes. Max. loading 110V, 2 AMP. Supply voltage 12-18V DC.  
**\$11.50 each**



FT-90 ELECTRONIC IC TIMER

## ELECTRONIC ALARM SIREN

COMPLETE UNIT  
Ideal for use as an Alarm Unit or hookup to your car back up to make a reverse indicator. Light Output up to 1300dB  
Voltage Supply 6-12V **\$7.50**



AU-999

## 19 KEY HEXADECIMAL KEY PAD

- 1-0
- Homekey
- ABCDEF
- ←→ Key

**SPECIAL \$10.50 ea.**



## Low Cost Hexadecimal 16 Key Pad

Designed for Calculator or Computer  
Data Entry Pad or Digital Lock  
All key tops blank with super good touch feeling **\$0.95 each**



## DIGITAL ELECTRONIC LOCK KIT

for auto ignition, entry door, burglar alarm, etc.  
CMOS I.C. 4 Digits Programmable to IN CIRCUIT  
**\$6.50 ea.** Any Combination



400A RELAY AND KEY PAD NOT INCLUDED

## BATTERY POWERED FLUORESCENT LANTERN

FEATURES

- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6W cool/daylight miniature fluorescent tube.
- 6 X 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing illumination of the lantern.



\$9.60 EACH  
MODEL 888-R

## POWER SUPPLY KIT



0-30V D.C. REGULATED  
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts.  
0-30V POWER SUPPLY **\$10.50 each**  
Transformer for Power Supply, 2 AMP 24V x 2 **\$6.50**  
30V DC Panel Meter **\$4.20**

## 12V DC MINI RELAY P.C. Board Solder Type

2AMP Contact SPDT \$1.30 EA  
2AMP Contact DPDT \$1.75 EA  
5AMP Contact 4PDT \$2.20 EA



## 12V D.C. AUTO DIGITAL CLOCK

Complete Unit  
Not a Kit!

0.4" blue color 4 digits display. Turn off readouts when car is not running. X'tal controlled time base for time accuracy. Special designed case for easy mounting on top of your dashboard. Ideal for car, boat and campers.  
**ONLY \$28.50 ea.** **SALE! \$24.50**



## ELECTRONIC SWITCH KIT CONDENSER TYPE

Touch On Touch Off uses 7473 I.C. and 12V relay  
**\$5.50 each**



## NEW! 4 EASY-TO-BUILD KIT

LED PROJECTS ON ONE BOARD

- HO-Gauge railroad crossing blinker
- Variable LED flasher
- Six-bit binary counter
- Wheel of Fortune

Kit includes all electronic components and PC Board  
Especially designed for experimenters  
Guaranteed - they all work!!  
(Battery not included)  
**\$12.50 PER KIT**



## LED ALARM CLOCK

COMPLETE UNIT  
NOT A KIT


- 0.5" RED LED READ OUT
- 24 HRS. ALARM SET
- 10 MINS. SNOOZE SET
- AM/PM ALARM INDICATORS
- SECOND DISPLAY SWITCH
- AUTOMATIC BRIGHTNESS CONTROL
- COMPACT AND HANDSOME PACKING
- 110V AC 60HZ INPUT

**\$17.50 EACH**


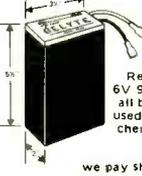
## GELYTE

Rechargeable Battery 6V 9AMP hour by Gould all batteries are new unused, solid with no liquid chemicals **\$9.50 EACH**



## Sub Mini Size PANEL METER

500 U.A.  
**ONLY \$1.20 ea**



## PANEL METER (D.C. Type)

Size 60MM X 66MM  
White Face Type

0-50 U.A.	0-30V
0-1MA	0-50V
0-5MA	0-100V

**\$5.50 ea.**



## TRANSFORMERS

ALL 117 VOLT INPUT

30V	4AMP	\$7.50 EA.
36V CT	3AMP	\$6.50 EA.
48V CT	3AMP	\$6.50 EA.
24V CT	3AMP	\$6.50 EA.
12 or 24V	2AMP	\$3.90 EA.
24V CT	0.8AMP	\$1.80 EA.
12V CT	0.8AMP	\$1.80 EA.



## AC POWER SUPPLY


Watt Type Transformer

12V AC	Output	200MA	\$2.75 EA.
16V CT AC	Output	100MA	\$2.10 EA.
6V DC	Output	120MA	\$1.90 EA.
12V DC	Output	100MA	\$1.90 EA.



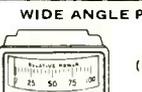
## WIDE ANGLE PANEL METER

1 3/8" x 3/8"  
1MA Full Scale (scale marks 0-100)  
**\$1.50 each**


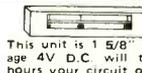
## HOUR INDICATOR

This unit is 1 5/8" long operating voltage 4V D.C. will tell you how many hours your circuit or machine has been in service up to 100 hours.  
Limited Quantity **ONLY \$1.75 ea.**



## HEAVY DUTY CLIP LEADS

10 pairs - 5 colors  
Alligator clips on a 22" long lead. Ideal for any testing.  
**\$1.85/pack**



## MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches!  
Receives all AM stations  
Batteries and ear phone included

**Only \$8.50**



## MINI-MINI TOGGLE SWITCH

Half size of submini toggle switch rated 3 amp 125V AC contact

	1-9	10-99
MS 2432P	SPST	0.80 0.80
MS 244	SPDT	1.00 0.90
MS 245	DPDT	1.20 1.10

LARGE QUANTITY AVAILABLE FOR OEM



## SUBMINIATURES TOGGLE SWITCHES

Mini size Rocker Type  
Also available at the same price

SPDT	On/Off	\$1.30 ea
DPDT	On/Off	\$1.50 ea
3PDT	On/Off	\$1.75 ea



## MINI SIZE REED RELAY

Approx. 1" square  
SPST Normal Open  
Contact rated 1AMP  
Coil 6-12V DC  
All brand new by AMF  
**3 for \$2.00**



## PUSH-BUTTON SWITCH

N/Open Contact  
Color: Red, White, Blue, Green, Black. **4/\$1.00**  
N/Close also  
Available 50 ea.  
LARGE QTY. AVAILABLE



## SOLID STATE ELECTRONIC BUZZER

Mini size 1" x 3/8" x 3/8"  
Supply voltage 1.5V 12V  
Ideal for Alarm or Tone Indicator  
**\$1.50 each**



MINIMUM ORDER \$10.00. California residents add 6% sales tax and 10% shipping. Out of state add 15% of total purchase for shipping charges, out of USA and Overseas add 25% of total purchase. SEND CHECK OR MONEY ORDER TO:



# FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 973-1921, (213) 679-5162  
STORE HOURS 10-7 Monday - Saturday



SEND \$1.00 FOR DETAILED CATALOG

CIRCLE 8 ON FREE INFORMATION CARD

# Special Functions

3050 VALMONT ROAD  
BOULDER, COLORADO 80301

## Terms

- Prices, specifications and availability subject to change without notice.
- U.S. & Canadian orders minimum \$10.00.
- All other foreign orders \$20.00 minimum.
- Please add \$1.00 postage and handling.
- Foreign orders (exc. Canada) add 15% for postage.
- Colorado residents add 3% sales tax.
- No C.O.D.'s please.
- Foreign orders send U.S. funds ONLY.

<b>Slide Switch</b> Smooth action, 4-pole, triple throw, J-5100 <b>80¢</b>	<b>Toggle Switch</b> Heavy duty, SPST toggle, rated @ 15A/125 volts. J-5004 <b>95¢</b>	<b>1N4148 Diode</b> Miniature glass type high speed switching diode. Case AA. J-1002 <b>12 for \$1.00</b>	<b>Connector</b> connector w/ unique tel. (on/solder interconnect piece. J-1100 <b>15¢ \$1.00</b>	<b>Transformer</b> 8V @ 500 ma or 12V @ 190ma. W/ specs. J-5005 <b>\$1.50</b>	<b>Wire Special</b> 22 ga. magnet wire w/ solder-through insulation. Appx. 500'. J-7003 <b>\$2.50</b>	<b>Mini Cap</b> .005 ul. 500 WVDC. 7 for \$1.00
<b>Jumbo LED</b> .200" factory prime LED's for experimenters. J4004 5 for <b>\$1.</b>	<b>LED Panel Clip</b> Black plastic clip for mounting LED in panels. J-4002 12/ <b>\$1.</b>	<b>28 Pin Socket</b> Standard, solder-type, low profile 28 pin IC socket. J-7101 <b>40¢</b>	<b>PC Board</b> glass-epoxy PC board blanks. .062" thick. 4 x 6 (J-8016) 5 for \$3.00 3 x 6 (J-8017) 5 for \$2.25 6 x 6 (J-8018) 5 for \$3.60 2 x 8 (J-8019) 5 for \$2.00	<b>Trimmer Cap</b> 1 3pf miniature PC trimmer cap for crystal circuits, etc. J-3000 <b>75¢</b>	<b>2N3055</b> Popular audio-type power transistor. J-1001 <b>65¢</b>	<b>Terminal Post</b> Ceramic insulated terminal post, 3/4". 10 for <b>\$1.00</b>
<b>Reed Relay</b> Sensitive 12 VDC reed relay, DPST, 1 1/2" long, with P-C leads. J-5047 <b>\$1.50</b>	<b>Hex Nuts</b> Standard size hex nuts for use on pots, switches, etc. 3/8" I.D. 25 for <b>\$1.00</b>	<b>5Ω Resistor</b> Wire Wound 1 Watt 25¢	<b>PC Trimmer</b> 20 turn miniature PC mount trimmer pot. 3/4" long, 5K ohm. J-2013 <b>1.10</b>	<b>BNC Connector</b> 3/8" female BNC type shielded connector with jacketed 6" leads. J-7102 <b>\$1.00</b>	<b>Rubber Edging</b> Black Flexible Rubber J-8008 10'/\$1.60 100'/\$12.00	
<b>Transformer</b> Unique split primary allows two outputs, 9 or 18 volts at 1.5 amps. W/ specs & data. J-5012 <b>\$2.50</b>	<b>PC Board Spacers</b> 1 1/4" long, 1/8" inside diameter. 20/\$1.00	<b>RO170 Diode</b> The famous RO-170 general replacement diode, rated 1000 piv at 2.5 amps. J-1000 <b>20¢</b> 100 for \$14.50	<b>Component Holder</b> component holder for mounting capacitors, power resistors, varis, bundles, etc. 10 for <b>50¢</b>	<b>Automotive</b> 2" to 2 1/2" steel screwdriver adjustable <b>Hose Clamp</b> J-4 <b>45¢</b>	<b>Lamp Socket</b> Standard automotive type, double contact 75¢	
<b>PC Trimmer Pot</b> 3/8" square, top adjustable, screwdriver slotted, single turn 20K ohm @ 1/2 watt Standard PC leads. <b>90¢</b>	<b>Potentiometer</b> Miniature 1/8" shaft, 1/4" mount potentiometer. 100 ohm value. J-2100 <b>70¢</b>	<b>PC Trimmer Pot</b> Horizontal type, 1K ohm PC Trimmer. J-2101 <b>25¢</b>	<b>POWER RESISTORS</b> 12 WATT 5% DALE 15Ω OHMITE 125Ω <b>79¢</b>	<b>Trimmer</b> New, CTS miniature screwdriver adjustable. 25K ohm, 4 for \$1.00	<b>Heat Shrink</b> Much easier and faster than electrical tape. Twelve 6" pieces, ass'd. J-7004 <b>\$1.45</b>	

## MORE NEW ITEMS!

<b>JUMBO LED READOUT ARRAY</b> By Bowmar. .5 in. character common cathode. Designed for use with multiplexed clock chips 4 digits in 1 pack! <b>\$1.95 LIMITED STOCK</b>	<b>NATIONAL SEMICONDUCTOR JUMBO CLOCK MODULE</b> MA1008A BRAND NEW! FEATURES: • FOUR JUMBO 1/2 INCH LED DISPLAYS • 12 HR REAL TIME FORMAT • 24 HR ALARM SIGNAL OUTPUT • 50 OR 60 HZ OPERATION • LED BRIGHTNESS CONTROL • POWER FAILURE INDICATOR • SLEEP & SNOOZE TIMERS • DIRECT LED DRIVE (LOW RFI) • COMES WITH FULL DATA <b>\$6.95</b> 2 FOR \$13 (AC XFMR \$1.95) ASSEMBLED! NOT A KIT! ZULU VERSION! We have a limited number of the 24 HR Real time version of this module in stock. #MA1008D — \$9.95 PERFECT FOR USE WITH A TIMEBASE. COMPARE AT UP TO TWICE OUR PRICE! MANUFACTURER'S CLOSEOUT!			
<b>MICRO-MINI TOGGLE SWITCH</b> SPDT. By RAYTHEON. MADE IN USA! WITH HDWR. <b>99¢ EACH</b> <b>6 FOR \$5</b>	<b>MOTOROLA 4K RAM's — 99¢ EACH (WITH DATA)</b> A major U.S. computer mfg. removed these parts from PC boards, then retested them to full specs. Best Memory Buy in the U.S.A! 4096 x 1 Bits One of the easiest Dynamic RAM's to use. A complete memory board design using these chips is detailed in the MOTOROLA M6800 APPLICATIONS MANUAL starting on page 4-70. The 6605 is the popular 22 Pin Dip. <b>8 FOR \$6.95</b> (4096 WORDS OF RAM) <b>SURPLUS BUY OF THE DECADE!</b>	<b>EXPERIMENTER'S CRYSTAL</b> 262 144KHZ. This frequency is 2 to the 18th power. Easily divided down to any power of 2, and even to 1HZ. New by CTS-Knight. A \$5 value! <b>\$1.25 each</b>	<b>LED IC Counter Kit</b> You Get: 1—7490; 1—7475; 1—7447; 1—Led Readout. All this for <b>\$1.99</b> (Led Readout is famous SLA-1. .33 in. By Opcoa.)	
<b>FAIRCHILD JUMBO READOUTS</b> .5 Inch Char. High Efficiency! FND-503-Common Cathode FND-510-Common Anode <b>YOUR CHOICE 69¢</b> 10 FOR \$5.75	<b>DISC CAPACITORS</b> .1 MFD 16V. P.C. leads. Most popular value! By Sprague. <b>20 for \$1.00</b>	<b>Full Wave Bridge 4 Amp 200 PIV 69¢ea. 10/5.75</b>	<b>MALLORY POWER SUPPLY CAPACITOR</b> 1500 MFD 16 WVDC <b>3/\$1.00 10/\$2.95</b> FACTORY FRESH! SMALL SIZE	<b>2N3904-House No. TO-92. NPN. VCEO-45. HFE 100 to 300 10 for \$1.00</b>
<b>FET SALE!</b> 2N4304 Brand New N Channel, Junction Fet. BVGD0-30V IDSS-15 MA Typ 1500 uMHOS TO-18 Plastic Case. Mfg by Teledyne. <b>6 FOR \$1</b>	<b>Motorola PNP Power!</b> 2N4905 TO-3 case. 90W VCEO-60. HFE-100 max. at 2.5A. Good mate for the 2N3055 PRIME! <b>75¢ ea. 4/\$2.50</b>	<b>COMPUTER CAPACITOR</b> By GE. 36,000 MFD 15W VDC. Small Size. 4 1/4 x 1 1/4 Inches. <b>SUPER DEAL! \$2.95 Each 3 FOR \$8</b>	<b>LS SERIES TTL</b> 74LS00-33c 74LS74-49c 74LS02-35c 74LS90-69c 74LS04-35c 74LS138-89c 74LS08-35c 74LS154-1.49 74LS10-33c 74LS175-1.10 74LS20-33c 74LS367-75c 74LS73-49c 74LS368-85c	<b>Motorola Quad Op-Amp MC3401. Pin for Pin Sub for popular LM3900. 3/\$1.00</b>

# Digital Research Corporation

(OF TEXAS)  
P. O. BOX 401247 B GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Orders under \$15. add 75c. No COD's. We accept VISA, MasterCard and American Express Cards. Money Back Guarantee on all items! Texas Residents add 5% Sales Tax. **WE PAY POSTAGE!**


**AVAILABLE NOW!** ONLY \$ 5.90  
Add \$1.00 postage and handling  
**JAPANESE TRANSISTOR SUBSTITUTION MANUAL**



An invaluable Japanese to Japanese substitution guide for approximately 3000 transistors.  
• Covers the 2SA, 2SB, 2SC, and 2SD series.  
• Introduction includes a guide to understanding Japanese transistors.  
• A 90 page, 8 1/2" by 11", soft cover book.
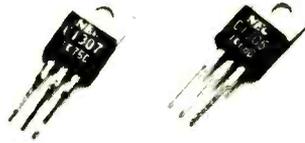
# JULY SPECIAL

**DON'T MISS OUT THIS TIME!**  
**ORDER NOW!**  
LIMITED Q'TY



2SC 1306 \$1.90 REG \$2.90  
2SC 1307 \$2.90 REG \$3.90

NO FURTHER DISCOUNT  
ON SPECIAL OFFER

## Seeking Original Japanese Replacement Parts for CB, TV and Stereo Repair Use?

<b>2SA</b>		2SA 744 4.90	2SB 537 1.60	2SC 696 1.95	2SC 1115 4.40	2SC 1675 .59	2SD 313 1.10	HA 1156 3.00	TA 78012M 6.60
2SA 49 .59	2SA 745R 4.90	2SB 539 4.90	2SC 708 1.90	2SC 1116 4.90	2SC 1678 2.25	2SD 314 1.20	HA 1158 5.30	TA 78012P 5.80	
2SA 52 .59	2SA 747 5.80	2SB 541 4.40	2SC 710 .45	2SC 1116A 6.60	2SC 1679 4.25	2SD 315 1.20	HA 1159 5.80	TA 78015M 6.50	
2SA 53 .59	2SA 748 1.00	2SB 554 10.00	2SC 711 .45	2SC 1124 1.30	2SC 1681 .70	2SD 325 1.10	HA 1196 4.90	TA 78015P 5.80	
2SA 70 1.10	2SA 750 .59	2SB 556 4.90	2SC 712 .59	2SC 1127 1.40	2SC 1682 .45	2SD 330 1.00	HA 1197 3.90	TBA 810 SH 3.70	
2SA 101 .45	2SA 755 1.60	2SB 557 3.40	2SC 717 .59	2SC 1161 1.90	2SC 1684 .59	2SD 341 5.60	HA 1201 1.50	TC 5080P 5.80	
2SA 102 .59	2SA 756 3.70	2SB 561B .70	2SC 727 1.90	2SC 1162 1.00	2SC 1687 .70	2SD 350 5.90	HA 1202 2.25	TC 5081P 3.40	
2SA 234 .59	2SA 758 5.80	2SB 564 .70	2SC 730 4.40	2SC 1166 .59	2SC 1688 .70	2SD 352 .90	HA 1211 1.50	TC 5082 3.90	
2SA 235 1.00	2SA 764 4.40	2SB 595 1.90	2SC 731 5.80	2SC 1167 6.60	2SC 1708 .59	2SD 356D 1.10	HA 1306W 3.70	TD 3505AP 8.50	
2SA 240 .90	2SA 765 4.90	2SB 596 1.60	2SC 732 .59	2SC 1170B 6.60	2SC 1728 1.90	2SD 357D 1.00	HA 1322 4.40	UHC 002 5.80	
2SA 329 .70	2SA 774 .59	2SB 600 7.00	2SC 733 .59	2SC 1172B 8.50	2SC 1730 .59	2SD 358 1.30	HA 1339 4.40		
2SA 342 .90	2SA 777 1.00		2SC 734 .59	2SC 1173 .90	2SC 1756 1.40	2SD 359 1.00	HA 1339A 4.40	UHC 005 5.80	
2SA 353 .70	2SA 794A 1.00		2SC 735 .59	2SC 1175 .90	2SC 1760 1.90	2SD 360 1.20	HA 1342A 4.40	UHC 004 5.80	
2SA 377 2.00	2SA 798 .70	<b>2SC</b>	2SC 738 .59	2SC 1177 14.00	2SC 1765 8.80	2SD 361 1.00	LA 1111P 2.50	UPC 20C 4.40	
2SA 436 2.50	2SA 814 1.90	2SC 183 .59	2SC 756 2.80	2SC 1189 1.20	2SC 1775 .45	2SD 370 3.00	LA 1201 2.50	UPC 41C 3.70	
2SA 440 .90	2SA 815 1.00	2SC 184 .59	2SC 756A 3.00	2SC 1209 .70	2SC 1816 3.90	2SD 371S 2.80	LA 1364 4.40	UPC 554C 2.80	
2SA 473 .70	2SA 816 .70	2SC 281 .59	2SC 763 .59	2SC 1210D .59	2SC 1846 .70	2SD 380 7.60	LA 3300 3.00	UPC 555H 2.25	
2SA 483 3.00	2SA 818 1.30	2SC 283 .59	2SC 772 .45	2SC 1212A 1.40	2SC 1885 .70	2SD 381 1.40	LA 3301 3.00	UPC 563 3.70	
2SA 484 2.50	2SA 837 2.80	2SC 284 1.20	2SC 773 .70	2SC 1213 .70	2SC 1908 .59	2SD 382 1.40	LA 4030P 3.40	UPC 566H 1.60	
2SA 485 2.00	2SA 839 2.15	2SC 317 1.20	2SC 774 2.00	2SC 1215 .70	2SC 1909 3.90	2SD 388 3.40	LA 4031P 3.00	UPC 576 3.70	
2SA 489 1.60	2SA 841 .59	2SC 352A 2.50	2SC 775 1.95	2SC 1222 .45	2SC 1913 1.20	2SD 388A 4.40	LA 4032P 3.40	UPC 577H 2.25	
2SA 490 .90	2SA 847 .59	2SC 353A 2.50	2SC 776 2.65	2SC 1226A .90	2SC 1945 5.60	2SD 389 .90	LA 4051P 3.70	UPC 592HZ 1.60	
2SA 493 .59	2SA 850 .59	2SC 367 .90	2SC 777 3.50	2SC 1237 2.25	2SC 1951 1.10	2SD 390 1.00	LA 4400 3.70	UPC 1001H 4.90	
2SA 495 .45	2SA 872A .59	2SC 369 .59	2SC 778 3.60	2SC 1239 3.90	2SC 1957 1.20	2SD 421 8.50	LD 3120 2.50	UPC 1008C 7.00	
2SA 496 1.10	2SA 885 .70	2SC 371 .59	2SC 781 2.65	2SC 1279 .70	2SC 1969 4.90	2SD 424 8.50	M51513L 4.90	UPC 1016C 3.70	
2SA 497 1.60	2SA 908 11.00	2SC 372 .45	2SC 783B 3.60	2SC 1306 2.90	2SC 1973 1.10	2SD 425 6.50	M5152L 2.50	UPC 1020H 3.00	
2SA 505 1.20	2SA 913 1.20	2SC 373 .45	2SC 784 .59	2SC 1307 3.90	2SC 1974 1.90	2SD 426 4.60	M51841P 2.80	UPC 1025 3.40	
2SA 509 .70		2SC 374 .59	2SC 785 .59	2SC 1310 .59	2SC 1975 4.40	2SD 427 3.00	M51841P 2.25	UPC 1026C 3.70	
2SA 525 .70	<b>2SB</b>	2SC 377 .70	2SC 789 1.00	2SC 1312 .59	2SC 2028 .90	2SD 525 1.60	M53273P 2.80	UPC 1032 2.25	
2SA 530 1.30	2SB 22 .59	2SC 380 .59	2SC 790 1.40	2SC 1313G .59	2SC 2029 3.90	2SD 526 1.10	M53274P 2.50	UPC 1152H 3.40	
2SA 537A 2.25	2SB 24 .59	2SC 381 .59	2SC 793 2.80	2SC 1316 8.50	2SC 2074 1.90	2SD 555A 6.60	M53393 7.60	UPC 1156 3.00	
2SA 539 .59	2SB 25 .59	2SC 382 .59	2SC 799 3.60	2SC 1317 .45	2SC 2076 .59	2SD 610 1.90	MS4730 P 8.80		
2SA 545 .59	2SB 27 .45	2SC 383 .90	2SC 802 3.60	2SC 1318 .45	2SC 2091 2.80	SG 613(tv) 5.95	MPS U31 1.90	UPD 858C 9.50	
2SA 561 .59	2SB 28 .45	2SC 383A .59	2SC 815 .59	2SC 1325A 7.60	2SC 2092 3.90		STK 011 7.60	PLL 01A 8.80	
2SA 562 .59	2SB 29 .45	2SC 388A 1.00	2SC 828 .45	2SC 1327 .59	2SC 2098 4.90		STK 014 9.50	PLL 02A 8.80	
2SA 564A .59	2SB 30 .45	2SC 394 .59	2SC 829 .45	2SC 1330 .70			STK 015 6.60	SN 7400 .19	
2SA 565 1.10	2SB 31 .45	2SC 403 .59	2SC 830H 5.90	2SC 1335 .70			STK 016 8.50	SN 7490 .60	
2SA 566 3.40	2SB 32 .45	2SC 430 .90	2SC 838 .59	2SC 1342 .59			STK 022 11.00		
2SA 606 1.60	2SB 33 .70	2SC 454 .59	2SC 839 .59	2SC 1344 .59			STK 032 14.00		
2SA 607 1.60	2SB 34 .45	2SC 458 .59	2SC 853 .90	2SC 1345D .59			STK 435 8.50		
2SA 624 1.10	2SB 35 .45	2SC 460 .59	2SC 867 4.25	2SC 1346 .70			STK 439 11.00		
2SA 627 3.60	2SB 36 .70	2SC 461 .59	2SC 870 .59	2SC 1347 .70			STK 502 8.80	78L05 1.10	
2SA 628 .59	2SB 37 .70	2SC 478 1.10	2SC 871 .59	2SC 1358 5.90			STK 503 9.60	IS 84 .25	
2SA 634 .70	2SB 38 .60	2SC 481 1.60	2SC 895 4.90	2SC 1359 .59			TA 7027M 3.70	IS 188 .25	
2SA 640 .59	2SB 39 .60	2SC 482 1.50	2SC 897 3.40	2SC 1360 1.00			TA 7045M 3.00	IS 332 .45	
2SA 642 .70	2SB 40 .60	2SC 484 1.60	2SC 898 4.40	2SC 1362 .59			TA 7054P 2.50	IS 953 .25	
2SA 643 .70	2SB 41 .60	2SC 485 1.60	2SC 900 .45	2SC 1364 .70			TA 7055P 3.00	IS 1007 .45	
2SA 653 2.80	2SB 42 .60	2SC 486 1.60	2SC 923 .45	2SC 1377 4.90			TA 7060P 1.60	IS 1209 .45	
2SA 659 .59	2SB 43 .60	2SC 493 3.90	2SC 929 .45	2SC 1383 .59			TA 7061AP 1.90	IS 1211 .45	
2SA 661 .70	2SB 44 .60	2SC 495 .90	2SC 930 .45	2SC 1384 .59			TA 7062P 1.90	IS 1555 .25	
2SA 663 4.90	2SB 45 .60	2SC 496 .90	2SC 941 .59	2SC 1396 .70			TA 7063P 1.60	IS 1588 .25	
2SA 666 .70	2SB 46 .60	2SC 497 1.60	2SC 943 .70	2SC 1398 1.10			TA 7064P 1.90	IS 1885 .25	
2SA 671 1.40	2SB 47 .60	2SC 509 .70	2SC 945 .45	2SC 1400 .59			TA 7066P 2.00	IS 2076 .25	
2SA 672 .70	2SB 48 1.40	2SC 515A 1.40	2SC 959 1.50	2SC 1402 4.90			TA 7074P 4.90	IS 2093 .45	
2SA 673 .70	2SB 49 .59	2SC 517 3.95	2SC 971 1.00	2SC 1403 4.90			TA 7075P 4.90	IS 2473 .25	
2SA 678 .70	2SB 50 1.20	2SC 535 .59	2SC 982 .90	2SC 1407 .90			TA 7076P 4.90	IN 34 .25	
2SA 679 4.90	2SB 51 1.40	2SC 536 .59	2SC 983 1.00	2SC 1419 1.10			TA 7079P 3.00	IN 60 .25	
2SA 680 4.90	2SB 52 .60	2SC 537 .59	2SC 984 .90	2SC 1444 2.80			TA 7102 5.80	10D1 .40	
2SA 682 1.50	2SB 53 .60	2SC 538A .70	2SC 994 3.90	2SC 1445 3.00			TA 7105P 4.90	10D10 .60	
2SA 683 .70	2SB 54 .60	2SC 562 .70	2SC 996 3.40	2SC 1447 1.60			TA 7108P 1.90	VO 6B .40	
2SA 684 .70	2SB 55 1.20	2SC 563 1.10	2SC 1000BL .59	2SC 1448 1.60			TA 7109P 3.40	VO 6C .40	
2SA 695 .70	2SB 56 1.60	2SC 605 .70	2SC 1012 1.50	2SC 1449 1.00			TA 7120P 1.90		
2SA 697 .70	2SB 57 1.20	2SC 619 .59	2SC 1013 1.10	2SC 1451 2.25			TA 7122AP 1.90		
2SA 699A .90	2SB 58 1.00	2SC 620 .59	2SC 1014 1.10	2SC 1454 5.60			TA 7124P 1.60		
2SA 705 .70	2SB 59 1.20	2SC 627 2.25	2SC 1017 1.40	2SC 1475 1.40			TA 7129P 1.90	WZ 050 .45	
2SA 706 1.60	2SB 60 1.00	2SC 631 .90	2SC 1018 1.20	2SC 1478S 1.70			TA 7130P 2.80	WZ 052 .45	
2SA 715 1.40	2SB 61 1.60	2SC 632A .45	2SC 1030C 2.80	2SC 1509 1.10			TA 7136P 1.30	WZ 061 .45	
2SA 719 .59	2SB 62 1.90	2SC 634A .59	2SC 1047 .70	2SC 1567 1.10			TA 7146P 4.20	WZ 071 .45	
2SA 720 .59	2SB 63 1.00	2SC 642A 5.90	2SC 1051 4.40	2SC 1567A 1.10			TA 7150P 4.40	WZ 075 .45	
2SA 721 .59	2SB 64 1.90	2SC 644 .45	2SC 1060 1.40	2SC 1584 8.50			TA 7159P 2.50	WZ 081 .45	
2SA 725 .59	2SB 65 1.30	2SC 645 .70	2SC 1061 1.40	2SC 1586 7.60			TA 7200P 4.60	WZ 192 .45	
2SA 726 .59	2SB 66 1.60	2SC 650 1.30	2SC 1076 39.00	2SC 1624 1.30			TA 7201P 4.60	WZ 260 .45	
2SA 733 .59	2SB 67 1.60	2SC 665H 8.50	2SC 1079 5.90	2SC 1626 1.10			TA 7203P 3.70	WZ 280 .45	
2SA 738 .70	2SB 68 1.60	2SC 668 .45	2SC 1080 4.40	2SC 1628 1.30			TA 7204P 3.40		
2SA 740 2.65	2SB 69 .90	2SC 680 2.80	2SC 1096 1.00	2SC 1647 1.00			TA 7205P 2.90		
2SA 743A 1.60	2SB 70 4.40	2SC 681A 5.80	2SC 1098 1.10	2SC 1667 3.40			TA 7310P 3.95		
		2SC 684 1.10	2SC 1111 3.40	2SC 1669 1.60			TA 78005M 5.80		
		2SC 693B 1.60	2SC 1114 3.70	2SC 1674 .59			TA 78005P 5.80		

PRICES MAY CHANGE WITHOUT NOTICE COD ORDERS WELCOMED

Minimum order \$5.00 Ohio residents add 4% sales tax. Add \$1.00 postage and handling  
Quantity discount prices. Ask For Our Complete Price List. Mfg. inquiries Welcomed  
All parts guaranteed against factory defect

IMMEDIATE DELIVERY  
WITHIN 48 HOURS

## TOLL FREE TELEPHONE

Nationwide 800 543-1607  
Ohio 800/582-1630  
Local 513/874-0220  
874-0223  
Hours: Mon. thru Fri. 10-7 Sat. 11-5

## FUJI-SVEA ENTERPRISE

a division of Fuji Svea Incorporated  
Dept. of Radio Electronics  
P.O. BOX 40325 CINCINNATI, OHIO 45240  
TELEX-214732

CIRCLE 7 ON FREE INFORMATION CARD

www.americanradiohistory.com

AUGUST 1978

# quantities of quality

## MEET THE ECONORAM FAMILY . . .

These static memory kits (one for the H8 buss, all others S-100 compatible) deliver outstanding performance at prices even the dynamics can't match. What others consider "extras" we consider necessities, such as full buffering on all lines, reliable DMA, sockets for all ICs, gold-plated card fingers, prime ICs . . . and all the other signs of quality that make up an Econoram. **No matter what machine you use, we want to be your memory supplier; and we know the best way to do that is to offer a superior product at the lowest possible price.**

### NEW! 16K x 8 ECONORAM IV™ KIT (\$329)

Guaranteed current consumption under 2000 mA. Manual write protect switches for 4K blocks; use with or without phantom line. Fully static. Comes with sockets and bypass caps soldered in place for easy assembly. Add \$35 for assembled/tested.

### NEW! 24K x 8 ECONORAM VII™ KIT (\$490)

Our densest board is your best value in 24K memory. Current consumption under 2500 mA; configured as two 4K blocks and two 8K blocks with independent manual write protect switches for each block. Use with or without phantom lines. comes with sockets and bypass caps soldered in place for easy assembly. Add \$35 for assembled/tested.

### 8K x 8 ECONORAM II™ KIT (\$135)


A truly cost-effective package that has drawn raves from both owners and reviewers (see the 1/78 Kilobaud for an example). If you have the space in your motherboard, there's no better way to get 24K of memory than taking advantage of our quantity offer (3 kits for \$375). Add \$20 to single kit price for assembled/tested.

### H8 COMPATIBLE ECONORAM VI™ KIT (\$235)

12K x 8 for the H8, with the same features that have made our S-100 boards so popular. Additionally, all sockets and bypass capacitors are already soldered in place so you can get right into the best part of kit building.
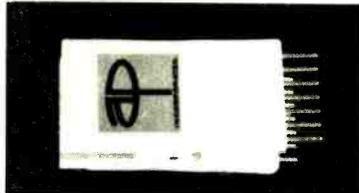
### TRS-80 16K CONVERSION KIT

This kit contains 8 uPD416 1x16K dynamic memories and instructions on converting your 4K TRS-80 to a 16K machine. You could pay up to \$290 elsewhere, but our kit is only \$190!



**SOMETHING TO MAKE LIFE EASY:** We carry AP test clips for both 14 pin and 16 pin ICs. Gold plated wiping action; sturdy pins for scope probes; also removes ICs from sockets without damage. Model TC-14 (14 pin): \$4.50; Model TC-16 (16 pin): \$4.75. We also carry the A.C.E. 201K breadboarding kit (with 1,032 solderless plug-in tie point capacity) for only \$24.95.

## MORE? Send for our flyer

TERMS: Please allow up to 5% for shipping; excess refunded. Add \$1 handling for orders under \$10. Cal res acid tax. COD OK with street address for UPS. For VISA® /Mastercharge® orders call our order desk (24 hrs) at (415) 582-0836. Prices good through cover month of magazine.

# GODBOUT

BILL GODBOUT ELECTRONICS  
BOX 2355, OAKLAND AIRPORT, CA 94614

CIRCLE 43 ON FREE INFORMATION CARD

# TAPE DISCOUNTS

Minimum order 1.0 tapes



### CASSETTES

TDK-DC-45	1.09
TDK-DC-60	1.29
TDK-DC-90	1.69
TDK-DC-180	2.99
TDK-SAC-60	1.99
TDK-SAC-90	2.99
TDK-ADC-80	1.79
TDK-ADC-90	2.89

### 8-TRACK

TDK-45 D 8tk	1.59
TDK-90 D 8tk	1.99
TDK-45 AD 8tk	2.29
TDK-90 AD 8tk	2.99

### OPEN REEL

TDK-L 1800	5.29
TDK-S 1800	4.29



### CASSETTES

C-60 Performance	1.10
C-90 Performance	1.99
C-120 Performance	2.99
C-90 Studio	2.99
C-90 Chrome	2.99

### 8-TRACK

45 BT Performance	1.89
64 BT Performance	2.19
90 BT Performance	2.99

**OUR BRAND! C-90 CASSETTES, 3 for \$1.59; 40 Min BTR CART. - 99c ea.**

LIFETIME PRODUCT GUARANTEE!

**ORDER NOW!** Orders shipped within 1-3 days  
Please add \$2.00 for shipping and handling per order N.Y.S. Res. add sales tax. NO C.O.D.'s.  
FREE CATALOG!


## CONSUMERS CO

P.O. Box 550 Dept. RE-8

Mt. Vernon, N.Y. 10551 Phone: (914) 664-2909

CIRCLE 80 ON FREE INFORMATION CARD

## OP-AMP and PARTS BOARD

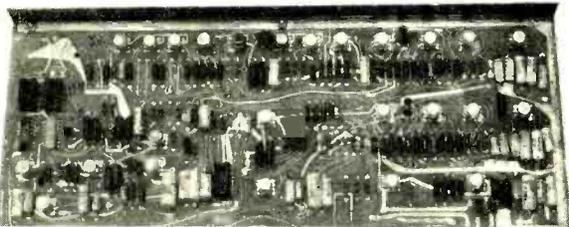

This giant board, 5"x13 1/2", is loaded with OP-AMPS. There is a minimum of 24 Type 741 op amps, plus over 50 1% resistors, plus 13 tantalum caps, over 30 tubular caps, many 1/4 watt resistors, diodes and much more. A bonanza of modern parts.  
STOCK NO. 6754R \$3.95 ea. 3/10.00

## INDICATOR LIGHT BOARD



Indicator board contains 7 grain of wheat incandescent bulbs, 3 to 5 volts @ 50 ma. Each lamp is in a socket, and has a colored lens. Each lamp has 2 2N3904 drivers, plus other parts.

STOCK NO. 6810R Indicator board. \$2.00 ea. 3/5.00

## UNIVERSAL TRANSFORMER

115 V primary, Sec. 1—12.6V @ 1.0 A. ct. Sec. 2—33.5 V, tapped @ 13.1 V @ 1.0A. Sec. 3—140V @ 100 ma. 2Lbs. 4"x2"x2 3/4".  
STOCK NO. 6772R \$2.95 ea. 2/5.00

## DELTA ELECTRONICS

P.O. Box 2, 7 Oakland St.  
Amesbury, Mass. 01913  
617-888-4705

### RETAIL OUTLET

ATLANTA, GA. DELTA ELECTRONIC HOBBIES  
5151 Buford Hwy. Doaraville, (Atlanta) Ga. 30340

Our new Giant 120 page catalog is ready. Send for it.



F. Reichert Sales  
1110 E. GARVEY AVE.  
W. COVINA, CA 91790

- \$20 MINIMUM ORDER
- FREE UPS DELIVERY ON U.S. ORDERS ONLY OR BY SURFACE MAIL IF SPECIFIED
- MONEY BACK GUARANTEE (MOS & LED DEVICES EXCLUDED)
- UNDER 8 HOUR PROCESSING ON MONEY ORDERS & CASHIERS CHECKS
- SORRY! NO COD'S, P.O.'S, OR CREDIT CARDS
- CALIF. RES. ADD 6% SALES TAX
- CANADA PUERTO RICO & U.S. POSSESSIONS ADD U.S. \$3.50 ALL OTHERS ADD U.S. \$7.00
- U.S. FUNDS ONLY!

## CHOICE CHIPS

ADD 25c FOR SPEC. SHEETS

LM100	2.37V ADJUSTABLE VOLTAGE REGULATOR	\$4.95
LM317	1-1/2 AMP 1.2-37V THREE TERMINAL ADJUSTABLE VOLTAGE REGULATOR	\$4.95
LM358	LOW POWER DUAL OPERATIONAL AMP	\$1.75
LM384	5 WATT AUDIO AMPLIFIER	\$1.60
LM387	LOW NOISE DUAL PREAMPLIFIER	\$1.75
LM390	LOW VOLTAGE 1W AUDIO AMPLIFIER	\$1.90
LM703	LOW POWER DRAIN RF/IF AMPLIFIER	\$0.89
LM733	DIFFERENTIAL VIDEO AMPLIFIER	\$1.95
LM1414	DUAL DIFFERENTIAL VOLTAGE COMPARATOR	\$2.95
LM1496	BALANCED MODULATOR/DEMODULATOR	\$1.95
LM1830	FLUID DETECTOR (PRESENCE, ABSENCE, LEVEL)	\$1.98
LM2907	FREQUENCY TO VOLTAGE CONVERTER	\$1.95
LM2917	FREQUENCY TO VOLTAGE CONVERTER WITH HI GAIN OP AMP COMPARATOR	\$1.95
MMS5330	4 1/2 DIGIT DVM LOGIC BLOCK	\$7.95
MMS5104	TV GAME CLOCK GENERATOR	\$2.95
MMS7100	COLOR TV 3 GAME CHIP	\$7.95
LM1889	TV VIDEO MODULATOR	\$5.75
TBA 820	2W MONOLITHIC AUDIO AMPLIFIER	\$1.95
ULN 2277P	STEREO AMPLIFIER 2W PER CHANNEL	\$1.95

FOR A MUCH WIDER SELECTION YOU MAY ALSO ORDER FROM OUR JUNE AND JULY ADS IN RADIO ELECTRONICS AND BYTE MAGAZINE

**DC-DC UP CONVERTER SWITCHING REGULATOR I.C.**  
BUILD YOUR OWN MICRO MINIATURE CONVERTER. \$149  
MINI DIP PKG WITH DATA

HEWLETT — PACKARD  
HI-INTENSITY MICRO LEDS  
SIOE STACKABLE AXIAL LEAD  
RED CLEAR YELLOW  
6/99c 5/99c 4/99c

**CARBIDE DRILL BITS for P.C. BOARD WORK**  
SIZES FROM NO 55 TO NO. 70  
OUR MIX 5/\$7.49 10/\$12.49

SUBMINIATURE	SOLAR CELLS
CRYSTAL FILTER	2 x 2 cm
455 KHZ WITH DATA	130 ma
\$2.95	\$159 ea.
	10/\$99.00

**I.C. SOCKETS**  
LOW PROFILE SOLDERTAIL

	GOLD INLEAD	TIN
8 PIN	10/\$1.59	10/\$1.35
14 PIN	10/\$1.89	10/\$1.49
16 PIN	10/\$1.99	10/\$1.59
18 PIN	5/\$1.49	5/\$1.29
22 PIN	5/\$1.69	5/\$1.49

**SUMMER SPECIALS**

24 PIN	5/\$1.09	5/\$0.89
28 PIN	5/\$1.19	5/\$0.99
40 PIN	4/\$1.19	4/\$0.99

PRICES & AVAILABILITY SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 48 ON FREE INFORMATION CARD

CIRCLE 34 ON FREE INFORMATION CARD

# ADVANCED COMPUTER PRODUCTS

## \$100 PRODUCTS

### LOGOS I 8K STATIC RAM

- ★ Low Power
- ★ Selectable Memory Protect
- ★ Totally Buffered
- ★ Battery Back-up
- ★ Address on I/O boundary
- ★ Requires no front panel
- ★ No wait states



### ASSEMBLED & TESTED

250ns. 199.95  
450ns. 179.95

### KIT

250ns. 149.95  
450ns. 125.95

**WE OFFER GROUP DISCOUNTS**

Bare PC Board w/Data \$21.95  
Now over 1 year successful field experience  
"Special Offer" Buy (4) 8K 450ns. Kits \$117.00 ea.

### IMS 16K STATIC RAM

- ★ Memory mapping
- ★ Phantom
- ★ Address 16K Bound
- ★ Use with 2 or w/ front panel
- ★ Power 2.1 amps typ.
- ★ Uses 2114

ASSEMBLED & TESTED ONLY  
450ns. \$439.95 250ns. \$495.95

### S-100 32K STATIC RAM

- ★ Address 32K Boundary
- ★ Power 450ms, 2.8 amps typ.
- ★ No wait states on 2MHz
- ★ Fully Buffered
- ★ Phantom can be added
- ★ 2114/TMS4045 or 9135

ASSEMBLED & TESTED KIT  
250ns. \$849.00 250ns. \$740.00  
450ns. \$799.00 450ns. \$700.00  
Bare PC Board w/Data \$59.95  
SPECIAL OFFER  
Kit without Memory only \$99.95. Add  
2114 Memory for \$160.00 per 8K

### PARATRONICS LOGIC ANALYZER KIT

MODEL 100A \$219.95  
(analyzes any type of digital system)  
Trigger Expander Model 10 \$229.00  
Baseplate \$9.95  
Model 10 Manual \$4.95  
Model 150 Bus Grabber Kit \$369.00

### DC HAYES DATA COMMUNICATIONS ADAPTER

★ Telephone/TWX ★ S-100 compatible  
★ Bell 103 freq. ★ Originate & answer mode  
Assembled & Tested \$279.95  
Bare PC Board w/Data \$ 49.95

### DATABASES & MANUALS

NSC TTL Data \$ 3.95  
NSC Linear Data 4.95  
NSC Linear APP/Note I 7.95  
NSC Linear APP/Note II 3.95  
NSC CMOS Data 2.95  
NSC Audio Data 3.95  
NSC Vol. Reg. Data 2.95  
NSC Memory Data 3.95  
NSC MOS/LSI Data 3.95  
NSC Power Transistors 2.95  
Intel Databook 3.95  
Intel MCS85 Manual 7.50  
Intel MCS80 Manual 4.95  
AMD 8080 Handbook 5.95  
AMD Linear Data 4.95  
AMD Schottky Data 4.95

AMI MOS/LSI Data 3.95  
GI MOS/LSI Data 4.95  
Osborne Intro to Micro Vol. I 7.50  
Osborne Intro to Micro Vol. II 7.50  
Osborne Intro to Micro Vol. III 7.50  
Osborne 8080 Programming 7.50  
Osborne 8080 Programming 7.50  
Osborne 8080 Programming 7.50  
TI Power Semis. Data 7.00  
TI TTL Data 6.95  
TI Transistors & Diodes 8.50  
TI Memory Data 3.95  
TI Optoelectronics 3.95  
TI Linear Data 3.95  
TI Buffer Memory 3.95  
TI Interface Data 4.95  
Motorola Semi Data 1, 2, 3 9.95

### Z-80/Z-80A CPU BOARD

★ On board 2708  
★ Power on jump  
★ 2708 included (450ns.)  
★ completely socketed  
Assembled and tested \$185.00  
Kit \$129.95  
Bare PC Board \$ 34.95  
★ For 4MHz Speed Add \$15.00

### TDL COMPATIBLE Z-80 CPU

★ Compatible to TDL ★ Can be upgraded software & hardware for 4MHz operation  
Assembled and tested \$199.95  
Kit \$139.95  
Bare PC Board \$ 34.95

### BYTE USER 8K EPROM BOARD

★ Power on Jump ★ Reset Jump  
Assembled & Tested \$4.95  
Kit \$64.95  
Bare PC Board \$21.95  
Special Offer: Buy 4 kits only \$59.95 each  
NOTE: 2708-6 only \$5.95

### 8080A CPU BOARD

S100 compatible with 8 level Vector interrupt fully socketed.  
Assembled & Tested \$149.95  
Kit \$ 99.95  
Bare PC Board w/data \$ 34.95

### TARBELL FLOPPY INTERFACE

★ S100 Compatible ★ Uses CPM  
★ Jumper Selectable ★ Persci, Shuart, etc  
Assembled and tested \$269.95  
Kit \$179.95  
Bare PC Board \$ 39.95  
NOTE: For CPM Add \$70.00  
Documentation Add \$20.00

### WMC REAL TIME CLOCK

★ S100 Compatible  
★ Two interrupts  
★ Software programmable  
★ 1MHz Crystal Oscillator  
Assembled and tested \$179.95  
Kit \$124.95  
Bare PC Board w/data \$ 29.95

### MICRODESIGN MR-16 2716 EPROM BOARD

(MR-8 Also Available at same price)  
★ Individual Program Address  
★ Uses Low cost 16K TI EPROMS  
★ Optional 1K RAM ★ Phantom-control  
Assembled and Tested \$174.95  
Kit \$99.50

## 6800 DESIGNER BOARDS MODULES PROTO BOARDS

★ Motorola Compatible Modules\*  
MEK 6800 D2 Kit \$235.00  
9600 6800 MPU Module 495.00  
9601 16 slot Mother Bd 175.00  
9602 16 slot Card Cage 75.00  
9603 8 slot Mother Bd 99.00  
9604 System Power Supply 250.00  
9610 Prototype Board 36.00  
9615 4KEPROM Module 250.00  
9620 16 port parallel I/O 375.00  
9626 8K Static RAM 295.00  
9626K 8K Static RAM Kit 225.00  
9630 Extender Card 60.00  
9640 Multiple Turn Prog 395.00  
9650 8 port Duplex Asyn. I/O 395.00  
Mot 43/86 Connectors w/or s/t 5.95  
Mot EVK 99 6800 sub kit 145.00  
AMI EVK 100 Kit 269.95

AMI EVK 200 Kit 449.95  
AMI EVK 300 Assembled 649.00  
EVK Kluge Board 95.00  
EVK 16K Byte Ram Board 75.00  
EVK 6 Slot Motherboard 35.00  
EVK Extender Board 45.00  
EVK Solid Frame Chassis 129.00  
EVK Connectors 6.50  
AMI 6800 Proto Rom 30.00  
AMI 6800 Proto Assembler Rom 30.00  
6800 Tiny Basic Paper Tape 20.00  
6800 Tiny Basic Eprom 125.00

### ZILOG COMPATIBLE BOARDS

Z-80 CPU 395.00  
ZDC Disc Controller 395.00  
MEM 16/65K Memory 595.00

THE FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES NOW LOWERS PRICES EVEN FURTHER!

- 1. Proven Quality** Factory tested products only, no re-tests or fallouts. Guaranteed money back. We stand behind our products.
- 2. Same Day Shipment** All prepaid orders with cashiers check, money order or charge card will be shipped same day as received.

### SUPPORT DEVICES

ADM5114n Processor \$195.00  
ADM517 DMA Controller 71.95  
ADM519 Universal Interrupt 24.95  
8881 (280 Pin) 11.25  
3881 (4 MHz) 14.95  
3882 (280 CTO) 11.25  
3882-4 (4MHz) 14.95  
8207/45138 Decoder 3.25  
8212 8 bit I/O 3.25  
8214 Priority Int. 7.95  
8216 Bus Driver 3.25  
8224 Clock Gen 3.95  
8224-4 (4MHz) 14.95  
8226 Bus Driver 3.95  
8126 Bus Driver 2.39  
8228 Bus Control 8.95  
8238 Sys Conl. 7.95  
8251 Prog. I/O 11.50  
8253 Int. Timer 21.95  
8255 Prog. I/O 11.50  
8257 Prog. DMA 27.95  
8258 Prog. Int. 27.95  
8275 CRT Controller 125.00  
8279 Prog. Keyboard 19.95  
8282 CPU 41.75  
6820 PIA 7.95  
6828 Priority Int. 11.95  
6829 16 Bit x 8 Eprom 12.95  
6800 ACIA 7.95  
6852 Serial Adapter 9.95  
6854 HD46505-CRT Contr. 29.95  
6800 Modem 14.50  
6862 Modulator 17.50  
6866 Dual W.W/S/Osc 8.50  
2350 USRT 4.95  
6880 Bus Driver 2.39  
1824 32 x 8 RAM 29.90  
1826 32 256 x 4 RAM 16.95  
1828 32 x 8 RAM 9.95  
1852 CD 8 bit I/O 10.95  
1856 CD I/O 8.95  
8258 CD I/O 8.95  
6520 PIA 8.95  
6522 Mult. 15.50  
6530 002 15.50  
6530-003 15.50  
6530-004 15.50  
6530-005 15.50  
3851 FB Prog. Store 14.95  
3853 FB Memory I/O 14.95

### MICROPROCESSORS

280 \$21.95  
280A  
F-8 (280 Pin) 19.95  
285 24.95  
CD 1802 19.95  
8008A 19.95  
8008B 19.95  
8008-1 14.95  
2901 21.95  
2901A 29.95  
1MS 9900JL 89.95  
CP1800 39.95  
6502 19.95  
IM6400 29.95  
6800 19.95  
8002P 32.95

### STATIC RAM HEADQUARTERS

27102 450ns	1.24	25-99	100
27102 250ns	1.30	15	11.95
27102	1.59	15	14.45
2102	1.25	115	11.00
81102APC	1.75	115	16.50
2111-1	4.10	395	3.75
2111-1	3.75	395	3.50
2111-2	4.25	410	3.95
2101-1	2.90	270	2.55
2113-3 300ms	9.95	975	8.25
2113-1 450ns	9.95	975	8.25
IMS4044	9.95	975	8.25
TMS4045	9.95	975	8.25
EMM400A	12.50	975	9.25
EMM402A	7.95	725	6.25
5101CE	7.95	795	7.25
upda10 (4200)	1.30	1025	2.25
AMD1940/41	10.95	1025	9.25
AMD1930/31	12.95	1115	10.25
F5C 4650/4616K CCD Only 518.85			
1101	1.95	175	1.25
P2125/93425 (45 ns)	7.95	735	7.25

### SOCKETS

8 Pin ww 32 14 Pin S/T 20  
14 Pin ww 37 16 Pin S/T 22  
16 Pin ww 38 18 Pin S/T 31  
18 Pin ww 80 22 Pin S/T 35  
22 Pin ww 90 24 Pin S/T 41  
22 Pin ww 93 28 Pin S/T 49  
8 Pin S/T 17 10 Pin S/T 63

### CONNECTORS

6 Pin Single S/E 1.49  
15/30 Dual S/E 1.95  
19/36 Dual S/E 2.35  
22/44 Dual S/E 2.95  
40/80 W/W 4.75  
43/86 Dual W/W/S/T 6.95  
50/100 MSAI W/W 4.95  
50/100 MSAI S/T 4.95  
50/100 MSAI W/W/S/T 5.95  
MSAI Card Guides 4/1.00

26 Pin D Subminiature  
DB25P 3.25  
DB25S 3.75  
DB25 1.75  
Set w/Hood 6.50

### NEW CTS DIPSWITCHES

CTS206 \$1.75 CTS208-8 \$1.95  
CTS206-6 \$1.75 CTS209-10 \$1.95  
CTS207-7 \$1.75

We also stock full of 7400, 741LS, 74L Linear and CMOS. Send for pricing or use our competitors STD catalog pricing.

### PCB PROGRAMMABLE CHARACTER GENERATOR

The hottest version of STARWARS available  
S-100 Compatible 2MHz Kit with Obsolete code only \$169.95

### NAKED PCB BOARD SALE S-100

Z-80 CPU (THACA) 34.95  
Z-80 CPU (TDL comp.) 34.95  
8080A CPU 34.95  
8K Static Logos 21.95  
8K EPROM Bus Driver 21.95  
32 Static S-100 59.95  
Tarbell Floppy I/O 29.95  
Vector Cassette 19.95  
Vector 8000 Photo 27.95  
ACP Extender w/conn 34.95  
RealTime Clock 15.95  
1771 13 Slot Mother Bd 33.00  
S-100 8 Slot Mother Bd 34.95  
Vector 8003 11 Slot M Bd 29.95  
SSM Video I/O 27.95  
SSM I/O Parallel I/O 27.95

### UV "E" Prom Eraser

Model 5-111 \$59.50  
Backed by 43 years UV experience  
Model 5-112 \$219.95  
Professional Industrial Model

### ATTENTION KIM USERS

ATTENTION KIM USERS  
KIM2 Expansion to S-100 125.00/80.00  
KIM2 Expansion to S-100 125.00/80.00

### ATTENTION PET USERS

ATTENTION PET USERS  
PET Expansion to S-100 105.00/80.00  
PET Expansion to S-100 105.00/80.00

### ATTENTION APPLE II USERS

ATTENTION APPLE II USERS  
Apple II Expansion to S-100 1175.00/975.00  
Apple II Expansion to S-100 1175.00/975.00

### ATTENTION APPLE II USERS

ATTENTION APPLE II USERS  
Apple II Expansion to S-100 1175.00/975.00  
Apple II Expansion to S-100 1175.00/975.00

### A/D CONVERTERS

A/D CONVERTERS  
8/100 8 bit Binary 13.50  
8/101 10 bit Binary 22.00  
8/102 12 bit Binary 32.95  
8/105 12 bit LS 42.95  
8/100A 10 bit Binary 13.50  
8/100B 10 bit Binary 13.50  
8/100C 10 bit Binary 13.50  
8/100D 10 bit Binary 13.50  
8/100E 10 bit Binary 13.50  
8/100F 10 bit Binary 13.50  
8/100G 10 bit Binary 13.50  
8/100H 10 bit Binary 13.50  
8/100I 10 bit Binary 13.50  
8/100J 10 bit Binary 13.50  
8/100K 10 bit Binary 13.50  
8/100L 10 bit Binary 13.50  
8/100M 10 bit Binary 13.50  
8/100N 10 bit Binary 13.50  
8/100O 10 bit Binary 13.50  
8/100P 10 bit Binary 13.50  
8/100Q 10 bit Binary 13.50  
8/100R 10 bit Binary 13.50  
8/100S 10 bit Binary 13.50  
8/100T 10 bit Binary 13.50  
8/100U 10 bit Binary 13.50  
8/100V 10 bit Binary 13.50  
8/100W 10 bit Binary 13.50  
8/100X 10 bit Binary 13.50  
8/100Y 10 bit Binary 13.50  
8/100Z 10 bit Binary 13.50

### TV INTERFACES

TV INTERFACES  
Pre-Viter 6.50  
TV 1 Viter Interface 8.95  
Picks & Trout TV 20.00

### WAVEFORM GENERATORS

8038 Function Gen 3.95  
MC-4024 VCO 1.95  
LM566 VCO 1.75  
XR2206 Function Generator 5.25

### CHARGE COUPLED DEVICES

16K CCD First time offered Fairchild 460 CCD  
16K Memory now you can experiment with CCD technology at a reasonable price. 17 page Application Note supplied with each order. Quantity Limited.  
**\$16.95 each (reg. 43.00)**

### CRYSTALS

Microprocessor Timexess TV Gama  
Frequency Price Frequency Price  
1.0MHz 58.85 6.0MHz 4.95  
1.8432 8.95  
2.0MHz 5.95 6.5536 4.95  
2.01MHz 2.95 10.0MHz 4.95  
2.297152MHz 4.95 18.432MHz 4.95  
2.4576MHz 5.95 14.3184 4.95  
3.279845MHz 1.50 18.0MHz 4.95  
4.0MHz 4.95 18.432MHz 4.95  
4.194304MHz 5.95 20.0MHz 4.95  
4.91520MHz 5.95 21.84MHz 5.95  
5.0MHz 4.95 27.0MHz 4.95  
5.0688 4.95 36.0MHz 5.95  
5.7143MHz 5.95 48.0MHz 5.95  
100K 12.95

### DISPLAYS/OPTO

DL 704/707/CC/CA 300 1.25  
DL2355 CC 300 95  
DL 500/507/CC/CA 500 1.35  
DL 500/510 CC/CA 500 99  
DL 800/807 CC/CA 800 2.50  
Bowmar 9 digit bubble 4.95  
FSC 8024 4 digit CC 800 4.95  
HP1740 HEX Display 19.95  
TL 305 5 4 7 Array 4.95  
TL 306 7 seg w/logic 8.95  
TL 308 7 seg w/logic 9.25  
TL 309 7 seg w/logic 7.95  
TL 311 HEX Display 9.25  
M-1002 12 auto clock 17.95  
MA-1002 4 digit clock module 9.95  
MA-1010 4 digit clock module 9.95  
NSM 2107/4 dual CC/CA 300 2.50  
NSM 783/784 dual CC/CA 700 2.50  
MCP 2 Opto Isolator 1.89  
MCP 2 Opto Isolator 1.89  
Red Led's 165 Dia 5/100  
Green/Yellow 4/100  
HP 50827731 7 seg 90

### MONTHLY SPECIALS

14 Pin S/T sockets 1000 pcs 10  
16 Pin S/T sockets 1000 pcs 11  
22 Pin S/T sockets 1000 pcs 12  
FSC460/464 16K CCD's 8 for 200.00  
AMD 9140CCD Static Ram 10.95  
4118-16 16K DCD's 8 for 200.00  
1488 or 1489 HS232 Driver 1.25  
8130 or 8131 1.95  
8813 or 8835 1.99  
74567 or 74358 6/500  
7451 162/53 19.25  
8726 Bus Driver 2.39  
78L05 Regulator 21.00  
MC172 OpAmp 2.95  
2510A Shift Register 2.95  
2515A Shift Register 2.95  
M5010 Shift Register 1.95  
LM7808 14 Converter 1.10  
DS0020 40 Clock Div 1.95  
DS0020C Clock Divider 2.50  
MFE D201 Bidirect. Register 3.49  
100M3A Shift Register 2.95  
9368

### NEW 1978 CATALOGUE

SEND 25¢ POSTAGE

### DISCOUNT COMPUTER CORNER

Discount Computer Cash Credit Card  
Apple II/16K \$1125.00 \$1155.00  
TEI P2708 4599.00 4699.00  
TEI MCS2-16 482.00  
Cromemco Z-2 536.00 551.00  
Cromemco SYS III 5499.00 5561.00  
Datacube II 1825.00  
Perisc 277 1230.00 1266.00  
Shugart HD30B1 536.00 551.00  
Perisc FD200 359.00 362.00  
MFE D201 730.00 744.95  
Shugart 500 369.95  
Horizon 1439.00 1479.00  
North Star 589.00 617.00  
Low Cost S-100 Bus 119.00 129.00  
ADM-3 Assem 849.95 865.00  
Socac IQ 120 895.00 945.00  
Intelligence Mod 43 119.00 129.00  
AMI 100 Contact Sales Dept 599.00 617.00  
Qwert 2708 275.00 288.00  
Pennsylvania Modem 129.95 299.95  
Cromemco 16K Ram 448.00 462.00  
Huzline 1500 1175.00 1185.00  
Oxkida 110 w/FR232 1725.00 1736.00  
Challenger 12-12 w/FR232 2795.00 2844.00  
KIM 6800 D2 Kit 235.00 Same  
KIM 1 6502 245.00 Same  
Intercept Kit 6100 281.00 Same  
Technico 9900 Kit 299.00 Same  
RCA VPI Corpac 275.00 Same  
AMI EVK 99 145.00 Same

P. O. BOX 17329 Irvine, California 92713 New Phone (714) 558-8813  
TWX: 910-595-1565

## STATE OF SOLID STATE

continued from page 77

one REF-02 as the sensor and a second one operated at constant temperature to generate  $V_{REF}$ .

The calibration procedure begins by measuring  $V_{TEMP}$  and the ambient centigrade temperature corresponding to that  $V_{TEMP}$  reading. A calibration ratio,  $r$ , is calculated from  $V_{TEMP}/(T + 273)$ , which equals  $R_a || R_b / (R_c + R_s || R_b)$ . The numbers in the previous example are  $T = 25^\circ\text{C}$ ,  $S = 10 \text{ mV}/^\circ\text{C}$  and  $V_{TEMP} = 632 \text{ mV}$ , so that  $r = 0.2121$ . Precisely 100 mV is applied to  $V_{OUT}$  with the power

off and  $V_{REF}$  shorted to ground. Variable resistor  $R_{bp}$  is adjusted so that  $V_B = r \times 100 \text{ mV}$  or  $21.21 \text{ mV}$ . Now the power is turned on and  $R_p$  is adjusted so that  $V_{OUT}$  equals  $0.25 \text{ volt}$ . For this procedure the voltmeter used to measure the temperature is convenient for setting up the 100-mV calibration source.

The thermometer is discussed in detail in "Application Note AN-18," Precision Monolithics, Incorporated, 1500 Space Park Drive, Santa Clara, CA 95050.

### Second-generation MC6800 MPU

Previously, improvements that were made to the MC6800 increased its fre-

quency limits and extended its temperature range. Now, a sufficiently major architectural change has been made that warrants providing the device with a new number.

The MC6802 is completely software- and hardware-compatible with all other members of the M6800 microprocessor family. The MC6802 is an MC6800 with an internal clock oscillator and driver, plus 128 bytes of RAM occupying the first 80 (0000 to 007F) memory addresses.

The MC6802 is available in a plastic package in quantities of 25 for \$22 each. Motorola Semiconductor Products, Inc., Box 20912, Phoenix, AZ 85036.

### Doppler detector diodes

Parametric Industries has announced the PD422 Doppler detector diodes for use in police radar systems and such motion-detection devices as braking systems and intrusion alarms. The diodes are glass encapsulated, hermetically sealed and encased in ceramic for high burnout resistance and high sensitivity. The operating frequency of the PD422 is  $10.525 \text{ GHz} \pm 250 \text{ MHz}$ , and the sensitivity is  $-60 \text{ dBm}$ . The PD0919, which operates at  $24.150 \text{ GHz} \pm 250 \text{ MHz}$ , is also available.

For more information, write Parametric Industries, Inc., 742 Main Street, Winchester, MA 01890. R-E

## Why is this the LARGEST SELLING low cost COUNTER KIT?

This counter is such a great seller because people like you have found that, feature for feature, the CT-50 gives you more for your money. Advanced LSI and CMOS circuitry has; lowered power consumption, increased performance, and reduced cost. Complete push button operation makes using the CT-50 a snap, and automatic decimal point positioning gives you quick, reliable readings. Battery operation is also possible because the CT-50 runs equally as well on 12VDC as it does on 110VAC. For ultra-accuracy we offer the CB-1 color burst adapter, it locks the CT-50's internal crystal to the television networks color standard for .001 ppm accuracy! Why sacrifice performance by using another counter when you can get professional quality at the unheard of price of \$89.95? Order yours today!



**SPECIFICATIONS**  
Sensitivity: less than 10 mV  
Frequency range: 5 Hz to 60 MHz, typically 65 MHz  
Gate time: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale  
Display: 8 digit red LED, 4" height  
Accuracy: 2 ppm, internal TCXO standard  
Input: BNC, 1 megohm direct, 50 Ohm with prescale option  
Power: 110 V ac 5 Watts or 12 V dc @ 300 400 ma  
Size: Approx. 6" x 4" x 2", high quality aluminum case

CT 50.60 MHz Counter Kit ..... \$89.95  
CT-50 w/ 60 MHz Counter Wired & Tested ..... \$159.95  
CT-600, 600 MHz prescaler option for CT-50, add \$29.95

### MINI-KITS

#### FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added super-sensitive mike preamp.  
FM-1 - \$2.95 FM-2 - \$4.95

#### SUPER-SLEUTH AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.  
Complete Kit, BN-9 ..... \$4.95

#### COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.  
Complete Kit, ML-1 ..... \$7.95

#### TONE DECODER KIT

A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.  
Complete Kit, TD-1 ..... \$4.95

#### LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.  
Complete Kit, BL-1 ..... \$2.95

#### POWER SUPPLY KIT

Complete triple regulated power supply provides variable +15 volts at 200 mA and  $\pm 5$  volts at 1 Amp, 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8V at 1 Amp and 18 to 30 VCT.  
Complete Kit, PS-3LT ..... \$6.95

#### SIREN KIT

Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.  
Complete Kit, SM-3 ..... \$2.95

#### VIDEO MODULATOR KIT

Converts any TV to video Monitor. Super stable tunable over Ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market.  
Complete Kit, VD-1 ..... \$6.95

## SIX DIGIT 12/24 HOUR CLOCK KIT

Here's a clock you can be proud of. The best looking, most complete kit on the market! Features include: time set push-buttons, jumbo .4" readouts, and extruded aluminum case available in 5 colors. All parts included. Colors: gold, silver, bronze, black, blue (specify)

Clock Kit, DC-5 ..... \$22.95 Alarm Clock, 12 Hr., DC-8 ..... 24.95  
Mobile Clock, DC-7 ..... 25.95 Clock with HAM ID timer DC-10 ..... 25.95

Assembled and tested clocks available, add \$10.00 to Kit price.

### 600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mV sensitivity. Specify -10 or -100. Wired, tested, PS-1B ..... \$59.95  
Kit, PS-1B ..... \$44.95

### TV TYPEWRITER KIT

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are: single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, power-on initialization, full 84-character ASCII display, block-type, search cursor, keyboard/computer control backspaces, forward spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard 75 ohm composite video.

TH3216 Kit, Assembled and Tested ..... \$149.95  
TH3216, Kit ..... 239.95  
VD-1 Video to RF Modulator Kit ..... 6.95

ICs	LINEAR	REGULATOR	TRANSISTORS
5314 Clock	\$2.95	555 ..... \$ .50	78MC ..... \$1.49
7001 Clock	6.95	556 ..... 1.75	309H ..... 89
5369 Cno	1.95	566 ..... 1.49	309H ..... 89
7447	79	567 ..... 1.49	340K ..... 12.99
7473	.35	1458 ..... 50	7805 ..... 89
7475	.50	LED DRIVER ..... 7812	89
7490A	.55	75491 ..... 50	7815 ..... 89
74143	3.50	75492 ..... 50	7818 ..... 89

ORDER BY PHONE OR MAIL  
Satisfaction guaranteed or money refunded. Add 5% for shipping and insurance. COD add \$1.00. Orders under \$10.00, add \$3. NY residents add 7% sales tax. Minimum order \$6.00.

**ramsey electronics**

BOX 40728 ROCHESTER, NY 14610 (716) 271-6487



### CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

**FEATURES:**  
• 6 Digits, 5" High LED ..... 12/24 Hour Format  
• Calendar shows mo./day ..... 5 minute button  
• True 24 Hour Alarm ..... 7001 chip does all!  
• Battery back up with built-in on chip time base.

Complete Kit, less case DC-9 ..... \$34.95

### CAR CLOCK KIT

12/24 Hour 12-Volt AC or DC  
• High Accuracy (1 minute/month)  
• 6 Jumbo 4" LED readouts  
• Easy, no-polarity hookup  
• Display blanks with ignition  
• Case mounting bracket included  
• Super instructions  
Complete Kit, DC-11 ..... \$27.95  
Auto dimmer for DC-11 ..... \$2.50

741 OP AMP SPECIAL  
Prime, Mini-dip 10/\$2.00.

## AMAZING EARADIO

THIS IS PROBABLY THE WORLD'S SMALLEST RADIO. IT WEIGHS ONLY 1/2 OUNCE AND IS WORN BEHIND THE EAR. CONTAINS AN IC AND SEVERAL DISCRETE DEVICES TO GIVE AN EQUIVALENT OF 12 TRANSISTORS. THE RADIO HAS A 1.5V DESIGN OPERATING FROM 1 STANDARD SIZE 1.5V HEARING AID BATTERY (INCLUDED). IT PROVIDES GOOD VOLUME TO EARPHONE ON SEVERAL STATIONS IN METROPOLITAN AREAS. DOESN'T REQUIRE ANY ANTENNA, GROUND OR OTHER ADDITIONAL WIRES - FULLY SELF-CONTAINED & TUNABLE. SIZE: 1 1/8" x 1 1/4" x 3/8".  
\$5.95

**Crystal 14.04 Mhz Oscillator**  
IC clock oscillator  
C23289 \$1.98  
C1038 SCR 200V .8 amp C23083 8 for \$1.00

LEAD CRYSTAL WATCH DISPLAY ..... \$1.25  
MOTOROLA 2N25 ..... \$1.00  
SLIDE SWITCH ASSEMBLY ..... \$1.00  
MICRO-MINIATURE ROTARY SWITCH 4 POLE ..... 79¢  
LASER 200 VOLT 3 AMP ..... \$1.00

### Electronic Warning Flasher Kit

This battery operated device continuously emits bursts of intense light. Great safety device for bicycle riders, skiers, hikers, boaters & campers. Comes complete w/ all electronic parts, quality glass epoxy P-C board & easy to understand instructions. Uses high-output xenon flash tubes which flashes 2 times per second when batteries are fresh. Operates continuously for 12 hours on 2 alkaline "C" batteries. You need only to supply the batteries and, if desired, a battery holder & case.  
C23207 \$6.95 (3 for \$18.00)

Strobe Light Kit ..... \$1.00  
6 HV TRIGGER COILS 2 for \$1  
Green Neon Same as NE2 but glows GREEN. Operates on 120V. 6 for \$1.00

PHOTOFLASH CAPS/ CALCULATOR BOARDS  
350 mf 330V/100 ..... \$1.00  
720 mf 360V 150 ..... \$1.50  
1600 mf 360V \$2.25  
WITH DISPLAY LESS KEYBOARD AND CASE (AS IS) \$1.50

STROBE TUBE ASST. Mini prime brand new fac. 100 prime strobe tubes. Assortment of 5 strobe tubes. w/ schematics C23280 \$3.00

MINIATURE REFLECTOR Appx. size 1-7/16" L x 7/8" W x 3/4" D C23227 \$1.00

**CHANEY electronics**  
• Minimum order \$5.00  
• Please include \$1 for postage  
• Visa, MC and COD accepted.  
• Phone orders are welcome.

P.O. BOX 27038, DENVER, CO 80227 Ph: (303) 973-1062  
Send for our FREE GIANT CATALOG of unique items!!!!

# INTERNATIONAL ELECTRONICS UNLIMITED

## TTL - 7400

Buy \$10.00 -any mix- deduct 10%  
Buy \$25.00 -any mix- deduct 15%

7400 .11	7441 .85	7493 .48	74165 .95
7401 .16	7442 .59	7494 .75	74166 .119
7402 .14	7443 .65	7495 .75	74170 .190
7403 .14	7444 .73	7496 .75	74173 .149
7404 .16	7445 .65	74100 .115	74174 .119
7405 .19	7446 .81	74107 .37	74175 .95
7406 .29	7447 .59	74121 .37	74176 .84
7407 .28	7448 .79	74122 .38	74177 .84
7408 .22	7450 .17	74123 .45	74180 .95
7409 .17	7451 .20	74125 .54	74181 .230
7410 .16	7453 .20	74126 .58	74182 .85
7411 .25	7454 .20	74132 .75	74185 2.20
7413 .43	7460 .20	74141 .85	74190 .125
7414 .65	7464 .35	74145 .90	74191 .115
7415 .25	7465 .35	74148 .85	74192 .89
7416 .35	7470 .38	74150 .98	74193 .85
7417 .35	7472 .35	74151 .88	74194 .115
7420 .16	7473 .35	74153 .60	74195 .74
7423 .37	7474 .31	74154 .120	74196 .98
7425 .35	7475 .49	74155 .75	74197 .95
7426 .22	7476 .34	74156 .75	74198 1.69
7427 .35	7483 .68	74157 .85	74199 1.69
7430 .20	7485 .88	74158 1.39	74200 3.95
7432 .23	7488 .38	74160 1.23	74219 .79
7437 .25	7489 2.25	74161 .95	
7438 .25	7490 .43	74162 1.39	
7439 .50	7491 .75	74163 .95	
7440 .15	7492 .48	74164 .95	

## TTL - 7400

tested and passed logic test-  
not full parametric specs  
minimum 10 pcs or \$1 per item

7400 .03	7460 .05
7401 .07	7472 .12
7402 .05	7473 .12
7403 .05	7474 .10
7404 .06	7476 .12
7405 .06	7483 .18
7406 .09	7485 .22
7407 .09	7486 .12
7409 .07	7491 .20
7410 .05	7493 .14
7416 .12	7495 .20
7420 .06	74100 .40
7423 .12	74107 .12
7425 .12	74123 .18
7426 .09	74125 .22
7427 .08	74126 .22
7430 .07	74132 .22
7432 .08	74141 .25
7437 .07	74145 .25
7438 .07	74150 .40
7440 .05	74151 .20
7441 .30	74153 .15
7442 .20	74154 .40
7443 .20	74163 .35
7444 .20	74164 .35
7445 .20	74177 .25
7446 .30	74180 .25
7448 .30	74182 .25
7450 .06	74191 .30
7451 .07	74192 .20
7453 .06	74194 .28
7454 .05	74195 .18

MAN 5	.27" Green CA LHD	.99
MAN 8	.27" Yellow CA LHD	.49
MAN 66	.60" Red CA LHD	1.19
MAN 72	.30" Red CA LHD	.59
MAN 82	.30" Red CA LHD	.99
DL 702	.30" Red CC LHD	.79
DL 707	.30" Red CC RHD	.79
MAN 461D	.40" Orange CC RHD	.59
MAN 666D	.56" Orange CA RHD	.59
DL 10A	.27" Red CA LHD	.99
NSN 74R	.30" Red CC RHD	.69
MAN 6610	2 Dig .56" Orng CA RHD	.69
MAN 6630	1-1/2 Dig .56" Orng CA RHD	.59
MAN 6650	1-1/2 Dig .56" Orng CC RHD	.59
MAN 6710	2 Dig .56" Red CA RHD	.69
MAN 6730	1-1/2 Dig .56" Red CA RHD	.59
MAN 6740	2 Dig .56" Red CA RHD	.69
MAN 6750	1-1/2 Dig .56" Red CC RHD	.59
OL 33B	3 Dig .17" Red CC	.29
OL 33B	2 Dig .17" Red CC	.49
NSN 33	3 Dig .17" Red CC	.39
HP 5082	4 Dig .11" Mag. RHD	.39
HP 5082	5 Dig .11" Mag. RHD	.49
SP425-09	9 Dig Gas Discharge	.69
Calc Disp	9 MAN 3s on board Red	.79
TI 434	9 Dig Red	.49

## JUMBO LED White- red light

14/\$1.00 150/\$10.00

2510	Dual 50 bit Shift Reg.	.95
2511	Dual 100 bit Shift Reg.	.95
2518	Hex 32 bit Shift Reg.	1.25
2522	Dual 132 bit Shift Reg.	.95
MM5016	50D/512 bit Shift Reg.	.95
SL-5-4025	Quad 25 bit Shift Reg.	.59

### BEZELS - with red filters

140-2	cut-out 1.125" x 2.375" max .062" panel thickness	\$1.75
140-4	cut-out 1.160" x 4.375" max .125" panel thickness	\$2.75

### Silicon SW diode assorted 400 mw

1M4148 (1N914)	Silicon diode 400 mw	.10
1N3064	Silicon SW diode 400 mw	.10
1N4006	Silicon rect. diode 600V 400mw	.10
Zener diode 400 mw - 2.4V, 3.6V, 5.1V, 6.5V, 8.2V, 10V, 12V, 14.5V, 15V, 120V		.15
Germanium diode 400 mw		.08

2N1132	PNP Gen Purp. Ampl T0-5	.69
2N2218A	PNP Low Power Trans T0-5	.69
2N2222A	PNP Low Power Trans T0-18	.29
2N2223	PNP Low Power Trans T0-5	.69
2N2369	PNP Low Power Trans T0-5	.29
2N2904	PNP Low Power Trans T0-5	.49
2N2905A	PNP Low Power Trans T0-5	.76
2N3227	PNP Low Power Trans T0-18	.69
2N3904	PNP Low Power Trans T0-92	.17
2N3906	PNP Low Power Trans T0-92	.17
SCA 13572	PNP Pwr Trans - 200V T0-5	1.75

## LOW POWER SCHOTTKY 74LS00 PRIME MOTOROLA IC'S

Buy \$15 -any mix- deduct 10%  
Buy \$25 -any mix- deduct 15%

74LS00	\$.18	74LS54	\$.18	74LS157	\$.44	74LS251	\$.66
74LS01	\$.18	74LS55	\$.18	74LS158	\$.53	74LS253	\$.66
74LS02	\$.18	74LS74	\$.26	74LS160	\$.63	74LS256	\$.63
74LS03	\$.18	74LS83	\$.60	74LS161	\$.63	74LS257	\$.44
74LS04	\$.20	74LS85	\$.71	74LS162	\$.63	74LS258	\$.66
74LS05	\$.20	74LS86	\$.30	74LS163	\$.63	74LS259	\$.83
74LS08	\$.18	74LS90	\$.42	74LS165	\$.86	74LS260	\$.18
74LS09	\$.18	74LS92	\$.43	74LS168	\$.84	74LS266	\$.29
74LS10	\$.18	74LS93	\$.43	74LS169	\$.84	74LS279	\$.31
74LS11	\$.18	74LS95	\$.74	74LS170	1.27	74LS283	\$.71
74LS13	\$.31	74LS109	\$.26	74LS173	\$.51	74LS290	\$.56
74LS14	\$.48	74LS112	\$.26	74LS174	\$.51	74LS293	\$.63
74LS15	\$.18	74LS113	\$.26	74LS175	\$.51	74LS295	\$.89
74LS16	\$.18	74LS114	\$.26	74LS181	2.17	74LS298	\$.89
74LS21	\$.18	74LS123	\$.63	74LS190	\$.96	74LS365	\$.36
74LS22	\$.21	74LS125	\$.36	74LS191	\$.81	74LS366	\$.36
74LS26	\$.18	74LS126	\$.36	74LS192	\$.64	74LS367	\$.36
74LS27	\$.18	74LS127	\$.36	74LS193	\$.64	74LS368	\$.36
74LS28	\$.18	74LS132	\$.59	74LS194	\$.66	74LS378	\$.69
74LS30	\$.18	74LS133	\$.18	74LS195	\$.64	74LS390	\$.96
74LS32	\$.18	74LS136	\$.28	74LS196	\$.76	74LS393	\$.96
74LS33	\$.21	74LS138	\$.51	74LS197	\$.76	74LS395	\$.96
74LS37	\$.21	74LS139	\$.59	74LS240	1.39	74LS490	1.78
74LS38	\$.21	74LS161	\$.44	74LS241	1.39	74LS670	1.89
74LS40	\$.20	74LS153	\$.44	74LS242	1.32		
74LS42	\$.60	74LS155	\$.76	74LS243	1.32		
74LS51	\$.18	74LS156	\$.76	74LS244	1.39		

### IC SOCKETS

Low Profile Solder Tail		Wire Wrap	
8 pin	\$.16	24 pin	\$.36
14 pin	.19	28 pin	.44
16 pin	.21	40 pin	.61
18 pin	.28	64 pin	.85

### CERAMIC DISC CAPACITORS - 50V

1pf	22pf	56pf	120pf	270pf	820pf	.022uf
5pf	27pf	68pf	150pf	390pf	.001uf	.030uf
7pf	33pf	82pf	180pf	470pf	.0047uf	.050uf
10pf	47pf	100pf	220pf	600pf	.01uf	.1uf

### CAPACITOR KIT - ceramic disc

50V, 24 values, 10 capacitors each

1pf	33pf	82pf	220pf	820pf	.022uf
5pf	47pf	100pf	270pf	.001uf	.030uf
10pf	56pf	150pf	470pf	.0047uf	.050uf
22pf	68pf	180pf	600pf	.01uf	.1uf

capacitors only...\$11.95

### TANTALUM CAPACITORS - solid dipped

.1u/35V	\$.20	6.8/6	\$.25	15/50	\$.40
.22/35	.20	6.8/16	.25	22/16	.40
.33/35	.20	6.8/50	.30	33/10	.50
1/35	.20	10/16	.30	47/6	.50
2.2/20	.25	10/25	.35	47/25	.55
2.2/35	.25	10/50	.35	56/6	.65
3.3/35	.25	15/10	.35	100/20	1.25
4.7/16	.25	15/20	.35		

### TANTALUM CAPACITOR KIT

solid dipped, 12 values, 5 each

.1u/35V	2.2/35	10/25	33/10
.33/35	4.7/16	15/20	47/25
1/35	6.8/16	22/16	56/6

capacitors only...\$14.95

### ELECTRONIC BUZZER

Miniature, Solid State	
6V 15ma (4-9V oper.)	\$1.29 ea.
12V 15ma (8-20V oper.)	\$1.29 ea.

### TRIMPOT - Single Turn

Mepco - Cermet 8014  
.5w, +100 PPM/°C +20%  
500 ohm, 2K, 10K, 20K, 50K, 100K, 500K, 1M.

1-9	10-99	100-999	1000-
\$.75ea	.69	.63	.57

### TRIMPOT - 25 turn

Bourns - Cermet 3299W  
PC Mount, vert. adj.  
2K, 10K, 20K

1-9	10-999	100-
\$1.65e	1.50	1.35

COMPLETE SATISFACTION GUARANTEED. SHIPMENT TO US AND CANADA PREPAID UNLESS INDICATED OTHERWISE. OTHER COUNTRIES ADD 10% - EXCESS REFUNDED. ORDERS SHIPPED IN 3 WORKING DAYS FROM RECEIPT. MINIMUM ORDER \$10.00. CALIFORNIA RESIDENTS ADD SALES TAX. MINIMUM COD OR CHARGE ORDER \$15.00


**INTERNATIONAL ELECTRONICS UNLIMITED**  
VILLAGE SQUARE, P.O. BOX 449, CARMEL VALLEY, CA 93924 USA  
TELEPHONE 408 659-3171

# SUMMER SALE

LINEAR CIRCUITS  
Buy \$10.00 -any mix- deduct 10%  
Buy \$25.00 -any mix- deduct 15%

LM300H	.71	LM372N	2.93	LM741CN(8)	.32
LM301CN	.29	LM376CN	.59	LM741CN(14)	.32
LM302H	.65	LM380N	1.29	LM741CN	.35
LM303H	.80	LM380N-RGN	.95	LM747H	.79
LM307CN	.26	LM381N	1.75	LM747N	.71
LM307H	.30	LM382N	1.75	LM748CN	.35
LM308H	.89	LM385K	.45	LM74130N	2.80
LM309H	1.05	NE531V	2.90	LM7414N	1.59
LM309K	1.05	NE540L	2.90	LM745CN	1.29
LM310CN	1.07	NE546A	1.09	LM7458CN	.59
LM311CN	.89	NE550A	.75	LM7496N	.89
LM311H	.89	NE555CN	.39	LM7800N	2.48
LM311N	.89	NE556A	.85	ULN2208	.89
LM319N	1.13	LM566G	2.95	ULN2209	.89
LM320K		LM661N	1.25	CA3046	1.19
		5,5,2,12,15	1.29	CA3081	1.49
LM320T		LM665H	1.39	CA3082	1.45
		5,12,15,19	1.19	LM3900N	.49
LM322N	1.59	LM667CN	1.29	LM7524	.79
LM324N		LM672N	1.49	LM7525	.79
(LM2902N)	1.52	LM703H	.59	75451CN	.35
LM339N	1.58	LM703CN	.39	75452CN	.35
LM340K		LM709N	.25	75453CN	.35
		5,6,8,12,15,18,24	1.29	75454CN	.35
LM340T		LM710N	.59	75481N	.71
		5,6,8,12,15,18,24	.79	LM711N	.39
		78-- Equiv.	1.19	LM723H	.55
				LM723N	.52
				LM733H	.79
				LM739N	.99

## BIMBOARD - BREADBOARD KIT

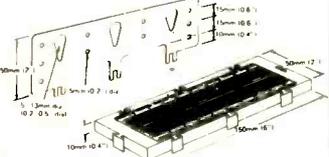

Solderless breadboard section has 94 breadboard strips of sockets each. 2 bus strips of 40 sockets each. Component bracket for switches lamps etc., accepts leads .01" to .035" diameter. \$11.95 ea.

MM5316	Clock Chip	.95
MM5370	Clock Chip	3.95
MM5375AA	Clock Chip	2.95
CT7001	Clock Chip	4.95
2513(caps)	Char. Gen.	3.95
2513(L.C.)	Char. Gen.	3.95
MM1101	256 bit RAM	.65
MM1103	1K RAM	.75
MM5261	1K RAM	.55
MM5262	1K RAM	.95
F93410	256 bit RAM	.95

CLOCK KIT - Mark I  
6 digit clock kit with one PC board. Accommodates MM5314 clock chip and 6 FND 359 displays contains all components except transformer. Includes 3 switches. Board has terminals for remote displays. \$10.95

### Carbon Film ± 5% 1/4 w or 1/2 w 15 ea. of 12 values:

100	220	470	1K	1.5K	3.3K
4.7K	6.8K	10K			

**IT'S NEW!  
FREE!**

**AMP**  
ten pole  
**DIP SWITCH**

WE HAVE ONE THOUSAND OF THESE HIGH QUALITY ROCKER TYPE AMP TEN POLE SWITCHES... SEND AN ORDER FOR \$15 OR MORE-MENTION THIS AD AND YOU GET FREE SHIPPING AND ONE AMP SWITCH... (prepaid and U.S. orders only).....

**BISTABLE RELAY**

SPDT 6VDC 200 OHM COILS  
1 AMP 20 WATT DC CONTACTS  
LONG LIFE (1 X 10<sup>9</sup>) OPER.  
HIGH SPEED (500 HZ)  
HERMETICALLY SEALED  
**\$2.95 ea.**  
3/8x3/8x3/4"

**600 MF  
360V  
PHOTO  
FLASH**  
14 PIN GOLD PLATED  
WIRE WRAP SOCKETS  
THREE LEVEL  
35¢ each  
25 for \$7.50  
100 for \$25.

**SUPER SAVER**  
**VARO SEMICONDUCTOR**  
EPOXY BRIDGE RECTIFIERS  
10 AMP 50V V1048  
**.90 ea. 10 for \$7.50 100-\$65**

**SPECIALS**

- 7402 quad nor gate.....\$ .14
- 7430 eight in NAND gate ... .14
- 7440 dual 4 input buffer ... .14
- 74H20 dual 4 input gate ... .16
- 74L71 and gated MS,FF ..... .20
- 7450 and/or gate ..... .16
- 7475 quad latch ..... .42
- 74L98 4 bit select/storage 1.00
- 74107 dual JK FF ..... .30
- 74178 (8270) shift regist. .30
- LU321 dual JK FF (utilogic) .25
- DM8836 (SP380) bus receiver .95
- 2504T 1024 bit dyn SR..... .80
- CD4025 CMOS gate ..... .19
- D4011 CMOS gate ..... .19
- MC4015 TTL quad latch .... 1.00
- ABM-1 (MPC6070) 1W audio .40
- LM386 lo V audio pwr amp 1.00
- 1N3810 15A 200 stud rect. .75
- 1N5235 6.4V .005% ref. .45
- 16VZ Motorola 16V 1W Zener .15
- 1N4728 3.3V 1W 5% zener .15
- Signal diodes Si or Ge 40/2.00
- 40327 TO-39 NPN 300V 1A 5W .35
- TIP31A (HN) NPN 60V 3A 40W .35
- f706BPC fairchild 5W audio amplifier w/heat sink 14 pin DIP w/staggered leads ..... 1.25
- uA776 programmable op/amp 1.00
- 75451 dual peripheral driver.30
- S270 functional sub for 7400 quad 2 in NAND gate .10
- 747 dual 741 op amp. .... .50
- Carbon film R 1/4W 5% 100/1.49 (specify single value only)
- 2N4304 N channel FET HEP 802 .25
- Complementary 10A TO-220 pwr. transistors 2N6101 & G.E.D45H8 (75-50W) pair 1.25
- Complementary Darlington TO-220 60V 5A 70W MJEL100 MJEL091 ..... pair 1.75

**FOR TRIACS and SCR's**

PULSE TRANSFORMER 1/1 toroid  
DIAC (trigger diode)  
**25¢ 10 for \$2** specify which one to ship!

**RCA 40374**

250V-2A NPN T066  
POWER TRANSISTOR MOUNTED ON A FACTORY ASSEMBLED HEAT SINK - 5-B WATTS @ AMBIENT OF 25°C  
**\$.75 ea. 10 for \$6**

**ultra sensitive relay**

Single pole normally open dry reed relay. Unbelievable sensitivity, 1800 ohm coil with 3 volt pull-in (that's less than 3 ma.) A TTL gate will drive many of these. A CMOS buffer will directly actuate this nifty relay....  
MFR. unknown, but I was told they came from IBM. 600 available  
**\$2.95 ea.**

**ELEC-TROL 12 vdc REED RELAY**

440 Ω coil  
4 dpst n.o.  
1.1" dia  
PICTURE IS APPROXIMATION, RELAY HAS FOUR PINS ON ONE END AND TWO ON OTHER. PINS ARE SPACED .1" X 1". 1/2A CONTACTS.  
**79¢ ea. 10 - \$6**

**POTTER BRUMFIELD**  
Type 100 Relay  
4 PNT 3A CONTACTS  
24VDC (211)  
650 ohms  
120WDC  
10.5MA  
**\$1.60 ea.**

**FANTASTIC OPTO ISOLATOR**  
FAIRCHILD FCD 820  
195¢ ea. 10 for \$7.95  
MFR. FAIRCHILD, MOUNTED ON THT GATES, DIRECT SHOP BY MAIL

**DIP TRIMMER**  
12 TURN  
5K or 200K only  
mfg. DALE  
TEN FOR \$4

**1/8 WATT RESISTORS**  
10 ea. - 390, 1.8k, 3.9k, 6.8k, 11k, 43k, 68k, 200k - 5 percent tol.  
**80 FOR \$4**

**TOLL-FREE TELEPHONE SERVICE**

24 HOURS A DAY \$15 minimum order  
7 DAYS A WEEK  
NOTE: Operators can only handle orders we please advise our inquiries and questions directly to our company.  
To order by phone  
**DIAL: 800 423 2355 EXT 307**  
Any Time Day or Night (California Residents Please Dial 800-232-2175)

PHONE ORDERS CAN ONLY BE CHARGED TO MASTER CHARGE OR VISA/BANKAMERICARD  
Orders shipped same day - \$5 minimum - we pay post or UPS on orders more than \$15. Smaller orders \$1.50 shipping fee. Foreign orders must be paid in U.S. funds including sufficient post. \$10 minimum on BAC & MC orders, shipping will be added. Open accounts accepted from government agencies, schools, and stock exchange listed firms (\$25 minimum-FOB Sacramento).....

**BABYLON ELECTRONICS**  
916 334 2161 95841  
4811 MYRTLE AVE  
BANKAMERICARD

**INTEGRATED ELECTRONICS**

540 Weddell Drive, #4, Sunnyvale, CA 94086 (408)734-8470

CMOS	74C08 .65	7427 .35	74161 1.00	8973 2.95	8334 4.00
4000 .15	74C14 1.75	7430 .15	74163 1.30	8974 2.95	8553 6.50
4001 .20	74C20 .26	7432 .30	74164 1.45	8976 2.95	8556 3.25
4002 .20	74C30 .26	7440 .18	74165 1.35	75107 3.25	8599 3.25
4007 .20	74C32 .30	7442 1.00	74173 1.70	75451 .80	
4010 .36	74C42 1.40	7445 .70	74175 1.05	75452 .80	
4011 .20	74C48 2.75	7446 .70	74177 .90	75453 .80	
4012 .20	74C73 1.25	7448 .70	74182 .95	75491 1.25	
4013 .35	74C74 .75	7450 .25	74191 1.20	75492 1.40	
4014 .80	74C86 1.00	7451 .25	74192 1.45	75494 1.50	
4015 .80	74C90 1.10	7453 .25	74193 1.35		
4016 .35	74C93 1.25	7454 .35	74195 1.00		
4017 .92	74C151 2.75	7460 .22	74196 1.10	8212 3.50	301N .35
4018 .92	74C154 3.00	7472 .40	74197 1.10	8214 8.50	307N .35
4019 .20	74C157 2.10	7473 .40	74199 2.25	8224 4.75	309H 1.00
4020 1.00	74C160 1.40	7474 .40	74367 .90	8228 9.90	309K 1.25
4022 .83	74C162 1.70	7475 .55		8228 9.90	309H 1.00
4023 .21	74C164 1.75	7476 .45	Interface	8251 11.50	318H 1.50
4024 .75	74C165 1.75	7483 1.05	0025 3.50	8255 10.50	320H 5 .88
4025 .20	74C174 1.50	7485 1.10	0026 1.75	2513 9.50	320H 5 1.25
4027 .34	74C902 .85	7486 .43	8640 1.25	2516 9.50	320T-12 1.75
4028 .79	74C904 .85	7489 2.00	8641 2.75	1013 6.50	324N 1.25
4029 1.00	74C905 3.00	7492 .75	8606 3.00		340T-5 1.25
4030 .20	74C914 1.95	7493 .65	8819 1.25	8120 3.25	340T-12 1.25
4035 .95		7495 .78	8820 5.00	8120 3.25	340T-15 1.25
4040 1.00		7496 .85	8830 4.90	8197 1.75	340T-24 1.25
4041 1.00	7400 .16	74121 .35	8833 2.45	8092 .95	340T-24 1.25
4042 .70	7401 .17	74122 .49	8835 2.45	8092 .95	387N 1.25
4044 .60	7403 .17	74123 .65	8836 1.25	8095 .80	388N 1.15
4049 .35	7404 .19	74126 .65	8837 2.45	8098 .90	390H 1.25
4051 1.10	7406 .40	74132 1.25	8838 2.45	8098 .90	390H 1.25
4056 .70	7407 .40	74141 1.10	8859 1.50	8121 2.25	393S 2.4C
4058 .40	7409 .25	74145 1.10	8865 1.50	8136 3.25	393S 2.4C
4069 .40	7410 .18	74148 1.20	8866 1.50	8220 3.25	74LSxx *
4075 .20	7413 .78	74150 .90	8867 1.85	8231 2.25	74LS00 .25
4082 .23	7414 .68	74153 1.10	8869 1.75	8242 1.75	through
74C00 .25	7417 .38	74154 1.25	8879 2.25	8250 1.75	74LS670 3.95
74C02 .45	7420 .18	74155 .75	8880 2.75	8260 2.25	
74C04 .32	7421 .35	74157 1.00	8884 2.45	8281 1.00	

\* For more 74LSxx, refer to our ad in the June issue of this magazine. If what you need is not listed, ask for it. Send self-addressed stamped envelope.

**SPECIAL -- 21L02/450ns (1.50/10up, 1.35/50up, 1.25/100up)**  
±3 Digit A/D LD130 **\$5.50**  
MM5865 Universal Timer **\$7.50**  
Minimum order \$5.00 US currency. Check or money order only. Add 5% to cover shipping and handling charges. Calif. residents add 6% sales tax. Santa Clara County residents add 6.5% sales tax.

**CIRCLE 44 ON FREE INFORMATION CARD**

**SOCKET SALE**

**WIRE WRAP SOCKETS**  
14 Pin Wire Wrap .30 27/400  
16 Pin Wire Wrap .32 29/350

**EDGE CARD CONNECTORS**

44 Pin ST Edge Card Connector 1.75 1.50/10  
100 Pin ST Edge Card Connector 3.50 3.00/10  
100 Pin WW Edge Card Connector 3.50 3.00/10  
All Sockets & Connectors Include Gold.

**SOLDERLESS BREADBOARDS SK 10 \$16.50**

2.2" x 6.5"  
INCLUDING:  
Over 100 pieces of precut wire in assorted lengths - free!  
Choose 1 color: Red, Black, Blue, Yellow, Green, White, Orange  
Or Assortment.

**PAGE DIGITAL ELECTRONICS**  
135 E. Chestnut Street 4A  
Monrovia, California 91016  
Phone (213) 357-5005

**ORDERING INFORMATION**  
• Orders under \$25 and COD's. add \$2  
• All others, shipped Ppd in U.S. via UPS  
• For Blue Label (Air) or 1st Class, add \$1  
• We accept Visa & Master Charge  
• Most orders shipped same day  
**Dealer Inquiries Invited**

**CIRCLE 20 ON FREE INFORMATION CARD**

RADIO-ELECTRONICS

# DIGI-KEY CORPORATION

Quality Electronic Components

FREE

MINNESOTA RESIDENTS

218-681-6674



**DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES**

**I.C.'S • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES  
CLOCK MODULES • OPTOELECTRONICS • BREADBOARDING & TESTING DEVICES • DRAFTING SUPPLIES  
DATA BOOKS • HEAT SINKS • WIRE • TOOLS... AND MORE... WRITE FOR FREE CATALOG.....**

## INTEGRATED CIRCUITS

7400	7410	7420	7430	7440	7450	7460	7470	7480	7490
7400	7410	7420	7430	7440	7450	7460	7470	7480	7490
7401	7411	7421	7431	7441	7451	7461	7471	7481	7491
7402	7412	7422	7432	7442	7452	7462	7472	7482	7492
7403	7413	7423	7433	7443	7453	7463	7473	7483	7493
7404	7414	7424	7434	7444	7454	7464	7474	7484	7494
7405	7415	7425	7435	7445	7455	7465	7475	7485	7495
7406	7416	7426	7436	7446	7456	7466	7476	7486	7496
7407	7417	7427	7437	7447	7457	7467	7477	7487	7497
7408	7418	7428	7438	7448	7458	7468	7478	7488	7498
7409	7419	7429	7439	7449	7459	7469	7479	7489	7499
7410	7420	7430	7440	7450	7460	7470	7480	7490	
7411	7421	7431	7441	7451	7461	7471	7481	7491	
7412	7422	7432	7442	7452	7462	7472	7482	7492	
7413	7423	7433	7443	7453	7463	7473	7483	7493	
7414	7424	7434	7444	7454	7464	7474	7484	7494	
7415	7425	7435	7445	7455	7465	7475	7485	7495	
7416	7426	7436	7446	7456	7466	7476	7486	7496	
7417	7427	7437	7447	7457	7467	7477	7487	7497	
7418	7428	7438	7448	7458	7468	7478	7488	7498	
7419	7429	7439	7449	7459	7469	7479	7489	7499	
7420	7430	7440	7450	7460	7470	7480	7490		
7421	7431	7441	7451	7461	7471	7481	7491		
7422	7432	7442	7452	7462	7472	7482	7492		
7423	7433	7443	7453	7463	7473	7483	7493		
7424	7434	7444	7454	7464	7474	7484	7494		
7425	7435	7445	7455	7465	7475	7485	7495		
7426	7436	7446	7456	7466	7476	7486	7496		
7427	7437	7447	7457	7467	7477	7487	7497		
7428	7438	7448	7458	7468	7478	7488	7498		
7429	7439	7449	7459	7469	7479	7489	7499		
7430	7440	7450	7460	7470	7480	7490			
7431	7441	7451	7461	7471	7481	7491			
7432	7442	7452	7462	7472	7482	7492			
7433	7443	7453	7463	7473	7483	7493			
7434	7444	7454	7464	7474	7484	7494			
7435	7445	7455	7465	7475	7485	7495			
7436	7446	7456	7466	7476	7486	7496			
7437	7447	7457	7467	7477	7487	7497			
7438	7448	7458	7468	7478	7488	7498			
7439	7449	7459	7469	7479	7489	7499			
7440	7450	7460	7470	7480	7490				
7441	7451	7461	7471	7481	7491				
7442	7452	7462	7472	7482	7492				
7443	7453	7463	7473	7483	7493				
7444	7454	7464	7474	7484	7494				
7445	7455	7465	7475	7485	7495				
7446	7456	7466	7476	7486	7496				
7447	7457	7467	7477	7487	7497				
7448	7458	7468	7478	7488	7498				
7449	7459	7469	7479	7489	7499				
7450	7460	7470	7480	7490					
7451	7461	7471	7481	7491					
7452	7462	7472	7482	7492					
7453	7463	7473	7483	7493					
7454	7464	7474	7484	7494					
7455	7465	7475	7485	7495					
7456	7466	7476	7486	7496					
7457	7467	7477	7487	7497					
7458	7468	7478	7488	7498					
7459	7469	7479	7489	7499					
7460	7470	7480	7490						
7461	7471	7481	7491						
7462	7472	7482	7492						
7463	7473	7483	7493						
7464	7474	7484	7494						
7465	7475	7485	7495						
7466	7476	7486	7496						
7467	7477	7487	7497						
7468	7478	7488	7498						
7469	7479	7489	7499						
7470	7480	7490							
7471	7481	7491							
7472	7482	7492							
7473	7483	7493							
7474	7484	7494							
7475	7485	7495							
7476	7486	7496							
7477	7487	7497							
7478	7488	7498							
7479	7489	7499							
7480	7490								
7481									
7482									
7483									
7484									
7485									
7486									
7487									
7488									
7489									
7490									

## NEW! The "NIBBLER" A MICROCOMPUTER AT A MICROPRICE!

**FEATURES:**

- Assembled and Tested, yet only \$149.95
- Standard 4.5" by 6.5" card with 72 pin edge connector pattern
- All IC's are socketed for easy maintenance
- Memory expandable to 28K
- 110 Baud Serial I/O
- It Speaks Basic Beautifully
- 4K NIBL Basic in ROM and 2K of RAM
- Easily Interfaced with CRT or Teletype


The NIBBLER is Digi-Key's new low cost personal/hobby computer. Based on National Semiconductor's 8K/MP-1 microprocessor, the NIBBLER includes 4K NIBL Basic in ROM and 2K of RAM. The NIBBLER requires 5 volts of 1/2 amp providing 110 baud serial ASCII I/O which is easily interfaced with a CRT or Teletype. And our low price of \$149.95 is for an assembled and tested system! Software/Hardware manual included with NIBBLER available separately for \$5.00.

**CATALOG NUMBER NIBL-ND \$149.95** (not discountable)  
**SOFTWARE/HARDWARE MANUAL MAN1-ND \$5.00** (not discountable)

### SILICON TRANSISTORS

| Part No. |
|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
| 2N918    |
| 2N919    |
| 2N920    |
| 2N921    |
| 2N922    |
| 2N923    |
| 2N924    |
| 2N925    |
| 2N926    |
| 2N927    |
| 2N928    |
| 2N929    |
| 2N930    |
| 2N931    |
| 2N932    |
| 2N933    |
| 2N934    |
| 2N935    |
| 2N936    |
| 2N937    |
| 2N938    |
| 2N939    |
| 2N940    |
| 2N941    |
| 2N942    |
| 2N943    |
| 2N944    |
| 2N945    |
| 2N946    | 2N946    | 2N946    |          |          |          |          |          |          |          |



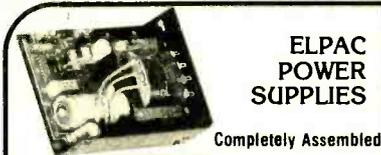

## ELPAC POWER SUPPLIES

Completely Assembled

### SPECIFICATIONS:

106-125/210-250 Vac, 47-440 Hz Input.  
 Line Regulation = ±0.1%  
 Load Regulation = ±0.1% no-load to rated-load  
 Output Ripple and Noise = ±0.1% p-p dc to 10 MHz  
 Input/Output Isolation = 100 megohm dc, 900 Vac  
 Short Circuit Current = 35% rated current

PART NO.	RATINGS			PRICE
	WATTS	VOLTS	AMPS	
SOLV15-5*	15	5	3	\$36.95
SOLV15-12*	15	12	1.5	36.95
SOLV30-5	30	5	6	59.95
SOLV30-12	30	12	3	59.95
OVP1	over voltage protection for SOLV30-5, -12			9.95
*SOLV15-5, 12 includes OVP installed				

## NEW! BULB-ENERGY SAVER



Bulb basis 3 or more times longer. Fits Standard Socket. 6 watts to 200 watts.

1. Acting as an electrical "shock absorber", turns the bulb on slowly, eliminating the "thermal shock". Bulb life increases 300 percent.
2. Bansishes Current "Surges". Cuts line voltage surges when other loads cut power line.
3. Reduces Energy Consumption.

BES-1	1-9	10+
	1.39 ea.	1.20

## CRYSTALS

THESE FREQUENCIES ONLY

PART NO.	FREQUENCY	CASE	PRICE
CY1A	1.000MHZ	HC33	5.95
CY1 B4	1.8432MHZ	HC33	5.95
CY2A	2.000MHZ	HC33	5.95
CY2 01	2.010MHZ	HC33	1.95
CY2 50	2.500MHZ	HC33	4.95
CY3 27	3.2768MHZ	HC33	4.95
CY3 57	3.579545MHZ	HC33	4.95
CY3A	4.000MHZ	HC18	4.95
CY4 91	4.916MHZ	HC18	4.95
CY7A	5.000MHZ	HC18	4.95
CY5 18	5.185MHZ	HC18	4.95
CY6 14	6.144MHZ	HC18	4.95
CY6 40	6.400MHZ	HC18	4.95
CY6 55	6.5536MHZ	HC18	4.95
CY12A	10.000MHZ	HC18	4.95
CY14A	14.31818MHZ	HC18	4.95
CY19A	18.000MHZ	HC18	4.95
CY18 43	18.432MHZ	HC18	4.95
CY22A	20.000MHZ	HC18	4.95
CY30A	32.000MHZ	HC18	4.95

## TRIMMERS

10MM size trimmers - .394" Dia.  
 Part No. 1-9 10-24 25-49 100+  
 TR-111(value), .35 .30 .25 .20

Resistance values - 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 1 meg

## TRIMPOTS

Single-Turn - 1/2 Watt  
 Square - Top Adjust - 3/8" Size  
 Part No. 1-9 10-24 25-49 50-99  
 63P(value) .99 .89 .80 .70

Resistance Values - 50, 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1 meg

## 15-Turn - 3/4 Watt

Rectangular Side Adjust 3/4" x 1/4" Size  
 Part No. 1-9 10-24 25-49 50-99  
 43P(value) 1.35 1.25 1.20 1.15

Resistance Values - 50, 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1 meg

## 1/16 VECTOR BOARD

PHENOLIC	D.1 Hole Spacing	P-Pattern		Price	
		L	W		
54P44 062XXXP	4.50	6.50	1.72	1.54	
169P44 062XXXP	4.50	17.00	3.69	3.32	
EPDXY	64P44 062WE	4.50	6.50	2.07	1.86
GLASS	64P44 062WE	4.50	8.50	2.56	2.31
	169P44 062WE	4.50	17.00	5.04	4.53
	169P84 062WE	8.50	17.00	9.23	8.26
EPOXY GLASS	169P44 062WEC1	4.50	17.00	6.80	6.12
COPPER CLAD					

## CONNECTORS

25 Pin-D Subminiature

DB25P(as pictured)	PLUG	\$3.25
DB25S	SOCKET	4.95
DB51226-1	Cover for DB25 P or S	1.75

## MOLEX CONNECTOR PINS

M-530-1	\$1.95/100 pins (minimum order)
	\$16.00/1000 pins

Pre-packaged in strips

## INSTRUMENT/CLOCK CASE

Injection molded unit. Complete with red bezel. 4 1/4" x 4" x 1-9/16"

\$3.49

## MICROPROCESSOR COMPONENTS

Part No.	Description	Price
PR085	CPU	\$29.95
8080A	CPU	10.95
8212	8-Bit Input/Output	4.95
8214	Priority Interrupt Control	7.95
8216	Bi-Directional Bus Driver	4.95
8224	Clock Generator/Driver	5.95
8228	System Controller/Bus Driver	5.95
8251	Prog. Comm. Interface	9.95
8255	Prog. Periph. Interface	10.95

RAM'S		PROM'S	
1101	256 x 1 Static	1702A	2048 x 1 Famous
1103	1024 x 1 Dynamic	5203	2048 x 1 Famous
2101	256 x 4 Static	8253	32 x 8 Open C
2102	1024 x 1 Static	825115	4096 x 1 Bipolar
2107/5280	4096 x 1 Dynamic	825123	32 x 8 Tri-state
2111	256 x 4 Static	745297	1024 x 1 Static
2112	256 x 4 Static	2708	8K EPROM
2114	4K x 1 Static 450ns	2716 T.1	16K EPROM
2114L	4K x 1 Static 450ns Low Power	2716 Intel	16K EPROM
2114-3	1K x 4 Static 300ns	8301-1	1024 x 1 Tri-State Bipolar
2114L-3	1K x 4 Static 300ns Low Power	6330-1	256 x 1 Open C Bipolar
7489	16 x 4 Static	74186	512 x 1 TTL Open Collector
8101	256 x 4 Static	74188	256 x 1 TTL Open Collector
8111	256 x 1 Static	9.95	
8599	16 x 4 Static	3.49	
21102	1024 x 1 Static	1.95	
74200	256 x 1 Static	6.95	
93421	256 x 1 Static	2.95	
MMS262	1K x 1 Dynamic	378.00	

ROM'S		SHIFT REGISTERS	
NK4027 (UPD414)	4K DYNAMIC 16 PIN	MM5013N	1024 Bit Accumulator-Dynamic
NK4116 (UPD416)	16K DYNAMIC 16 PIN	MM5016H	500/512 Bit Dynamic
TMS4044-45N	4K STATIC	MM5017N	Dual 500/512 Bit Dynamic
2513(2140)	Character Generator (upper case)	2504T	1024 Dynamic
2513(3021)	Character Generator (lower case)	2518	Hex 32 Bit Static
2518	Character Generator	2519	Hex 40 Bit Static
MMS230N	2048 Bit Read Only Memory	2522	Dual 132 Bit Static
		2524	512 Dynamic
		2525	1024 Dynamic
		2527	Dual 256 Bit Static
		2528	Dual 250 Static
		2529	Dual 240 Bit Static
		2532	Quad 80 Bit Static
		2533	1024 Static
		3341	File
		74LS670	4 X 4 Register

USER MANUALS		UART'S	
1602M	CDP1802 Manual	\$7.50	
2600M	Z80 Manual	7.50	
2650M	2650 Manual	5.00	AY-5-1013 30k BAUD \$ 5.95

## SPECIAL REQUESTED ITEMS

TELEPHONE KEYBOARD CHIPS	LOW CHIPS	MEMORIES ONLY	MISCELLANEOUS
AY-5-9100 \$14.95	ICM7045 \$24.95	MM6571 \$13.50	11C300 \$19.95
AY-5-9200 14.95	ICM7205 19.95	MM6574 13.50	MC1001P \$11.95
AY-5-9500 4.95	ICM7207 7.50	MM6575 13.50	MC1408L7 4.95
AY-5-2376 14.95	ICM7209 9.95		MC1408L8 5.75
HD0186 7.95	ICM7209 9.95		959890 11.95
74C922 9.95			

TV GAME CHIP SET LD 1101 \$25.00/set  
 AY-3-8500-1 Chip and 2.010 MHz Crystal \$7.95  
 MC4016(74416) 7.50  
 4N33 3.95

### PARATRONICS Logic Analyzer Kit Model 100A \$229.00/kit

- Analyzes any type of digital system
- Checks data rates in excess of 8 million words per second
- Trouble shoot TTL, CMOS, OTL, RTL, Schottky and MOS families
- Displays 16 logic states up to 8 digits wide
- See ones and zeros displayed on your CRT, octal or hexadecimal format
- Tests circuits under actual operating conditions
- Easy to assemble - comes with step-by-step construction manual which includes 80 pages on logic analyzer operation (Model 100A Manual - \$4.95)

### PARATRONICS TRIGGER EXPANDER - Model 10

Adds 16 additional bits. Provides digital delay and qualification of input clock and 24-bit trigger word. - Connects trigger to Model 100A for integrated unit.

Model 10 Kit - \$229.00  
 Baseplate - \$9.95  
 Model 10 Manual - \$4.95

### ESG 100 MHz 8-Digit Counter

- 20 Hz-100 MHz Range
- 8 LED Display
- Optical controlled timebase
- Fully Automatic
- Portable - completely self-contained
- Size: 6" x 4" x 4"
- 5.83"

Four power sources: i.e. Batteries: 110 or 220V with auto charger, 12V with auto lighter adapter and external 7.2-10V power supply

MAX-100 \$134.95

### Model 2800 \$99.95

Comes with test leads, operating manual and spare fuse

Accessories:  
 AC Adapter BC-28 \$9.00  
 Rechargeable Batteries BP-26 20.00  
 Carrying Case LC-28 7.50

### 63-Key Unencoded KEYBOARDS Hexadecimal Encoder

This is a 63-key, terminal keyboard newly manufactured by a large computer manufacturer. It is unencoded with SPST keys, unattached to any kind of PC board. A very solid molded plastic 13 x 4" base suits most applications. IN STOCK \$29.95/each

19-key pad includes 1-10 keys, ABCDEF and 2 optional keys and a shift key. \$10.95/each

\$5.00 Minimum Order - U.S. Funds Only  
 California Residents - Add 6% Sales Tax

Spec Sheets - 25¢  
 1978A Catalog Available - Send 35¢ stamp

## Jameco ELECTRONICS

MAIL ORDER ELECTRONICS - WORLDWIDE  
 1021 HOWARD AVENUE, SAN CARLOS, CA 94070  
 Advertisd Prices Good Thru August

PHONE ORDERS WELCOME (415) 592-8097

## The Incredible "Pennywhistle 103"

### \$129.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modern and terminal for telephone "banning" and communications for the deaf. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

Data Transmission Method: Frequency-Shift Keying, full-duplex (half-duplex selectable)  
 300 Baud  
 Maximum Data Rate: Asynchronous Serial (return to mark level required between each character)  
 Data Format: Asynchronous Serial (full to mark level required between each character)

Receive Channel Frequencies: 2025 Hz for space, 2225 Hz for mark.  
 Transmit Channel Frequencies: Switch selectable. Low (normal) = 1070 space, 1270 mark, High = 005 space, 2225 mark.

Receive Sensitivity: -46 dbm acoustically coupled.  
 Transmit Level: -15 dbm nominal. Adjustable from -6 dbm to -20 dbm.

Receive Frequency Tolerance: Frequency reference automatically adjusts to allow for operation between 1800 Hz and 2400 Hz.  
 Digital Data Interface: EIA RS-232C or 20 mA current loop (receiver is optoisolated and non-polar).  
 Power Requirements: 120 VAC, single phase, 10 Watts.  
 Physical: All components mounted on a single 5" by 9" printed circuit board. All components included.  
 Requires a VOM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align.

## The Original the 3rd Hand \$9.95 each

- Leaves two hands free for working
- Clamps on edge of bench, table or work bench
- Position board on angle or flat position for soldering or clipping
- Sturdy, aluminum construction for hobbyist, manufacturer or school rooms

## DIGITAL STOPWATCH

- Bright 8-Digit LED Display
- Times to 99 minutes 59.99 seconds
- Crystal Controlled Time Base
- Three Stopwatches in One
- Times Single Event - Split & Taylor
- Size 5" x 2 1/2" x 90 (4 1/2" ounces)
- Uses 3 Penrite Cells

Kit - \$39.95  
 Assembled - \$49.95  
 Heavy Duty Carry Case \$5.95

Stop Watch Chip Only (7205) \$19.95

## IMC 3 1/2 DIGIT DPM KIT

- New Bipolar Unit
- Auto Zeroing
- 5" LED
- Auto Polarity
- Low Power
- Single IC Unit

Model K8500 DPM Kit \$49.00  
 Model K8503 5V Power Kit \$17.50

## JE700 CLOCK

The JE700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2 1/2" x 1 1/2". It utilizes a MAN72 high brightness readout and the MMS314 clock chip.

115 VAC KIT ONLY \$16.95

## JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) = HIGH, (L) = LOW, (P) = PULSE, (F) = The Probe can detect high frequency pulses to 45 MHz. It can be used as MOS levels or circuit damage will result.

\$9.95 Per Kit printed circuit board

## T<sup>2</sup>L 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

JE225 \$9.95 Per Kit

## PROTO BOARDS

PROTO BOARD 6 \$15.95 (6" long X 4" wide)

PB100 - 4.5" x 6"	\$ 19.95
PB101 - 5.8" x 4.5"	29.95
PB102 - 7" x 4.5"	39.95
PB103 - 9" x 6"	59.95
PB104 - 9.5" x 8"	79.95
PB203 - 9.75 x 6 1/2 x 2 1/4	80.00
PB203A - 9.75 x 6 1/2 x 2 1/4	129.95 (includes power supply)

PROTO CLIPS

14 PIN	\$4.50
16 PIN	4.75
24 PIN	8.50
40 PIN	13.75



### Jumbo LED Car Clock Kit

#### FEATURES:

- A Bowmar Jumbo .5 inch LED array
  - B MOSTEK — 50250 — Super clock chip
  - C On board precision crystal time base
  - D 12 or 24 hour Real Time format
  - E Perfect for cars, boats, vans, etc.
  - F PC board and all parts (less case) inc.
- Alarm Option — \$1.50  
AC XFMR — \$1.50



**\$16.95**

### MUSICAL HORN

One tune supplied with each kit. Additional tunes — \$6.95 each. Special tunes available. Standard tunes now available: — Dixie — Eyes of Texas — An On Wisconsin — Yankee Doodle Dandy — Notre Dame — Pink Panther — Aggie War Song — Anchors Aweigh — Never on Sunday — Yellow Rose of Texas — Deep in the Heart of Texas — Boomer Sooner — Bridge over River Kwai.

Special Design Assembled Case \$3.50 & Tested Add \$10.00

CAR & BOAT KIT HOME KIT  
34.95 29.95

### TELEPHONE RELAY

Assembled & Tested **\$29.95**


Automatically Starts & Stops Tape Recorders  
Surreptitious interception of telephone conversation is a violation of Federal Law and this device is not intended for such use.

### 6 DIGIT ALARM CLOCK KIT

Features: Litronix dual 1/2" displays, Mostek 50250 super clock chip, single I.C. segment driver, SCR digit drivers. Kit includes all necessary parts (except case). Xfmr optional. Eliminate the hassle.

AC XFMR — \$1.50 Case **\$3.50**

**\$12.95**

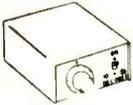

Plugs into earphone or external speaker of any Scanner or Monitor. Guaranteed to unscramble any 1085 call.

### NEW IMPROVED UNSCRAMBLER!

**\$25.00**

Punched and Printed Case

- Easily tuned
- Full instruction included
- Drilled fiberglass P.C. Board
- One Hour Assembly

### 12V 1 AMP POWER SUPPLY

INPUT VOLTAGE 25V MAX. OUTPUT CURRENT 1 AMP. MAX. LOAD REGULATION 50mV. OUTPUT VOLTAGE 12V. LINE REGULATION 0.01%. KIT CONTAINS ALL PARTS EXCEPT FOR LINE CORD AND TRANSFORMER.

**ONLY \$4.50**

### 7400 TTL DIGITAL CIRCUITS

7400	11	7442	47	7490	65	74156	89
7401	13	7443	59	7491	61	74157	52
7402	13	7444	59	7492	43	74160	52
7403	13	7447	68	7493	43	74161	65
7404	15	7448	71	7494	67	74163	65
7405	29	7450	13	7495	67	74164	65
74504	44	7451	13	7496	67	74165	89
7406	16	7453	13	74100	30	74174	85
7408	19	7450	19	74104	49	74175	85
7410	13	7470	27	74107	28	74180	67
7411	18	7472	25	74109	31	74181	93
7412	26	7473	29	74121	29	74182	68
7416	15	7474	29	74123	48	74191	98
7420	13	7475	47	74132	99	74192	79
7423	25	7476	31	74136	99	74193	81
7425	29	7480	31	745138	95	74194	81
7433	26	7481	55	74141	75	74195	69
7437	23	7482	47	74147	75	9316	85
7438	23	7483	67	74153	61	9601	31
7440	13	7485	89	74154	98	9604	35
7441	76	7489	125	74155	89	9604	35

### LINEARS

709	Operational Amplifier	25
711	Differential Comparators	40
712	Dual Differential Comp	25
712	Hall Adder	25
749	Stereo Pre-Amp by Fairchild 21/51	45
LM 301	Operational Amplifier	30
LM 307	Operational Amplifier	30
LM 308	Operational Amplifier	30
LM 309K	5V Lamp Regulator	1.49
LM 710	Voltage Comparator	25
LM 311	Voltage Comparator	65
LM 318	Operational Amplifier	1.15
LM 723	Voltage Regulator	85
LM 324	Quad Operational Amplifier	1.20
LM 377	Dual 2V Amplifier	1.85
LM 3900	Quad Op-Amp	40
LM 741	Operational Amplifier	75
LM 748	Operational Amplifier	25
NE 553	Quad Timer	1.95
NE 555	Timer	95
NE 556	Dual Timer	95
NE 567	Tone Decoder	1.25
1458	Dual Op-Amp	25
75491	Quad Segment Driver	35
75492	Hex Digit Driver	35
3043	IF Amplifier	30
8038	Voltage Cont. Osc	3.95

### MICROPROCESSOR SUPPORT CHIPS

8212	-1/D port	3.50
8214	- P.I.C.	12.95
8216	- Non Invert Bus	4.95
8224	- Clock Gen.	4.95
8226	- Invert Bus	3.95
8228	- 80	14.95
8228	- 80	14.95
8228	Sys. Controller	8.20
8251	Prog. comm. interface	10.95
8255	Prog. perp. interface	13.50
8280	Dual Line Recr.	1.75
8280	Dual Line Dr.	1.75
8283	Char. Bus. Recvr.	7.50
74LS138N	- 1/8 decoder	99
8T97	- Hex Tri-State Buffer	1.25
1488/1489	RS232	1.50
TR1602B	UART	3.95
TR1863	UART	8.50

### CLOCK & COUNTER CHIPS

MK50252	Clock Chip	\$4.99
MK50250	Alarm Clock	3.75
MK50380	Alarm Chip	2.95
FCM7010	Direct Drive Clock Chip	4.95
MK5005	4 Digit Counter w/Latch	4.95
MK5002	4 Digit Counter	8.95
MK50395	6 Digit UP/Down Counter	12.95
MK50397	6 Digit Elapsed Timer	8.95
CT5005	Calculator Chip w/Specs	14.95
MK5021	Cal. Chip w/50 Hz	2.50

SOCKET SPECIAL!  
28 PIN IC SOCKET  
3 FOR \$1  
WHEN PURCHASED  
W/CLOCK IC

### HOUSE # TTL IC'S

7400	10/1/00	Please specify 7437	6/1/00	
7404	10/1/00	that you	7438	6/1/00
7408	10/1/00	are ordering	74153	3/1/00
7420	10/1/00	are ordering	74153	3/1/00

### CRYSTALS

300 KHz	\$1.50
3.57945	1.25

### 74LS00 LOW POWER SCHOTTKY

74LS00	21	74LS47	73	74LS136	37	74LS258	71
74LS02	21	74LS51	26	74LS138	71	74LS260	26
74LS03	21	74LS54	26	74LS139	71	74LS266	26
74LS04	28	74LS55	26	74LS145	10	74LS279	55
74LS05	28	74LS57	35	74LS151	70	74LS293	61
74LS08	21	74LS74	35	74LS153	70	74LS293	61
74LS09	28	74LS76	49	74LS155	69	74LS295	95
74LS10	21	74LS83	73	74LS156	70	74LS298	95
74LS11	21	74LS85	35	74LS157	75	74LS365	55
74LS13	45	74LS86	36	74LS158	71	74LS366	55
74LS14	99	74LS90	55	74LS160	85	74LS367	55
74LS15	26	74LS92	55	74LS161	85	74LS368	55
74LS20	24	74LS93	55	74LS162	85	74LS390	175
74LS21	28	74LS109	38	74LS163	85	74LS393	145
74LS22	28	74LS112	38	74LS164	149	74LS670	230
74LS26	32	74LS113	38	74LS168	85	74LS192	95
74LS27	32	74LS116	49	74LS169	85	74LS193	95
74LS30	26	74LS122	49	74LS170	85	74LS194	95
74LS32	32	74LS124	99	74LS173	110	74LS195	85
74LS37	32	74LS125	47	74LS174	100	74LS196	85
74LS38	32	74LS126	47	74LS175	81	74LS197	85
74LS40	26	74LS131	79	74LS180	95	74LS251	81
74LS42	65	74LS133	35	74LS191	95	74LS253	81
				74LS257	71		

### TTL SPECIAL!

9000 series parts  
Prime from ITT  
Pin for Pin  
compatible with  
7400 series

### ITT LED DRIVERS

ITT 501	Quad Seg Dr	35
ITT 502	Hex Digit Dr	49
ITT 503	Quad Seg Dr	49
ITT 506	Hex Digit Dr	49
ITT 508	8 Digit Dr	49
ITT 509	8 Seg Dr	49
ITT 511	Quad Seg Dr	55
ITT 514	8 Digit Dr	59

### FAIRCHILD RTL's

The most popular digital IC's ever Produced. Very hard to find!

UL914 DUAL 2 INPUT NOR 99  
UL923 JK FLIP FLOP \$1.19

### PROMS

1702A	- 1K - 1.5us	3.95 or 10/35
2708	- 8K Intel - 450ns	14.95
5204	- 4K	7.95
825129	- 1K	2.50
2708S	- 8K signetics	650ns 9.95

### DIODES

IN 4002	1 Amp 100 PIV	40/\$1
IN 4004	1 Amp 400V	15/\$1
IN 4007	1 Amp 1000V	10/\$1

### GERMANIUM DIODES

IN 54A		\$8/\$1
IN 270		10/\$1

### ZENER DIODES

IN 746	3.3V 400M	4/\$1
IN 752	5.6V 400M	4/\$1
IN 1958	8.2V 400M	4/\$1
IN 5259	39V 500M	10/\$1
IN 5271	100V 500M	10/\$1
IN 5280	180V 500M	10/\$1

### HOUSE # ZENER

4.7V	500 MW	10/\$1
9. V	500 MW	10/\$1
10V	1 Watt	8/\$1
15V	500 MW	10/\$1
22V	5 Watt	6/\$1

### SWITCHING DIODES

IN 4148/IN914	Long Leads	20/\$1
IN 4148/IN914	Cut Leads	40/\$1
IN 4148/IN914	PC Leads	100/\$2

### CMOS

CD4000	19	CD4017	95	CD4040	100	CD4071	19
CD4001	19	CD4018	95	CD4041	69	CD4081	19
CD4002	19	CD4019	19	CD4042	69	CD4087	35
CD4006	120	CD4020	97	CD4043	60		
CD4007	19	CD4021	97	CD4044	60	CD4510	100
CD4009	47	CD4022	97	CD4046	139	CD4512	110
CD4010	39	CD4023	19	CD4047	150	CD4516	79
CD4011	19	CD4024	75	CD4049	35	CD4518	110
CD4012	29	CD4025	19	CD4050	39	CD4520	89
CD4013	32	CD4027	39	CD4051	119	CD4528	85
CD4014	78	CD4028	85	CD4053	119	74C02	45
CD4015	78	CD4029	99	CD4056	115	74C04	32
CD4016	32	CD4030	35	CD4066	78	74C107	79

### SOCKETS

• 8 Pin Low Profile	20	• 18 Pin Low Profile	30
• 14 Pin Low Profile	22	• 28 Pin Low Profile	69
• 16 Pin Low Profile	25	• 40 Pin Low Profile	89

### Bowmar 4 Digit LED Readout Array

Full 1/2" Litronix Jumbo Dual Digit LED Displays  
4 JUMBO 50' DIGITS ON ONE STICK!  
WITH COLONS & AM/PM INDICATOR

DL 722 - C.C. DL 728 - C.C.  
DL 721 B.C.A. DL 727 - C.A.

99c \$1.29

### UNMARKED

### 1702A EPROMS

3.50 Ea. or 10/\$32.00  
LIMITED SUPPLY

### IMSAI SPECIAL

★ S-100 Connector ★  
\$3.95 Ea.

### CAPACITORS ELECTROLYTIC

AXIAL TYPE			RADIAL TYPE		
20MFD 250V	5/51		47MFD 35V PC Leads	10/\$1	
35MFD 25V	15/\$1		68MFD 25V PC Leads	8/\$1	
500MFD 35V	5/51		330MFD 50V PC Leads	5/\$1	
			1000MFD 35V PC Leads	4/\$1	
			150 PF MICA 5%	10/\$1	

COMPUTER GRADE 3/52  
1.900MFD 35VWDC (Min) 95 cents each  
8.000MFD 15VWDC \$4.00 Each  
33.000MFD 40VWDC

TANTALUM  
1MFD 20VWDC PC Leads 15/\$1  
4.7MFD 10VWDC PC Leads 5/\$1  
33MFD 10VWDC 6/\$1  
22PF 10 10/\$1

CERAMIC DISC  
68PF 50V 001MFD 50V  
100PF 100V 002MFD 200V  
150PF 50V 01MFD 200V  
220PF 50V 0.2MFD 200V  
330PF 50V 3.3PF 500V  
001MFD 500V 100PF 500V  
PC Leads 25/89 cents No Mix

### JOY STICKS

★ ★ JOY STICKS ★ ★  
FOUR 100 K-OHMS POTS  
Ideal for electronic games **\$3.95**

### MICRO-DIP \$1.95

New - Series 2300  
The World's Smallest  
Coded BCD Dual-In-Line  
Switch! PC Mount

2300 02G BCD 1-2-4-8  
2300 12G BCD 1-2-4-8  
Compliment

### BRIDGE RECTIFIERS

1 Amp 200V	6/\$1	21L02-500NS	8/11 50
6 Amp 50V 1 10		21L02-250NS	8/15 95
10 Amp 50V 1 25		2	



# POLY PAKS' 10¢ REBELLION

WE'RE FIGHTING BACK INFLATION WITH THIS EXCLUSIVE 10¢ SALE

**RIBBON CABLE!**  
Order by Cat. #R-3939  
and Conductors

Cond.	Size	1¢ Sale
26	4-ft. 1.98	8-ft. 1.99
36	3-ft. 1.98	6-ft. 1.99
40	3-ft. 1.98	6-ft. 1.99

BUY 1 AT SALE PRICE, GET 2ND FOR 10¢ MORE!!!

**PENNIES FOR YOUR MEMORIES!**

Type	Description	1¢ Sale	Order by Cat. No.
1103	1K Dynamic RAM	1.25	SR3459
1207	2K	2.95	SR3459 & 5
5262	2K x 1 Dynamic RAM	.99	1.00
1702A	256 x 8 EPROM	4.95	4.96

## TTL'S AT "CENT-CIBLE" PRICES

Order By Cat. No. SR1981	Type No.	Each	2 for	Type No.	Each	2 for	Type No.	Each	2 for
SN7400	5.19	\$ 2.00	SN7462	.35	.36	SN74140	.49	.50	
SN7401	.19	.20	SN7464	.19	.20	SN74141	1.79	1.80	
SN7403	.25	.26	SN7465	.19	.20	SN74145	.69	.70	
SN7404	.19	.20	SN7470	.19	.20	SN74151	1.29	1.30	
SN7405	.19	.20	SN7471	.35	.36	SN74153	1.29	1.30	
SN7406	.19	.20	SN7472	.19	.20	SN74154	1.75	1.76	
SN7407	.39	.40	SN7473	.59	.60	SN74155	.79	.80	
SN7409	.39	.40	SN7474	.59	.60	SN74156	.39	.40	
SN7410	.25	.26	SN7475	.69	.70	SN74157	.99	1.00	
SN7411	.79	.80	SN7476	.79	.80	SN74158	.99	1.00	
SN7413	1.19	1.20	SN7480	.19	.20	SN74161	1.25	1.26	
SN7416	.35	.36	SN7482	.29	.30	SN74163	1.39	1.40	
SN7417	.35	.36	SN7483	.99	1.00	SN74164	.79	.80	
SN7420	.32	.33	SN7486	.49	.50	SN74165	.99	1.00	
SN7421	.49	.50	SN7488	.79	.80	SN74166	1.99	2.00	
SN7423	.49	.50	SN7489	3.49	3.50	SN74173	1.79	1.80	
SN7426	.19	.20	SN7490	.99	1.00	SN74174	1.79	1.80	
SN7430	.29	.30	SN7491	1.29	1.30	SN74175	.99	1.00	
SN7432	.45	.46	SN7492	.79	.80	SN74177	.79	.80	
SN7437	.35	.36	SN7493	.69	.70	SN74179	2.00	2.00	
SN7438	.25	.26	SN7494	.79	.80	SN74180	.49	.50	
SN7440	.19	.20	SN7495	.59	.60	SN74182	.49	.50	
SN7443	.59	.60	SN7496	.29	.30	SN74190	1.59	1.60	
SN7445	.29	.30	SN7498	.79	.80	SN74191	1.75	1.76	
SN7446	.85	1.26	SN74100	1.99	2.00	SN74192	.85	.86	
SN7447	1.25	1.26	SN74107	.29	.30	SN74193	.99	1.00	
SN7448	1.35	1.36	SN74113	.39	.40	SN74194	1.25	1.26	
SN7451	.19	.20	SN74144	.25	.26	SN74197	.75	.76	
SN7453	.19	.20	SN74121	.59	.60	SN74199	1.50	1.51	
SN7454	.29	.30	SN74123	.69	.70	SN74200	3.50	3.51	
SN7456	.35	.36	SN74126	1.00	1.01	SN74251	4.50	4.51	
			SN74132	1.35	1.36	SN74258	5.99	6.00	
			SN74136	.49	.50	SN74298	3.75	3.76	

## POP-AMPS AT "CENT-CIBLE" PRICES

Case code: T=TO-220 Power Tab; V=Mini dip; K=TO-3; H=TO-5; N=DIP.

Type No.	Each	2 for	Type No.	Each	2 for	Type No.	Each	2 for
LM300H	\$ .79	\$ .80	LM340T-6	1.49	1.50	LM703N	.59	.60
LM300N	.49	.50	LM340T-8	1.49	1.50	LM704H	.19	.20
LM301V	.45	.46	LM340T-12	1.49	1.50	LM709H	.19	.20
LM301H	.45	.46	LM340T-15	1.49	1.50	LM709N	.49	.50
LM307V	.45	.46	LM340T-18	1.49	1.50	LM709P	.79	.80
LM308V	.29	.30	LM340T-24	1.49	1.50	LM741H	.25	.26
LM308H	.69	.70	LM350N	.49	.50	LM741H	.30	.31
LM309K	1.49	1.50	LM370N	1.99	2.00	LM741H	1.59	1.60
LM311V	.29	.30	LM376V	.29	.30	LM741H	1.59	1.60
LM311H	1.49	1.50	LM377N	2.25	2.26	LM3130	1.79	1.80
LM318V	.99	1.00	LM380N	1.39	1.40	LM1312	2.49	2.50
LM320H-5	.99	1.00	LM381H	2.99	3.00	LM1414V	1.19	1.20
LM320H-12	.99	1.00	LM386H	1.49	1.50	LM1458V	.39	.40
LM320H-15	.99	1.00	LM387H	1.49	1.50	LM1800N	.79	.80
LM320T-6	1.49	1.50	LM352N	.25	.26	LM3028H	.65	.66
LM322N	1.19	1.20	LM353H	.29	.30	LM3900N	.59	.60
LM324H	1.79	1.80	NE404H	5.95	5.96	LM3909V	1.25	1.26
LM333N	1.79	1.80	LM555V	.75	.76	LM4250	1.20	1.21
LM340K-5	1.49	1.50	LM556N	1.79	1.80	LM75451	.69	.70
LM340K-6	1.49	1.50	LM558V	.39	.40	LM75453	1.49	1.50
LM340K-8	1.49	1.50	LM558N	.39	.40	LM75491	.80	.81
LM340K-12	1.49	1.50	LM561N	1.00	1.01	LM75492	.80	.81
LM340K-15	1.49	1.50	LM565N	1.00	1.01	LM75494	.60	.61
LM340K-18	1.49	1.50	LM565H	1.01	1.02	PA213	1.25	1.26
LM340K-24	1.49	1.50	LM566	2.49	2.50	DM864N	1.29	1.30
LM340T-5	1.49	1.50	LM567	2.39	2.40			

## Parts & Semi One Centers

Quant.	Description (Order by Cat. No. in parentheses)	1¢ Sale	1CSALE
1	140 CHANNEL CB SELECTOR, w/knob, for PLL circuits (#R5045)	1.00	2 for 1.01
1	123 CHANNEL CB SELECTOR, w/knob, for PLL & xtal (#R5044)	1.00	2 for 1.01
1	10-IC "PIC", microscopic circuits, teaches theory (#R5065)	1.19	20 for 1.20
1	10-SPST SWITCH, full pots, for cam-home (#R5294)	1.95	2 for 1.96
1	1-LED WATCH GUTS, men's, how good? We don't know (#R5267)	1.95	2 for 1.96
1	1-JHF TUNER, solid state, standard type (#R2927)	1.00	2 for 1.01
1	10-SLIDING SWITCHES, ass't pop styles (#R2927)	1.00	20 for 1.01
1	1-TANTALUM CAPACITORS, all volt, 5V, dipped (#R5281)	1.00	8 for 1.01
5	1-PANCAKE PHOTOCELLS, 600 to 15K ohms (#R2939)	1.00	10 for 1.01
1	1-100KHZ MARKER CRYSTALS, approx for marker gen. (#R3896)	1.95	2 for 1.96
1	1-MOTHER SHIELD CONNECTOR, 106 pins, 15" (#R3987)	1.95	2 for 1.96
1	1-30-PIN EDGE CONNECTOR, 160' spacing (#R3963)	1.95	2 for 1.96
1	1-METER, 50uA, 1/4" square, 0-20db (#R3705)	1.19	2 for 1.20
1	1-SPST RELAY, norm. open 12-24 VDC, 1250 ohms, dip style (#R5175)	1.00	2 for 1.01
1	1-VEEDED ROOT COUNTER, 600-800, resettable, panel mt (#R5058)	1.49	2 for 1.50
2	1-OIL GATE MOSFET, sim. to 3N200, 3N187, for RT & Mixer (#R5101)	1.00	4 for 1.01
2	1-LCD THERMAL INDICATORS, BR-108-F, 7x1", flexible (#R5195)	1.00	4 for 1.01
1	1-JOYSTICK, four 100K pots, with knob (#R3808A)	4.95	2 for 4.96
1	1-ECCD THUMBWHEEL SWITCH, BCD, 0-7 (#R2870A)	1.95	2 for 1.96
1	1-20" 50' SPEAKER, full pots, for cam-home (#R5043)	1.19	2 for 1.20
1	1-PLESSEY TV SIDEBAND FILTER, for chan. 3 or 4 (#R3975)	1.95	2 for 1.96
1	1-30-R WIRE WRAP WIRE, 30 gage, for ICA, terminals (#R3803)	1.00	60-ft for 1.01
1	1-29V NI-CAD CHARGER PAK, plug-in, 125ma, 125 VAC pr (#R4098)	1.49	2 for 1.50
20	20-DATA ENTRY SWITCH-SWITCHES, approx 1000, for mem. (#R5279)	2.00	150 for 2.01
60	60-YIELD JACKIE MTLT C-CAPACITORS, untested 50% yield, pop types (#R2415)	2.00	200 for 2.01
100	100-MINI DIP ICs, untested 50% yield, pop types (#R3245)	2.00	200 for 2.01
75	75-LINEARS, OP AMPS, untested 50% yield, amps-dips-minidips (#R2416)	2.00	200 for 2.01
100	100-TTL & LINEAR MIXED, with 7400, 7400, 7400, 7400 (#R2431)	2.00	200 for 2.01
1	1-2" 1/2" SWITCH, full pots, for computers, TV games (#R5037)	2.95	2 for 2.96
1	1-BRACK TAPE HEAD, with plug 'n' cord (#R3468)	2.50	2 for 2.51
150	150-PREFORMED DISC CAPACITORS, marked values, ass't'd (#R2605)	2.00	300 for 2.01
150	150-TRIMMER CAPACITORS, mica compression, piston, ass't'd (#R3714)	2.00	120 for 2.01
100	100-YIELD JACKIE MTLT C-CAPACITORS, untested 50% yield, pop values (#R3476)	2.00	150 for 2.01
150	150-GLASS ZENERS, 400 MW, untested, better than 50% marked (#R2740)	2.00	300 for 2.01
75	75-CARBON FILM RESISTORS, 1/4, 1/2 watt, 5 & 10% marked, ass't's (#R3542)	2.00	150 for 2.01
250	250-UNMARKED CAPACITORS, polystyrene, molded, pop values (#R3805)	2.00	600 for 2.01
100	100-1/4" 1/2" SWITCHES, silicon, mod. etc. (#R3263)	2.00	600 for 2.01
8	8-IC SOCKETS, 14, 18 pin, solder tail. (#R3621)	2.00	16 for 2.01
100	100-1N4148/9/14 SWITCHING DIODES, 50% yield, untested (#R2418)	2.00	200 for 2.01
30	30-PC TRIM POTENTIOMETERS, thumbwheel, screwdriver ass't's (#R3345)	2.00	30 for 2.01
2	2-50' 1/2" SWITCHES, silicon, mod. etc. (#R3057)	2.00	30 for 2.01
75	75-4" CABLE TIES, plastic, like "Ty-wrap" (#R5218)	2.00	150 for 2.01
10	10-CALCULATOR KEYBOARDS, 20 keys and more (#R3524)	2.00	20 for 2.01
10	10-CRYSTALS, may include CB, Ham & more (#R3250)	2.00	20 for 2.01
100	100-TERMAL STRIPS, 2" long, 2" wide, 100' (#R2613)	2.00	60 for 2.01
1	1-NE-ZENER DIODES, all 100% good (#R2613)	2.00	60 for 2.01
40	40-R SHIELDED CABLE, 1 cond, mikes, phones, (#R3577)	2.00	80 ft for 2.01
50	50-TRANSISTOR ELECTROS, ass't'd values, styles (#R2747)	2.00	100 for 2.01
3	3-SOUND INDICATOR TRIGGERS, ass't'd values, styles (#R2625)	2.00	6 for 2.01
10	10-CRYSTALS, for phase lock loop, HAM, HC/18 (#R5050)	2.00	20 for 2.01
100	100-DISC CAPACITORS, long leads, marked, ass't'd (#R2598)	2.00	200 for 2.01
10	10-VOLTAGE REGULATORS, hobby LM320, 340, TO-3 (#R3330)	2.00	200 for 2.01
3	3-PIEL SWITCHES, silicon, mod. etc. (#R3263)	2.00	60 for 2.01
200	200-RESISTOR SPECIAL, 1/4 to 1W, carbon, metal (#R3054)	2.00	400 for 2.01
200	200-HALF WATTERS, resistors, carbon, metal (#R3046)	2.00	400 for 2.01
100	100-NATIONAL IC BOMANZA, linears, 7400s ROMS (#R2860)	2.00	200 for 2.01
15	15-LM340T VOLTAGE REGULATORS, 5 to 24V, TO-220 (#R2635)	2.00	30 for 2.01
100	100-POLYSTYRENE CAPS, ass't'd values, voltage, HQ (#R2728)	2.00	200 for 2.01
50	50-TRIMMISTORS, resistors that change with temp (#R4089)	2.00	100 for 2.01
20	20-BRIDGES, untested, 2, 4, 6, 10, amp. (#R4022)	2.00	50 for 2.01
15	15-MIXED READOUTS, hobby, untested, 127, 3, 5, etc. (#R3619)	2.00	30 for 2.01
150	150-QUARTER WATTERS, resistors, metal film, marked (#R3413)	2.00	300 for 2.01
100	100-PLASTIC TRANSISTORS, untested, TO-92 (#R2664)	2.00	200 for 2.01
1	1-CLOCK SWITCH, national, hobby & untested, alarm (#R5069)	2.00	60 for 2.01
200	200-PRECISION RESISTORS, 1/4, 1/2, 1W, 1% marked (#R2608)	2.00	400 for 2.01
60	60-DIPPLE MYLARS, shiny finish, ass't'd values (#R2597)	2.00	120 for 2.01
30	30-COLUME CONTROLS, audio, linear, ass't'd values (#R2411)	2.00	60 for 2.01
1	1-CLOCK SWITCH, national, hobby & untested, alarm (#R5069)	2.00	60 for 2.01
30	30-M5262 2K RAMS, hobby, untested (#R3940)	2.00	60 for 2.01
10	10-PUSH SWITCHES, push-to-break, spst, alarm (#R5289)	2.00	20 for 2.01
25	25-CD4000 SERIES CMOS, untested, 50% useable yield (#R5284)	2.00	50 for 2.01
1	1-CHARACTER GENERATOR, 5 x 7 Motek MK 2002P (#R3898)	4.95	2 for 4.96

## 7-SEGMENT READOUTS

Quant.	Description	1¢ Sale	ONE CENT SALE
3	3-DIGIT LCD WRISTWATCH DISPLAY, (#R3960)	3 for \$1.19	6 for \$1.20
3	3-SPERRY FLAT NIXIES, orange, 3" dual dig (#R5014)	3 for 1.19	6 for 1.20
3	3-SPERRY FLAT NIXIES, orange, 3", 1 1/2" dig (#R5015)	3 for 1.19	6 for 1.20
3	3-MAN-3 BUBBLE READOUT, 13" red, com cath, (#R3338)	6 for 1.00	12 for 1.01
2	2-FND-10 BLOCK READOUT, 122" com cathode, (#R3083)	2 for 1.00	4 for 1.01
2	2-DIGIT READOUT, led, com cathode, red (#R5190)	1 for 1.95	2 for 1.96
1	1-FND-503, 5" red, com cathode, 7-seg. (#R2949)	1.50	2 for 1.51

## RELAYS!

Quant.	Description	1¢ Sale	2 for
1	SPDT 12V BLOCK RELAY, 5A contacts (#R4032)	\$1.98	\$1.99
1	SPDT 12V REED RELAY, 1A contacts (#R4094)	1.49	1.50
1	SPDT 12V SEISMIC RELAY, 2000-ohm coil (#R3046)	1.95	1.96
1	1-SPST 24V REED RELAY, norm. open, dip style, 1250 ohms (#R5175)	1.49	1.50

## AMPLIFIERS!

Quant.	Description	1¢ Sale	2 for
3	3 WATTS ON A CHIP, Toshiba TA7200 (#R5057)	4.95	4.96
3	3 WATTS ON A CHIP, G-E PA 263 (#R1522)	1.50	1.51

## DIP SWITCHES!

Quant.	Description	Each	2 for
2	2 SWITCHES ON A DIP (#R3668)	\$.77	\$.78
3	3 SWITCHES ON A DIP (#R3669)	.88	.89
6	6 SWITCHES ON A DIP (#R3671)	1.29	1.30

# LIQUIDATION

LIQUIDATION

LIQUIDATION


*Sansui*



**Model  
QC-04**  
**CD-4 FOUR  
CHANNEL  
QUADRAPHONIC  
RECORD  
DEMODULATOR!**

**12<sup>95</sup>**  
EACH!  
\$9.95 ea. Lots of 3!  
\$8.95 ea. Lots of 100!

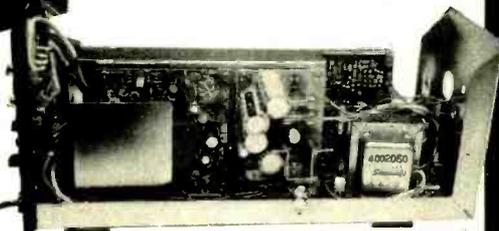\* Operates on  
110/220 vac.  
50/60 Hz.



**HUNDREDS OF PARTS!  
AN ELECTRONICS GOLD MINE!**

Order ETCO No.  
020HP099

1500  
IN STOCK!

**A TOP QUALITY SANSUI UNIT!**

Model QC-04 is an all-in-one, self-contained assembly designed to accept the output from a CD-4 quad stereo phono cartridge, and demodulate the four channel information to produce four discrete quadrasonic stereo channels, ready to feed into two stereo or one quadrasonic amplifier!  
We don't have too much information on this unit, but it's obviously a top-of-the-line unit. It seems to be designed for insertion into an existing stereo amplifier or preamp — three sides are bare as illustrated; the front panel has standard phono inputs and outputs, and the back panel has two interlocking control switches.

**CD-4 RECORDS ARE STILL AVAILABLE!**

—so you may want to use this unit for its original purpose. They're sold as is, but could probably be made to operate with a minimum of work. Some parts may be missing. A schematic diagram is included with each unit.

**A GOLD MINE OF UNIQUE AND VALUABLE PARTS!**

In parts alone, the QC-04 is worth many times our low price! Included on the chassis are: a 25 vdc regulated power supply complete with 110 vac power transformer; four low pass filters and two high pass filters of the best quality; integrated circuits, many regular and field-effect transistors, mini trimmer resistors, controls, capacitors, resistors, switches, etc.

**SOPHISTICATED CIRCUITRY COULD HAVE MANY USES!**

CD-4 Quadrasonic sound is similar in many ways to multiplex stereo. In effect, each channel on the CD-4 recorded is modulated with a high frequency carrier in addition to the audio signal. The carrier is modulated with rear channel information. The QC-04 contains audio and high frequency amplifiers, and two complete multiplex demodulators. There are probably lots of interesting uses for this unit — some of you bright fellows out there are sure to figure them out!

**DEALERS WANTED** for this and hundreds of other interesting items. Electronics stores, surplus dealers, Distributors, exporters — write on your letterhead for wholesale prices list. You can make money buying from ETCO!



Summer "AA" edition. Many more bargains such as this one! Circle the number shown below on the reader information card.

**24 HOUR-A-DAY, 7 DAY-A-WEEK** telephone order DESK! Phone in your chargecard orders at low week-end and evening rates! Call 1-518-561-8700.

**SURPLUS WANTED** — Contact our buying office at 1-514-695-0400 or send list and samples to Plattsburgh address below.

**CANADIANS** — Ordering from this ad is simple. Please remit in U.S. funds (or add 13% to overall total and remit in Canadian funds). - (Chargex and Mastercharge welcome). We do the paperwork and ship to you direct from the U.S.A. at low American prices. You pay duty and tax to Canadian Customs (Canadian schools are exempt). We have stores in Canada, too! Write for Canadian catalogs. We invite you to visit our Plattsburgh store — just 50 minutes from Montreal on U.S. 87!



**ETCO**

T.M.

Rush Your Order Today . . . .

**ETCO ELECTRONICS CORP. U.S.A.**  
North Country Shopping Center,  
Route No. 9, Plattsburgh, N.Y. 12901.

**ELECTRONICS** LIQUIDATORS OF EXCESS ELECTRONIC INVENTORIES

**MERCHANDISE SUBJECT TO PRIOR SALE.** Full remittance with each order, please. Money Order, Certified check, BANKAMERICARD, VISA, MASTERCARD or CHARGEX. Add 15% for UPS (or postage) and handling (we refund excess). Please try to bring your order total to \$10 or more. Worldwide export orders solicited. Open account to Government agencies, schools, institutions and triple "A" rated industrial & commercial accounts. Special quotes for quantities. N.Y. state residents: add 7% sales tax.

RADIO-ELECTRONICS

SAVE

# COMPUTER INTERFACES & PERIPHERALS

SAVE

For free catalog including parts lists and schematics, send a self-addressed stamped envelope.

## APPLE II SERIAL I/O INTERFACE \*

Part no. 2


• Baud rates up to 30,000 • Plugs into Apple Peripheral connector • Low-current drain • RS-232 Input and Output. SOFTWARE • Input and Output routine from monitor or BASIC to teletype or other serial printer. • Program for using an Apple II for a video or an intelligent terminal. Also can output in correspondence code to interface with some selectrics. Board only — \$15.00; with parts — \$42.00; assembled and tested — \$62.00.


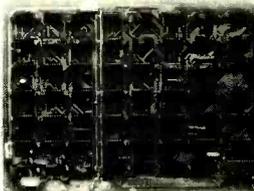
## T.V. TYPEWRITER

Part no. 106


• Stand alone TVT • 32 char/line, 16 lines, modifications for 64 char/line included • Parallel ASCII (TTL) input • Video output • 1K on board memory • Output for computer controlled cursor • Auto scroll • Non-destructive cursor • Cursor inputs: up, down, left, right, home, EOL, EOS • Scroll up, down • Requires +5 volts at 1.5 amps, and -12 volts at 30 mA • All 7400, TTL chips • Char gen. 2513 • Upper case only • Board only \$39.00; with parts \$145.00


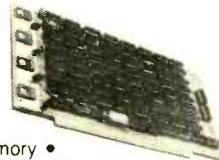
## 8K STATIC RAM

Part no. 300

• 8K Altair bus memory • Uses 2102 Static memory chips • Memory protect • Gold contacts • Wait states • On board regulator • S-100 bus compatible • Vector input option • TRI state buffered • Board only \$22.50; with parts \$160.00



## MODEM\*

Part no. 109


• Type 103 • Full or half duplex • Works up to 300 baud • Originate or Answer • No coils, only low cost components • TTL input and output-serial • Connect 8 ohm speaker and crystal mic. directly to board • Uses XR FSK demodulator • Requires +5 volts • Board \$7.60; with parts \$27.50


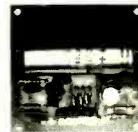
## RF MODULATOR\*

Part no. 107

• Converts video to AM modulated RF, Channels 2 or 3. So powerful almost no tuning is required. On board regulated power supply makes this extremely stable. Rated very highly in Doctor Dobbs' Journal. Recommended by Apple. • Power required is 12 volts AC C.T., or +5 volts DC • Board \$7.60; with parts \$13.50




## DC POWER SUPPLY\*

Part no. 6085

• Board supplies a regulated +5 volts at 3 amps., +12, -12, and -5 volts at 1 amp. • Power required is 8 volts AC at 3 amps., and 24 volts AC C.T. at 1.5 amps. • Board only \$12.50; with parts excluding transformers \$42.50



## TIDMA\*

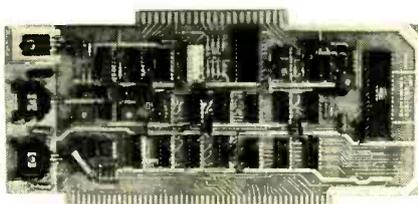


Part no. 112

• Tape Interface Direct Memory Access • Record and play programs without bootstrap loader (no prom) has FSK encoder/decoder for direct connections to low cost recorder at 1200 baud rate, and direct connections for inputs and outputs to a digital recorder at any baud rate. • S-100 bus compatible • Board only \$35.00; with parts \$110.00
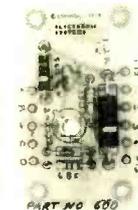
## RS 232/TTY INTERFACE\*

Part no. 600

• Converts RS-232 to 20mA current loop, and 20mA current loop to RS-232 • Two separate circuits • Requires +12 and -12 volts • Board only \$4.50, with parts \$7.00



## TAPE INTERFACE \*

Part no. 111


• Play and record Kansas City Standard tapes • Converts a low cost tape recorder to a digital tape recorder • Works up to 1200 baud • Digital in and out are TTL-serial • Output of board connects to mic. in of recorder • Earphone of recorder connects to input on board • No coils • Requires +5 volts, low power drain • Board \$7.60; with parts \$27.50


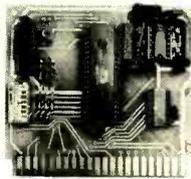
## UART & BAUD RATE GENERATOR\*

Part no. 101


• Converts serial to parallel and parallel to serial • Low cost on board baud rate generator • Baud rates: 110, 150, 300, 600, 1200, and 2400 • Low power drain +5 volts and -12 volts required • TTL compatible • All characters contain a start bit, 5 to 8 data bits, 1 or 2 stop bits, and either odd or even parity • All connections go to a 44 pin gold plated edge connector • Board only \$12.00; with parts \$35.00 with connector add \$4.00


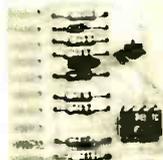
## RS 232/TTL INTERFACE\*

Part no. 232

• Converts TTL to RS-232, and converts RS-232 to TTL • Two separate circuits • Requires -12 and +12 volts • All connections go to a 10 pin gold plated edge connector • Board only \$4.50; with parts \$7.00 with connector add \$3.00



## ELECTRONIC SYSTEMS

Dept. CC, P.O. Box 21638, San Jose, Calif. USA 95151

### To Order:

Mention part number and description. For parts kits add "A" to part number. In USA, shipping paid for orders accompanied by check, money order, or Master Charge, BankAmericard, or VISA number, expiration date and signature. Shipping charges added to C.O.D. orders. California residents add 6.5% for tax. Outside USA add 10% for air mail postage, no C.O.D.'s. Checks and money orders must be payable in US dollars. Parts kits include sockets for all ICs, components, and circuit board. Documentation is included with all products. All items are in stock, and will be shipped the day order is received via first class mail. Prices are in US dollars. No open accounts. To eliminate tariff in Canada boxes are marked "Computer Parts." Dealer inquiries invited. 24 Hour Order Line: (408) 226-4064




\*Designed by John Bell


NEW LSI TECHNOLOGY  
**FREQUENCY COUNTER**

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION (PORTABLE BATTERY OPERATION IS NOW PRACTICAL), DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!

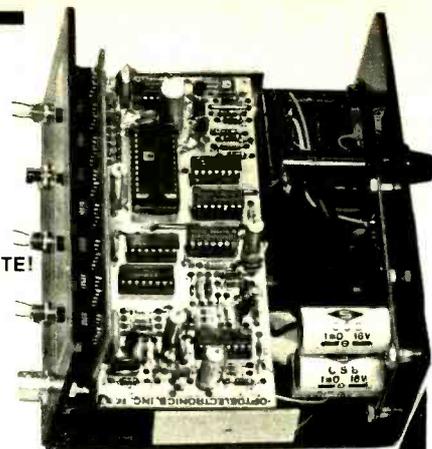- KIT #FC-50C ..... 60 MHZ COUNTER WITH CABINET & P.S. .... **\$119<sup>95</sup>** COMPLETE!
- KIT #PSL-650 ..... 650 MHZ PRESCALER (NOT SHOWN) ..... 29.95
- MODEL #FC-50WT ..... 60 MHZ COUNTER WIRED, TESTED & CAL. .... 165.95
- MODEL #FC-50/600WT ..... 600 MHZ COUNTER WIRED, TESTED & CAL. .... 199.95



SIZE:  
3" High  
6" Wide  
5 1/2" Deep

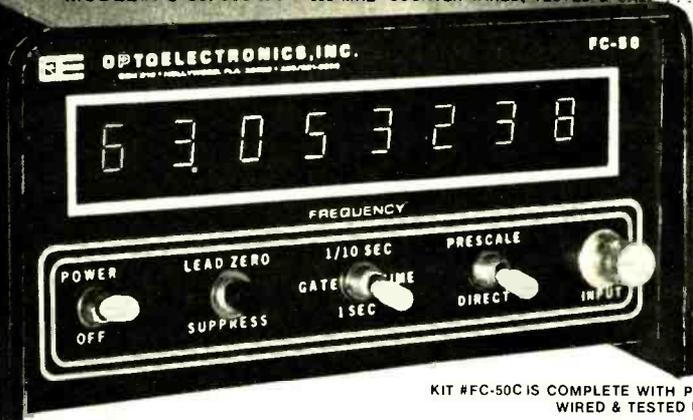

**FEATURES AND SPECIFICATIONS:**  
 DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT  
 GATE TIMES: 1 SECOND AND 1/10 SECOND  
 PRESCALER WILL FIT INSIDE COUNTER CABINET  
 RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.  
 FREQUENCY RANGE: 10 HZ TO 60 MHZ. (65 MHZ TYPICAL).  
 SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.  
 INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.  
 [DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]  
 ACCURACY: ± 1 PPM [± .0001%]; AFTER CALIBRATION TYPICAL.  
 STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [.001% XTAL]  
 IC PACKAGE COUNT: 8 [ALL SOCKETED]  
 INTERNAL POWER SUPPLY: 5 V DC REGULATED.  
 INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.  
 POWER CONSUMPTION: 4 WATTS

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED.

**PLEXIGLAS CABINETS**

Great for Clocks or any LED Digital project Clear-Red Chassis serves as Bezel to increase contrast of digital displays.


- CABINET I**  
3"H, 6 1/4"W, 5 1/2"D Black, White or Clear Cover
  - CABINET II**  
2 1/2"H, 5"W, 4"D \$6.50 ea.
- RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS  
3"x6"x1/8" 95¢ ea 4/93

**SEE THE WORKS Clock Kit**  
Clear Plexiglas Stand

- 6 Big 4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included

Plexiglas is Pre-cut & drilled  
Kit #B50-4CP

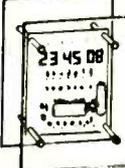Size: 6"H, 4 1/2"W, 3"D  
Assembled  
\$23<sup>50</sup> ea. 2/45. \$29<sup>95</sup>



**60 HZ.**

**XTAL TIME BASE**  
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC. 1"x2" PC Board Power Req: 5-15V (2.5 MA. TYP.) Easy 3 wire hookup Accuracy: ± 2PPM  
#TB-1 (Adjustable) Complete Kit \$4<sup>95</sup> Wir & Cal \$9.95

**SPECIAL PRICING!**  
PRIME - HIGH SPEED RAM  
**21L02-3** 400 NS  
LOW POWER - FACTORY FRESH

1-24	\$1.75 ea.	100-199	\$1.45 ea.
25-99	1.60 ea.	200-999	1.39 ea.


1000 AND OVER **\$1.29** ea.

**5-DIGIT LED CLOCK CALENDAR KIT**  
DATE-TIME-SNOOZE ALARM & MORE... KIT 7001

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME - 29-30-31 DAY CALENDAR. ALARM. SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

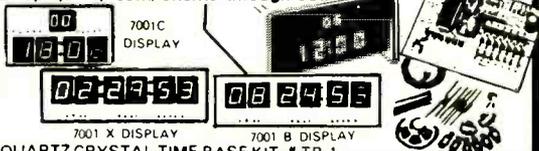- KIT 7001B WITH 6 .5" DIGITS ..... \$39.95
- KIT 7001C WITH 4 .6" DIGITS & 2 .3" DIGITS FOR SECONDS ..... \$42.95
- KIT 7001X WITH 6 .6" DIGITS ..... \$45.95



KITS ARE COMPLETE (LESS CABINET)

ALL 7001 KITS FIT CABINET I AND ACCEPT QUARTZ CRYSTAL TIME BASE KIT # TB-1

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout.

Specify for 7001

B. Cor X - \$7.95

**AUTO BURGLAR ALARM KIT**

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND KEYLESS ALARM HAS PROVISION FOR POS. & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1/2 RATE OR DRIVE SIREN KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED CMOS RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DON'T BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED




KIT #ALR-1 \$9.95  
#ALR-1WT WIRED & TESTED \$19.95

**VARIABLE REGULATED 1 AMP POWER SUPPLY KIT**

- VARIABLE FROM 4.10-14V
  - SHORT CIRCUIT PROOF
  - 723 IC REGULATOR
  - 2N3055 PASS TRANSISTOR
  - CURRENT LIMITING AT 1 Amp
- KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (Less TRANSFORMER) KIT #PS-01 \$8.95  
 TRANSFORMER 24V CT will provide 300MA at 12v and 1 Amp at 5V. \$3.50

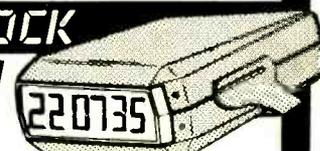**MOBILE LED CLOCK**

12/24 HR .4" DIGITS!  
MODEL 12 VOLT AC or #2001 DC POWERED



- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
  - SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
  - STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
  - BRIDGE POWER INPUT CIRCUITRY - TWO WIRE NO POLARITY HOOK-UP
  - OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
  - TOP QUALITY PC BOARDS & COMPONENTS - INSTRUCTIONS.
  - MOUNTING BRACKET INCLUDED
- KIT #2001 COMPLETE KIT \$27<sup>95</sup> 3 OR \$25<sup>95</sup> 115 VAC Power Pack #AC-1 \$25<sup>00</sup> EA. MORE
- ASSEMBLED UNITS WIRED & TESTED ORDER #2001 WT [LESS 9V. BATTERY] \$37<sup>95</sup> EA 3 OR \$35<sup>95</sup> MORE \$35<sup>95</sup> EA. MORE

ORDER BY PHONE OR MAIL  
COD ORDERS WELCOME

**OPTOELECTRONICS, INC.**

5821 N.E. 14th AVENUE,  
FORT LAUDERDALE, FLA. 33334  
PHONE (305) 771-2050 / 771-2051

ORDERS TO USA & CANADA ADD 5% FOR SHIPPING, HANDLING & INSURANCE. ALL OTHERS ADD 10%. ADDITIONAL \$1.00 CHARGE FOR ORDERS UNDER \$15.00 - COD FEE \$1.00. FLA. RES. ADD 4% STATE TAX.



**KEPCO**

**Ferroresonant Power Supply**

Input 110V 3A Factory Price \$206  
Output 24V 8A Our Price \$80

Please add \$5.00 extra postage to this item

**Car Battery Eliminator**

\$16.95 KIT-700

KIT INCLUDES: Transformer, PC Board, Large heat sink, Large filtering capacitor

**TRINICO INTERNATIONAL**  
(Formerly Trico)

2795 W. Lincoln Ave., Suite L, Anaheim, Ca. 92801

**TERMS: Money Back Guarantee**  
CALIF. RESIDENTS ADD 4% SALES TAX  
Please add \$1.00 for postage inside Calif., \$2.00 for  
Out of State, Overseas add 10% of order.  
Minimum Order \$5.00 C.O.D. \$20.00 (\$1.00 handling)  
STORE HOURS: Mon.-Sat. 10-7

BankAmericard  Master Charge

PHONE 714/821-0234

**CRYSTALS ± 0.002%**  
LOWEST PRICE EVER  
HIGHEST ACCURACY

Frequency MHz	Price
1.000	1.8432

@4.90

Frequency MHz	Price
2.000	2.0100
2.097152	2.4576
2.567	3.000
3.200	3.2768
3.5795	

@4.50

Frequency MHz	Price
4.0000	4.1943
4.9152	5.0000
5.0000	5.0688
5.1850	5.7143
6.0000	6.144
6.400	6.536
8.0000	

@3.65 8.0000

Frequency MHz	Price
10.000	14.318
14.391	18.000
18.000	18.4320
20.0000	22.1184
27.0000	27.0000
32.0000	36.0000
36.0000	48.0000

@2.85

**OVER 3000 SOLD**  
30 MHz LOW COST  
FREQUENCY COUNTER KIT

COMPARE  
and  
SAVE!  
**\$54.95**



Features:  
Frequency Range-100Hz to 30MHz min. resolution 100 Hz  
All TTL Circuitry-No tears in the eyes when replacing ICs  
FET Input Stage-Offers high input impedance  
High Sensitivity-15mV typical  
X'ytal Time Base-0.001% 10MHz for better accuracy  
On Board Regulator-No external power supply needed  
All ICs Socketed-Easy to service  
Easy to Operate-No switches to flip  
Tin Plated & Screened Board-For easy assembly

**Instrument Case**  
Perfect for our 30 MHz Frequency



PRICE: \$17.50

**MINIATURE DPDT** .20 each  
**SLIDE SWITCH** 10 for \$1.75  
100 for \$15.00

**PUSH BUTTON SWITCH** White, green and yellow  
30 ea. ea.  
4/\$1.00

**TANTALUM CAP**

AXIAL LEADS	Price
1 10V 15c	
1 35V 20c	
3 35V 25c	
10 50V 30c	
22 35V 30c	

**6-DIGIT AUTO CLOCK KIT WITH ALARM**

Features:  
A. Flashing 0.5" FND 500 Series Display  
B. Display Board may be remote  
C. X'tal time base  
D. P.C. Boards, speaker, IC's and all parts  
E. Detailed instructions

**\$19.95** KIT # T-1302

**4 and 6 Digit Alarm Clock Kit**  
Kit includes P.C. Boards, x'tormer 4-Digit \$10.95 and all parts. (Limited Qty.)  
6-Digit \$12.95

**DIP SWITCHES**

No. of Sw.	Price
2	1.80
3	1.90
4	2.15
5	2.45
6	2.70
7	2.90
8	3.10
9	3.30
10	3.50

**DIP PLUGS**

5 pcs	10 pcs	100 pcs
14-pin	3.25	6.00 55.00
16-pin	3.50	6.50 60.00
40-pin	9.50	18.00 150.00

**Wire Wrap Wire Special Purchase**  
500 ft. roll @ 5.00 ea.  
White only

**1N4148 Diodes**

Quantity	Price
10/75c	
50/3.25	
100/5.00	

**POWER TRANSISTORS MATCHED PAIR**

Model	Price
TI TIP2955 PNP	75c
TIP 3055 NPN	75c
10 AMP 60 VOLT 90-141 T's	4.75
\$2.25 PER PAIR	

**L.E.D. T-Segment Displays**

Model	Price
FND 500 Com Cat. 0.5"	75c
FND 510 Com Anode 0.5"	75c
1720R Com Anode 1"	4.75
1723R Com Cat. 1"	4.75

**9V Battery Clips**  
10c ea., 10/75c, 50/3.00, 100/5.00

**0.2" L.E.D. Lamps**


Color	Price
Red	15c
Green	20c
Yellow	20c
Amber	20c

**WIRE WRAP WIRE**  
PRECUT

#30 Kynar available in red, blue, yellow, orange, green, black, and white. Saves time cutting and stripping, and yet is about the same in cost as on rolls. Other lengths and sizes available. All lengths are overall, with 1" strip on each end. Colors and lengths cannot be mixed for quantity pricing. Wires come in plastic bags or plastic tubes available at 25c each.

Length	100	500	1000	5000
2 1/2 in.	.78	2.40	4.30/K	3.89/K
3 in.	.82	2.60	4.71/K	4.22/K
3 1/2 in.	.86	2.80	5.12/K	4.55/K
4 in.	.90	3.00	5.52/K	4.88/K
4 1/2 in.	.94	3.21	5.93/K	5.21/K
5 in.	.98	3.42	6.34/K	5.52/K
5 1/2 in.	1.02	3.65	6.75/K	5.86/K
6 in.	1.06	3.85	7.16/K	6.19/K
6 1/2 in.	1.15	4.05	7.57/K	6.52/K
7 in.	1.20	4.25	7.98/K	6.85/K
7 1/2 in.	1.25	4.45	8.39/K	7.18/K
8 in.	1.29	4.65	8.80/K	7.53/K
8 1/2 in.	1.32	4.85	9.21/K	7.84/K
9 in.	1.36	5.05	9.62/K	8.17/K
9 1/2 in.	1.40	5.25	10.03/K	8.50/K
10 in.	1.45	5.50	10.44/K	8.83/K
Addl. in.	10	.41	82/K	.66/K

**HAMMOND BREADBOARD KIT**

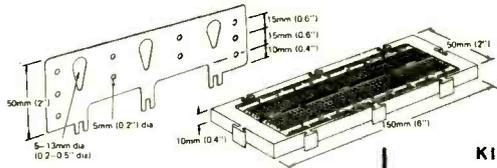

**BIMBOARD 1 \$9.95 ea.**

Accepts DIP packages without adaptors or damaging component leads. Contacts are double sided, nickel silver, current carrying capacity of 1 Amp with less than 10 milliohms contact resistance. Total of 550 sockets identified by a letter and number matrix for recording experiments. Buss strip section runs up each side of board.

Component bracket (included with each board) will fit on any of the four edges or down the center.

**BIMBOARD 2 \$24.**

2 Bimboards and 2 component brackets  
1 Aluminum base with 4 insulated Terminals

**BIMBOARD 3 \$34.**

3 Bimboards and 3 component brackets  
1 Aluminum base with 4 insulated terminals

**BIMBOARD 4 \$43.**

4 Bimboards and 4 component brackets  
1 Aluminum base with 4 insulated terminals.

KIT \$	8K	16K
250 ns	\$ 230.00	390.00
450 ns	\$ 215.00	328.00

**Z-80 CPU BOARD/KIT**

On board 2708 EPROM addressable to any 4K boundary above 32K. Power-on-jump to any 4K boundary above 32K, or the on board 2708. On board run-stop flip-flop and optional generation of Memory Write allow front panel-less operation.

**BARE BOARD \$34.00**  
**KIT \$130.00 (2MHz) \$145.00 (4MHz)**

**8080 A CPU BOARD/KIT**

With 8 level vector interrupt. CUP chip clock chip. 8224: x'ytal Freq. 18MHz; vector interrupt chip. 8214.

**BARE BOARD \$28.50 KIT \$95.00**

**REAL TIME CLOCK FOR S-100 BUSS**

On board 1MHz Crystal Oscillator; two independent interrupts. 16 bit counter in 10 s steps; and decade steps from 100 s to 10 sec.

**BARE BOARD \$24.00**  
**KIT \$120.00**

**8K STATIC RAM MEMORY KIT**

**Bareboard \$24. KITS-**  
**\$120.00 (450ns) \$135.00 (350ns) \$160.00 (250ns)**

**16K RAM MEMORY KIT**

**Bareboard \$24 KIT \$365- 450ns \$415-**

**32K RAM MEMORY KIT**

**Bareboard \$30**

**SOLDER WIK**  
Quick solder remover

Size	Price
1/32" 5 ft.	
1/16" 5 ft.	
1/8" 5 ft. 1 ea. ea.	
1/4" 2 1/2 ft.	

**28 AWG 7/26 Strand CABLE**  
LAMINATED - GRAY

No. of Conductors	Width	Price/ft.
10	0.45"	0.33
14	0.65"	0.46
16	0.75"	0.53
20	0.95"	0.66
26	1.25"	0.88
34	1.65"	1.15
40	1.95"	1.35
50	2.45"	1.65
60	2.95"	2.00

**LAMINATED - COLOR CODED**


No. of Conductors	Width	Price/ft.
20	0.45"	0.54
14	0.65"	0.75
16	0.75"	0.86
20	0.95"	1.05
26	1.25"	1.40
34	1.65"	1.85
40	1.95"	2.15
50	2.45"	2.70
60	2.95"	3.25

**I.C. SOCKETS**


I.C. Socket	Lo-pro			3-Level Wire Wrap		
	5 pcs	10 pcs	100 pcs	5 pcs	10 pcs	100 pcs
8-pin	0.80	1.50	12.00	1.90	3.50	32.00
14-pin	0.95	1.75	15.00	2.10	3.90	36.00
16-pin	1.05	2.00	17.00	2.50	4.20	39.00
18-pin	1.40	2.50	23.00	3.20	6.00	55.00
20-pin	1.60	3.10	28.00	3.50	6.50	60.00
22-pin	1.80	3.40	32.00	3.75	7.00	65.00
24-pin	1.85	3.50	33.00	4.25	8.00	75.00
28-pin	2.20	4.20	39.00	4.75	9.00	85.00
40-pin	3.50	6.20	59.00	6.50	12.00	100.00

**CASES (bottoms) PANELS (tops)**

Case/Panel	A	B	C	D	E	F	Color	Price
<b>15° SLOPING PANELS</b>								
4.0 5.5 2.0	1.1	3.3	2.2	1-B	1-G	1-L	5.50	1-W
6.5 5.5 2.0	1.1	3.3	2.2	2-B	2-G	2-L	6.10	2-W
6.5 8.5 2.0	1.1	3.3	5.2	3-B	3-G	3-L	6.70	3-W
<b>30° SLOPING PANELS</b>								
6.0 5.5 3.0	1.1	3.7	2.2	9-B	9-G	9-L	5.50	9-W
6.5 5.5 3.0	1.1	3.7	2.2	10-B	10-G	10-L	6.10	10-W
6.5 7.2 4.0	1.1	5.7	2.2	11-B	11-G	11-L	6.70	11-W
<b>FLAT PANELS</b>								
10.0 5.5 3.0	1.1	3.7	2.2	12-B	12-G	12-L	7.30	12-W
10.0 7.2 4.0	1.1	5.7	2.2	13-B	13-G	13-L	7.80	13-W
10.0 10.2 4.0	1.1	5.7	5.2	14-B	14-G	14-L	8.40	14-W
<b>VERTICAL PANELS</b>								
14.0 7.2 4.0	1.1	5.7	2.2	15-B	15-G	15-L	8.80	15-W
14.0 10.2 4.0	1.1	5.7	5.2	16-B	16-G	16-L	9.70	16-W

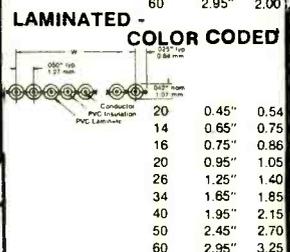

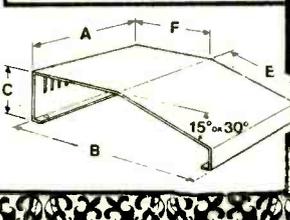**74 Keys Keyboard**  
Manufactured by Micro Switch for Honeywell. Full encoded. (Limited Quantity)  
**\$50.00**





# \$24.95 PROBE?

You bet! Meet CSC's Multi-family Logic Probe 2.

Wherever you need fast, safe, accurate digital testing—you need CSC's new LP-2. It's a compact, enormously versatile circuit-powered unit that's become indispensable. As a level detector. Pulse detector. And pulse stretcher.

**Easier to use.** Set LP-2's switch to the proper logic family, connect two clip-leads to the circuit's supply, touch the probe to the node under test—and you get an instant picture of circuit conditions. Separate LED's indicate logic "1", logic "0", and all pulse transitions. And a 300K-plus input impedance insures minimum circuit loading.

At just \$24.95\*, you don't have to think twice about owning the LP-2. Especially when you see how it simplifies testing, debugging and servicing all types of digital circuits.

**Order today.** Call 203-624-3103 (East Coast) or 415-421-8E72 (West Coast): 9 a.m.-5 p.m. local time. Major credit cards accepted. Or see your CSC dealer. Prices slightly higher outside USA.

**Logic Family Switch**—TTL/HTL or CMOS matches Logic "1" and "0" levels for greater versatility. CMOS position also compatible with HTL, HiNIL and MOS logic.

**PULSE LED**—Indicates positive and negative pulse and level transitions. Stretches pulses as narrow as 300 nanoseconds to full 1/10 sec. (10Hz pulse rate).

**HI/LO LED's**—Display level (HI-logic "1", LO-logic "0") of signal activity.

**Interchangeable ground lead connection**—Provides ground-side input connection via optional cables.

**Interchangeable probe tips**—Straight tip supplied; optional alligator clip and insulated quick-connecting clip available.

**Plug-in leads**—24" supplied, with alligator clips. Virtually any length leads may be connected.

## Specifications

Input impedance better than 300K $\Omega$ .

Thresholds (switch selectable)	DT_/TTL	HTL/CMOS
logic 1 thresholds (HI-LED)	2.25V $\pm$ .10V	70% Vcc = 10%
logic 0 thresholds (LO-LED)	0.80V $\pm$ .05V	30% Vcc = 10%

Min. detectable pulse width 300 nsec.

**Pulse detector (PULSE LED)** 1/10-sec. pulse stretcher makes high-speed pulse train or single events (+ or - transitions) visible.

**Input protection** overload,  $\approx$  25V continuous; 117 VAC for less than 10 sec.; reverse-polarity, 50V

**Power requirements** 5-15 volts Vcc; 30mA max.




**Operating temperature**  $-50^{\circ}\text{C}$

**Physical size (l x w x d)**

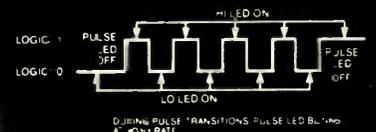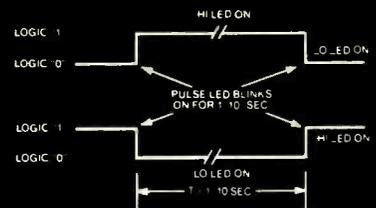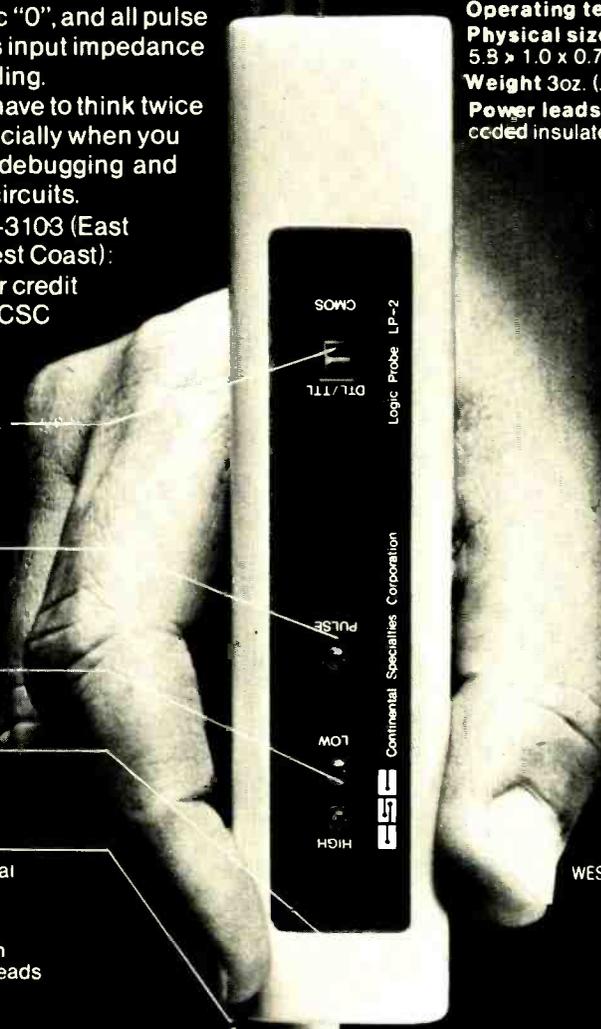5.9 x 1.0 x 0.7" (147 x 25.4 x 17.8mm)

**Weight** 3oz. (.085Kg)

**Power leads** detachable 24" (610 mm) with color-coded insulated clips, others available



CONTINENTAL SPECIALTIES CORPORATION



70 Fulton Terrace, Box 1492, New Haven, CT 06509  
 203-624-3103 TWX 710-465-1227  
 WEST COAST 351 California St., San Francisco, CA 94104  
 415-421-8872 TWX 910-372-7992  
 GREAT BRITAIN: CSC UK LTD  
 Spur Road, North Feltham Trading Estate,  
 Feltham, Middlesex, England  
 01-890-0782 Int'l Telex 851-8E1-3669

\*Manufacturer's Recommended Resale  
 © 1978 Continental Specialties Corporation

CIRCLE 5 ON FREE INFORMATION CARD

NEW LP-2!

**We're  
so convinced  
our high-  
performance K40  
will outperform  
every CB antenna,**



**WE'LL SELL YOU ONE FOR \$38.50 TO PROVE IT!**

The K40 is more than just a premium antenna.

It's specifically guaranteed, in writing, to outperform any antenna it replaces.

**1 TRANSMITS FURTHER.  
RECEIVES CLEARER.**

We mean just that! We'll back you 100% if the K40 doesn't transmit further or receive clearer than the antenna it replaces. We know it will. We've tested it with 771 CBer's just like you for one year.

**2 WHEN YOU PAY MORE, YOU EXPECT MORE.**

For a full year we'll let your dealer replace any part you're not happy with. You make the decision, not us. Our guarantee includes rust. It includes broken whips. It includes everything.

**3 IT'S AMERICAN MADE.**

No need to be concerned about replacement parts. There is not one component that is made anywhere else but in America.

**4 MOUNTS ANYWHERE, EVERYWHERE.**

With the spectacular Unimount, you can fit your K40 to any mounting surface—anywhere. And that's guaranteed too. 100%. That means this single K40 antenna can easily fit any vehicle you own—or you'll ever own. That includes choppers, dune buggies, gutters, mirror mounts, luggage racks, trunks, hatch-backs, through roofs, semi's, pick-up's & RV's.

**5 SOLD BY PROFESSIONAL DEALERS THAT TAKE PRIDE IN SERVICING CBER'S.**

Like pro-golf clubs, the K40 antenna is sold through pro-CB/Electronic stores only. It's not being sold to mass merchandisers. It's not being sold to Sears or Penney's or any retail outlets that cannot offer full-time professional support to the service you need. We control that because we personally qualify each and every retailer before we sign him on.

**6 HERE'S OUR DEAL.**


Make a check for \$38.50. Rip out this page and run over to your local CB shop for your very own K40. If he is out of K40's, have him call us immediately. We'll get it out to him in 24 hours. Here's how:

**REACH!**

for your dealer's phone and dial,

**312-697-7400**

**GO FOR IT.**

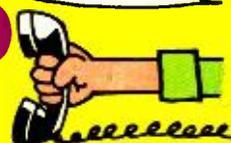

Our boys will be waiting for him at  
**AMERICAN ANTENNA, Elgin, Illinois.**

An All-American Product by an All-American Company.

CIRCLE 32 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)